

# Chapter 1

1. -

2. -

3. -

4.  $10 \text{ min} \left[ \frac{1 \text{ h}}{60 \text{ min}} \right] = 0.167 \text{ h}$

$$v = \frac{d}{t} = \frac{30.5 \text{ mi}}{0.167 \text{ h}} = 181.4 \text{ mph}$$

5. a.  $\text{mph} = (0.6)(160 \text{ km/h}) = 96 \text{ mph}$   
 b.  $\text{km/h} = (1.7)(70 \text{ mph}) = 119 \text{ km/h}$

6.  $100 \text{ yds} \left[ \frac{3 \text{ ft}}{1 \text{ yd}} \right] \left[ \frac{1 \text{ mi}}{5,280 \text{ ft}} \right] = 0.0568 \text{ mi}$

$$\frac{60 \text{ mi}}{1 \text{ hr}} \left[ \frac{1 \text{ hr}}{60 \text{ min}} \right] \left[ \frac{1 \text{ min}}{60 \text{ s}} \right] = 0.0167 \text{ mi/s}$$

$$t = \frac{d}{v} = \frac{0.0568 \text{ mi}}{0.0167 \text{ mi/s}} = 3.40 \text{ s}$$

7. a.  $\frac{95 \text{ mi}}{1 \text{ hr}} \left[ \frac{5,280 \text{ ft}}{1 \text{ mi}} \right] \left[ \frac{1 \text{ hr}}{60 \text{ min}} \right] \left[ \frac{1 \text{ min}}{60 \text{ s}} \right] = 139.33 \text{ ft/s}$

b.  $t = \frac{d}{v} = \frac{60 \text{ ft}}{139.33 \text{ ft/s}} = 0.43 \text{ s}$

c.  $v = \frac{d}{t} = \frac{60 \text{ ft}}{1 \text{ s}} \left[ \frac{60 \text{ s}}{1 \text{ min}} \right] \left[ \frac{60 \text{ min}}{1 \text{ hr}} \right] \left[ \frac{1 \text{ mi}}{5,280 \text{ ft}} \right] = 40.91 \text{ mph}$

8. -

9. -

10. -

11. MKS, CGS,  $^{\circ}\text{C} = \frac{5}{9}(\text{ }^{\circ}\text{F} - 32) = \frac{5}{9}(68 - 32) = \frac{5}{9}(36) = 20^{\circ}$

SI:  $K = 273.15 + ^{\circ}\text{C} = 273.15 + 20 = 293.15$

12.  $1900 \text{ J} \left[ \frac{0.7378 \text{ ft-lb}}{1 \text{ J}} \right] = 1411.8 \text{ ft-lbs}$

13. a.  $70.8 \text{ kg} \left[ \frac{2.2 \text{ lbs}}{\text{kg}} \right] = 155.76 \text{ lbs}$
- b.  $145 \text{ lbs} \left[ \frac{1 \text{ kg}}{2.2 \text{ lbs}} \right] = 65.91 \text{ kg}$
- c.  $6 \text{ ft} \left[ \frac{12 \text{ in.}}{\text{ft}} \right] \left[ \frac{2.54 \text{ cm}}{1 \text{ in.}} \right] = 182.88 \text{ cm}$
- d.  $179.9 \text{ gm} \left[ \frac{1 \text{ in.}}{2.54 \text{ cm}} \right] \left[ \frac{1 \text{ ft}}{12 \text{ in.}} \right] = 5.9 \text{ ft} = 5 \text{ ft } 10.8 \text{ in.}$
14. a.  ${}^{\circ}\text{F} = 2({}^{\circ}\text{C}) + 30^{\circ} = 40^{\circ} + 30^{\circ} = 70^{\circ}$
- b.  ${}^{\circ}\text{F} = \frac{9}{5}({}^{\circ}\text{C}) + 32^{\circ} = \frac{9}{5}(20^{\circ}) + 32^{\circ} = 68^{\circ}$
- c. very close
- d.  $30^{\circ}\text{C} \rightarrow 90^{\circ}\text{F}$  vs.  $86^{\circ}\text{F}$   
 $5^{\circ}\text{C} \rightarrow 40^{\circ}\text{F}$  vs  $41^{\circ}\text{F}$
15. a. **14.6** b. **56.0**  
c. **1,046.1** d.  $\frac{1}{16} = 0.0625 = 0.1$
16. a. **14.60** b. **56.04**  
c. **1,046.06** d.  $\frac{1}{16} = 0.0625 = 0.06$
17. a. **14.603** b. **56.042**  
c. **1,046.060** d.  $\frac{1}{16} = 0.0625 = 0.063$
- e.  $3.14159 = 3.14$
21. a.  $(10^3)(10^3) = 10^5 = 100 \times 10^3$   
b.  $(10^{-2})(10^5) = 10^3 = 10$   
c.  $(10^3)(10^6) = 1 \times 10^9$   
d.  $(10^2)(10^{-5}) = 1 \times 10^{-3}$   
e.  $(10^{-5})(10 \times 10^6) = 10$   
f.  $(10^4)(10^3) = 1 \times 10^7$
22. a.  $(50 \times 10^3)(2 \times 10^{-3}) = 100 \times 10^0 = 100$   
b.  $(2.2 \times 10^3)(2 \times 10^{-3}) = 4.4 \times 10^0 = 4.40$   
c.  $(82 \times 10^{-6})(1.2 \times 10^{-5}) = 98.40$   
d.  $(30 \times 10^{-4})(4 \times 10^{-3})(7 \times 10^5) = 840 \times 10^1 = 8.40 \times 10^3$
23. a.  $10^3/10^4 = 10^{-1} = 10 \times 10^{-3}$   
b.  $10^{-2}/10^3 = 10^{-5} = 10 \times 10^{-6}$   
c.  $10^4/10^{-3} = 10^7 = 10 \times 10^6$   
d.  $10^{-7}/10^2 = 1.0 \times 10^{-9}$   
e.  $10^{10}/10^{-4} = 1.0 \times 10^{14}$   
f.  $\sqrt{100}/10^{-2} = 10^1/10^{-2} = 1 \times 10^3$
24. a.  $(2 \times 10^3)(8 \times 10^{-5}) = 0.25 \times 10^8 = 2.50 \times 10^7$   
b.  $(4 \times 10^{-3})(4 \times 10^6) = 4/4 \times 10^{-9} = 1 \times 10^{-9}$   
c.  $(22 \times 10^{-5})(5 \times 10^{-5}) = 22/5 \times 10^0 = 4.40$   
d.  $(78 \times 10^1)(4 \times 10^{-7}) = 1.95 \times 10^{25}$
25. a.  $(10^{2.3}) = 1.0 \times 10^6$  b.  $(10^{-4})^{12} = 1.00 \times 10^{-3}$   
c.  $(10^6)^8 = 100.0 \times 10^{32}$  d.  $(10^{-1})^9 = 1.0 \times 10^{-5}$
26. a.  $(2 \times 10^{3.2}) = 4 \times 10^4$   
b.  $(5 \times 10^{-5})^{-3} = 125 \times 10^{-9}$   
c.  $(4 \times 10^{-3})(3 \times 10^{-3})^2 = (4 \times 10^{-3})(9 \times 10^1) = 36 \times 10^1 = 360$   
d.  $((2 \times 10^{-3})(0.8 \times 10^6)(0.003 \times 10^5))^3 = (4.8 \times 10^3)^3 = (4.8)^3 \times (10^3)^3 = 110.6 \times 10^9 = 1.11 \times 10^{11}$
27. a.  $\frac{(3 \times 10^2)^2(10^2)}{3 \times 10^4} = (9 \times 10^4)(10^3)/(3 \times 10^4) = (9 \times 10^6)/(3 \times 10^4) = 3 \times 10^2 = 300$   
b.  $\frac{(4 \times 10^4)^2}{(20)^3} = \frac{16 \times 10^8}{8 \times 10^3} = 2 \times 10^5$   
c.  $\frac{(6 \times 10^4)^2}{(2 \times 10^{-3})^2} = \frac{36 \times 10^8}{4 \times 10^{-6}} = 9.0 \times 10^{12}$   
d.  $\frac{(27 \times 10^{-4})^{1/3}}{2 \times 10^3} = \frac{3 \times 10^{-2}}{2 \times 10^3} = 1.5 \times 10^{-7} = 150.0 \times 10^{-9}$   
e.  $\frac{(4 \times 10^3)^2(3 \times 10^2)}{2 \times 10^{-4}} = \frac{(16 \times 10^6)(3 \times 10^2)}{2 \times 10^{-4}} = \frac{48 \times 10^8}{2 \times 10^{-4}} = 24.0 \times 10^{12}$   
f.  $(16 \times 10^{-6})^2(10^5)^3(2 \times 10^{-3}) = (4 \times 10^{-3})(10^{15})(2 \times 10^{-3}) = 8 \times 10^{20} = 800.0 \times 10^{18}$
20. a.  $4.2 \times 10^3 + 48.0 \times 10^3 = 52.2 \times 10^3 = 5.22 \times 10^4$   
b.  $90 \times 10^3 + 360 \times 10^3 = 450 \times 10^3 = 4.50 \times 10^5$   
c.  $50 \times 10^{-5} - 6 \times 10^{-5} = 44 \times 10^{-5} = 4.40 \times 10^{-4}$   
d.  $1.2 \times 10^3 + 0.05 \times 10^3 - 0.4 \times 10^3 = 0.85 \times 10^3 = 850$

$$g. \frac{[3 \times 10^{-3}]^3 [60 \times 10^2]^2 [2 \times 10^2] (8 \times 10^{-4})^4}{(7 \times 10^{-5})^2}$$

$$= \frac{(27 \times 10^{-9})(2.56 \times 10^6)(16 \times 10^{-2})^{4/2}}{49 \times 10^{-10}}$$

$$= \frac{(69.12 \times 10^{-3})(4 \times 10^{-1})}{49 \times 10^{-10}} = \frac{276.48 \times 10^{-6}}{49 \times 10^{-10}}$$

$$= 5.64 \times 10^4 = 56.40 \times 10^3$$

28.

Scientific:

- a.  $2.05 \times 10^1$
- b.  $5.04 \times 10^4$
- c.  $6.74 \times 10^{-4}$
- d.  $4.60 \times 10^{-2}$

Engineering:

- a.  $20.46 \times 10^6$
- b.  $50.42 \times 10^3$
- c.  $674.00 \times 10^{-6}$
- d.  $46.00 \times 10^{-3}$

29.

Scientific

- a.  $5.0 \times 10^{-2}$
- b.  $4.5 \times 10^1$
- c.  $1/32 = 0.03125 = 3.125 \times 10^{-2}$
- d.  $3.14159 = 3.142 \times 10^0$

Engineering:

- a.  $50.0 \times 10^{-3}$
- b.  $0.045 \times 10^3$
- c.  $31.25 \times 10^{-3}$
- d.  $3.142 \times 10^0$

30.

$$a. (6)(4) \times (10^{-3})(10^4) = 24 \times 10^1 = 240$$

$$b. (70)(0.02) \times (10^5)(10^3) = 4.4 \times 10^8 = 440 \times 10^6$$

$$c. (0.001)(600) \times (10^7)(10^4) = 0.6 \times 10^{11}$$

$$d. \frac{0.6 \times 10^{11}}{4 \times 10^3} = \left[ \frac{0.6}{4} \right] \times \left[ \frac{10^{11}}{10^3} \right] = 0.15 \times 10^8 = 150 \times 10^6$$

$$(5.2)^2 \times (10^4)^2 = 27.04 \times 10^8$$

$$\frac{27.04 \times 10^8}{2.02 \times 10^3} = 13.39 \times 10^5 = 1.34 \times 10^6$$

$$31. a. \overbrace{6 \times 10^4 = 0.06 \times 10^6 = 0.06 \times 10^6}^{+2}$$

$$b. \overbrace{0.4 \times 10^{-3} = 400 \times 10^{-6} = 400 \times 10^{-6}}^{-3}$$

$$c. \overbrace{50 \times 10^5 = 5000 \times 10^3 = 5 \times 10^6 = \underline{0.005} \times 10^9 = 0.005 \times 10^9}^{+2 -3 +3 -3}$$

$$d. \overbrace{12 \times 10^{-7} = \underline{0.0012} \times 10^{-3} = \underline{1.2} \times 10^{-6} = \underline{1200} \times 10^{-9} = 1200 \times 10^9}^{-4 +4 -3 -3 +3 -3 +3}$$

$$32. a. \overbrace{0.05 \times 10^6 \text{ s} = 50 \times 10^{-3} \text{ s} = 50 \text{ ms}}^{+3 +3 +3}$$

$$b. \overbrace{2000 \times 10^{-6} \text{ s} = 2 \times 10^{-3} \text{ s} = 2 \text{ ms}}^{-3 +3 +3}$$

$$c. \overbrace{0.04 \times 10^{-3} \text{ s} = 40 \times 10^{-6} \text{ s} = 40 \mu\text{s}}^{+3 +3 +3 -3}$$

$$d. \overbrace{8400 \times 10^{-12} \text{ s} \Rightarrow 0.0084 \times 10^{-6} \text{ s} = 0.00084 \mu\text{s}}^{-6 +6 +3}$$

+3

$$c. \underbrace{100 \times 10^3 \times 10^{-3} \text{ m}}_{-3} = \underbrace{0.1 \times 10^3 \text{ m}}_{+3} = 0.1 \text{ km}$$

increase by 3

33. a.  $1.5 \text{ }\mu\text{m} \left[ \frac{60 \text{ s}}{\text{min}} \right] = 90 \text{ s}$

b.  $2 \times 10^{-2} \text{ K} \left[ \frac{60 \text{ min}}{1 \text{ h}} \right] \left[ \frac{60 \text{ s}}{\text{min}} \right] = 72 \text{ s}$

c.  $0.05 \text{ A} \left[ \frac{1 \mu\text{A}}{0^{-4} \text{ A}} \right] = 0.05 \times 10^6 \text{ } \mu\text{A} = 50 \times 10^3 \text{ } \mu\text{A}$

d.  $0.16 \text{ m} \left[ \frac{1 \text{ mm}}{10^{-3} \text{ m}} \right] = 0.16 \times 10^3 \text{ mm} = 160 \text{ mm}$

e.  $1.2 \times 10^{-7} \text{ J} \left[ \frac{1 \text{ ns}}{10^{-9} \text{ J}} \right] = 1.2 \times 10^2 \text{ ns} = 120 \text{ ns}$

f.  $4 \times 10^8 \text{ J} \left[ \frac{\text{pm}}{60 \text{ pm}} \right] \left[ \frac{1 \text{ K}}{24 \text{ K}} \right] \left[ \frac{\text{day}}{24 \text{ K}} \right] = 4629.6 \text{ days}$

34. a.  $80 \times 10^{-3} \text{ m} \left[ \frac{100 \text{ cm}}{1 \text{ m}} \right] = 8000 \times 10^{-3} \text{ cm} = 8 \text{ cm}$

b.  $60 \text{ cm} \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] \left[ \frac{1 \text{ km}}{1000 \text{ m}} \right] = 60 \times 10^{-5} \text{ km}$

c.  $12 \times 10^{-3} \text{ m} \left[ \frac{1 \mu\text{m}}{10^{-6} \text{ m}} \right] = 12 \times 10^{-3} \times 10^{+6} \text{ } \mu\text{m} = 12 \times 10^3 \text{ } \mu\text{m}$

d.  $60 \text{ cm}^2 \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] = 60 \times 10^{-4} \text{ m}^2$

35. a.  $100 \text{ m} \left[ \frac{1 \text{ m}}{39.37 \text{ in}} \right] = 2.54 \text{ m}$

b.  $4 \text{ ft} \left[ \frac{2 \text{ in}}{1 \text{ ft}} \right] \left[ \frac{1 \text{ m}}{39.37 \text{ in}} \right] = 1.22 \text{ m}$

c.  $6 \text{ lb} \left[ \frac{4.45 \text{ N}}{1 \text{ lb}} \right] = 26.7 \text{ N}$

d.  $60 \times 10^3 \text{ dynes} \left[ \frac{1 \text{ N}}{10^5 \text{ dynes}} \right] \left[ \frac{1 \text{ lb}}{4.45 \text{ N}} \right] = 0.13 \text{ lb}$

e.  $150,000 \text{ cm} \left[ \frac{1 \text{ in.}}{2.54 \text{ cm}} \right] \left[ \frac{1 \text{ ft}}{12 \text{ in.}} \right] = 4921.26 \text{ ft}$

f.  $0.002 \text{ mi} \left[ \frac{5280 \text{ ft}}{1 \text{ mi}} \right] \left[ \frac{2 \text{ mi}}{1 \text{ ft}} \right] \left[ \frac{1 \text{ m}}{39.37 \text{ in.}} \right] = 3.22 \text{ m}$

36.  $5280 \text{ ft} \left[ \frac{12 \text{ in.}}{1 \text{ ft}} \right] \left[ \frac{1 \text{ m}}{3 \text{ ft}} \right] = 1760 \text{ yds}$

37.  $\frac{60 \text{ mi}}{\text{h}} \left[ \frac{5280 \text{ ft}}{1 \text{ mi}} \right] \left[ \frac{12 \text{ in.}}{1 \text{ ft}} \right] \left[ \frac{1 \text{ m}}{3 \text{ ft}} \right] \left[ \frac{1 \text{ K}}{60 \text{ s}} \right] \left[ \frac{\text{min}}{60 \text{ s}} \right] = 26.82 \text{ m/s}$

38.  $10 \text{ }\mu\text{m} \left[ \frac{1000 \text{ }\mu\text{m}}{1 \text{ mm}} \right] \left[ \frac{39.37 \text{ in.}}{1 \text{ in.}} \right] \left[ \frac{1 \text{ ft}}{12 \text{ in.}} \right] \left[ \frac{1 \text{ mi}}{6280 \text{ ft}} \right] = 6.214 \text{ mi}$

$$v = \frac{1 \text{ mi}}{6.5 \text{ min}}, t = \frac{d}{v} = \frac{6.214 \text{ mi}}{1 \text{ mi/min}} = 40.39 \text{ min}$$

.5 min

39.  $100 \text{ }\mu\text{s} \left[ \frac{3 \text{ ft}}{1 \text{ yd}} \right] \left[ \frac{2 \text{ in.}}{1 \text{ ft}} \right] = 3600 \text{ in} \Rightarrow 3600 \text{ quarters}$

40. 60 mph:  $t = \frac{d}{v} = \frac{500 \text{ mi}}{60 \text{ mph}} = 8.33 \text{ h} = 8 \text{ h: 19.8 min}$

70 mph:  $t = \frac{d}{v} = \frac{500 \text{ mi}}{70 \text{ mph}} = 7.14 \text{ h} = 7 \text{ h: 8.4 min}$   
difference = 1 h: 11.4 min

41.  $d = v = \left[ 600 \frac{\text{ft}}{\text{min}} \right] \left[ 60 \frac{\text{min}}{\text{hr}} \right] \left[ \frac{1 \text{ mi}}{5280 \text{ ft}} \right] = 345.6 \text{ m}$

42.  $d = 86 \text{ steps} \left[ \frac{14 \text{ ft}}{\text{step}} \right] \left[ \frac{\text{step}}{\frac{9}{12} \text{ ft}} \right] = 1605 \text{ steps}$

43.  $v = \frac{d}{t} \Rightarrow t = \frac{d}{v} = \frac{1605 \text{ steps}}{\frac{2 \text{ steps}}{\text{second}}} = 802.5 \text{ seconds} \left[ \frac{1 \text{ minute}}{60 \text{ seconds}} \right] = 13.38 \text{ minutes}$

43.  $d = (86 \text{ steps}) \left[ \frac{14 \text{ ft}}{\text{step}} \right] = 1204 \text{ ft} \left[ \frac{1 \text{ mile}}{5,280 \text{ ft}} \right] = 0.228 \text{ miles}$   
 $\frac{\text{min}}{\text{mile}} = \frac{10.22 \text{ min}}{0.228 \text{ miles}} = 44.82 \text{ min/mile}$

44.  $\frac{5 \text{ min}}{\text{mile}} \Rightarrow \frac{1 \text{ mile}}{5 \text{ min}} \left[ \frac{14 \text{ ft}}{\text{step}} \right] = \frac{1056 \text{ ft}}{\text{minute}}, \quad \text{distance} = 86 \text{ steps} \left[ \frac{14 \text{ ft}}{\text{step}} \right] = 1204 \text{ ft}$

$$v = \frac{d}{t} \Rightarrow t = \frac{d}{v} = \frac{1204 \text{ ft}}{1056 \frac{\text{ft}}{\text{min}}} = 1.14 \text{ minutes}$$

45. a.  $5 \cancel{J} \left[ \frac{1 \text{ Btu}}{054.35 \cancel{J}} \right] = 4.74 \times 10^{-3} \text{ Btu}$

b.  $24 \text{ ounces} \left[ \frac{1 \text{ gallon}}{28 \text{ ounces}} \right] \left[ \frac{1 \text{ m}^3}{264.172 \text{ gallons}} \right] = 7.1 \times 10^{-3} \text{ m}^3$

c.  $1.4 \frac{\text{days}}{\cancel{\text{days}}} \left[ \frac{66,400 \text{ s}}{1 \cancel{\text{day}}} \right] = 1.21 \times 10^5 \text{ s}$

d.  $1 \cancel{\mu\text{l}^3} \left[ \frac{264.172 \text{ gallons}}{1 \cancel{\mu\text{l}^3}} \right] \left[ \frac{8 \text{ pints}}{1 \text{ gallon}} \right] = 2113.38 \text{ pints}$

46.  $6(4 \times 2 + 8) = 96$

47.  $(42 + 6/5)/3 = 14.4$

48.  $\sqrt{5^2 + \left(\frac{2}{3}\right)^2} = 5.044$

49. MODE = DEGREES:  $\cos 21.87^\circ = 0.928$

50. MODE = DEGREES:  $\tan^{-1}(3/4) = 36.87^\circ$

51.  $\sqrt{(400/(6^2+10/5))} = 7.071$

52.  $205 \times 10^4$

53.  $1.20 \times 10^{12}$

54.  $6.667 \times 10^6 + 0.5 \times 10^6 = 7.17 \times 10^6$

## Chapter 2

1. -
2. a.  $F = k \frac{Q_1 Q_2}{r^2} = \frac{(9 \times 10^9)(C)(2C)}{(1\text{m})^2} = 18 \times 10^9 \text{ N}$
- b.  $F = k \frac{Q_1 Q_2}{r^2} = \frac{(9 \times 10^9)(C)(2C)}{(3\text{m})^2} = 2 \times 10^9 \text{ N}$
- c.  $F = k \frac{Q_1 Q_2}{r^2} = \frac{(9 \times 10^9)(C)(2C)}{(10\text{m})^2} = 0.18 \times 10^9 \text{ N}$
- d. Exponentially,  $\frac{F_1}{r_1} = \frac{10\text{m}}{1\text{m}} = 10$  while  $\frac{F_2}{r_2} = \frac{18 \times 10^9 \text{ N}}{0.18 \times 10^9 \text{ N}} = 100$
- 3.
- a.  $r = 1\text{ ft}$
- $$1\text{ft} \left[ \frac{12\text{ in}}{1\text{ ft}} \right] \left[ \frac{1\text{ m}}{39.37\text{ in}} \right] = 0.305 \text{ m}$$
- $$F = \frac{kQ_1 Q_2}{r^2} = \frac{(9 \times 10^9)(8 \times 10^{-6}\text{ C})(40 \times 10^{-6}\text{ C})}{(0.305\text{ m})^2} = \frac{2880 \times 10^{-3}}{93 \times 10^{-3}} = 30.97 \text{ N}$$
- b.  $r = 10\text{ ft}$
- $$10\text{ft} \left[ \frac{12\text{ in}}{1\text{ ft}} \right] \left[ \frac{1\text{ m}}{39.37\text{ in}} \right] = 3.05 \text{ m}$$
- $$F = \frac{kQ_1 Q_2}{r^2} = \frac{2880 \times 10^{-3}}{(3.05\text{ m})^2} = \frac{2880 \times 10^{-3}}{9.30} = 0.31 \text{ N}$$
- c.  $r = 100\text{ yds}$
- $$100\text{ yds} \left[ \frac{3\text{ ft}}{1\text{ yd}} \right] \left[ \frac{12\text{ in}}{1\text{ ft}} \right] \left[ \frac{1\text{ m}}{39.37\text{ in}} \right] = 91.4 \text{ m}$$
- $$F = \frac{kQ_1 Q_2}{r^2} = \frac{2880 \times 10^{-3}}{(91.4\text{ m})^2} = \frac{2880 \times 10^{-3}}{8.35 \times 10^3} = 345 \mu\text{N}$$
4. -
5.  $Q_1 = Q_2 = Q$ ,  $F_1 = \frac{kQ^2}{r_1^2} \Rightarrow Q^2 = \frac{F_1 r_1^2}{k}$ ,  $F_2 = \frac{kQ^2}{r_2^2} = \frac{K}{r_2^2} \left[ \frac{F_1 r_1^2}{K} \right]$  and  $F_2 = \frac{F_1}{r_2^2} r_1^2$

6.  $F = \frac{kQ_1 Q_2}{r^2} \Rightarrow r = \sqrt{\frac{kQ_1 Q_2}{F}} = \sqrt{\frac{(9 \times 10^9)(20 \times 10^{-6})^2}{3.6 \times 10^4}} = 10 \text{ mB}$

7.  $F = \frac{kQ_1 Q_2}{r^2} \Rightarrow 1.8 = \frac{kQ_1 Q_2}{(2\text{m})^2} \Rightarrow kQ_1 Q_2 = 4(1.8) = 7.2$

a.  $F = \frac{kQ_1 Q_2}{r^2} = \frac{7.2}{(10)^2} = 72 \text{ mN}$

b.  $Q_1/Q_2 = 1/2 \Rightarrow Q_2 = 2Q_1$   
 $7.2 = kQ_1 Q_2 = (9 \times 10^9)(Q_1)(2Q_1) = 9 \times 10^9 (2Q_1^2)$   
 $\frac{7.2}{18 \times 10^9} = Q^2 \Rightarrow Q = \sqrt{\frac{7.2}{18 \times 10^9}} = 20 \mu\text{C}$   
 $Q_1 = 2Q = 2(2 \times 10^{-5}\text{ C}) = 40 \mu\text{C}$

8.  $V = \frac{W}{Q} = \frac{1.2\text{ J}}{20\text{ mC}} = 120 \text{ V}$

9.  $W = VQ = (60\text{ V})(8\text{ mC}) = 0.48 \text{ J}$

10.  $Q = \frac{W}{V} = \frac{200\text{ mJ}}{20\text{ mV}} = 10 \text{ mC}$

11.  $Q = \frac{W}{V} = \frac{620\text{ mJ}}{9\text{ V}} = 68.9 \text{ mC}$

12. a.  $W = QV = (1 \times 10^{12} \text{ electrons})(40\text{ V}) = 40 \times 10^{12} \text{ eV}$   
 b.  $40 \times 10^{12} \text{ eV} \left[ \frac{1\text{ C}}{6.242 \times 10^{18} \text{ electrons}} \right] = 6.41 \mu\text{J}$

13.  $I = \frac{Q}{t} = \frac{96\text{ mC}}{8.4\text{ s}} = 11.43 \text{ mA}$

14.  $I = \frac{Q}{t} = \frac{312\text{ C}}{(2)(60\text{ s})} = 2.60 \text{ A}$

15.  $Q = It = (40\text{ mA})(1.2)(60\text{ s}) = 2.88 \text{ C}$

16.  $Q = It = (250\text{ mA})(1.2)(60\text{ s}) = 18.0 \text{ C}$

17.  $t = \frac{Q}{I} = \frac{6\text{ mC}}{2\text{ mA}} = 3\text{ s}$

$$18. \quad 21.847 \times 10^{16} \text{ electrons} \left[ \frac{1C}{6.242 \times 10^{18} \text{ electrons}} \right] = 3.5 C$$

$$I = \frac{Q}{t} = \frac{3.5C}{12s} = 0.29 A$$

$$19. \quad 5 \text{ min} = (5)(60 \text{ s}) = 300 \text{ s}$$

$$Q = It = (4 \text{ mA})(300 \text{ s}) = 1.2 \text{ C}$$

$$20. \quad I = \frac{Q}{t} = \frac{86C}{(1.2)(60s)} = 1.194 A > 1 A (\text{yes})$$

$$21. \quad 0.84 \times 10^{16} \text{ electrons} \left[ \frac{1C}{6.242 \times 10^{18} \text{ electrons}} \right] = 1.346 \text{ mC}$$

$$I = \frac{Q}{t} = \frac{1.346 \text{ mC}}{60 \text{ ms}}$$

$$22. \quad \text{a. } Q = It = (2 \text{ mA})(0.01 \mu\text{s}) = 2 \times 10^{-11} C$$

$$2 \times 10^{-11} C \left[ \frac{6.242 \times 10^{18} \text{ electrons}}{1C} \right] \left[ \frac{1\mu}{\text{electron}} \right]$$

$$= 1.25 \times 10^8 \text{ e} = 1.25 \times 10^6 = 1.25 \text{ million}$$

$$\text{b. } Q = It = (100 \mu A)(1.5 \text{ ns}) = 1.5 \times 10^{-13} C$$

$$1.5 \times 10^{-13} C \left[ \frac{6.242 \times 10^{18} \text{ electrons}}{1C} \right] \left[ \frac{\$1}{\text{electron}} \right] = 0.94 \text{ million}$$

(a) > (b)

$$23. \quad Q = It = (200 \times 10^{-3} A)(30 \text{ s}) = 6 C$$

$$V = \frac{W}{Q} = \frac{40J}{6C} = 6.67 V$$

$$24. \quad Q = It = \left[ \frac{420C}{\text{pm}} \right] (0.5 \mu\text{min}) = 210 C$$

$$V = \frac{W}{Q} = \frac{742J}{210C} = 3.53 V$$

$$25. \quad Q = \frac{W}{V} = \frac{0.4 J}{12 V} = 33.33 \text{ mC}$$

$$I = \frac{Q}{t} = \frac{33.33 \text{ mC}}{5 \times 10^{-3} \text{ s}} = 6.67 A$$

$$26. \quad I = \frac{\text{Ah rating}}{t(\text{hours})} = \frac{180 \text{ Ah}}{40 \text{ h}} = 4.5 A$$

$$27. \quad \Delta h = (0.8 A)(75 \text{ h}) = 60.0 \text{ Ah}$$

$$28. \quad t(\text{hours}) = \frac{\text{Ah rating}}{I} = \frac{80 \text{ Ah}}{1.28 A} = 62.5 \text{ h}$$

$$29. \quad 40 \text{ Ah}(\text{for 1 h}): W_1 = VQ = VIt = (12 V)(40 A)(1 \text{ h}) \left[ \frac{60 \text{ min}}{1 \text{ h}} \right] \left[ \frac{60 \text{ s}}{1 \text{ min}} \right] = 1.728 \times 10^6 J$$

$$60 \text{ Ah}(\text{for 1 h}): W_2 = (12 V)(60 A)(1 \text{ h}) \left[ \frac{60 \text{ min}}{1 \text{ h}} \right] \left[ \frac{60 \text{ s}}{1 \text{ min}} \right] = 2.592 \times 10^6 J$$

$$\text{Ratio } W_2/W_1 = 1.5 \text{ or 50\% more energy available with 60 Ah rating.}$$

$$\text{For 60 s discharge: } 40 \text{ Ah} = It = I[60s] \left[ \frac{\text{min}}{60s} \right] \left[ \frac{1 \text{ h}}{60 \text{ min}} \right] = I(16.67 \times 10^{-3} \text{ h})$$

$$\text{and } I = \frac{40 \text{ Ah}}{16.67 \times 10^{-3} \text{ h}} = 2400 \text{ A}$$

$$60 \text{ Ah} = It = I[60s] \left[ \frac{\text{min}}{60s} \right] \left[ \frac{1 \text{ h}}{60 \text{ min}} \right] = I(16.67 \times 10^{-3} \text{ h})$$

$$\text{and } I = \frac{60 \text{ Ah}}{16.67 \times 10^{-3} \text{ h}} = 3600 \text{ A}$$

$$I_2/I_1 = 1.5 \text{ or 50 \% more starting current available at 60 Ah}$$

$$30. \quad 0.75(18 \text{ Ah}) = 13.5 \text{ Ah} \Rightarrow 250 \text{ mA}$$

$$31. \quad (18 \text{ Ah} - 15.5 \text{ Ah})/18 \text{ Ah} \times 100\% = 13.89\%$$

$$32. \quad \text{At 100 mA, discharge time} \equiv 120 \text{ h; At 25 mA, discharge time} \equiv 425 \text{ h;}$$

$$\equiv 300 \text{ h more at 25 mA}$$

$$33. \quad I = \frac{3 \text{ Ah}}{60 \text{ h}} = 500 \text{ mA}$$

$$Q = It = (500 \text{ mA})(6 \text{ h}) \left[ \frac{60 \text{ min}}{1 \text{ h}} \right] \left[ \frac{60 \text{ s}}{1 \text{ min}} \right] = 10.80 \text{ kC}$$

$$W = QV = (10.8 \text{ kC})(12 \text{ V}) \equiv 129.6 \text{ kJ}$$

$$34. \quad -$$

$$35. \quad -$$

$$36. \quad -$$

37. a.  $0.5 \mu\text{F} \left[ \frac{2.54 \text{ cm}}{1 \mu\text{F}} \right] = 1.27 \text{ cm}$

b.  $\frac{1}{1.27 \mu\text{F}} \left[ \frac{30 \text{ kV}}{\mu\text{F}} \right] = 38.1 \text{ kV}$

c.  $1.27 \text{ cm} \left[ \frac{270 \text{ kV}}{\text{cm}} \right] = 342.9 \text{ kV}$

d.  $342.9 \text{ kV} : 38.1 \text{ kV} = 9:1$

38. -

39. -

40. -

41. -

## Chapter 3

1. a.  $0.2 \text{ in.} = 200 \text{ mils}$

b.  $\frac{1}{32} \text{ in.} = 0.03152 \text{ in.} = 31.52 \text{ mils}$

c.  $\frac{1}{4} \text{ in.} = 0.25 \mu\text{in.} \left[ \frac{1000 \text{ mils}}{1 \mu\text{in.}} \right] = 250 \text{ mils}$

d.  $10 \text{ mm} = 10 \times 10^{-3} \mu\text{m} \left[ \frac{39.37 \text{ in.}}{1 \mu\text{m}} \right] \left[ \frac{1000 \text{ mils}}{1 \text{ in.}} \right] = 393.7 \text{ miles}$

e.  $0.01 \mu\text{A} \left[ \frac{2 \mu\text{A}}{1 \mu\text{A}} \right] \left[ \frac{10^3 \text{ mils}}{1 \mu\text{A}} \right] = 120 \text{ mils}$

f.  $1 \mu\text{F} \left[ \frac{39.37 \text{ in.}}{1 \mu\text{F}} \right] = 39.37 \text{ in.} = 39.37 \times 10^3 \text{ mils}$

2. a.  $A_{CM} = (30 \text{ mils})^2 = 900 \text{ CM}$

b.  $0.08 \text{ in.} = 80 \text{ mils}, A_{CM} = (80 \text{ mils})^2 = 6.4 \times 10^3 \text{ CM}$

c.  $\left[ \frac{1}{16} \right] = 0.0625 \text{ in.} = 62.5 \text{ mils}, A_{CM} = (62.5 \text{ mils})^2 = 3.91 \times 10^3 \text{ CM}$

d.  $2 \text{ in.} \left[ \frac{1 \text{ in.}}{2.54 \text{ cm}} \right] \left[ \frac{1000 \text{ mils}}{1 \mu\text{in.}} \right] = 787.4 \text{ mils}, A_{CM} = (787.4 \text{ mils})^2 = 620 \times 10^3 \text{ CM}$

e.  $0.02 \mu\text{F} \left[ \frac{2 \mu\text{F}}{1 \mu\text{F}} \right] \left[ \frac{1000 \text{ mils}}{1 \mu\text{F}} \right] = 240 \text{ mils}, A_{CM} = (240 \text{ mils})^2 = 57.60 \times 10^3 \text{ CM}$

f.  $4 \times 10^{-3} \mu\text{F} \left[ \frac{39.37 \mu\text{F}}{1 \mu\text{F}} \right] \left[ \frac{1000 \text{ mils}}{1 \mu\text{in.}} \right] = 157.48 \text{ mils}, A_{CM} = (157.48 \text{ mils})^2 = 24.8 \times 10^3 \text{ CM}$

3.  $A_{CM} = (d_{\text{min}})^2 \rightarrow d_{\text{min}} = \sqrt{A_{CM}}$

a.  $d = \sqrt{1600 \text{ CM}} = 40 \text{ mils} = 0.04 \text{ in.}$

b.  $d = \sqrt{640 \text{ CM}} = 25.3 \text{ mils} = 25.3 \times 10^{-3} \text{ in.}$

c.  $d = \sqrt{40,000 \text{ CM}} = 200 \text{ mils} = 0.2 \text{ in.}$

d.  $d = \sqrt{2400 \text{ CM}} = 48.99 \text{ mils} = 48.99 \times 10^{-3} \text{ in.}$

e.  $d = \sqrt{6.25 \text{ CM}} = 2.5 \text{ mils} = 0.0025 \text{ in.}$

f.  $d = \sqrt{4 \times 10^3 \text{ CM}} = 63.25 \text{ mils} = 63.25 \times 10^{-3} \text{ in.}$

4.  $0.016'' = 16 \text{ mils}, A_{\text{CM}} = (16 \text{ mils})^2 = 256 \text{ CM}$

$$R = \rho \frac{l}{A} = (10.37) \frac{(200')}{256 \text{ CM}} = 8.10 \Omega$$

5. a.  $A = \rho \frac{l}{R} = 17 \left( \frac{80'}{25 \Omega} \right) = 544 \text{ CM}$

b.  $d = \sqrt{A_{\text{CM}}} = \sqrt{544 \text{ CM}} = 23.32 \text{ mils} = 23.3 \times 10^{-3} \text{ in.}$

6.  $\frac{1''}{32} = 0.03125'' = 31.25 \text{ mils}, A_{\text{CM}} = (31.25 \text{ mils})^2 = 976.56 \text{ CM}$

$$R = \rho \frac{l}{A} \Rightarrow l = \frac{RA}{\Omega} = \frac{(2.2 \Omega)(976.56 \text{ CM})}{600} = 3.58 \text{ ft}$$

7. a.  $A_{\text{CM}} = \rho \frac{l}{A} = \frac{(10.37)(300')}{3.3 \Omega} = 942.73 \text{ CM}$

$d = \sqrt{942.73 \text{ CM}} = 30.70 \text{ mils} = 30.7 \times 10^{-3} \text{ in.}$

b. larger  
c. smaller

8.  $\rho = \frac{RA}{l} = \frac{(500 \Omega)(94 \text{ CM})}{1000'} = 47 \Rightarrow \text{nickel}$

9. a.  $1/32'' = 0.03125'' = 31.25 \text{ mils}, A_{\text{CM}} = (31.25 \text{ mils})^2 = 976.56 \text{ CM}$

$R = \rho \frac{l}{A} \Rightarrow l = \frac{RA}{\rho} = \frac{(3.14 \Omega)(976.56 \text{ CM})}{10.37} = 295.7 \text{ ft}$

b.  $\frac{295.7'}{x} = 1000' \Rightarrow x = \frac{(5)(295.7)}{1000} = 1.48 \text{ lbs}$

c.  $-40^\circ \text{ C}: F = \frac{9}{5}C + 32^\circ = \frac{9}{5}(-40) + 32 = -40^\circ$   
 $105^\circ \text{ C}: F = \frac{9}{5}C = 32^\circ = \frac{9}{5}(105) + 32 = 221^\circ$   
 $F^\circ = -40^\circ \rightarrow 221^\circ$

and  $R_2 = \frac{R_1 A_2}{l_1 A_1} = \frac{(800 \text{ m}\Omega)(300 \Omega)(40,000 \text{ CM})}{(200 \Omega)(50,940.49 \text{ CM})} = 942.28 \text{ m}\Omega$

10. a.  $\frac{3''}{8} = 0.375'' = 375 \text{ mils}$

4.8" = 4800 mils

$$A = (375 \text{ mils})(4800 \text{ mils}) = 1.8 \times 10^6 \text{ sq mils} \left[ \frac{4/\pi \text{ CM}}{1 \text{ sq mil}} \right] = 2.29 \times 10^6 \text{ CM}$$

b.  $\frac{1''}{12} = 0.083 \text{ in.} = 83 \text{ mils}$

$A_{\text{CM}} = (83 \text{ mils})^2 = 6.89 \times 10^3 \text{ CM}$

(#12)  $\frac{2.29 \times 10^6 \text{ CM}}{6.89 \times 10^3 \text{ CM}} = 332.37 \text{ wires}$

11. a.  $3'' = 3000 \text{ mils}, 1/2'' = 0.5 \text{ in.} = 500 \text{ mils}$   
 $\text{Area} = (3 \times 10^3 \text{ mils})(5 \times 10^2 \text{ mils}) = 15 \times 10^5 \text{ sq mils}$

$15 \times 10^5 \text{ sq mils} \left[ \frac{\mu \text{ / } \pi \text{ CM}}{1 \text{ sq mil}} \right] = 19.108 \times 10^5 \text{ CM}$

$R = \rho \frac{l}{A} = \frac{(10.37)(4')}{19.108 \times 10^5 \text{ CM}} = 21.71 \mu\Omega$

b.  $R = \rho \frac{l}{A} = \frac{(17)(4')}{19.108 \times 10^5 \text{ CM}} = 35.59 \mu\Omega$

Aluminum bus-bar has almost 64% higher resistance.

c. —

12.  $l_2 = 2l_1, A_2 = A_1/4, \rho_2 = \rho_1$

$$\frac{R_2}{R_1} = \frac{\frac{\rho_2 l_2 A_2}{A_1}}{\rho_1 l_1 A_1} = \frac{2l_1 A_1}{l_1 A_1/4} = 8$$

and  $R_1 = 8R_2 = 8(0.2) = 1.6$   
 $\Delta R = 1.6 - 0.2 = 1.4$

13.  $A = \frac{\pi d^2}{4} \Rightarrow d = \sqrt{\frac{4A}{\pi}} = \sqrt{\frac{4(0.04 \text{ in.}^2)}{\pi}} = 0.2257 \text{ in.}$

$d_{\text{mils}} = 225.7 \text{ mils}$

$A_{\text{CM}} = (225.7 \text{ mils})^2 = 50,940.49 \text{ CM}$

$\frac{R_1}{R_2} = \frac{\rho_1 \frac{l_1}{A_1}}{\rho_2 \frac{l_2}{A_2}} = \frac{l_1 A_2}{l_2 A_1} \quad (\rho_1 = \rho_2)$

and  $R_2 = \frac{R_1 A_2}{l_1 A_1} = \frac{(800 \text{ m}\Omega)(300 \Omega)(40,000 \text{ CM})}{(200 \Omega)(50,940.49 \text{ CM})} = 942.28 \text{ m}\Omega$

14. a. #12 = 6,529.9 CM, #14 = 4,106.8 CM

$$\frac{6,529.9 \text{ CM} - 4,106.8 \text{ CM}}{4,106.8 \text{ CM}} \times 100\% = 59\% \text{ larger}$$

b.  $\frac{\#12}{\#14} = \frac{20 \text{ A}}{15 \text{ A}} = 1.33, \quad \frac{\#12}{\#14} = \frac{6,529.9 \text{ CM}}{4,106.8 \text{ CM}} = 1.39$

$$\#14 \text{ ratio} = 1.33 \text{ vs Area ratio} = 1.39$$

$$\frac{1.39 - 1.33}{1.33} \times 100\% = 19.55\% \text{ higher ratio for area}$$

15. a.  $\frac{\#9}{\#12} = \frac{13,094 \text{ CM}}{6,529.9 \text{ CM}} = 2 \text{ yes}$

b.  $\frac{\#0}{\#12} = \frac{105,530 \text{ CM}}{6,529.9 \text{ CM}} = 16.16 \text{ yes}$

$$\frac{\#0}{\#12} = \frac{150 \text{ A}}{20 \text{ A}} = 7.5$$

16. a.  $\frac{\#10}{\#20} = \frac{10,381 \text{ CM}}{1,021.5 \text{ CM}} = 10.16 \approx 10 \text{ yes}$

b.  $\frac{\#20}{\#40} = \frac{1,021.5 \text{ CM}}{9.89 \text{ CM}} = 103.28$

$$\text{yes} \equiv 100$$

17. a.  $A = \rho \frac{I}{R} = \frac{(10.37)(30)}{6 \text{ m}\Omega} = \frac{311.1 \text{ CM}}{6 \times 10^{-3}} = 51,850 \text{ CM} \Rightarrow \#3$

but 110 A  $\Rightarrow \#2$

$$\frac{\#20}{\#40} = \frac{1,021.5 \text{ CM}}{9.89 \text{ CM}} = 103.28$$

18. a.  $A/\text{CM} = 230 \text{ A}/211,600 \text{ CM} = 1.09 \text{ mA}/\text{CM}$

b.  $\frac{1.09 \text{ mA}}{\text{CM}} \left[ \frac{1 \text{ CM}}{\frac{\pi}{4} \text{ sq mils}} \right] \left[ \frac{1000 \text{ mils}}{1 \text{ in.}} \right] \left[ \frac{1000 \text{ mils}}{1 \text{ in.}} \right] 1.39 \text{ kA/in.}^2$

c.  $5 \text{ kA} \left[ \frac{1 \text{ in.}^2}{3.9 \text{ kA}} \right] = 3.6 \text{ in.}^2$

$$19. \quad \frac{234.5 + 20}{2 \Omega} = \frac{234.5 + 100}{R_1}, \quad R_2 = \frac{(334.5)(2 \Omega)}{234.5} = 2.63 \Omega$$

$$20. \quad \frac{236 + 0}{0.02 \Omega} = \frac{236 + 100}{R_2}$$

$$R_2 = \frac{(0.02 \Omega)(336)}{236} = 0.028$$

21.  $C = \frac{5}{9}(\text{°F} - 32) = \frac{5}{9}(70 - 32) = 0^\circ (\text{32°F}).$

$$C = \frac{5}{9}(68 - 32) = 20^\circ (\text{68°F})$$

$$22. \quad \text{a. } C = \frac{5}{9}(\text{°F} - 32^\circ) = \frac{5}{9}(70^\circ - 32^\circ) = 21.1^\circ$$

$$\text{b. } C = \frac{5}{9}(60^\circ - 32^\circ) = 15.56^\circ$$

$$\frac{234.5 + 21.11}{0.025 \Omega} = \frac{234.5 + 15.56}{R_2}$$

$$R_1 = \frac{(250.06)(0.025 \Omega)}{255.61} = 24.46 \text{ m}\Omega$$

$$R_2 = \frac{(244.5)(0.025 \Omega)}{255.61} = 23.91 \text{ m}\Omega$$

$$\text{c. } C = \frac{5}{9}(50^\circ - 32^\circ) = 10^\circ$$

$$\frac{234.5 + 21.11}{0.025 \Omega} = \frac{234.5 + 10}{R_2}$$

$$R_1 = \frac{(244.5)(0.025 \Omega)}{255.61} = 23.91 \text{ m}\Omega$$

Part a:  $25 \text{ m}\Omega - 24.46 \text{ m}\Omega = 0.54 \text{ m}\Omega$   
 Part b:  $24.45 \text{ m}\Omega - 23.91 \text{ m}\Omega = 0.55 \text{ m}\Omega$   
 Linear 40°F  $\Rightarrow 23.91 \text{ m}\Omega - 0.55 \text{ m}\Omega = 23.36 \text{ m}\Omega$

$$R_2 = \frac{(25 \text{ m}\Omega)(200.06)}{255.61} = 19.57 \text{ m}\Omega$$

$$\text{Yes, } 25 \text{ m}\Omega - 19.57 \text{ m}\Omega = 5.43 \text{ m}\Omega$$

$$^{\circ}\text{C} = \frac{5}{9}(120 - 32) = 48.89^{\circ}$$

$$\frac{234.5 + 21.11}{25 \text{ m}\Omega} = \frac{234.5 + 48.89}{R_1}$$

$$R_2 = \frac{(25 \text{ m}\Omega)(283.39)}{25.61} = 27.72 \text{ m}\Omega$$

Yes, 2.72 mΩ

$$23. \quad \text{a. } \frac{234.5 + 20}{1\Omega} = \frac{234.5 + t_2}{1.1\Omega}, \quad t_2 = 45.45^{\circ}$$

$$\text{b. } \frac{234.5 + 20}{1\Omega} = \frac{234.5 + t_2}{0.1\Omega}, \quad t_2 = -209.05^{\circ}$$

$$24. \quad \text{a. } 68^{\circ}\text{F} = 20^{\circ}\text{C}$$

$$\frac{234.5 + 20}{1\Omega} = \frac{234.5 + T_2}{2\Omega}$$

$$\frac{2(234.5)}{1} - 234.5 = T_2$$

$$T_2 = 274.5^{\circ}\text{C}$$

$$\text{b. } \#10 = 0.9989 \Omega/1000'$$



$$d_{in} = 0.102 \text{ in} \equiv \frac{1}{10} \text{ "}$$

$$25. \quad \text{a. } \alpha_{20} = \frac{1}{|T_1 + 20^{\circ}\text{C}|} = \frac{1}{234.5 + 20} = \frac{1}{254.5} = 0.003929 \equiv 0.00393$$

$$\text{b. } R = R_{20}[1 + \alpha_{20}(t - 20^{\circ}\text{C})]$$

$$\begin{aligned} 1\Omega &= 0.8\Omega [1 + 0.00393(t - 20^{\circ})] \\ 1.25 &= 1 + 0.00393(-0.0786) \\ 1.25 - 0.9214 &= 0.00393t \end{aligned}$$

$$0.3286 = 0.00393t$$

$$t = \frac{0.3286}{0.00393} = 83.61^{\circ}\text{C}$$

$$26. \quad R = R_{20}[1 + \alpha_{20}(t - 20^{\circ}\text{C})] \\ = 0.4\Omega [1 + 0.00393(16 - 20)] = 0.4\Omega [1 - 0.01572] = 0.39\Omega$$

$$27. \quad \text{Table: } 1000' \text{ of } \#12 \text{ copper wire} = 1.588 \Omega @ 20^{\circ}\text{C}$$

$$\begin{aligned} \text{C}^{\circ} &= \frac{5}{9}(F^{\circ} - 32) = \frac{5}{9}(115 - 32) = 46.11^{\circ}\text{C} \\ R &= R_{20}[1 + \alpha_{20}(t - 20^{\circ}\text{C})] \\ &= 1.588\Omega [1 + 0.00393(46.11 - 20)] \\ &= 1.75\Omega \end{aligned}$$

$$28. \quad \Delta R = \frac{R_{\text{nominal}}}{10^6} (\text{PPM})(\Delta T) = \frac{22\Omega}{10^6} (100)(50^{\circ} - 20^{\circ}) = 0.198\Omega$$

$$R = R_{\text{nominal}} + \Delta R = 22.198\Omega$$

$$29. \quad \Delta R = \frac{R_{\text{nominal}}}{10^6} (\text{PPM})(\Delta T) = \frac{100\Omega}{10^6} (100)(50^{\circ} - 20^{\circ}) = 0.30\Omega$$

$$R = R_{\text{nominal}} + \Delta R = 100\Omega + 0.30\Omega = 100.30\Omega$$

$$30. \quad \text{a. } 2 \text{ times larger}$$

$$\text{b. } 4 \text{ times larger}$$

$$31. \quad 10k - 3.5k = 6.5k\Omega$$

$$32. \quad 6.25\text{ k}\Omega \text{ and } 18.75\text{ k}\Omega$$

$$33. \quad -$$

$$34. \quad \text{a. } 820\Omega \pm 5\%, 820\Omega \pm 41\Omega, 779\Omega \leftrightarrow 861\Omega$$

$$\text{b. } 220\Omega \pm 10\%, 220\Omega \pm 22\Omega, 198\Omega \leftrightarrow 242\Omega$$

$$\text{c. } 91\text{k}\Omega \pm 20\%, 91\text{k}\Omega \pm 18.2\text{k}\Omega, 77.8\text{k}\Omega \leftrightarrow 109.2\text{k}\Omega$$

$$\text{d. } 9.1\text{k}\Omega \pm 5\%, 9100\Omega \pm 455\Omega, 8.645\Omega \leftrightarrow 9.555\text{k}\Omega$$

$$\text{e. } 3.9\text{ M}\Omega \pm 20\%, 3.9\text{ M}\Omega \pm 0.78\text{ M}\Omega, 3.12\text{ M}\Omega \leftrightarrow 4.68\text{ M}\Omega$$

$$35. \quad \text{a. } 68\Omega = \text{Blue, Gray, Black, Silver}$$

$$\text{b. } 0.33\Omega = \text{Orange, Orange, Silver, Silver}$$

$$\text{c. } 22\text{k}\Omega = \text{Red, Red, Orange, Silver}$$

$$\text{d. } 5.6\text{ M}\Omega = \text{Green, Blue, Green, Silver}$$

$$36. \quad \text{a. } 10\Omega \pm 20\% \Rightarrow 8\Omega - 12\Omega \quad \left. \begin{array}{l} \text{b. } 15\Omega \pm 20\% \Rightarrow 12\Omega - 18\Omega \end{array} \right\} \text{ no overlap, continuation}$$

$$\text{b. } 10\Omega \pm 10\% \Rightarrow 9\Omega - 11\Omega \quad \left. \begin{array}{l} \text{c. } 15\Omega \pm 10\% \Rightarrow 13.5\Omega - 16.5\Omega \end{array} \right\} \text{ no overlap}$$

$$37. \quad 470\Omega \pm 10\% = 470\Omega \pm 47\Omega$$

$$= 423\Omega \leftrightarrow 517\Omega$$

$$\text{Yes}$$

$$\text{38. No change}$$

39. a.  $621 = 62 \times 10^3 \Omega = 620 \Omega = 0.62 \text{ k}\Omega$   
 b.  $333 = 33 \times 10^3 \Omega = 33 \text{ k}\Omega$   
 c.  $Q_2 = 3.9 \times 10^2 \Omega = 390 \Omega$   
 d.  $C_6 = 1.2 \times 10^6 \Omega = 1.2 \text{ M}\Omega$

40. a.  $G = \frac{1}{R} = \frac{1}{120 \Omega} = 8.33 \text{ mS}$

b.  $G = \frac{1}{4 \text{k}\Omega} = 0.25 \text{ mS}$

c.  $G = \frac{1}{2.2 \text{ M}\Omega} = 0.46 \mu\text{S}$

$G_a > G_b > G_c$  vs.  $R_c > R_b > R_a$

41. a. Table 3.2,  $\Omega/1000' = 1.588 \Omega$

$$G = \frac{1}{R} = \frac{1}{1.588 \Omega} = 629.72 \text{ mS}$$

$$\text{or } G = \frac{A}{pl} = \frac{6529.9 \text{ CM (Table 3.2)}}{(10.37)(1000')} = 629.69 \text{ mS (Cu)}$$

b.  $G = \frac{6529.9 \text{ CM}}{(17)(1000')} = 384.11 \text{ mS (Al)}$

- c. increases  
d. decreases

42. a.  $G_1 = \frac{1}{10 \Omega} = 100 \text{ mS}, G_2 = \frac{1}{20 \Omega} = 50 \text{ mS}, G_3 = \frac{1}{100 \Omega} = 10 \text{ mS}$

- b.  $G_2/G_1 = 50 \text{ mS}/100 \text{ mS} = 1:2$  whereas  $R_2/R_1 = 20 \Omega/10 \Omega = 2:1$ . The rate of change is the same although one is increasing and the other decreasing.

- c. inverse - linear

43.  $A_2 = \frac{1}{3} A_1 = \frac{5}{3} A_1, l_2 = \left(1 - \frac{2}{3}\right) l_1 = \frac{1}{3}, \rho_2 = \rho_1$

$$\frac{G_1}{G_2} = \frac{\rho_1 \frac{A_1}{l_1}}{\rho_2 \frac{A_2}{l_2}} = \frac{\rho_1 \frac{1}{3} A_1}{\rho_2 \frac{5}{3} A_1} = \frac{1}{5}$$

$G_2 = 5G_1 = 5(100 \text{ S}) = 500 \text{ S}$

44. -

45. -

46. -

47. -

48.  $\frac{1}{12} \text{ in.} = 0.083 \lambda n \left( \frac{2.54 \text{ cm}}{\lambda n} \right) = 0.21 \text{ cm}$

$$A = \frac{\pi d^2}{4} = \frac{(3.14)(0.21 \text{ cm})^2}{4} = 0.035 \text{ cm}^2$$

$$l = \frac{R}{\rho} = \frac{(2 \Omega)(0.035 \text{ cm}^2)}{1.724 \times 10^{-6}} = 40,603 \text{ cm} = 406.03 \text{ m}$$

49. a.  $\frac{1''}{2} \left[ \frac{2.54 \text{ cm}}{1''} \right] = 1.27 \text{ cm}, 3 \text{ in.} \left[ \frac{2.54 \text{ cm}}{1 \text{ in.}} \right] = 7.62 \text{ cm}$

$$4 \text{ in.} \left[ \frac{2 \text{ in.}}{1 \text{ in.}} \right] \left[ \frac{2.54 \text{ cm}}{1 \text{ in.}} \right] = 121.92 \text{ cm}$$

$$R = \rho \frac{l}{A} = \frac{l (1.724 \times 10^{-6} \Omega)(121.92 \text{ cm})}{(1.27 \text{ cm})(7.62 \text{ cm})} = 21.71 \mu\Omega$$

b.  $R = \rho \frac{l}{A} = \frac{(2.825 \times 10^{-6} \Omega)(121.92 \text{ cm})}{(1.27 \text{ cm})(7.62 \text{ cm})} = 35.59 \mu\Omega$

- c. increases

- d. decreases

50.  $R_s = \frac{\rho}{d} = 100 \Rightarrow d = \frac{\rho}{100} = \frac{250 \times 10^{-6}}{100} = 2.5 \mu\text{m}$

51.  $R = R_s \frac{l}{w} \Rightarrow w = \frac{R_s l}{R} = \frac{(150 \Omega)(1/2 \text{ in.})}{500 \Omega} = 0.15 \text{ in.}$

52. a.  $d = 1 \text{ in.} = 1000 \text{ mils}$

$$A_{CM} = (10^3 \text{ mils})^2 = 10^6 \text{ CM}$$

$$\rho_1 = \frac{Ra}{l} = \frac{(1 \text{ m}\Omega)(10^6 \text{ CM})}{10^3 \text{ ft}} = 1 \text{ CM}\cdot\Omega/\text{ft}$$

b.  $1 \text{ in.} = 2.54 \text{ cm}$

$$A = \frac{\pi d^2}{4} = \frac{\pi (2.54 \text{ cm})^2}{4} = 5.067 \text{ cm}^2$$

$$l = 1000 \text{ ft} \left[ \frac{2 \text{ in.}}{1 \text{ ft}} \right] \left[ \frac{2.54 \text{ cm}}{1 \text{ in.}} \right] = 30,480 \text{ cm}$$

$$\rho_2 = \frac{Ra}{l} = \frac{(1 \text{ m}\Omega)(5.067 \text{ cm}^2)}{30,480 \text{ cm}} = 1.66 \times 10^{-7} \Omega\cdot\text{cm}$$

c.  $k = \frac{P_2}{R_1} = \frac{1.66 \times 10^{-7} \Omega\text{-cm}}{1 \text{ CM}\cdot\Omega/\text{A}} = 1.66 \times 10^{-7}$

53. -

54. -

55. -

56. -

57. -

58. a.  $-50^\circ\text{C}$  specific resistance  $\equiv 10^3 \Omega\text{-cm}$   
 $50^\circ\text{C}$  specific resistance  $\equiv 500 \Omega\text{-cm}$   
 $200^\circ\text{C}$  specific resistance  $\equiv 7 \Omega\text{-cm}$

b. negative

c. No

d.  $\rho = \frac{\Delta Q - \text{cm}}{\Delta T} = \frac{300 - 30}{125 - 50} = \frac{270 \Omega\text{-cm}}{75^\circ\text{C}} \equiv 3.6 \Omega\text{-cm}^\circ\text{C}$

59. a. Log scale:

10 fc  $\Rightarrow 3 \text{k}\Omega$

b. negative

100 fc  $\Rightarrow 0.4 \text{k}\Omega$

c. no—log scales imply linearity

1 k $\Omega$   $\Rightarrow 30 \text{fc}$

10 k $\Omega$   $\Rightarrow 2 \text{fc}$

$$\left| \frac{\Delta R}{\Delta f} \right| = \frac{10 \text{k}\Omega - 1 \text{k}\Omega}{30 \text{fc} - 2 \text{fc}} = 321.43 \Omega/\text{fc}$$

$$\text{and } \frac{\Delta R}{\Delta f} = 321.43 \Omega/\text{fc}$$

a. @ 0.5 mA,  $V \equiv 195 \text{V}$


@ 1 mA,  $V \equiv 200 \text{V}$

@ 5 mA,  $V \equiv 215 \text{V}$

b.  $\Delta V_{\text{total}} = 215 \text{V} - 195 \text{V} = 20 \text{V}$

c. 5 mA/0.5 mA = 10:1

215 V/200 V = 1.08:1

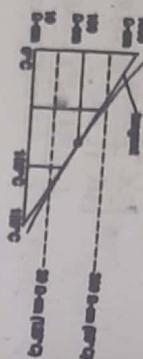

## Chapter 4

1.  $V = IR = (5.6 \text{ mA})(220 \Omega) = 1.23 \text{ V}$

2.  $I = \frac{V}{R} = \frac{24 \text{ V}}{2.2 \text{ k}\Omega} = 10.91 \text{ mA}$

3.  $R = \frac{V}{I} = \frac{24 \text{ V}}{1.5 \text{ mA}} = 16 \text{ k}\Omega$

4.  $I = \frac{V}{R} = \frac{12 \text{ V}}{40 \times 10^3 \Omega} = 300 \text{ A}$

5.  $V = IR = (3.6 \mu\text{A})(100 \text{ k}\Omega) = 0.36 \text{ V} = 360 \text{ mV}$

6.  $I = \frac{V}{R} = \frac{120 \text{ V}}{50 \text{ k}\Omega} = 2.4 \text{ mA}$

7.  $R = \frac{V}{I} = \frac{120 \text{ V}}{2.2 \text{ A}} = 54.55 \Omega$

8.  $I = \frac{V}{R} = \frac{120 \text{ V}}{8 \text{ k}\Omega} = 15 \text{ mA}$

9.  $R = \frac{V}{I} = \frac{120 \text{ V}}{4.2 \text{ A}} = 28.57 \Omega$

10.  $R = \frac{V}{I} = \frac{4.5 \text{ V}}{80 \text{ mA}} = 56.25 \Omega$

11.  $R = \frac{V}{I} = \frac{24 \text{ mV}}{20 \mu\text{A}} = 1.2 \text{ k}\Omega$

12.  $V = IR = (12 \text{ A})(0.5 \Omega) = 6 \text{ V}$

13. a.  $R = \frac{V}{I} = \frac{120 \text{ V}}{9.5 \text{ A}} = 12.63 \Omega$

b.

$$W = P_t = VIt^2 \\ = (120 \text{ V})(9.5 \text{ A})(7200 \text{ s}) \\ = 8.21 \times 10^6 \text{ J}$$

14.  $V_{\text{avg}}/R = (5.6 \text{ mA})(3.3 \text{ M}\Omega) = 18.48 \text{ V}$

15. -

16.

$$I = \frac{P}{V} = \frac{1 \text{ W}}{4.7 \text{ mV}} = 461.27 \mu\text{A}$$

17.

$$I = \frac{P}{V} = \frac{100 \text{ W}}{120 \text{ V}} = 0.833 \text{ A}$$

18.

$$I = \frac{P}{V} = \frac{(42 \text{ mW})(2.2 \text{ k}\Omega)}{\sqrt{PR}} = \sqrt{92.40} = 9.61 \text{ V}$$

19.

$$I = \frac{W}{t} = \frac{540 \text{ J}}{3.6 \text{ min}} = \frac{540 \text{ J}}{216 \text{ s}} = 2.5 \text{ W}$$

20.

$$I = \frac{W}{t} = \frac{60 \text{ s}}{1 \text{ min}} = 60 \text{ s}$$

$$I = \frac{W}{P} = \frac{640 \text{ J}}{40 \text{ J/s}} = 16 \text{ s}$$

$$R = \frac{V}{I} = \frac{120 \text{ V}}{0.833 \text{ A}} = 144.06 \Omega$$

21.

$$I = \frac{P}{V} = \frac{450 \text{ W}}{120 \text{ V}} = 3.75 \text{ A}$$

22.

$$I = \frac{W}{P} = \frac{12 \text{ J}}{8 \text{ W}} = 1.5 \text{ J}$$

23.

$$P = VI = (3 \text{ V})(14 \text{ A}) = 42.0 \text{ W}$$

$$I = \frac{W}{P} = \frac{12 \text{ J}}{4.2 \text{ W}} = 2.86 \text{ s}$$

$$W = Pt = (8 \text{ W})(28,000 \text{ s}) = 224 \text{ kJ}$$

24.

$$P = EI = (12 \text{ V})(40 \text{ A}) = 480 \text{ W}$$

$$P = I^2 R = (7.2 \text{ mA})^2 4 \text{ k}\Omega = 207.36 \text{ mW}$$

$$P = I^2 R \Rightarrow I = \sqrt{\frac{P}{R}} = \sqrt{\frac{240 \text{ mW}}{2.2 \text{ k}\Omega}} = 10.44 \text{ mA}$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{2 \text{ W}}{82 \Omega}} = 156.17 \text{ mA}$$

$$V = IR = (156.17 \text{ mA})(82 \Omega) = 12.81 \text{ V}$$

$$I = \frac{E}{R} = \frac{22 \text{ V}}{16.8 \text{ k}\Omega} = 1.31 \text{ mA}$$

$$P = I^2 R = (1.31 \text{ mA})^2 16.8 \text{ k}\Omega = 28.83 \text{ mW}$$

$$W = Pt = (28.83 \text{ mW}) \left( 1 \text{ h} \left[ \frac{60 \text{ min}}{1 \text{ h}} \right] \left[ \frac{60 \text{ s}}{1 \text{ min}} \right] \right) = 103.79 \text{ J}$$

$$E = \frac{P}{I} = \frac{10 \text{ kW}}{48 \text{ A}} = 208.33 \text{ V}$$

$$30. \quad I = \sqrt{\frac{P}{R}} = \sqrt{\frac{1 \text{ W}}{4.7 \text{ mV}}} = 461.27 \mu\text{A}$$

no

$$31. \quad V = \sqrt{PR} = \sqrt{(42 \text{ mW})(2.2 \text{ k}\Omega)} = \sqrt{92.40} = 9.61 \text{ V}$$

$$32. \quad P = VI, I = \frac{P}{V} = \frac{100 \text{ W}}{120 \text{ V}} = 0.833 \text{ A}$$

$$R = \frac{V}{I} = \frac{120 \text{ V}}{0.833 \text{ A}} = 144.06 \Omega$$

$$33. \quad V = \frac{P}{I} = \frac{450 \text{ W}}{3.75 \text{ A}} = 120 \text{ V}$$

$$R = \frac{V}{I} = \frac{120 \text{ V}}{3.75 \text{ A}} = 32 \Omega$$

34.

$$\text{a. } P = EI \text{ and } I = \frac{P}{E} = \frac{0.4 \times 10^{-3} \text{ W}}{3 \text{ V}} = 0.13 \text{ mA}$$

$$\text{b. Ah rating} = (0.13 \text{ mA})(500 \text{ h}) = 66.5 \text{ mA}$$

$$35. \quad I = \sqrt{\frac{P}{R}} = \sqrt{\frac{100 \text{ W}}{20 \text{ k}\Omega}} = \sqrt{5 \times 10^{-3}} = 70.71 \text{ mA}$$

$$V = \sqrt{PR} = \sqrt{(100 \text{ W})(20 \text{ k}\Omega)} = 1.42 \text{ kV}$$

$$36. \quad P = EI = (240 \text{ V})(30 \text{ A}) = 7.2 \text{ kW}$$

$$P_{\text{HP}} = \frac{7.2 \text{ kW}}{746 \text{ W/HP}} = 9.65 \text{ hP}$$

$$37. \quad \text{a. } W = Pt = \left( \frac{V^2}{R} \right) t = \left( \frac{12 \text{ V}}{10 \Omega} \right)^2 60 \text{ s} = 86.4 \text{ J}$$

b. Energy doubles, power the same

$$38. \quad W = Pt \Rightarrow t = \frac{W}{P} = \frac{12 \times 10^3 \text{ Wh}}{1500 \text{ W}} = 8 \text{ h}$$

$$39. \quad \frac{12 \text{ h}}{1 \text{ week}} \left[ \frac{1 \text{ week}}{1 \text{ month}} \right] [5 \text{ months}] = 260 \text{ h}$$

$$\text{kWh} = \frac{(230 \text{ W})(260 \text{ h})}{1000} = 59.80 \text{ kWh}$$

40. a.  $W = P_t = (60 \text{ W})(10 \text{ h}) \left( \frac{60 \text{ min}}{1 \text{ h}} \right) \left( \frac{60 \text{ s}}{1 \text{ min}} \right) = 2.16 \times 10^6 \text{Ws}$

b.  $1 \text{ Wh} = 1 \text{ J} \therefore 2.16 \times 10^6 \text{ J}$

c.  $W = Pt = (60 \text{ W})(10 \text{ h}) = 600 \text{ Wh}$

d.  $\frac{600 \text{ Wh}}{1000 \text{ Wh}/\text{kWh}} = 0.6 \text{ kWh}$

e. Cost =  $(0.6 \text{ kWh})(12 \text{ ¢/kWh}) = 7.2 \text{ ¢}$

41. a.  $\text{kWh} = \frac{Pt}{1000} \Rightarrow P = \frac{(1000)(\text{kWh})}{t} = \frac{(1000)(1200 \text{ kWh})}{10 \text{ h}} = 120 \text{ kW}$

b.  $I = \frac{P}{E} = \frac{120 \times 10^3 \text{ Wh}}{240 \text{ V}} = 500 \text{ A}$

c.  $P_{\text{load}} = P_i - P_o = P_i - \eta P_i = P_i(1 - \eta) = 120 \text{ kW}(1 - 0.76) = 28.8 \text{ kW}$

$\text{kWh}_{\text{load}} = \frac{P_i}{1000} = \frac{(28.8 \text{ kW})(10 \text{ h})}{1000} = 288 \text{ kWh}$

42. #kWh =  $\frac{\$1.00}{12 \text{ ¢}} = 8.33$

$\text{kWh} = \frac{Pt}{1000} \Rightarrow t = \frac{(\text{kWh})(1000)}{P} = \frac{(8.33)(1000)}{250 \text{ W}} = 33.32 \text{ h}$

43. a.  $\frac{\$120}{30 \text{ days}} = \$4/\text{day}$

b.  $\frac{\$4/\text{day}}{15 \text{ h/day}} = 26.7 \text{ ¢/h}$

c.  $\frac{26.7 \text{ ¢/h}}{12 \text{ ¢/kWh}} = 2.23 \text{ kW}$

d.  $\frac{2.23 \text{ kW}}{60 \text{ W}} = 37.17 \equiv 37 \text{ bulbs}$

e. no

44.  $\frac{\$1.00}{12 \text{ ¢/kWh}} = 8.33 \text{ kWh}$

$$\frac{8.33 \text{ kWh}}{187 \text{ W}} = 44.55 \text{ h}$$

45.  $t = 5 \text{ h/day}(365 \text{ days}) = 1825 \text{ h}$

$\text{kWh} = \frac{P \cdot t}{1000} = \frac{(339 \text{ W})(1825 \text{ h})}{1000} = 618.68 \text{ kWh}$

Cost =  $(618.68 \text{ kWh})(12 \text{ ¢/kWh}) = \$74.24$

$\text{kWh} = \frac{P \cdot t}{1000} = \frac{(213 \text{ W})(1825 \text{ h})}{1000} = 388.73 \text{ kWh}$

Cost =  $(388.73 \text{ kWh})(12 \text{ ¢/kWh}) = \$46.65$

Cost Savings =  $\$74.24 - \$46.65 = \$27.59$

46.  $\text{kWh} = \frac{P \cdot t}{1000} = \frac{(78 \text{ W})(4 \text{ h/day})(31 \text{ days})}{1000} = 9.67 \text{ kWh}$

Cost =  $(12 \text{ ¢/kWh})(9.67 \text{ kWh}) = \$1.16$

47. a.  $P = EI = (120 \text{ V})(100 \text{ A}) = 12 \text{ kW}$

b.  $P_T = 2(250 \text{ W}) + 3000 \text{ W} + (10)(60 \text{ W}) + 2400 \text{ W} + 2 \text{ kW} + 1000 \text{ W} = 9.5 \text{ kW}$   
Yes, 12 kW > 9.5 kW

c.  $W = Pt = (9.5 \text{ kW})(2 \text{ h}) = 19 \text{ kW}$

48.  $\text{kWh} = \frac{(1600 \text{ W})(8 \text{ h}) + (1200 \text{ W})(1/3 \text{ h}) + (4800 \text{ W})(1 \text{ h}) + (900 \text{ W})(1/4 \text{ h}) + (200 \text{ W})(1.2 \text{ h}) + (50 \text{ W})(3.5 \text{ h})}{1000}$

$= \frac{12,800 \text{ Wh} + 400 \text{ Wh} + 4800 \text{ Wh} + 225 \text{ Wh} + 240 \text{ Wh} + 175 \text{ Wh}}{1000} = 18.64 \text{ kWh}$

$(18.64 \text{ kWh})(12 \text{ ¢/kWh}) = \$2.24$

49.  $\text{kWh} = \frac{(200 \text{ W})(4 \text{ h}) + (6)(60 \text{ W})(6 \text{ h}) + (1200 \text{ W})(0.5 \text{ h}) + (175 \text{ W})(3.5 \text{ h}) + (250 \text{ W})\left(\frac{4}{3} \text{ h}\right) + (30 \text{ W})(8 \text{ h})}{1000}$

$= \frac{800 \text{ Wh} + 2160 \text{ Wh} + 600 \text{ Wh} + 612.5 \text{ Wh} + 1083.32 \text{ Wh} + 240 \text{ Wh}}{1000} = 5.496 \text{ kWh}$

$= \frac{5.496 \text{ kWh}}{12 \text{ ¢/kWh}} = 65.95 \text{ ¢}$

50.  $\eta = \frac{P_o}{P_i} \times 100\% = \frac{(0.5 \text{ hp}) \left[ \frac{46 \text{ W}}{\text{hp}} \right]}{410 \text{ W}} \times 100\% = \frac{3/73}{410} \times 100\% = 90.98\%$

51.  $\eta = \frac{P_o}{P_i}, P_i = \frac{P_o}{\eta} = \frac{(1.8 \text{ hp})(746 \text{ W}/\text{hp})}{0.72} = 1865 \text{ W}$

$P_i = EI, I = \frac{P_i}{E} = \frac{1865 \text{ W}}{120 \text{ V}} = 15.54 \text{ A}$

52.  $\eta = \frac{P_o}{P_i} \times 100\% = \frac{(0.81 \text{ hp})(746 \text{ W}/\text{hp})}{(4 \text{ A})(220 \text{ V})} \times 100\% = \frac{686.65}{880} \times 100\% = 78.03\%$

53.

a.  $P_i = EI = (120 \text{ V})(1.8 \text{ A}) = 216 \text{ W}$   
 $P_i = P_o + P_{\text{load}}, P_{\text{load}} = P_i - P_o = 216 \text{ W} - 50 \text{ W} = 166 \text{ W}$

b.  $\eta\% = \frac{P_o}{P_i} \times 100\% = \frac{50 \text{ W}}{216 \text{ W}} \times 100\% = 23.15\%$

54.  $P_i = EI = \frac{P_o}{\eta} \Rightarrow I = \frac{P_o}{\eta E} = \frac{(3.6 \text{ kip})(746 \text{ W/kip})}{(0.76)(240 \text{ V})} = 14.72 \text{ A}$

55. a.  $P_i = \frac{P_o}{\eta} = \frac{(2 \text{ kip})(746 \text{ W/kip})}{0.9} = 1657.78 \text{ W}$

b.  $P_i = EI = 1657.78 \text{ W}$   
 $(110 \text{ V})I = 1657.78 \text{ W}$

$$I = \frac{1657.78 \text{ W}}{120 \text{ V}} = 13.81 \text{ A}$$

c.  $P_i = \frac{P_o}{\eta} = \frac{(2 \text{ kip})(746 \text{ W/kip})}{0.7} = 2131.43 \text{ W}$   
 $P_i = EI = 2131.43 \text{ W}$   
 $(120 \text{ V})I = 2131.43 \text{ W}$

$$I = \frac{2131.43 \text{ W}}{120 \text{ V}} = 17.76 \text{ A}$$

56.  $P_i = \frac{P_o}{\eta} = \frac{(15 \text{ kip})(746 \text{ W/kip})}{(0.84)} = 13,321 \text{ W}$

$$I = \frac{P_i}{E} = \frac{13,321 \text{ W}}{240 \text{ V}} = 55.5 \text{ A}$$

57.  $\eta_T = \eta_1 \cdot \eta_2$   
 $0.75 = 0.85 \times \eta_2$   
 $\eta_2 = 0.88, \eta_2 = 88\%$

58.  $\eta_T = \eta_1 \cdot \eta_2 = (0.87)(0.75) = 0.6525 \Rightarrow 65.25\%$

59.  $\eta_T = \eta_1 \cdot \eta_2 = 0.78 = 0.9\eta_2$   
 $\eta_2 = \frac{0.78}{0.9} = 0.867 \Rightarrow 86.7\%$

# Chapter 5

- 1.**
- a.  $E$  and  $R_1$
  - b.  $R_1$  and  $R_2$
  - c.  $E_1, E_2$ , and  $R_1$
  - d.  $E$  and  $R_1$ ;  $R_3, R_4$ , and  $R_5$
- 2.**
- a.  $E_1$  and  $R_1$ ;  $E_2, R_3$ , and  $R_4$
  - b.  $E_1$  and  $R_1$ ;  $R_3$  and  $R_6$
  - c.  $R_2$  and  $R_3$
  - d.  $E_1$  and  $R_1$
- 3.**
- a.  $R_T = 0.1 \text{ k}\Omega + 0.39 \text{ k}\Omega + 1.2 \text{ k}\Omega + 6.8 \text{ k}\Omega = 8.49 \text{ k}\Omega$
  - b.  $R_T = 1.2 \Omega + 2.7 \Omega + 8.2 \Omega = 12.1 \Omega$
  - c.  $R_T = 1.2 \Omega + 2.2 \Omega + 3.3 \Omega + 4.7 \Omega = 11.4 \Omega$
- 4.**
- a.  $R_T = 8.2 \text{ k}\Omega + 10 \text{ k}\Omega + 9.1 \text{ k}\Omega + 1.8 \text{ k}\Omega + 2.7 \text{ k}\Omega = 31.8 \text{ k}\Omega$
  - b.  $R_T = 47 \Omega + 820 \Omega + 91 \Omega + 1.2 \text{ k}\Omega = 2158.0 \Omega$
  - c.  $R_T = 3.3 \Omega + 10 \text{ k}\Omega = 13.3 \text{ k}\Omega$
- 5.**
- a.  $R_T = 1.2 \text{ k}\Omega + 1 \text{ k}\Omega + 2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega = 7.7 \text{ k}\Omega$
  - b.  $R_T = 1 \text{ k}\Omega + 2 \text{ k}\Omega + 3 \text{ k}\Omega + 4.7 \text{ k}\Omega + 6.8 \text{ k}\Omega = 17.5 \text{ k}\Omega$
- 6.**
- a. **1 MΩ**
  - b. **100 Ω, 1 kΩ**
  - c.  $R_T = 100 \Omega + 1 \text{ k}\Omega + 1 \text{ M}\Omega + 200 \text{ k}\Omega = 1.2011 \text{ M}\Omega$  vs. **1.2 MΩ** for part b.
- 7.**
- a. Reading =  $10 \Omega + 33 \Omega + 56 \Omega + 68 \Omega = 167 \Omega$
  - b. Reading =  $0.82 \text{ k}\Omega + 1.2 \text{ k}\Omega + 3.3 \text{ k}\Omega = 5.32 \text{ k}\Omega$
- 8.**
- a.  $R_T = 129 \text{ k}\Omega = R + 56 \text{ k}\Omega + 22 \text{ k}\Omega + 33 \text{ k}\Omega$ , Reading = **18 kΩ**
  - b.  $R_T = 103 \text{ k}\Omega = 24 \text{ k}\Omega + R_1 + 43 \text{ k}\Omega + 2R_1 = 67 \text{ k}\Omega + 3R_1$ ,  $R_1 = 12 \text{ k}\Omega$
  - c.  $R_2 = 24 \text{ k}\Omega$
- 9.**
- a.  $1.2 \text{ k}\Omega + 2.2 \text{ k}\Omega = 3.4 \text{ k}\Omega$
  - b. **0 Ω**
  - c. **∞ Ω**
- 10.**
- a.  $R_T = 10 \Omega + 12 \Omega + 18 \Omega = 40 \Omega$
  - b.  $I_s = \frac{E}{R_s} = \frac{72 \text{ V}}{40 \Omega} = 1.8 \text{ A}$
  - c.  $V_1 = I_1 R_1 = (1.8 \text{ A})(10 \Omega) = 18 \text{ V}$
  - d.  $V_3 = I_3 R_3 = (1.8 \text{ A})(18 \Omega) = 32.4 \text{ V}$
  - e.  $P_s = E I_s = (72 \text{ V})(1.8 \text{ A}) = 129.6 \text{ W}$
  - f.  $P_{18\Omega} = V_2 I_3 = (32.4 \text{ V})(1.8 \text{ A}) = 58.32 \text{ W}$
- 11.**
- a. the most:  $R_3$ , the least:  $R_1$ .
  - b.  $R_3, R_T = 1.2 \text{ k}\Omega + 6.8 \text{ k}\Omega + 82 \text{ k}\Omega = 90 \text{ k}\Omega$
- $$I_s = \frac{E}{R_s} = \frac{45 \text{ V}}{90 \text{ k}\Omega} = 0.5 \text{ mA}$$
- c.**
- $$V_1 = I_1 R_1 = (0.5 \text{ mA})(1.2 \text{ k}\Omega) = 0.6 \text{ V}, V_2 = I_2 R_2 = (0.5 \text{ mA})(6.8 \text{ k}\Omega) = 3.4 \text{ V},$$
- $$V_3 = I_3 R_3 = (0.5 \text{ mA})(82 \text{ k}\Omega) = 41 \text{ V}, \text{ results agree with part (a)}$$
- d.**
- $$P_s = E I_s = (72 \text{ V})(1.8 \text{ A}) = 129.6 \text{ W}$$
- e.**
- $$P_{18\Omega} = V_2 I_3 = (32.4 \text{ V})(1.8 \text{ A}) = 58.32 \text{ W}$$
- f.**
- $$E = I_s R_T = (4 \text{ mA})(22 \text{ k}\Omega) = 88 \text{ V}$$
- $$R_T = 12 \Omega + 22 \Omega + 82 \Omega + 10 \Omega = 126 \Omega$$
- $$E = I_s R_T = (500 \text{ mA})(126 \Omega) = 63 \text{ V}$$
- 12.**
- a.  $R_T = 12 \text{ k}\Omega + 4 \text{ k}\Omega + 6 \text{ k}\Omega = 22 \text{ k}\Omega$
  - b.  $R_T = 12 \Omega + 22 \Omega + 82 \Omega + 10 \Omega = 126 \Omega$
- 13.**
- |   |   |   |
|---|---|---|
| I.  | II.   | III.  |
| a. $I = \frac{V}{R} = \frac{5.2 \text{ V}}{13 \Omega} = 4 \text{ A}$                        | a. $I = \frac{V}{R} = \frac{6.6 \text{ V}}{22 \text{ k}\Omega} = 3 \text{ mA}$              | a. $I = \frac{V}{R} = \frac{9 \text{ V}}{3 \text{ mA}} = 3 \text{ k}\Omega$                 |
| b. $V_{33\Omega} = (3 \text{ mA})(3.3 \text{ k}\Omega) = 9.9 \text{ V}$                     | b. $E = 6.6 \text{ V} + 9 \text{ V} + 9.9 \text{ V} = 25.5 \text{ V}$                       | b. $R = \frac{V}{I} = \frac{9 \text{ V}}{3 \text{ mA}} = 3 \text{ k}\Omega$                 |
| c. $V_{21\Omega} = 6.6 \text{ V}, V_{33\Omega} = 9 \text{ V}, V_{55\Omega} = 9.9 \text{ V}$ | c. $V_{21\Omega} = 6.6 \text{ V}, V_{33\Omega} = 9 \text{ V}, V_{55\Omega} = 9.9 \text{ V}$ | c. $V_{21\Omega} = 6.6 \text{ V}, V_{33\Omega} = 9 \text{ V}, V_{55\Omega} = 9.9 \text{ V}$ |
- 14.**
- a.  $I_m = \frac{E}{R_T} = \frac{36 \text{ V}}{4.4 \text{ k}\Omega} = 8.18 \text{ mA}, V_m = \frac{1}{2} E = \frac{1}{2} (36 \text{ V}) = 18 \text{ V}$
  - b.  $R_T = 1 \text{ k}\Omega + 2.4 \text{ k}\Omega + 5.6 \text{ k}\Omega = 9 \text{ k}\Omega$
- $$I_m = \frac{E}{R_T} = \frac{22.5 \text{ V}}{9 \text{ k}\Omega} = 2.5 \text{ mA}, V_m = 2.5 \text{ mA}(2.4 \text{ k}\Omega + 5.6 \text{ k}\Omega) = 20 \text{ V}$$

15. a.  $I = \frac{10 \text{ V}}{30 \Omega} = 0.333 \text{ A}$   
 $V = 0 \text{ V}$

b.  $I = 0 \text{ A}, V = IR = \frac{80 \text{ V}}{60 \Omega} = 5.33 \text{ V}$

16. a.  $R_T = 3 \text{ k}\Omega + 1 \text{ k}\Omega + 2 \text{ k}\Omega = 6 \text{ k}\Omega$   
 $I_t = \frac{E}{R_T} = \frac{120 \text{ V}}{6 \text{ k}\Omega} = 20 \text{ mA}$

$V_{R_1} = (20 \text{ mA})(3 \text{ k}\Omega) = 60 \text{ V}$   
 $V_{R_2} = (20 \text{ mA})(1 \text{ k}\Omega) = 20 \text{ V}$   
 $V_{R_3} = (20 \text{ mA})(2 \text{ k}\Omega) = 40 \text{ V}$

b.  $P_{R_1} = I_t^2 R_1 = (20 \text{ mA})^2 \cdot 3 \text{ k}\Omega = 1.2 \text{ W}$

$P_{R_2} = I_t^2 R_2 = (20 \text{ mA})^2 \cdot 1 \text{ k}\Omega = 0.4 \text{ W}$

$P_{R_3} = I_t^2 R_3 = (20 \text{ mA})^2 \cdot 2 \text{ k}\Omega = 0.8 \text{ W}$

c.  $P_T = P_{R_1} + P_{R_2} + P_{R_3} = 1.2 \text{ W} + 0.4 \text{ W} + 0.8 \text{ W} = 2.4 \text{ W}$

d.  $P_T = EI_t = (120 \text{ V})(20 \text{ mA}) = 2.4 \text{ W}$

e. the same

f.  $R_1$  - the largest

g. dissipated

h.  $R_1: 2 \text{ W}, R_2: 1/2 \text{ W}, R_3: 1 \text{ W}$

17. a.  $P = (I \text{ A})^2 R, R = 21 \Omega$   
 $V_1 = I_1 R_1 = (1 \text{ A})(2 \Omega) = 2 \text{ V}, V_2 = I_2 R_2 = (1 \text{ A})(1 \Omega) = 1 \text{ V}$   
 $V_3 = I_3 R_3 = (1 \text{ A})(21 \Omega) = 21 \text{ V}$   
 $V_4 = V_1 + V_2 + V_3 = 2 \text{ V} + 1 \text{ V} + 21 \text{ V} = 24 \text{ V}$

18. a.  $P = 8 \text{ W} = I^2 R, I = \sqrt{8} = 2.828 \text{ A}$   
 $P = 16 \text{ W} = I^2 R_1 = (2.828 \text{ A})^2 R_1, R_1 = 2 \Omega$   
 $R_T = 32 \Omega = 2 \Omega + R_2 + 1 \Omega = 3 \Omega + R_2, R_2 = 29 \Omega$   
 $E = IR_T = (2.828 \text{ A})(32 \Omega) = 90.5 \text{ V}$

19. a.  $R_T = NR_1 = 8 \left( 28 \frac{1}{8} \Omega \right) = 225 \Omega$   
 $V = 0 \text{ V}$

b.  $I = \frac{E}{R_T} = \frac{120 \text{ V}}{225 \Omega} = 0.53 \text{ A}$

$P = I^2 R = \left( \frac{8}{15} \text{ A} \right)^2 \left( 28 \frac{1}{8} \Omega \right) = \left( \frac{64}{225} \right) \left( \frac{225}{8} \right) = 8 \text{ W}$

c.  $V = IR = \left( \frac{8}{15} \text{ A} \right) \left( \frac{225}{8} \Omega \right) = 15 \text{ V}$

d. All go out!

20. a.  $P_T = P_{R_1} + P_{R_2} + P_{R_3},$   
 $E/J = I^2 R_1 + I^2 R_2 + 24$   
 $(R_1 + R_2)J^2 - E/J + 24 = 0$

$6I^2 - 24I + 24 = 0$

$I = \frac{-(-4) \pm \sqrt{(-4)^2 - 4(1)(4)}}{2(1)} = \frac{4 \pm \sqrt{16 - 16}}{2} = \frac{4}{2} = 2 \text{ A}$

$P = 24 \text{ W} = (2 \text{ A})^2 R, R = \frac{24 \Omega}{4} = 6 \Omega$

21. a.  $V_{ab} + 4 \text{ V} + 9 \text{ V} - 12 \text{ V} = 0, V_{ab} = -13 \text{ V} + 12 \text{ V} = -1 \text{ V}$   
 $V_{ab} + 4 \text{ V} + 8 \text{ V} - 4 \text{ V} = 0, V_{ab} = 4 \text{ V} - 12 \text{ V} = -8 \text{ V}$   
 $V_{ab} + 12 \text{ V} - 5 \text{ V} + 6 \text{ V} - 12 \text{ V} = 0, V_{ab} = -18 \text{ V} + 17 \text{ V} = -1 \text{ V}$

22. a.  $E_T = 8 \text{ V} - 32 \text{ V} + 20 \text{ V} = -4 \text{ V}, I = \frac{-4 \text{ V}}{10.3 \Omega} = 388.3 \text{ mA}$   
 $E_T = -4 \text{ V} + 10 \text{ V} - 12 \text{ V} = -6 \text{ V}, I = \frac{-6 \text{ V}}{11.5 \Omega} = 1.39 \text{ A}$

23. a.  $P = 8 \text{ mW} = I^2 R, R = \frac{8 \text{ mW}}{I^2} = \frac{8 \text{ mW}}{(2 \text{ mA})^2} = 2 \text{ k}\Omega$

b.  $I = \frac{E}{R} = \frac{20 \text{ V} - E}{3 \text{ k}\Omega + 2 \text{ k}\Omega} = 2 \text{ mA (CW)}, E = 10 \text{ V}$

$I = \frac{E}{R} = \frac{E - 4 \text{ V} - 10 \text{ V}}{2 \text{ k}\Omega + 1.5 \text{ k}\Omega} = \frac{E - 14 \text{ V}}{3.5 \text{ k}\Omega} = 8 \text{ mA (CCW)}$

24. a.  $-6 \text{ V} + 4 \text{ V} - 12 \text{ V} - V = 0, V = -18 \text{ V} + 4 \text{ V} = -14 \text{ V}$

b.  $+30\text{ V} - 7\text{ V} - 8\text{ V} - V' = 0, V' = 30\text{ V} - 15\text{ V} = 15\text{ V}$

c.  $-14\text{ V} - 22\text{ V} - V_1 + 12\text{ V} = 0, V_1 = -36\text{ V} + 12\text{ V} = -24\text{ V}$   
 $V_1 - V_2 - 12\text{ V} = 0, V_2 = V_1 - 12\text{ V} = -24\text{ V} - 12\text{ V} = -36\text{ V}$

25. a.  $I = \frac{12\text{ V}}{8\Omega} = 1.5\text{ A}$

b.  $V_1 = IR = (1.5\text{ A})(2\Omega) = 3\text{ V}$

c.  $60\text{ V} - 12\text{ V} - V_1 - 3\text{ V} = 0$   
 $V_1 = 60\text{ V} - 15\text{ V} = 45\text{ V}$

26. a.  $+10\text{ V} - V_2 = 0$   
 $V_2 = 10\text{ V}$

+10 V - 6 V -  $V_1 = 0$   
 $V_1 = 4\text{ V}$

+24 V - 10 V -  $V_1 = 0$   
 $V_1 = 14\text{ V}$

+10 V -  $V_2 + 8\text{ V} = 0$   
 $V_2 = 18\text{ V}$

27. a.  $V_{1,\text{iso}} = IR = (3\text{ A})(1.8\Omega) = 5.4\text{ V}$   
 $24\text{ V} - V_1 - 10\text{ V} - 5.4\text{ V} = 0, V_1 = 24\text{ V} - 15.4\text{ V} = 8.6\text{ V}$

$V_{2,\text{iso}} = IR = (3\text{ A})(2.7\Omega) = 8.1\text{ V}$   
 $10\text{ V} - 8.1\text{ V} - V_2 = 0$   
 $V_2 = 10\text{ V} - 8.1\text{ V} = 1.9\text{ V}$

b.  $+10\text{ V} - V_1 + 6\text{ V} - 2\text{ V} - 3\text{ V} = 0, V_1 = 11\text{ V}$   
 $+10\text{ V} - V_2 - 3\text{ V} = 0, V_2 = 7\text{ V}$

28.  $\frac{IV}{2\Omega} = \frac{50\text{ V}}{R_2} = \frac{(50\text{ V})(2\Omega)}{1\text{ V}} = 100\text{ Ω}$

$\frac{IV}{2\Omega} = \frac{100\text{ V}}{R_3} = \frac{(100\text{ V})(2\Omega)}{1\text{ V}} = 200\text{ Ω}$

29. a.  $10\text{ kΩ}$

b.  $V_3, V_2 = 10\text{ kΩ}, 1\text{ kΩ} = 10:1$   
 $V_3, V_1 = 10\text{ kΩ}, 100\text{ Ω} = 100:1$

c.  $V_3 = \frac{R_3 E}{R_2} = \frac{(10\text{ kΩ})(60\text{ V})}{0.1\text{ kΩ} + 1\text{ kΩ} + 10\text{ kΩ}} = 54.05\text{ V}$

d.  $V' = \frac{(R_2 + R_3)E}{R_2} = \frac{(1\text{ kΩ} + 10\text{ kΩ})(60\text{ V})}{11.1\text{ kΩ}} = 59.46\text{ V}$

30. a.  $V = \frac{40\text{ Ω}(30\text{ V})}{40\text{ Ω} + 20\text{ Ω}} = 20\text{ V}$

b.  $V = \frac{(2\text{ kΩ} + 3\text{ kΩ})(40\text{ V})}{4\text{ kΩ} + 1\text{ kΩ} + 2\text{ kΩ} + 3\text{ kΩ}} = \frac{(5\text{ kΩ})(40\text{ V})}{10\text{ kΩ}} = 20\text{ V}$

c.  $\frac{(1.5\Omega + 0.6\Omega + 0.9\Omega)(0.72\text{ V})}{(2.5\Omega + 1.5\Omega + 0.6\Omega + 0.9\Omega + 0.5\Omega)} = \frac{(3\Omega)(0.72\text{ V})}{6\text{ kΩ}} = 0.36\text{ V}$

31. a.  $\frac{V_1}{12\Omega} = \frac{20\text{ V}}{2\Omega}, V_1 = \frac{(12\Omega)(20\text{ V})}{2\Omega} = 12\text{ V}$   
 $\frac{V_2}{6.8\Omega} = \frac{20\text{ V}}{2\Omega}, V_2 = \frac{(6.8\Omega)(20\text{ V})}{2\Omega} = 68\text{ V}$

$E = V_1 + 20\text{ V} + V_2 = 12\text{ V} + 20\text{ V} + 68\text{ V} = 100\text{ V}$

b.  $120\text{ V} - V_1 - 80\text{ V} = 0, V_1 = 40\text{ V}$   
 $80\text{ V} - 10\text{ V} - V_3 = 0, V_3 = 70\text{ V}$

32. a.  $\frac{1000\text{ V}}{100\Omega} = \frac{V_2}{68\Omega}, V_2 = \frac{68\Omega(1000\text{ V})}{100\Omega} = 680\text{ V}$   
 $\frac{1000\text{ V}}{100\Omega} = \frac{V_1}{2\Omega}, V_1 = \frac{2\Omega(1000\text{ V})}{100\Omega} = 20\text{ V}$   
 $E = V_1 + V_2 + 1000\text{ V}$   
 $= 20\text{ V} + 680\text{ V} + 1000\text{ V}$   
 $= 1700\text{ V}$

b.  $V_1 = 0\text{ V}$   
 $V_2 = \frac{10\text{ kΩ}(50\text{ V} - 30\text{ V})}{18\text{ kΩ}} = \frac{10\text{ kΩ}(20\text{ V})}{18\text{ kΩ}} = 11.11\text{ V}$

$V_x = E_1 - V_{3,\text{iso}}$   
 $V_{3,\text{iso}} = \frac{3.3\text{ kΩ}(20\text{ V})}{18\text{ kΩ}}$   
 $= 3.67\text{ V}$   
 $V_x = 50\text{ V} - 3.67\text{ V} = 46.33\text{ V}$

33.  $\frac{2\text{ V}}{1\text{ kΩ}} = \frac{V_2}{2\text{ kΩ}}, V_2 = \frac{2\text{ kΩ}(2\text{ V})}{1\text{ kΩ}} = 4\text{ V}$

$\frac{2\text{ V}}{1\text{ kΩ}} = \frac{V_4}{3\text{ kΩ}}, V_4 = \frac{3\text{ kΩ}(2\text{ V})}{1\text{ kΩ}} = 6\text{ V}$

$I = \frac{2\text{ V}}{1\text{ kΩ}} = 2\text{ mA}$   
 $E = 2\text{ V} + 4\text{ V} + 12\text{ V} + 6\text{ V} = 24\text{ V}$

34. a.  $4 \text{ V} = \frac{R(20 \text{ V})}{2.2 \text{ k}\Omega + 1.8 \text{ k}\Omega + R}$

$$\begin{aligned} 4(4 \text{ k}\Omega + R) &= 20R \\ 16 \text{ k}\Omega + 4R &= 20R \\ 16R &= 16 \text{ k}\Omega \end{aligned}$$

$$R = \frac{16}{16} \text{ k}\Omega = 1 \text{ k}\Omega$$

b.  $110 \text{ V} = \frac{(6 \text{ M}\Omega + R)(140 \text{ V})}{6 \text{ M}\Omega + R + 3 \text{ M}\Omega}$

$$\begin{aligned} 110(9 \text{ M}\Omega + R) &= 840 \text{ M}\Omega + 140R \\ 990 \text{ M}\Omega + 110R &= 840 \text{ M}\Omega + 140R \\ 30R &= 150 \text{ M}\Omega \end{aligned}$$

$$R = \frac{150}{30} \text{ M}\Omega = 5 \text{ M}\Omega$$

35. a.  $R_{\text{bulb}} = \frac{8 \text{ V}}{50 \text{ mA}} = 160 \Omega$

$$V_{\text{bulb}} = 8 \text{ V} = \frac{R_{\text{bulb}}(12 \text{ V})}{R_{\text{bulb}} + R_x} = \frac{160 \Omega(12 \text{ V})}{160 \Omega + R_x}, R_x = 80 \Omega \text{ in series with the bulb}$$

b.  $V_R = 12 \text{ V} - 8 \text{ V} = 4 \text{ V}, P = \frac{V^2}{R} = \frac{(4 \text{ V})^2}{80 \Omega} = 0.2 \text{ W}, \therefore 1/4 \text{ W okay}$

36.  $V_{k_1} + V_{k_2} = 72 \text{ V}$

$$\frac{1}{5}V_{k_1} + V_{k_2} = 72 \text{ V}$$

$$V_{R_2} \left[ 1 + \frac{1}{5} \right] = 72 \text{ V}, V_{k_2} = \frac{72 \text{ V}}{1.2} = 60 \text{ V}$$

$$R_2 = \frac{V_{k_2}}{I_{k_2}} = \frac{60 \text{ V}}{4 \text{ mA}} = 15 \text{ k}\Omega, R_1 = \frac{V_{k_1}}{I_{k_1}} = \frac{72 \text{ V} - 60 \text{ V}}{4 \text{ mA}} = \frac{12 \text{ V}}{4 \text{ mA}} = 3 \text{ k}\Omega$$

37.  $R_T = R_1 + R_2 + R_3 = 2R_3 + 7R_3 + R_3 = 10R_3$

$$V_{k_3} = \frac{R_3(60 \text{ V})}{10R_3} = 6 \text{ V}, V_{k_1} = 2V_{k_3} = 2(6 \text{ V}) = 12 \text{ V}, V_{k_2} = 7V_{k_3} = 7(6 \text{ V}) = 42 \text{ V}$$

38. a.  $V_{k_1} = 4V_{k_2} = 4(3V_{k_1}) = 12V_{k_1}$

$$E = V_{k_1} + 3V_{k_1} + 12V_{k_1} \therefore R_T = R_1 + 3R_1 + 12R_1 = 16R_1 = \frac{64 \text{ V}}{10 \text{ mA}} = 6.4 \text{ k}\Omega$$

$$R_1 = \frac{6.4 \text{ k}\Omega}{16} = 400 \Omega, R_2 = 3R_1 = 1.2 \text{ k}\Omega, R_3 = 12R_1 = 4.8 \text{ k}\Omega$$

b.  $R_T = \frac{64 \text{ V}}{10 \mu\text{A}} = 64 \text{ M}\Omega, R_1 = \frac{6.4 \text{ M}\Omega}{16} = 400 \text{ k}\Omega, R_2 = 1.2 \text{ M}\Omega, R_3 = 4.8 \text{ M}\Omega$

$$\begin{aligned} \frac{I_1}{I'} &= \frac{10 \text{ mA}}{10 \mu\text{A}} = 10^3 \text{ and } \frac{R'_1}{R_1} = \frac{400 \text{ k}\Omega}{400 \Omega} = 10^3 \text{ also} \end{aligned}$$

39. a.  $V_a = 12 \text{ V} + 5 \text{ V} = 17 \text{ V}$   
 $V_b = 5 \text{ V} + 16 \text{ V} = 21 \text{ V}$   
 $V_{ab} = 17 \text{ V} - 21 \text{ V} = -4 \text{ V}$

b.  $V_a = -6 \text{ V}$   
 $-6 \text{ V} + 6 \text{ V} + 10 \text{ V} - V_b = 0, V_b = 10 \text{ V}$   
 $V_{ab} = V_a - V_b = -6 \text{ V} - 10 \text{ V} = -16 \text{ V}$

c.  $-8 \text{ V} + 3 \text{ V} - V_a = 0, V_a = -5 \text{ V}$   
 $V_b = -8 \text{ V}$   
 $V_{ab} = V_a - V_b = -5 \text{ V} - (-8 \text{ V}) = -5 \text{ V} + 8 \text{ V} = +3 \text{ V}$

40. a.  $I \downarrow = \frac{60 \text{ V} + 20 \text{ V}}{18 \text{ }\Omega + 82 \text{ }\Omega} = \frac{80 \text{ V}}{100 \text{ }\Omega} = 0.8 \text{ A}$   
 $V_a = 60 \text{ V} - I(18 \text{ }\Omega) = 60 \text{ V} - (0.8 \text{ A})(18 \text{ }\Omega) = 60 \text{ V} - 14.4 \text{ V} = 45.6 \text{ V}$

b.  $\overrightarrow{I} = \frac{100 \text{ V} - 60 \text{ V}}{42 \text{ k}\Omega} = \frac{40 \text{ V}}{8 \text{ k}\Omega} = 5 \text{ mA}$   
 $V_a - I(2 \text{ k}\Omega) + 100 \text{ V} = 0$   
 $V_a = (I/2 \text{ k}\Omega) - 100 \text{ V} = (5 \text{ mA}/2 \text{ k}\Omega) - 100 \text{ V} = 10 \text{ V} - 100 \text{ V} = -90 \text{ V}$

41.  $I = \frac{47 \text{ V} - 20 \text{ V}}{2 \text{ k}\Omega + 3 \text{ k}\Omega} = \frac{27 \text{ V}}{9 \text{ k}\Omega} = 3 \text{ mA (CCW)}$   
 $V_{2k\Omega} = 6 \text{ V}, V_{3k\Omega} = \therefore V_{4k\Omega} = 12 \text{ V}$

a.  $V_a = 20 \text{ V}, V_b = 20 \text{ V} + 6 \text{ V} = 26 \text{ V}, V_c = 20 \text{ V} + 6 \text{ V} + 9 \text{ V} = 35 \text{ V}$   
 $V_d = -17 \text{ V}, \therefore = 0 \text{ V}$

b.  $V_{ab} = -6 \text{ V}, V_{dc} = -47 \text{ V}, V_{da} = 9 \text{ V}$   
c.  $V_{ac} = -15 \text{ V}, V_{db} = -47 \text{ V} + 9 \text{ V} = -38 \text{ V}$

42.  $I_{k_1} = \frac{4 \text{ V} + 4 \text{ V}}{8 \text{ }\Omega} = \frac{8 \text{ V}}{8 \text{ }\Omega} = 1 \text{ A}, R_1 = \frac{V_{k_1}}{I} = \frac{12 \text{ V} - 4 \text{ V}}{1 \text{ A}} = \frac{8 \text{ V}}{1 \text{ A}} = 8 \text{ }\Omega,$   
 $R_1 = \frac{V_{k_1}}{I} = \frac{8 \text{ V} - 4 \text{ V}}{1 \text{ A}} = \frac{4 \text{ V}}{1 \text{ A}} = 4 \text{ }\Omega$

43.  $V_b = 48 V - 12 V = 36 V$

$$R_3 = \frac{V_b}{I} = \frac{36 V}{16 \text{ mA}} = 2.25 \text{ k}\Omega$$

$$V_A = 12 V - 0 V = 12 V$$

$$R_3 = \frac{V_b}{I} = \frac{12 V}{16 \text{ mA}} = 0.75 \text{ k}\Omega$$

$$V_A = 20 V$$

$$R_4 = \frac{V_A}{I} = \frac{20 V}{16 \text{ mA}} = 1.25 \text{ k}\Omega$$

$$V_{R_1} = E - V_{R_2} - V_{R_3} - V_{R_4}$$

$$= 100 V - 36 V - 12 V - 20 V = 32 V$$

$$R_1 = \frac{V_{R_1}}{I} = \frac{32 V}{16 \text{ mA}} = 2 \text{ k}\Omega$$

44.

a.  $V_a = -8 V + 14 V = +6 V, V_b = 14 V$   
 $V_c = +((10 \Omega) - 6 V \text{ with})$

$$I = \frac{|4 V + 6 V|}{10 \Omega + 10 \Omega} = \frac{20 V}{20 \Omega} = 1 A$$

Therefore,  $V_c = (1 A)(10 \Omega) - 6 V = 10 V - 6 V = 4 V$

b.  $V_{ab} = V_a - V_b = 6 V - 14 V = -8 V$

$$V_{cb} = V_c - V_b = 4 V - 14 V = -10 V$$

$$V_{ad} = V_c - V_d = 4 V - 0 V = 4 V$$

c.  $V_{ad} = V_a - V_d = 6 V - 0 V = 6 V$

$$V_{ca} = V_c - V_a = 4 V - 6 V = -2 V$$

45.

$$V_0 = 0 V, V_1 = (2 \text{ k}\Omega)(6 \text{ mA}) + 3 V = 12 V + 3 V = 15 V, V_7 = 4 V$$

$$V_{20} = V_1 - V_0 = 12 V - 0 V = 12 V, V_{23} = V_2 - V_3 = 4 V - (-8 V) = 4 V + 8 V = 12 V$$

$$V_{56} = V_5 - V_6 = 3 V - 4 V = -1 V, I_1 = \frac{4 V + 8 V}{4 \Omega} = \frac{12 V}{4 \Omega} = 3 A$$

46.

$$\begin{aligned} V_0 &= 0 V, V_{10} = V_0 - V_5 = 0 V - 0 V = 0 V, V_2 = (3 \text{ mA})(3.3 \text{ k}\Omega) = 9.9 V \\ V_{23} &= V_2 - V_3 = 9.9 V - 0 V = 9.9 V, V_{12} = V_1 - V_2 = 20 V - 9.9 V = 10.1 V \\ \Sigma I_1 &= \Sigma I_6 \\ I_1 &= 4 \text{ mA} + 3 \text{ mA} + 10 \text{ mA} = 17 \text{ mA} \end{aligned}$$

47. a.  $V_L = I_L R_L = (2 A)(28 \Omega) = 56 V$   
 $V_{in} = 60 V - 56 V = 4 V$

$$R_{in} = \frac{V_{in}}{I} = \frac{4 V}{2 A} = 2 \Omega$$

b.  $VR = \frac{V_{ML} - V_{RL}}{V_{RL}} \times 100\% = \frac{60 V - 56 V}{56 V} \times 100\% = 7.14\%$

48. a.  $V_L = \frac{3.3 \Omega(12 V)}{3.3 \Omega + 43 \text{ mA}} = \frac{39.6 V}{3.343 \Omega} = 11.85 V$

b.  $VR = \frac{V_{ML} - V_{RL}}{V_{RL}} \times 100\% = \frac{12 V - 11.85 V}{11.85 V} \times 100\% = 1.27\%$

c.  $I_s = I_L = \frac{11.85 V}{3.3 \Omega} = 3.59 A$

$$\begin{aligned} P_s &= EI_s = (12 V)(3.59 A) = 43.08 W \\ P_{in} &= I^2 R_{in} = (3.59 A)^2 43 \Omega = 0.554 W \end{aligned}$$

49. a.  $I = \frac{E}{R_L} = \frac{12 V}{2 \text{ k}\Omega + 6.8 \text{ k}\Omega} = \frac{12 V}{8.8 \text{ k}\Omega} = 1.36 \text{ mA}$

b.  $I = \frac{E}{R_L} = \frac{12 V}{8.8 \text{ k}\Omega + 0.25 \text{ k}\Omega} = \frac{12 V}{9.05 \text{ k}\Omega} = 1.33 \text{ mA}$

c. not for most applications.

## Chapter 6

1. a.  $R_2$  and  $R_3$   
     b.  $E$  and  $R_3$   
     c.  $R_2$  and  $R_1$   
     d.  $R_2$  and  $R_3$
2. a.  $E, R_1, R_2, R_3$ , and  $R_4$   
     b.  $E, R_1, R_2$ , and  $R_3$   
     c.  $E$  and  $R_1$   
     d. none
3. a.  $R_3$  and  $R_4$ ,  $R_5$  and  $R_6$   
     b.  $E$  and  $R_1, R_6$  and  $R_7$
4. a.  $R_T = \frac{(36\Omega)(18\Omega)}{36\Omega + 18\Omega} = 12\Omega$
- b.  $R_T = \frac{1}{\frac{1}{1k\Omega} + \frac{1}{2k\Omega} + \frac{1}{30k\Omega}} = \frac{1}{1 \times 10^{-3}S + 0.5 \times 10^{-3}S + 33.33 \times 10^{-6}S} = \frac{1}{0.652k\Omega} = 1.533 \times 10^{-3}S$
- c.  $R_T = \frac{1}{\frac{1}{1.2\Omega} + \frac{1}{120k\Omega} + \frac{1}{12k\Omega}} = \frac{1}{8.3333 \times 10^{-6}S + 8.33 \times 10^{-3}S + 83.33 \times 10^{-3}S} = \frac{1}{92.49 \times 10^{-3}S} = 10.81\Omega$
- d.  $R'_T = \frac{18k\Omega}{3} = 6k\Omega$
- e.  $R_T = \frac{(6k\Omega)(6k\Omega)}{6k\Omega + 6k\Omega} = 3k\Omega$
- f.  $R'_T = \frac{22\Omega}{4} = 5.5\Omega, R_T' = \frac{10\Omega}{2} = 5\Omega$
- g.  $R_T = \frac{(5.5\Omega)(5\Omega)}{5.5\Omega + 5\Omega} = 2.62\Omega$
- h.  $R_T = \frac{1}{\frac{1}{1\Omega} + \frac{1}{1k\Omega} + \frac{1}{1M\Omega}} = \frac{1}{1000 \times 10^{-3}S + 1 \times 10^{-3}S + 0.001 \times 10^{-3}S} = \frac{1}{1001.001 \times 10^{-3}S} = 0.99\Omega$
- i.  $R_T = \frac{1}{\frac{1}{1k\Omega} + \frac{1}{1.2k\Omega} + \frac{1}{0.3k\Omega}} = \frac{1}{1 \times 10^{-3}S + 0.833 \times 10^{-3}S + 3.333 \times 10^{-3}S} = 1.2k\Omega$
5. a.  $R_T = \frac{1}{1.02\Omega} = \frac{1}{563.73 \times 10^{-6} + \frac{1}{R}} = \frac{1}{575 \times 10^{-3} + \frac{1.020k\Omega}{R}} = 1$
- b.  $R = \frac{1.020k\Omega}{425 \times 10^3} = 2.4k\Omega$
- c.  $R_T = \frac{1}{R_1 + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{1.11k\Omega + \frac{1}{8.2k\Omega} + \frac{1}{10k\Omega} + \frac{1}{2k\Omega}} = \frac{1}{900.9 \times 10^{-3}S + \frac{1}{R} + 121.95 \times 10^{-6}S + 100 \times 10^{-6}S + 500 \times 10^{-8}S} = \frac{1}{R} = 178.95 \times 10^{-6}S$
- d.  $R = \frac{1}{178.95 \times 10^{-6}S} = 5.588k\Omega \approx 5.6k\Omega$
6. a.  $R_T = \frac{1}{1k\Omega + 1.2k\Omega + 0.3k\Omega} = \frac{1}{1 \times 10^{-3}S + 0.833 \times 10^{-3}S + 3.333 \times 10^{-3}S} = 1.2k\Omega$
- b. about 1 kΩ
7. a.  $R'_T = 3\Omega \parallel 6\Omega = 2\Omega$   
 $R_T = 1.61\Omega = \frac{(2\Omega)(R)}{2\Omega + R}, R = 8\Omega$
- b.  $R'_T = \frac{6k\Omega}{3} = 2k\Omega$   
 $R_T = 1.8k\Omega = \frac{(2k\Omega)(R)}{2k\Omega + R}, R = 18k\Omega$
- c.  $R_T = 5.08k\Omega = \frac{(20k\Omega)(R)}{20k\Omega + R}, R = 6.8k\Omega$
- d.  $R_T = 1.02\Omega = \frac{1}{2.4k\Omega + \frac{1}{R} + \frac{1}{6.8k\Omega}} = \frac{1}{416.67 \times 10^{-6}S + \frac{1}{R} + 147.06 \times 10^{-6}S}$
- e.  $1.02k\Omega = \frac{1}{563.73 \times 10^{-6} + \frac{1}{R}} = 1$

$$c. R_T = \frac{1}{\frac{1}{1.2k\Omega} + \frac{1}{22k\Omega} + \frac{1}{22M\Omega}}$$

$$= \frac{1}{833.333 \times 10^{-6} S + 45.455 \times 10^{-6} S + 4.545 \times 10^{-6} S + 0.455 \times 10^{-6} S}$$

$$= \frac{1}{883.788 \times 10^{-6} S} = 1.131 k\Omega$$

$$d. 220 k\Omega, 2.2 M\Omega: R_T = \frac{(1.2k\Omega)(22k\Omega)}{1.2k\Omega + 22k\Omega} = 1.138 k\Omega$$

e.  $R_T$  reduced.

$$10. a. R_T = \frac{1}{\frac{1}{4\Omega} + \frac{1}{2\Omega} + \frac{1}{10\Omega}} = \frac{1}{0.25S + 0.50S + 0.10S} = \frac{1}{0.85S} = 1.18\Omega$$

b.  $\infty \Omega$

c.  $R_T = 3\Omega \parallel 6\Omega = 2\Omega$

$$11. 24\Omega \parallel 24\Omega = 12\Omega$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (\text{Two of the } 24\Omega \text{ resistors "shorted" out.})$$

$$0.1S = \frac{1}{R_1} + 0.08333S + 0.00833S$$

$$0.1S = \frac{1}{R_1} + 0.09167S$$

$$\frac{1}{R_1} = 0.1S - 0.09167S = 0.00833S$$

$$R_1 = \frac{1}{0.00833S} = 120\Omega$$

$$12. a. R_T = \frac{(8\Omega)(24\Omega)}{8\Omega + 24\Omega} = 6\Omega$$

b.  $V_{R_1} = V_{R_2} = 36V$

$$c. I_1 = \frac{E}{R_1} = \frac{36V}{6\Omega} = 6A$$

$$I_1 = \frac{V_{R_1}}{R_1} = \frac{36V}{8\Omega} = 4.5A$$

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{36V}{24\Omega} = 1.5A$$

d.  $I_T = I_1 + I_2$

$$6A = 4.5A + 1.5A = 6A \text{ (checks)}$$

d.  $I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{60 \text{ V}}{20 \text{ k}\Omega} = 3.0 \text{ mA}$ ,  $I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{60 \text{ V}}{10 \text{ k}\Omega} = 6 \text{ mA}$

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{60 \text{ V}}{1 \text{ k}\Omega} = 60.0 \text{ mA}$$
,  $I_{R_4} = \frac{V_{R_4}}{R_4} = \frac{60 \text{ V}}{91 \text{ k}\Omega} = 0.659 \text{ mA}$

$$I_t = \frac{E}{R_t} = \frac{60 \text{ V}}{862.07 \text{ k}\Omega} = 69.6 \text{ mA}$$

e.  $I_t = 3 \text{ mA} + 6 \text{ mA} + 60 \text{ mA} + 0.659 \text{ mA} = 69.66 \text{ mA}$  (checks)

$$I_t = 3 \text{ mA} + 6 \text{ mA} + 60 \text{ mA} + 6.59 \text{ mA} = 69.66 \text{ mA}$$

$$I_t = 3 \text{ mA} + 6 \text{ mA} + 60 \text{ mA} + 0.659 \text{ mA} = 69.66 \text{ mA}$$

f. always greater

16. a.  $R_T = 6 \Omega = \frac{(18 \Omega)(R_2)}{18 \Omega + R_2}$

$$108 \Omega + 6R_2 = 18R_2$$

$$12R_2 = 108 \Omega$$

$$R_2 = \frac{108 \Omega}{12} = 9 \Omega$$

b.  $P = 81 \text{ W} = \frac{V^2}{R} = \frac{E^2}{R} = \frac{E^2}{9 \Omega}$

and  $E^2 = (9)(81)$   
or  $E = \sqrt{729} = 27 \text{ V}$

17. a.  $P = \frac{V^2}{R} = \frac{E^2}{R}$  and  $E = \sqrt{PR} = \sqrt{(100 \text{ W})(4 \Omega)} = \sqrt{400} = 20 \text{ V}$

b.  $R_2 = \frac{E}{I_2} = \frac{20 \text{ V}}{2 \text{ A}} = 10 \Omega$

c.  $I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{20 \text{ V}}{10 \Omega} = 2 \text{ A}$

d.  $I_t = I_1 + I_2 = 2 \text{ A} + 2 \text{ A} + \frac{20 \text{ V}}{4 \Omega} = 4 \text{ A} + 5 \text{ A} = 9 \text{ A}$

e.  $P_t = EI_t = (20 \text{ V})(9 \text{ A}) = 180 \text{ W}$

f.  $P_{R_1} = \frac{E^2}{R_1} = \frac{(20 \text{ V})^2}{10 \Omega} = 40 \text{ W}$ ,  $P_{R_2} = \frac{E^2}{R_2} = \frac{(20 \text{ V})^2}{\left(\frac{20 \text{ V}}{2 \text{ A}}\right)} = \frac{400 \text{ W}}{10} = 40 \text{ W}$ ,

g.  $P_t = P_1 + P_2 + P_3$   
 $180 \text{ W} = 40 \text{ W} + 40 \text{ W} + 100 \text{ W} = 180 \text{ W}$  (checks)

18. a.  $I_t = \frac{(20 \Omega)(0.8 \text{ A})}{20 \Omega + 4 \Omega} = 9 \text{ A}$

$$E = V_{R_2} = I_t R_2 = (9 \text{ A})(4 \Omega) = 36 \text{ V}$$

$$I_{R_1} = 12.3 \text{ A} - 10.8 \text{ A} = 1.5 \text{ A}$$

$$R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{36 \text{ V}}{1.5 \text{ A}} = 24 \Omega$$

19. a.  $V = 48 \text{ V}$

b.  $I_t = \frac{48 \text{ V}}{18 \text{ k}\Omega} = 2.67 \text{ mA}$

c.  $I_1 = \frac{48 \text{ V}}{3 \text{ k}\Omega} + \frac{48 \text{ V}}{12 \text{ k}\Omega} + I_2 = 16 \text{ mA} + 4 \text{ mA} + 2.67 \text{ mA} = 22.67 \text{ mA}$

d.  $P = \frac{V^2}{R} = \frac{E^2}{R} = \frac{(48 \text{ V})^2}{12 \text{ k}\Omega} = 192 \text{ mW}$

20. a.  $I_{R_1} \uparrow = 4 \text{ A} - 1 \text{ A} = 3 \text{ A}$ ,  $R_1 = \frac{V_{R_1}}{I_1} = \frac{E}{I_1} = \frac{12 \text{ V}}{3 \text{ A}} = 4 \Omega$

b.  $R_3 = \frac{V_{R_3}}{I_3} = \frac{E}{I_3} = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$

c.  $I_1 \uparrow = \frac{12 \text{ V}}{2 \Omega} = 6 \text{ A}$ ,  $I_t = I_1 + 4 \text{ A} = 6 \text{ A} + 4 \text{ A} = 10 \text{ A}$

21. —

22. a.  $R_T = \frac{1}{\frac{1}{1 \text{ k}\Omega} + \frac{1}{4.7 \text{ k}\Omega} + \frac{1}{10 \text{ k}\Omega}} = \frac{1}{1.313 \times 10^{-3} \text{ S}} = 761.61 \Omega$

$$I_R = \frac{V_R}{R_1} = \frac{60 \text{ V}}{1 \text{ k}\Omega} = 60 \text{ mA}$$
,  $I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{60 \text{ V}}{4.7 \text{ k}\Omega} = 12.77 \text{ mA}$

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{60 \text{ V}}{10 \text{ k}\Omega} = 6 \text{ mA}$$

b.  $P_{R_1} = V_{R_1} \cdot I_{R_1} = (60 \text{ V})(60 \text{ mA}) = 3.6 \text{ W}$

$$P_{R_2} = V_{R_2} \cdot I_{R_2} = (60 \text{ V})(12.77 \text{ mA}) = 766.2 \text{ mW}$$

$$P_{R_3} = V_{R_3} \cdot I_{R_3} = (60 \text{ V})(6 \text{ mA}) = 360 \text{ W}$$

c.  $I_s = \frac{E}{R_s} = \frac{60 \text{ V}}{761.61 \Omega} = 78.78 \text{ mA}$

$P_s = E I_s = (60 \text{ V})(78.78 \text{ mA}) = 4.73 \text{ W}$

d.  $P_t = 4.73 \text{ W} + 3.6 \text{ W} + 766.2 \text{ mW} + 360 \text{ mW} = 4.73 \text{ W}$  (checks)

e.  $R_i$  = the smallest parallel resistor

23.

a.  $I_{\text{bulk}} = \frac{E}{R_{\text{bulk}}} = \frac{120 \text{ V}}{1.8 \text{ k}\Omega} = 66.667 \text{ mA}$

b.  $R_T = \frac{R}{N} = \frac{1.8 \text{ k}\Omega}{8} = 225 \Omega$

c.  $I_s = \frac{E}{R_T} = \frac{120 \text{ V}}{225 \Omega} = 0.533 \text{ A}$


d.  $P = \frac{V^2}{R} = \frac{(120 \text{ V})^2}{1.8 \text{ k}\Omega} = 8 \text{ W}$

e.  $P_s = 8(8 \text{ W}) = 64 \text{ W}$

f. none,  $I_s$  drops by 66.667 mA

24.

Network redrawn:

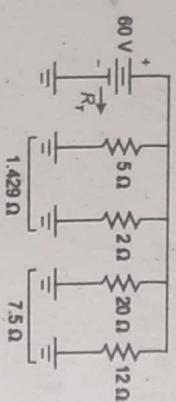

$$R_T = 1.429 \Omega \parallel 7.5 \Omega = 1.2 \Omega$$

$$P_s = \frac{E^2}{R_s} = \frac{(60 \text{ V})^2}{1.2 \Omega} = 3 \text{ kW}$$

25. a.  $5 \times 60 \text{ W} = 300 \text{ W}$

$$I_{\text{bulb}} = \frac{300 \text{ W}}{120 \text{ V}} = 2.5 \text{ A}$$

$$I_{\text{micro}} = \frac{1200 \text{ W}}{120 \text{ V}} = 10 \text{ A}$$

$$I_{\text{TV}} = \frac{320 \text{ W}}{120 \text{ V}} = 2.67 \text{ A}$$

$$I_{\text{bvd}} = \frac{25 \text{ W}}{120 \text{ V}} = 208.33 \text{ mA}$$

b.  $I_s = \Sigma I = 2.5 \text{ A} + 10 \text{ A} + 2.67 \text{ A} + 208.33 \text{ mA} = 15.38 \text{ A}$

No

c.  $R_T = \frac{E}{I_s} = \frac{120 \text{ V}}{15.38 \text{ A}} = 7.8 \Omega$

d.  $P_s = E I_s = (120 \text{ V})(15.38 \text{ A}) = 1,845.60 \text{ W}$

e.  $P_t = 1845.60 \text{ W} = 300 \text{ W} + 1200 \text{ W} + 320 \text{ W} + 25 \text{ W} = 1845 \text{ W}$  (checks)

26. a.  $8 \Omega \parallel 12 \Omega = 4.8 \Omega, 4.8 \Omega \parallel 4 \Omega = 2.182 \Omega$

$$I_1 = \frac{24 \text{ V} + 8 \text{ V}}{2.182 \Omega} = 14.67 \text{ A}$$

$$\text{b. } P_4 = \frac{V^2}{R} = \frac{(24 \text{ V} + 8 \text{ V})^2}{4 \Omega} = 256 \text{ W}$$

$$\text{c. } I_2 = I_1 = 14.67 \text{ A}$$

$$\text{27. } I_1 = 8 \text{ mA} + 6 \text{ mA} = 14 \text{ mA}$$

$$I_2 = 6 \text{ mA} - 2 \text{ mA} = 4 \text{ mA}$$

28. a.  $\Sigma I = \Sigma I_o$   
 $5 \text{ A} + 7 \text{ A} + 3 \text{ A} = 9 \text{ A} + I$   
 $15 \text{ A} = 9 \text{ A} + I$   
 $6 \text{ A} = I$

b.  $\Sigma I_f = \Sigma I_o$   
 $8 \text{ mA} = 2 \text{ mA} + I_1$   
 $I_1 = 8 \text{ mA} - 2 \text{ mA} = 6 \text{ mA}$   
 $\Sigma I_f = \Sigma I_o$

$I_1 + 9 \text{ mA} = I_2$   
 $I_2 = 6 \text{ mA} + 9 \text{ mA} = 15 \text{ mA}$   
 $\Sigma I_f = \Sigma I_o$

$I_2 = 10 \text{ mA} + I_3$   
 $I_3 = 15 \text{ mA} - 10 \text{ mA} = 5 \text{ mA}$

$I_1 = 9 \text{ mA} + I_4$   
 $I_4 = 6 \text{ mA} + 9 \text{ mA} = 15 \text{ mA}$   
 $I_1 + I_3 = I_4$   
 $I_1 + 5 \text{ A} + 3 \text{ A} = 3 \text{ A}$

29. a.  $\Sigma I_f = \Sigma I_o$   
 $8 \text{ A} = 3 \text{ A} + I_2$   
 $I_2 = 8 \text{ A} - 3 \text{ A} = 5 \text{ A}, I_3 = 3 \text{ A}$

$\Sigma I_f = \Sigma I_o$   
 $I_2 + I_3 = I_4$   
 $I_4 = 5 \text{ A} + 3 \text{ A} = 8 \text{ A}$

b.  $\Sigma I_f = \Sigma I_o$   
 $I_5 = 36 \text{ mA} + 4 \text{ mA} = 40 \text{ mA}$   
 $\Sigma I_f = \Sigma I_o$

$36 \text{ mA} = I_1 + 20 \text{ mA}$   
 $I_1 = 36 \text{ mA} - 20 \text{ mA} = 16 \text{ mA}$

$\Sigma I_f = \Sigma I_o$   
 $4 \text{ mA} + 20 \text{ mA} = I_4$   
 $I_4 = 24 \text{ mA}$

$I_5 = I_4 = 40 \text{ mA}$

$$30. \quad I_{k_1} = 5 \text{ mA} - 2 \text{ mA} = 3 \text{ mA}$$

$$E = V_{k_1} = (3 \text{ mA})(4 \text{ k}\Omega) = 12 \text{ V}$$

$$R_1 = \frac{V_{k_1}}{I_{k_1}} = \frac{12 \text{ V}}{(9 \text{ mA} - 5 \text{ mA})} = \frac{12 \text{ V}}{4 \text{ mA}} = 3 \text{ k}\Omega$$

$$R_3 = \frac{V_{k_3}}{I_{k_3}} = \frac{12 \text{ V}}{2 \text{ mA}} = 6 \text{ k}\Omega$$

$$R_T = \frac{E}{I_T} = \frac{12 \text{ V}}{9 \text{ mA}} = 1.33 \text{ k}\Omega$$

b.  $R_1 = \frac{E}{I_1} = \frac{10 \text{ V}}{2 \text{ A}} = 5 \text{ }\Omega$

$$I_2 = I - I_1 = 3 \text{ A} - 2 \text{ A} = 1 \text{ A}$$

$$R = \frac{E}{I_2} = \frac{10 \text{ V}}{1 \text{ A}} = 10 \Omega$$

b.  $E = I_1 R_1 = (2 \text{ A})(6 \Omega) = 12 \text{ V}$

$$I_2 = \frac{E}{R_2} = \frac{12 \text{ V}}{9 \Omega} = 1.33 \text{ A}$$

$$I_3 = \frac{P}{V} = \frac{12 \text{ W}}{12 \text{ V}} = 1 \text{ A}$$

$$R_3 = \frac{E}{I_3} = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$$

$$I = I_1 + I_2 + I_3 = 2 \text{ A} + 1.33 \text{ A} + 1 \text{ A} = 4.33 \text{ A}$$

31. a.  $R_1 = \frac{E}{I_1} = \frac{10 \text{ V}}{2 \text{ A}} = 5 \text{ }\Omega$

$$I_2 = I - I_1 = 3 \text{ A} - 2 \text{ A} = 1 \text{ A}$$

$$R = \frac{E}{I_2} = \frac{10 \text{ V}}{1 \text{ A}} = 10 \Omega$$

$$E = I_1 R_1 = (2 \text{ A})(6 \Omega) = 12 \text{ V}$$

$$I_2 = \frac{E}{R_2} = \frac{12 \text{ V}}{9 \Omega} = 1.33 \text{ A}$$

$$I_3 = \frac{P}{V} = \frac{12 \text{ W}}{12 \text{ V}} = 1 \text{ A}$$

$$R_3 = \frac{E}{I_3} = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$$

$$I = I_1 + I_2 + I_3 = 2 \text{ A} + 1.33 \text{ A} + 1 \text{ A} = 4.33 \text{ A}$$

32. a.  $I_1 = \frac{64 \text{ V}}{1 \text{ k}\Omega} = 64 \text{ mA}$

$$I_3 = \frac{64 \text{ V}}{4 \text{ k}\Omega} = 16 \text{ mA}$$

$$I_1 = I_2 + I_3 = 100 \text{ mA} - 64 \text{ mA} - 16 \text{ mA} = 20 \text{ mA}$$

$$R = \frac{E}{I_2} = \frac{64 \text{ V}}{20 \text{ mA}} = 3.2 \text{ k}\Omega$$

$$I = I_2 + I_3 = 20 \text{ mA} + 16 \text{ mA} = 36 \text{ mA}$$

33. a.  $R_1 = \frac{E}{I_1} = \frac{10 \text{ V}}{2 \text{ A}} = 5 \text{ }\Omega$

$$I_2 = I - I_1 = 3 \text{ A} - 2 \text{ A} = 1 \text{ A}$$

$$R = \frac{E}{I_2} = \frac{10 \text{ V}}{1 \text{ A}} = 10 \Omega$$

$$E = I_1 R_1 = (2 \text{ A})(6 \Omega) = 12 \text{ V}$$

$$I_2 = I - I_1 = 3 \text{ A} - 2 \text{ A} = 1 \text{ A}$$

b.  $P_{R_1} = I_1^2 R_1 = (0.5 \text{ A})^2 \cdot 60 \Omega = 15 \text{ W}$

$I_2 = I_1 = \frac{1}{2} I_1 = \frac{1}{2}(9 \text{ A}) = 4.5 \text{ A}$

$I_3 = \frac{6 \Omega}{12 \Omega} I_1 = \frac{1}{2} I_1 = \frac{1}{2}(9 \text{ A}) = 4.5 \text{ A}$

$I_4 = \frac{6 \Omega}{18 \Omega} I_1 = \frac{1}{3} I_1 = \frac{1}{3}(9 \text{ A}) = 3 \text{ A}$

$I_T = I_1 + I_2 + I_3 + I_4 = 9 \text{ A} + 4.5 \text{ A} + 27 \text{ A} + 3 \text{ A} = 43.5 \text{ A}$

a.  $R_1 = \frac{8 \text{ k}\Omega(20 \text{ mA})}{2 \text{ k}\Omega + 8 \text{ k}\Omega} = 16 \text{ mA}$

$I_2 = 20 \text{ mA} - 16 \text{ mA} = 4 \text{ mA}$

$I_3 = \frac{1 \text{ k}\Omega(I_T)}{1 \text{ k}\Omega + 2.4 \text{ k}\Omega} = \frac{1 \text{ k}\Omega(I_T)}{3.4 \text{ k}\Omega}$

and  $I_T = \frac{3.4 \text{ k}\Omega(2.5 \text{ A})}{1 \text{ k}\Omega} = 8.5 \text{ A}$

$I_1 = I_T - 2.5 \text{ A} = 8.5 \text{ A} - 2.5 \text{ A} = 6 \text{ A}$

35. a.  $R_T = \frac{1}{\frac{1}{40} + \frac{1}{8\Omega} + \frac{1}{12\Omega}} = \frac{1}{\frac{1}{458.333 \times 10^{-3}}} = 2.18 \Omega$

$I_T = \frac{R_T}{E} I, \quad I_1 = \frac{2.18\Omega}{4\Omega} (6 \text{ A}) = 3.27 \text{ A}$

$I_2 = \frac{2.18\Omega}{8\Omega} (6 \text{ A}) = 1.64 \text{ A}$

$I_3 = \frac{2.18\Omega}{12\Omega} (6 \text{ A}) = 1.09 \text{ A}$

$I_4 = 6 \text{ A}$

b.  $4\Omega \parallel 4\Omega = 2\Omega$

$$I_2 = \frac{20\Omega(8A)}{20\Omega + 2\Omega + 8\Omega} = \frac{20\Omega(8A)}{30\Omega} = 5.33A$$

$$I_1 = \frac{I_2}{2} = \frac{5.33A}{2} = 2.67A$$

$$I_3 = 8A - I_2 = 8A - 5.33A = 2.67A$$

$$I_4 = 8A$$

36. a.  $I_1 \equiv \frac{9}{10}(10A) = 9A$

b.  $I_3/I_2 = 10\Omega/1\Omega = 10, \quad I_2 = \frac{I_1}{10} = \frac{9A}{10} = 0.9A$

c.  $I_3/I_4 = 1k\Omega/1\Omega = 1000, I_3 = I_3/1000 = 9A/1000 \equiv 9mA$

d.  $I_3/I_4 = 100k\Omega/1\Omega = 100,000, \quad I_4 = I_3/100,000 = 9A/100,000 \equiv 90\mu A$

e. very little effect,  $I/100,000$

f.  $R_T = \frac{1}{1\Omega} + \frac{1}{10\Omega} + \frac{1}{1k\Omega} + \frac{1}{100k\Omega}$

$$= \frac{1}{1S + 0.1S + 1 \times 10^{-3}S + 10 \times 10^{-6}S}$$

$$= \frac{1}{1.10S} = 0.91\Omega$$

g.  $I_3 = \frac{R_2}{R_1}I, \quad I_1 = \frac{0.91\Omega}{1\Omega}(10A) = 9.1A \text{ excellent (9A)}$

h.  $I_2 = \frac{0.91\Omega}{10\Omega}(10A) = 0.91A \text{ excellent (0.9A)}$

i.  $I_3 = \frac{0.91\Omega}{100k\Omega}(10A) = 91\mu A \text{ excellent (90}\mu\text{A)}$

37. a. CDR:  $I_{120} = \frac{3\Omega I}{3\Omega + 36\Omega} = 1A, \quad I = \frac{39\Omega(1A)}{3\Omega} = 13A = I_2$

$$I_1 = J - 1A = 13A - 1A = 12A$$

b.  $I_3 = J = 24mA, V_{120} = IR = (4mA)(12k\Omega) = 48V$

$$I_2 = \frac{V}{R} = \frac{48V}{4k\Omega} = 12mA$$

$$\begin{aligned} I_1 &= J - 4mA - I_2 \\ &= 24mA - 4mA - 12mA \\ &= 8mA \end{aligned}$$

38. a.  $R = 3(2k\Omega) = 6k\Omega$

$$V_2 = \frac{21.956 \text{ k}\Omega(20 \text{ V})}{21.956 \text{ k}\Omega + 4.7 \text{ k}\Omega} = 16.47 \text{ V} \text{ (very close to ideal)}$$

c.

$$R_m = 20 \text{ V}[20,000 \Omega/\text{V}] = 400 \text{ k}\Omega$$

$$R'_T = 400 \text{ k}\Omega \parallel 22 \text{ k}\Omega = 20.853 \text{ k}\Omega$$

$$V_2 = \frac{20.853 \text{ k}\Omega(20 \text{ V})}{20.853 \text{ k}\Omega + 4.7 \text{ k}\Omega} = 16.32 \text{ V} \text{ (still very close to ideal)}$$

d.

$$\text{a. } V_2 = \frac{200 \text{ k}\Omega(20 \text{ V})}{200 \text{ k}\Omega + 100 \text{ k}\Omega} = 13.33 \text{ V}$$

$$\text{b. } R'_T = 200 \text{ k}\Omega \parallel 11 \text{ M}\Omega = 196.429 \text{ k}\Omega$$

$$\text{c. } V_2 = \frac{(196.429 \text{ k}\Omega)(20 \text{ V})}{196.429 \text{ k}\Omega + 100 \text{ k}\Omega} = 13.25 \text{ V} \text{ (very close to ideal)}$$

$$\text{d. } R_m = 400 \text{ k}\Omega$$

$$R'_T = 400 \text{ k}\Omega \parallel 200 \text{ k}\Omega = 133.333 \text{ k}\Omega$$

$$\text{e. } V_2 = \frac{(133.333 \text{ k}\Omega)(20 \text{ V})}{133.333 \text{ k}\Omega + 100 \text{k}\Omega} = 11.43 \text{ V} \text{ (a 1.824 V drop from } R_m = 11 \text{ M}\Omega \text{ level)}$$

DMM level of 11 MΩ not a problem for most situations

VOM level of 400 kΩ can be a problem for some situations.

4.

$$\text{a. } V_{ab} = 20 \text{ V}$$

$$\text{b. } V_{ab} = \frac{11 \text{ M}\Omega(20 \text{ V})}{11 \text{ M}\Omega + 1 \text{ M}\Omega} = 18.33 \text{ V}$$

$$\text{c. } R_m = 200 \text{ V}[20,000 \Omega/\text{V}] = 4 \text{ M}\Omega$$

$$\text{d. } V_{ab} = \frac{4 \text{ M}\Omega(20 \text{ V})}{4 \text{ M}\Omega + 1 \text{ M}\Omega} = 16.0 \text{ V} \text{ (significant drop from ideal)}$$

$$\text{e. } R_m = 20 \text{ V}[20,000 \Omega/\text{V}] = 400 \text{ k}\Omega$$

$$V_{ab} = \frac{400 \text{ k}\Omega(20 \text{ V})}{400 \text{ k}\Omega + 1 \text{ M}\Omega} = 5.71 \text{ V} \text{ (significant error)}$$

not operating properly, 6 kΩ not connected

$$\text{a. } R_T = \frac{6 \text{ V}}{1.71 \text{ mA}} = 1.71 \text{ k}\Omega$$

$$\text{b. } R_T = 3 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 1.71 \text{ k}\Omega$$

$$\text{c. } V_{ab} = E + I_{4 \text{ k}\Omega} \cdot R_{4 \text{ k}\Omega}$$

$$\text{d. } I_{4 \text{ k}\Omega} = \frac{12 \text{ V} - 4 \text{ V}}{1 \text{ k}\Omega + 4 \text{ k}\Omega} = \frac{8 \text{ V}}{5 \text{ k}\Omega} = 1.6 \text{ mA}$$

$$\text{e. } V_{ab} = 4 \text{ V} + (1.6 \text{ mA})(4 \text{ k}\Omega) = 4 \text{ V} + 6.4 \text{ V} = 10.4 \text{ V}$$

4 V supply connected in reverse so that

$$\text{f. } I = \frac{12 \text{ V} + 4 \text{ V}}{1 \text{ k}\Omega + 4 \text{ k}\Omega} = \frac{16 \text{ V}}{5 \text{ k}\Omega} = 3.2 \text{ mA}$$

and  $V_{ab} = 12 \text{ V} - (3.2 \text{ mA})(1 \text{ k}\Omega) = 12 \text{ V} - 3.2 \text{ V} = 8.8 \text{ V}$  obtained

## Chapter 7

1. a.  $R_1, R_2$ , and  $E$  are in series;  $R_3, R_4$  and  $R_5$  are in parallel.  
b.  $E$  and  $R_1$  are in series;  $R_2, R_3$  and  $R_4$  are in parallel.  
c.  $E$  and  $R_1$  are in series;  $R_2, R_3$  and  $R_4$  are in parallel.


2. a.  $E_1$  and  $R_1$  in series;  $R_2$  and  $R_3$  in parallel.  
b.  $E$  and  $R_1$  in series,  $R_2, R_3$  and  $R_4$  in parallel.  
c.  $E, R_1, R_2$  and  $R_3$  are in parallel;  $R_2$  and  $R_3$  are in parallel.

3. a.  $R_T = 4 \Omega + 10 \Omega \parallel (4 \Omega + 4 \Omega) + 4 \Omega = 4 \Omega + 10 \Omega \parallel 8 \Omega + 4 \Omega$   
 $= 4 \Omega + 4.44 \Omega + 4 \Omega = 12.44 \Omega$

- b.  $R_T = 10 \Omega + \frac{10 \Omega}{2} = 10 \Omega + 5 \Omega = 15 \Omega$

- c.  $R_T = 6.8 \Omega + 10 \Omega \parallel (8.2 \Omega + 1.2 \Omega)$   
 $= 6.8 \Omega + 10 \Omega \parallel 9.4 \Omega$   
 $= 6.8 \Omega + 4.85 \Omega = 11.65 \Omega$

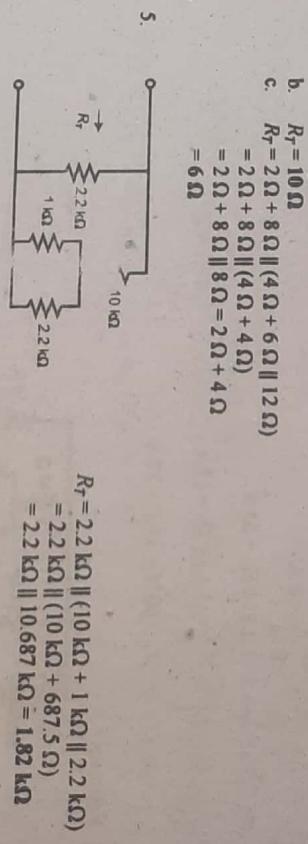4. a.  $R_T = \frac{4 \Omega}{2} + 10 \Omega = 2 \Omega + 10 \Omega = 12 \Omega$
- b.  $R_T = 10 \Omega$
- c.  $R_T = 2 \Omega + 8 \Omega \parallel (4 \Omega + 6 \Omega \parallel 12 \Omega)$   
 $= 2 \Omega + 8 \Omega \parallel (4 \Omega + 4 \Omega)$   
 $= 2 \Omega + 8 \Omega \parallel 8 \Omega = 2 \Omega + 4 \Omega$   
 $= 6 \Omega$



$$6. \quad R_T = 7.2 \text{ k}\Omega = R_1 \parallel \left( R_2 + \frac{R_3}{2} \right) = R_1 \parallel 1.5R_1$$

$$\text{so that } 7.2 \text{ k}\Omega = \frac{(R_1)(1.5R_1)}{R_1 + 1.5R_1} = \frac{1.5R_1^2}{2.5R_1} = \frac{1.5R_1}{2.5}$$

$$\text{and } R_1 = \frac{2.5(7.2 \text{ k}\Omega)}{1.5} = 1.2 \text{ k}\Omega$$

7.

- a. yes
- b.  $I_2 = I_1 - I_3 = 10 \text{ A} - 4 \text{ A} = 6 \text{ A}$
- c. yes
- d.  $V_3 = E - V_2 = 14 \text{ V} - 8 \text{ V} = 6 \text{ V}$

$$\text{e. } R'_T = 4 \Omega \parallel 2 \text{ }\Omega = 1.33 \text{ }\Omega, R''_T = 4 \Omega \parallel 6 \text{ }\Omega = 2.4 \text{ }\Omega$$

$$R_T = R'_T + R''_T = 1.33 \text{ }\Omega + 2.4 \text{ }\Omega = 3.73 \text{ }\Omega$$

f.  $R'_T = R''_T = \frac{20\Omega}{2} = 10\Omega$ ,  $R_T = R'_T + R''_T = 10\Omega + 10\Omega = 20\Omega$

$I_f = \frac{E}{R_f} = \frac{20V}{20\Omega} = 1A$

g.  $P_f = EI_f = P_{\text{absorbed}} = (20V)(1A) = 20W$

8. a.  $R'_T = R_1 \parallel R_2 = 10\Omega \parallel 15\Omega = 6\Omega$

$R_T = R'_T \parallel (R_3 + R_4) = 6\Omega \parallel (10\Omega + 2\Omega) = 6\Omega \parallel 12\Omega = 4\Omega$

b.  $I_f = \frac{E}{R_f} = \frac{36V}{4\Omega} = 9A$ ,  $I_1 = \frac{E}{R'_T} = \frac{36V}{6\Omega} = 6A$

$I_2 = \frac{E}{R_j + R_k} = \frac{36V}{10\Omega + 2\Omega} = 12\Omega = 3A$

$I_3 = \frac{E}{R_j} = \frac{36V}{4\Omega} = 9A - 6A = 3A$

$V_o = I_2 R_4 = (3A)(2\Omega) = 6V$

9. a.  $R_T = 11\Omega + \frac{27\Omega}{3} = 11\Omega + 9\Omega = 20\Omega$


$I_f = \frac{E}{R_f} = \frac{60V}{20\Omega} = 3A$

b.  $V_1 = I_f R_1 = (3A)(11\Omega) = 33V$

c.  $V_3 = I_2 \left( \frac{27\Omega}{3} \right) = (3A)(9\Omega) = 27V$

or  $V_3 = E - V_f = 60V - 33V = 27V$

10. Redrawn:

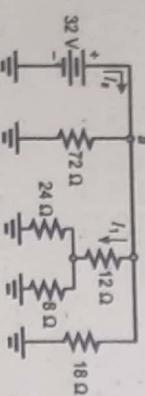

a.  $V_o = 32V$

$8\Omega \parallel 24\Omega = 6\Omega$

$V_o = \frac{6\Omega(32V)}{6\Omega + 12\Omega} = 10.67V$

b.  $I_1 = \frac{32V}{12\Omega + 6\Omega} = \frac{32V}{18\Omega} = 1.78A$


$R_T = 72\Omega \parallel \underbrace{18\Omega \parallel 18\Omega}_{9\Omega} = 8.12\Omega$

$I_f = \frac{E}{R_f} = \frac{32V}{8.12\Omega} = 3.94A$

11. a.  $V_a = 36V$ ,  $V_b = 60V$ ,  $V_c = \frac{5k\Omega(60V)}{5k\Omega + 10k\Omega} = 20V$

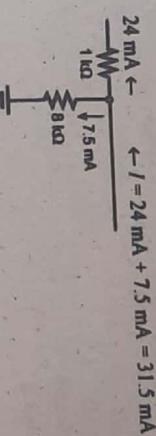b.  $I_f = \frac{60V - 36V}{1k\Omega} = 24mA$

$I_{\text{ano}} = \frac{60V}{8k\Omega} = 7.5mA$ ,  $I_{\text{hao}} = \frac{60V}{15k\Omega} = 4mA$



$\leftarrow I_2 = 31.5mA + 4mA = 35.5mA$

$\leftarrow I_f = 1.2k\Omega + 6.8k\Omega = 8k\Omega$ ,  $R'_T = 2k\Omega \parallel R''_T = 2k\Omega \parallel 8k\Omega = 1.6k\Omega$

$R''_T = R'_T + 2.4k\Omega = 1.6k\Omega + 2.4k\Omega = 4k\Omega$

$R_T = 1k\Omega \parallel R''_T = 1k\Omega \parallel 4k\Omega = 0.8k\Omega$

b.  $I_f = \frac{E}{R_f} = \frac{48V}{0.8k\Omega} = 60mA$

c.  $V = \frac{R'_T E}{R'_T + 24k\Omega} = \frac{(1.6k\Omega)(48V)}{1.6k\Omega + 2.4k\Omega} = 19.2V$

13.  $R_T = 2R \parallel 2R \parallel (R+R) = 2R \parallel 2R \parallel 2R = \frac{2R}{3}$

$R_T = \frac{E}{I} = \frac{120V}{8A} = 15\Omega$

$15\Omega = \frac{2R}{3}$  and  $R = \frac{3}{2}(15\Omega) = 22.5\Omega$

$2R = 45\Omega$

14.  $R_T = 1\Omega \parallel (1\Omega + 1\Omega + R_f) = 1\Omega \parallel (2\Omega + R_f)$

$$= \frac{2\Omega + R_f}{1\Omega + 2\Omega + R_f} = \frac{2\Omega + R_f}{3\Omega + R_f}$$

$R_f(3\Omega + R_f) = 2\Omega + R_f$

$3R_f + R_f^2 = 2\Omega + R_f$

$R_f^2 + 2R_f - 2\Omega = 0$

$$R_T = \frac{-2 \pm \sqrt{(2)^2 - 4(1)(-2)}}{2} \\ = \frac{-2 \pm \sqrt{4 + 8}}{2} = \frac{2 \pm \sqrt{12}}{2} = \frac{-2 \pm 2\sqrt{3}}{2} = \frac{2\sqrt{3} - 2}{2}$$

$R_f = -1 \pm 1.732 = 0.732\Omega$  or  $-2.732\Omega$

Since  $R_f < 1\Omega$  and positive choose  $R_f = 0.732\Omega$

15.

$$\begin{aligned}
 a. \quad R_T &= (R_1 \parallel R_2 \parallel R_3) \parallel (R_6 + R_4 \parallel R_5) \\
 &= (12 \text{k}\Omega \parallel 12 \text{k}\Omega \parallel 3 \text{k}\Omega) \parallel (10.4 \text{k}\Omega + 9 \text{k}\Omega \parallel 6 \text{k}\Omega) \\
 &= 2 \text{k}\Omega \parallel 14 \text{k}\Omega = 1.75 \text{k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 I_T &= \frac{E}{R_T} = \frac{28 \text{V}}{1.75 \text{k}\Omega} = 16 \text{mA}, \quad I_2 = \frac{E}{R_2} = \frac{28 \text{V}}{12 \text{k}\Omega} = 2.33 \text{mA} \\
 R' &= R_1 \parallel R_3 \parallel R_5 = 2 \text{k}\Omega \\
 R'' &= R_6 + R_4 \parallel R_5 = 14 \text{k}\Omega \\
 I_6 &= \frac{R'(I_T)}{R'+R''} = \frac{2 \text{k}\Omega(16 \text{mA})}{2 \text{k}\Omega + 14 \text{k}\Omega} = 2 \text{mA}
 \end{aligned}$$

b.  $V_1 = E = 28 \text{V}$

$$\begin{aligned}
 R' &= R_4 \parallel R_3 = 6 \text{k}\Omega \parallel 9 \text{k}\Omega = 3.6 \text{k}\Omega \\
 V_5 &= I_6 R' = (2 \text{mA})(3.6 \text{k}\Omega) = 7.2 \text{V}
 \end{aligned}$$

$$\begin{aligned}
 c. \quad P &= \frac{V_{R_3}^2}{R_3} = \frac{(28 \text{V})^2}{3 \text{k}\Omega} = 261.33 \text{ mW}
 \end{aligned}$$

16.

$$\begin{aligned}
 a. \quad I_1 \downarrow &= \frac{24 \text{V}}{4 \text{\Omega}} = 6 \text{A}; \quad V_{R_1} = 24 \text{V} - 8 \text{V} = 16 \text{V}, \quad I_2 \downarrow = V_{R_2} / R_2 = 16 \text{V}/2 \text{\Omega} = 8 \text{A} \\
 I_1 \downarrow &= \frac{8 \text{V}}{10 \text{\Omega}} = 0.8 \text{A}, \quad I = I_1 + I_2 = 6 \text{A} + 8 \text{A} = 14 \text{A}
 \end{aligned}$$

$$\begin{aligned}
 17. \quad I_1 &= \frac{20 \text{V}}{47 \text{\Omega}} = 425.5 \text{ mA} \\
 I_2 &= \frac{14 \text{V}}{160 \text{\Omega} \parallel 270 \text{\Omega}} = \frac{14 \text{V}}{100.47 \text{\Omega}} = 139.35 \text{ mA}
 \end{aligned}$$

18.

$$\begin{aligned}
 a. \quad R' &= R_4 + R_3 = 14 \text{\Omega} + 6 \text{\Omega} = 20 \text{\Omega} \\
 R'' &= R_2 \parallel R' = 20 \text{\Omega} \parallel 20 \text{\Omega} = 10 \text{\Omega} \\
 R''' &= R'' + R_1 = 10 \text{\Omega} + 10 \text{\Omega} = 20 \text{\Omega} \\
 R_T &= R_3 \parallel R''' = 5 \text{\Omega} \parallel 20 \text{\Omega} = 4 \text{\Omega} \\
 I_1 &= \frac{E}{R_T} = \frac{20 \text{V}}{4 \text{\Omega}} = 5 \text{A}
 \end{aligned}$$

$$b. \quad V_a = I_3 R_3 - I_4 R_5 = (4 \text{A})(5 \text{\Omega}) - (0.5 \text{A})(6 \text{\Omega}) = 20 \text{V} - 3 \text{V} = 17 \text{V}$$

$$V_{bc} = \left(\frac{I_1}{2}\right) R_2 = (0.5 \text{A})(20 \text{\Omega}) = 10 \text{V}$$

$$19. \quad a. \quad I_1 = \frac{E_1 - E_2}{R_1} = \frac{20 \text{V} - 15 \text{V}}{3 \text{\Omega}} = 1.67 \text{ A}$$

$$b. \quad I_2 = \frac{E_2}{R_2 + R_3 \parallel R_5} = \frac{15 \text{V}}{3 \text{\Omega} + 6 \text{\Omega} \parallel 6 \text{\Omega}} = \frac{15 \text{V}}{3 \text{\Omega} + 3 \text{\Omega}} = \frac{15 \text{V}}{6 \text{\Omega}} = 2.5 \text{ A}$$

$$I_3 = \frac{1}{2} I_2 = \frac{1}{2}(2.5 \text{A}) = 1.25 \text{A}$$

$$V_a = E_2 - I_2 R_2 = 15 \text{V} - (2.5 \text{A})(3\text{\Omega}) = 15 \text{V} - 7.5 \text{V} = 7.5 \text{V}$$

$$\begin{aligned}
 20. \quad a. \quad I_E &= \frac{V_E}{R_E} = \frac{2 \text{V}}{1 \text{k}\Omega} = 2 \text{mA} \\
 I_C &= I_E = 2 \text{mA}
 \end{aligned}$$

$$\begin{aligned}
 b. \quad I_B &= \frac{V_B}{R_B} = \frac{V_{CE} - (V_{BE} + V_T)}{R_B} = \frac{8 \text{V} - (0.7 \text{V} + 2 \text{V})}{220 \text{k}\Omega} \\
 &= \frac{8 \text{V} - 2.7 \text{V}}{220 \text{k}\Omega} = \frac{5.3 \text{V}}{220 \text{k}\Omega} = 24 \text{ pA}
 \end{aligned}$$

$$\begin{aligned}
 c. \quad V_B &= V_{BE} + V_E = 2.7 \text{V} \\
 V_C &= V_{CC} - I_C R_C = 8 \text{V} - (2 \text{mA})(22 \text{k}\Omega) = 8 \text{V} - 4.4 \text{V} = 3.6 \text{V}
 \end{aligned}$$

$$d. \quad V_{CE} = V_C - V_E = 3.6 \text{V} - 2 \text{V} = 1.6 \text{V}$$

$$V_{BC} = V_B - V_C = 2.7 \text{V} - 3.6 \text{V} = -0.9 \text{V}$$

$$21. \quad a. \quad I_2 = \frac{E_1}{R_1 + R_2} = \frac{2 \text{V}}{4 \text{\Omega} + 18 \text{\Omega}} = \frac{22 \text{V}}{22 \text{\Omega}} = 1 \text{A}$$

$$b. \quad +22 \text{V} + V_1 - 22 \text{V} = 0, \quad V_1 = 22 \text{V} - 22 \text{V} = 0 \text{V}$$

$$c. \quad I_1 = I_2 + \frac{V_1}{R_1} = 1 \text{A} + \frac{0 \text{V}}{R_1} = 1 \text{A}$$

$$I_1 = \frac{20 \text{V}}{R_1 + R''} = \frac{20 \text{V}}{10 \text{\Omega} + 10 \text{\Omega}} = \frac{20 \text{V}}{20 \text{\Omega}} = 1 \text{A}$$

$$I_3 = \frac{20 \text{V}}{5 \text{\Omega}} = 4 \text{A}$$

$$I_4 = \frac{I_1}{2} = (\text{since } R' = R_2) = \frac{1 \text{A}}{2} = 0.5 \text{A}$$

22. a. All resistors in parallel (between terminals a & b)



$$R_T = \underbrace{16\Omega}_{E} \parallel \underbrace{16\Omega}_{R_1} \parallel 8\Omega \parallel 4\Omega \parallel 32\Omega$$

$$\underbrace{8\Omega \parallel 18\Omega}_{8\Omega} \parallel 4\Omega \parallel 32\Omega$$

$$\underbrace{4\Omega \parallel 4\Omega}_{4\Omega} \parallel 32\Omega$$

$$2\Omega \parallel 32\Omega = 1.89\Omega$$

- b. All in parallel. Therefore,  $V_1 = V_4 = E = 32V$

$$I_3 = V_3/R_3 = 32V/4\Omega = 8A \leftarrow$$

$$d. I_1 = I_1 + I_2 + I_3 + I_4 + I_5$$

$$= \frac{32V}{16\Omega} + \frac{32V}{8\Omega} + \frac{32V}{4\Omega} + \frac{32V}{32\Omega} + \frac{32V}{16\Omega}$$

$$= 2A + 4A + 8A + 1A + 2A$$

$$= 17A$$

$$R_T = \frac{E}{I_T} = \frac{32V}{17A} = 1.88\Omega \text{ as above}$$

23. a.  $V_a = -6V, V_b = -20V$

$$b. I_{S1} \downarrow = \frac{20V}{5\Omega} = 4A$$

$$I_{S2} \rightarrow = \frac{V_{ab}}{2\Omega} = \frac{14V}{2\Omega} = 7A$$

$$I_{S3} \uparrow = \frac{6V}{3\Omega} = 2A$$

$$I_{ab} = I_{S1} + I_{S2} \uparrow, I_{bv} = I_{ab} - I_{S2} = 2A - 7A = -5A$$

$$I + I_{bv} = I_{S3}, I = I_{S3} - I_{bv} = 4A - (-5A) = 9A$$

$$c. V_{ab} = V_a - V_b = (-6V) - (-20V) = -6V + 20V = +14V$$

24. a. Applying Kirchoff's voltage law in the CCW direction in the upper "window":

$$+18V + 20V - V_{ab} = 0$$

$$V_{ab} = 38V$$

$$I_{ab} = \frac{38V}{8\Omega} = 4.75A$$

$$I_{S1} = \frac{18V}{3\Omega + 6\Omega} = \frac{18V}{9\Omega} = 2A$$

$$\text{KCL: } I_{18V} = 4.75A + 2A = 6.75A$$

$$b. V = (I_{ab})(6\Omega) + 20V = (2A)(6\Omega) + 20V = 12V + 20V = 32V$$

$$25. I_2 R_2 = I_3 R_3 \text{ and } I_2 = \frac{I_2 R_2}{R_2} = \frac{2R_3}{20} = \frac{R_3}{10} \text{ (since the voltage across parallel elements is the same)}$$

$$I_1 = I_2 + I_3 = \frac{R_3}{10} + 2$$


$$\text{KVL: } 120 = I_1 12 + I_3 R_3 = \left(\frac{R_3}{10} + 2\right) 12 + 2R_3$$

$$\text{and } 120 = 1.2R_3 + 24 + 2R_3$$

$$3.2R_3 = 96\Omega$$

$$R_3 = \frac{96\Omega}{3.2} = 30\Omega$$

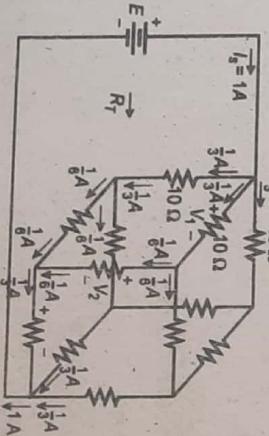26. Assuming  $I_T = 1A$ , the current  $I_T$  will divide as determined by the load appearing in each branch. Since balanced  $I_T$  will split equally between all three branches.



$$V_1 = \left(\frac{1}{3}A\right)(10\Omega) = \frac{10}{3}V$$

$$V_2 = \left(\frac{1}{6}A\right)(10\Omega) = \frac{10}{6}V$$

$$V_3 = \left(\frac{1}{3}A\right)(10\Omega) = \frac{10}{3}V$$

$$E = V_1 + V_2 + V_3 = \frac{10}{3}V + \frac{10}{6}V + \frac{10}{3}V = 8.33V$$

$$R_T = \frac{E - 8.33V}{I} = \frac{1A}{1A} = 8.33\Omega$$

27.

a.

$$R'_T = R_3 \parallel (R_6 + R_7) = 6\Omega \parallel 3\Omega = 2\Omega$$

$$R''_T = R_3 \parallel (R_4 + R'_T) = 4\Omega \parallel (2\Omega + 2\Omega) = 2\Omega$$

$$R_T = R_1 + R_2 + R''_T = 3\Omega + 5\Omega + 2\Omega = 10\Omega$$

$$I = \frac{240V}{10\Omega} = 24A$$

$$b. \quad I_4 = \frac{4\Omega(I)}{4\Omega+4} = \frac{4\Omega(24A)}{8} = 12A$$

$$I_7 = \frac{6\Omega(12A)}{6\Omega+3} = \frac{72A}{9} = 8A$$

$$c. \quad V_3 = I_3R_3 = (I - I_4)R_3 = (24A - 12A)4\Omega = 48V$$

$$V_5 = I_5R_5 = (I_4 - I_7)R_5 = (4A)6\Omega = 24V$$

$$V_7 = I_7R_7 = (8A)2\Omega = 16V$$

$$d. \quad P = I_7^2R_7 = (8A)^22\Omega = 128W$$

$$P = EI = (240V)(24A) = 5760W$$

28.

a.

$$R'_T = R_4 \parallel (R_6 + R_7 + R_8) = 2\Omega \parallel 7\Omega = 1.56\Omega$$

$$R''_T = R_2 \parallel (R_3 + R_5 + R'_T) = 2\Omega \parallel (4\Omega + 1\Omega + 1.56\Omega) = 1.53\Omega$$

$$R_T = R_1 + R''_T = 4\Omega + 1.53\Omega = 5.53\Omega$$

$$b. \quad I = 40V/5.53\Omega = 7.23A$$

$$c. \quad I_3 = \frac{2\Omega(I)}{2\Omega+6.56} = \frac{2\Omega(7.23A)}{2\Omega+6.56\Omega} = 1.69A$$

$$I_7 = \frac{2\Omega(1.69A)}{2\Omega+7\Omega} = 0.375mA$$

$$P_{k_1} = I^2R = (0.375A)^22\Omega = 0.281W$$

$$29. \quad a. \quad E = (40mA)(1.6k\Omega) = 64V$$

$$b. \quad R_{L_2} = \frac{48V}{12mA} = 4k\Omega$$


$$R_{L_1} = \frac{24V}{8mA} = 3k\Omega$$

$$c. \quad I_{k_1} = 72mA - 40mA = 32mA$$

$$I_{k_2} = 32mA - 12mA = 20mA$$

$$I_{k_3} = 20mA - 8mA = 12mA$$

31.

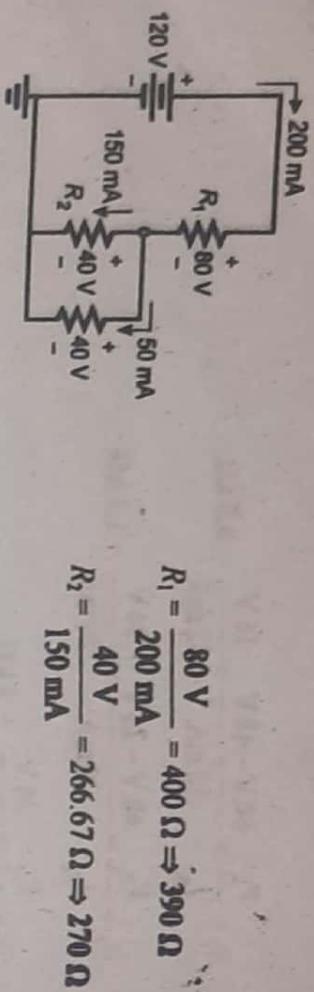32. a. yes,  $R_L \gg R_{\max}$  (potentiometer)

b. VDR:  $V_{k_1} = 3\text{ V} = \frac{R_2(12\text{ V})}{R_1 + R_2} = \frac{R_2(12\text{ V})}{1\text{ k}\Omega}$

$$R_2 = \frac{3\text{ V}(1\text{ k}\Omega)}{12\text{ V}} = 0.25\text{ k}\Omega = 250\Omega$$

$$R_1 = 1\text{ k}\Omega - 0.25\text{ k}\Omega = 0.75\text{ k}\Omega = 750\Omega$$

c.  $V_{k_1} = E - V_L = 12\text{ V} - 3\text{ V} = 9\text{ V}$  (Chose  $V_{k_1}$  rather than  $V_{k_2}$  since numerator of VDR equation "cleaner")

$$V_{k_1} = 9\text{ V} = \frac{R_1(12\text{ V})}{R_1 + (R_2 \parallel R_L)}$$

$$9R_1 + 9(R_2 \parallel R_L) = 12R_1$$

$$\left. \begin{aligned} R_1 &= 3(R_2 \parallel R_L) \\ R_1 + R_2 &= 1\text{ k}\Omega \end{aligned} \right\} \text{2 eq. 2 unk}(R_L = 10\text{ k}\Omega)$$

$$R_1 = \frac{3R_2R_L}{R_2 + R_L} \Rightarrow \frac{3R_2}{R_2 + 10\text{ k}\Omega}$$

and  $R_1(R_2 + 10\text{ k}\Omega) = 30\text{ k}\Omega R_2$

$$R_1R_2 + 10\text{ k}\Omega R_1 = 30\text{ k}\Omega R_2$$

$$R_1 + R_2 = 1\text{ k}\Omega: (1\text{ k}\Omega - R_2)R_2 + 10\text{ k}\Omega(1\text{ k}\Omega - R_2) = 30\text{ k}\Omega R_2$$

$$R_2^2 + 39\text{ k}\Omega R_2 - 10\text{ k}\Omega^2 = 0$$

$$R_2 = 0.255\text{ k}\Omega, -39.255\text{ k}\Omega$$

$$R_2 = 255\Omega$$

$$R_1 = 1\text{ k}\Omega - R_2 = 745\Omega$$

33. a.  $V_{ab} = \frac{80\Omega(40\text{ V})}{100\Omega} = 32\text{ V}$

$$V_{bc} = 40\text{ V} - 32\text{ V} = 8\text{ V}$$

b.  $80\Omega \parallel 1\text{ k}\Omega = 74.07\Omega$

$$20\Omega \parallel 10\text{k}\Omega = 19.96\Omega$$

$$V_{ab} = \frac{74.07\Omega(40\text{ V})}{74.07\Omega + 19.96\Omega} = 31.51\text{ V}$$

$$V_{bc} = 40\text{ V} - 31.51\text{ V} = 8.49\text{ V}$$

c.  $P = \frac{(31.51\text{ V})^2}{80\Omega} + \frac{(8.49\text{ V})^2}{20\Omega} = 12.411\text{ W} + 3.604\text{ W} = 16.02\text{ W}$

38.

a.  $I_{\text{C}} = 1 \text{ mA}$

b.  $R_{\text{out}} = \frac{k_I I_{\text{C}}}{I_{\text{L}} - I_{\text{C}}} = \frac{(1\text{k}\Omega)(50\mu\text{A})}{25\text{mA} - 0.05\text{mA}} = \frac{0.1}{20\text{A} - 1\text{mA}} = \frac{0.1}{20} \Omega = 5 \text{ m}\Omega$

39.  $25 \text{ mA}: R_{\text{out}} = \frac{(1\text{k}\Omega)(50\mu\text{A})}{25\text{mA} - 0.05\text{mA}} \equiv 2 \Omega$

$$\begin{aligned}50 \text{ mA}: R_{\text{out}} &= \frac{(1\text{k}\Omega)(50\mu\text{A})}{50\text{mA} - 0.05\text{mA}} = 1 \Omega \\100 \text{ mA}: R_{\text{out}} &\equiv 0.5 \Omega\end{aligned}$$

40. a.  $R_s = \frac{V_{\text{out}} - V_{\pi}}{I_{\text{C}}} = \frac{15\text{V} - (50\mu\text{A})(1\text{k}\Omega)}{50\mu\text{A}} = 300 \text{ k}\Omega$

b.  $\Omega/\text{V} = 1/I_{\text{C}} = 1/50 \mu\text{A} = 20,000$

41.  $5 \text{ V}: R_s = \frac{5\text{V} - (1\text{mA})(1000\Omega)}{1\text{mA}} = 4 \text{ k}\Omega$

$$50 \text{ V}: R_s = \frac{50\text{V} - 1\text{V}}{1\text{mA}} = 49 \text{ k}\Omega$$

$$500 \text{ V}: R_s = \frac{500\text{V} - 1\text{V}}{1\text{mA}} = 499 \text{ k}\Omega$$

42.  $10 \text{ M}\Omega = (0.5 \text{ V})(\Omega/\text{V}) \Rightarrow \Omega/\text{V} = 20 \times 10^6$

$$I_{\text{C}} = 1/(\Omega/\text{V}) = \frac{1}{20 \times 10^6} = 0.05 \mu\text{A}$$

43. a.  $R_s = \frac{E}{I_{\text{L}}} - R_{\text{in}} - \frac{\text{zero adjust}}{2} = \frac{3\text{V}}{100\mu\text{A}} - 1 \text{ k}\Omega - \frac{2\text{k}\Omega}{2} = 28 \text{ k}\Omega$

b.  $R_s = \frac{E}{I_{\text{L}}} + R_{\text{in}} + \frac{\text{zero adjust}}{2} + R_{\text{out}}$


$$R_{\text{out}} = \frac{E}{xI_{\text{L}}} - \left( R_{\text{in}} + R_{\text{in}} + \frac{\text{zero adjust}}{2} \right)$$

$$= \frac{3\text{V}}{x100\mu\text{A}} - 30 \text{ k}\Omega \Rightarrow \frac{30 \times 10^3}{x} - 30 \times 10^3$$

$$x = \frac{3}{4}, R_{\text{out}} = 10 \text{ k}\Omega; x = \frac{1}{2}, R_{\text{out}} = 30 \text{ k}\Omega; x = \frac{1}{4}, R_{\text{out}} = 90 \text{ k}\Omega$$

44.

# Chapter 8

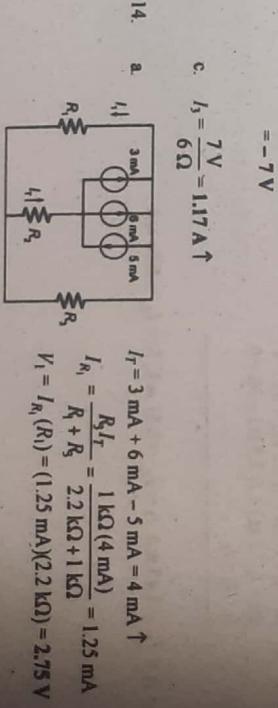1. a.  $I_1 = \frac{8\Omega(6A)}{8\Omega + 2\Omega} = 4.8A$     $I_2 = 6A - I_1 = 6A - 4.8A = 1.2A$   
 b.  $V_T = I_1 R_1 = (4.8A)(2\Omega) = 9.6V$
2. a.  $I_1 = I_2 = 20mA$
3. a.  $V_2 = I_2 R_2 = (20mA)(3.3k\Omega) = 66V$   
 $V_T = I_2 R_T = (20mA)(1.2k\Omega + 3.3k\Omega) = 20mA(4.5k\Omega) = 90V$
4. a.  $V_T = E = 24V$   
 b.  $I_2 = \frac{E}{R_1 + R_2} = \frac{24V}{1\Omega + 3\Omega} = \frac{24V}{4\Omega} = 6A$   
 c.  $I + I_2 = I_3$ ,  $I_2 = I_3 - I = 6A - 2A = 4A$
5.  $V_T = V_2 = V_T = IR_T = 0.6A[6\Omega || 24\Omega] = 0.6A[6\Omega || 12\Omega] = 2.4V$   
 $I_2 = \frac{V_2}{R_2} = \frac{2.4V}{24\Omega} = 0.1A$
- $V_3 = \frac{R_3 V_T}{R_2 + R_3} = \frac{16\Omega(24V)}{24\Omega} = 1.6V$
6. a.  $I_1 = \frac{E}{R_1} = \frac{24V}{2\Omega} = 12A$ ,  $I_4 = \frac{E}{R_2 + R_3} = \frac{24V}{6\Omega + 2\Omega} = \frac{24\Omega}{8\Omega} = 3A$   
 KCL:  $I + I_2 - I_1 - I_4 = 0$   
 $I_2 = I_1 + I_4$ ,  $-I = 12A + 3A - 4A = 11A$
- b.  $V_T = E = 24V$   
 VDR:  $V_3 = \frac{R_3 E}{R_2 + R_3} = \frac{2\Omega(24V)}{6\Omega + 2\Omega} = \frac{48V}{8\Omega} = 6V$
7. a.  $I = \frac{E}{R_p} = \frac{22V}{4.7\Omega} = 4.68A$ ,  $R_p = R_s = 4.7\Omega$   
 b.  $I = \frac{E}{R_p} = \frac{E}{R_s + R_p} = \frac{9V}{1.2k\Omega + 2.2k\Omega} = \frac{9V}{3.4k\Omega} = 2.65A$   
 $R_p = 3.4k\Omega$
8. a.  $E = IR_p = (6A)(12\Omega) = 72V$ ,  $R_s = 12\Omega$   
 b.  $R_p = R_s || R_2 = 2.7k\Omega || 8.1k\Omega = 2.03k\Omega$   
 $E = IR_p = (18mA)(2.03k\Omega) = 36.54V$ ,  $R_s = 2.03k\Omega$
9. a. CDR:  $I_L = \frac{R_s(I)}{R_s + R_L} = \frac{(91\Omega)(12mA)}{91\Omega + 10\Omega} = 10.81mA$   
 $I = \frac{E_s}{R_s + R_L} = \frac{1.092V}{91\Omega + 10\Omega} = 10.81mA$
10. a.  $E = IR_2 = (2A)(5.6\Omega) = 11.2V$ ,  $R = 5.6\Omega$   
 b.  $E_T = 12V + 11.2V = 23.2V$ ,  $R_T = 10\Omega + 5.6\Omega = 15.6\Omega$   
 c.  $I_3 = \frac{E_T}{R_T + 91\Omega} = \frac{23.2V}{15.6\Omega + 91\Omega} = 217.64mA$
11. a.  $I_T = 6.2A - 1.2A + 0.8A = 7A - 1.2A = 5.8A$   
 b.  $V_s = I_T R = (5.8A)(4\Omega) = 23.2V$
12. a.  $I_T \uparrow = 7A - 3A = 4A$   
 CDR:  $I_1 = \frac{R_2(I_T)}{R_1 + R_2} = \frac{6\Omega(4A)}{4\Omega + 6\Omega} = 2.4A$   
 $V_1 = I_1 R_1 = (2.4A)(4\Omega) = 9.6V$
13. a.  $I_T = \frac{E_2}{R_2} - \frac{E_1}{R_1} = \frac{20V}{2\Omega} - \frac{9V}{3\Omega}$   
 $= 10A - 3A = 7A \downarrow$
- b.  $V_{ab} = -I_T(R_1 || R_2 || R_3)$   
 $= -7A(3\Omega || 6\Omega || 2\Omega)$   
 $= -7A(1\Omega)$   
 $= -7V$
- c.  $I_3 = \frac{7V}{6\Omega} = 1.17A \uparrow$
14. a. 

15.

$$\text{a. } \begin{array}{l} I_1 \downarrow I_2 \uparrow I_3 \uparrow I_4 \\ 4 - 4I_1 - 8I_2 = 0 \\ 6 - 2I_2 - 8I_3 = 0 \\ I_1 + I_2 = I_3 \end{array}$$

$$I_1 = -\frac{1}{7}\text{A}, I_2 = \frac{5}{7}\text{A}, I_3 = \frac{4}{7}\text{A}$$

$$I_4 = I_1 = -\frac{1}{7}\text{A}, I_5 = I_2 = \frac{5}{7}\text{A}, I_6 = I_3 = \frac{4}{7}\text{A}$$

$$\text{18. a. } \begin{array}{l} I_1 \uparrow I_2 \uparrow I_3 \\ -1.2\text{k}\Omega I_1 + 9 - 8.2\text{k}\Omega I_3 = 0 \\ -10.2\text{k}\Omega I_2 + 8.2\text{k}\Omega I_3 + 6 = 0 \\ I_1 + I_2 = I_3 \end{array}$$

$$I_1 = 2.03\text{ mA}, I_2 = 1.23\text{ mA}, I_3 = 0.8\text{ mA}$$

$$I_4 = I_1 = 2.03\text{ mA}$$

$$I_5 = I_3 = 0.8\text{ mA}$$

$$I_6 = I_2 = I_3 = 1.23\text{ mA} = I_9\text{ mA}$$

$$\text{b. } V_o = I_3 R_3 = \left(\frac{4}{7}\text{A}\right)(8\Omega) = 4.57\text{ V}$$

16.

$$\text{a. } \begin{array}{l} I_1 \downarrow I_2 \uparrow I_3 \uparrow I_4 \\ 10 + 12 - 3I_3 - 4I_1 = 0 \\ 12 - 3I_3 - 12I_2 = 0 \\ I_1 + I_2 = I_3 \end{array}$$


$$\begin{array}{l} I_1 = 3.06\text{ A} \\ I_2 = 0.19\text{ A} \\ I_3 = 3.25\text{ A} \end{array}$$

$$\begin{array}{l} I_4 = I_1 = 3.06\text{ A}, I_5 = I_2 = 0.19\text{ A} = I_{120} \\ I_6 = I_3 = 3.25\text{ A} \end{array}$$

$$\text{19. } V_J = I_2 R_4 = (1.23\text{ mA})(1.1\text{k}\Omega) = 1.35\text{ V}$$

$$V_o = 6\text{ V} - V_J = 6\text{ V} - 1.35\text{ V} = 4.65\text{ V}$$
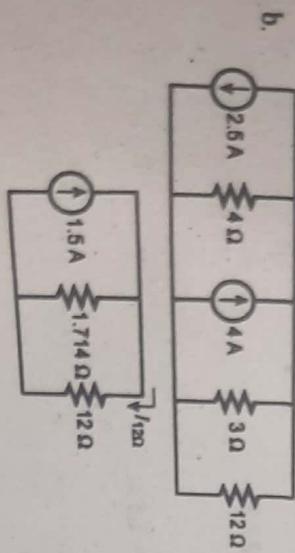
$$\begin{array}{l} I_1 = I_4 \text{ (CW)}, I_2 = I_5 \text{ (down)}, I_3 = I_6 \text{ (CW)}, I_4 = I_6 \text{ (down)} \\ I_5 = I_6 \text{ (CW)} \end{array}$$



$$I_{120} = \frac{(1.714\Omega)(1.5\text{ A})}{1.714\Omega + 12\Omega} = 0.19\text{ A}$$

17.

$$\begin{array}{l} I_1 \downarrow I_2 \uparrow I_3 \uparrow I_4 \\ 10 - I_1 5.6\text{k}\Omega - I_2 2.2\text{k}\Omega + 20 = 0 \\ -20 + I_3 2.2\text{k}\Omega + I_2 3.3\text{k}\Omega - 30 = 0 \\ I_1 + I_2 = I_3 \end{array}$$

c. the same

$$\text{d. } I_3 = I_4 = -63.69\text{ mA (CW)}$$

$$I_1 = I_4 = 1.45\text{ mA}, I_2 = I_6 = 8.51\text{ mA}, I_3 = I_5 = 9.96\text{ mA}$$

$$20. \quad a. \quad \overline{I_1 I_2} \quad \frac{4 - 4I_1 - 8(I_1 - I_2) = 0}{-8(I_2 - I_1) - 2I_1 - 6 = 0}$$

$$I_1 = -\frac{1}{7}\text{A}, I_2 = -\frac{5}{7}\text{A}$$

$$I_3 = I_1 = -\frac{1}{7}\text{A}$$

$$I_4 = I_2 = -\frac{5}{7}\text{A}$$

$$I_1 = -3.31\text{ A}$$

$$I_2 = I_1 - I_2 = \left( \frac{1}{7}\text{A} \right) - \left( -\frac{5}{7}\text{A} \right) = \frac{4}{7}\text{A} \text{ (dir. of } I_1)$$

$$b. \quad V_a = I_{R_3} R_3 = \left( \frac{4}{7}\text{A} \right) (8\Omega) = 4.57\text{ V}$$

$$21. \quad a. \quad \overline{I_1 I_2} \quad \frac{-10 - 4I_1 - 3(I_1 - I_2) - 12 = 0}{12 - 3(I_2 - I_1) - 12I_2 = 0}$$

$$I_1 = -3.06\text{ A}, I_2 = 0.19\text{ A}$$

$$I_4 = 3.06\text{ A} \text{ (CCW)}$$

$$I_2 = I_1 - I_2 = (-3.06\text{ A}) - (0.19\text{ A}) = -3.25\text{ A}$$

$$b. \quad P_R = I_k E_2 = (3.25\text{ A})(12\text{ V}) = 39\text{ W}$$

$$P_R = I_k^2 R_2 = (0.19\text{ A})^2 12\Omega = 433.2\text{ mW}$$

$$22. \quad a. \quad \overline{I_1 I_2} \quad \frac{10 - I_1(5.6\text{ k}\Omega) - 2.2\text{ k}\Omega(I_1 - I_2) + 20 = 0}{-20 - 2.2\text{ k}\Omega(I_2 - I_1) - I_2 3.3\text{ k}\Omega - 30 = 0}$$

$$I_1 = 1.45\text{ mA}, I_2 = 8.51\text{ mA}$$

$$I_4 = I_1 = 1.45\text{ mA}, I_3 = I_2 = 8.51\text{ mA}$$

$$I_4 = I_2 - I_1 = 7.06\text{ mA} \text{ (direction of } I_2)$$

$$b. \quad V_{33\Omega} = I_2 R_2 = (8.51\text{ mA})(3.3\text{ k}\Omega) = 28.1\text{ V}$$

$$23. \quad a. \quad \overline{I_1 I_2} \quad \frac{-I_1(1.2\text{ k}\Omega) + 9 - 8.2\text{ k}\Omega(I_1 - I_2) = 0}{-I_2(1.1\text{ k}\Omega) + 6 - I_2(9.1\text{ k}\Omega) - 8.2\text{ k}\Omega(I_2 - I_1) = 0}$$

$$I_1 = 2.03\text{ mA}, I_2 = 1.23\text{ mA}$$

$$I_4 = I_1 = 2.03\text{ mA}, I_3 = I_2 = 1.23\text{ mA}$$

$$b. \quad V_a = 6\text{ V} - I_2(1.1\text{ k}\Omega) = 6\text{ V} - (1.23\text{ mA})(1.1\text{ k}\Omega) = 6\text{ V} - 1.35\text{ V} = 4.65\text{ V}$$

$$24. \quad a. \quad I_1 I_2 I_3 \quad \frac{10 - I_2 - 1(I_1 - I_3) = 0}{I_3 - I_1 + 0 = 10}$$

$$\frac{-(I_2 - I_1) - I_2 4 - 5(I_2 - I_3) = 0}{-5(I_2 - I_1) - I_3 3 - 6 = 0}$$

$$\frac{3I_1 - I_2 + 0 = 10}{-I_1 + 10I_2 - 5I_3 = 0}$$

$$\frac{0 - 5I_2 + 8I_3 = -6}{I_1 = 3.31\text{ A}, I_2 = -63.69\text{ mA}, I_3 = -789.8\text{ mA}}$$

b, c. Ignore

$$d. \quad I_{10V} \uparrow = I_1 = 3.31\text{ A}$$

$$I_{10V} \uparrow = -I_3 = -(-789.8\text{ mA}) = 789.8\text{ mA}$$

$$25. \quad a. \quad I_1 I_2 I_3 \quad \frac{-I_1 2.2\text{ k}\Omega - (I_1 - I_2) 9.1\text{ k}\Omega + 18\text{ V} = 0}{-18\text{ V} - (I_2 - I_1) 9.1\text{ k}\Omega - 7.5\text{ k}\Omega I_2 - (I_2 - I_3) 6.8\text{ k}\Omega = 0}$$

$$-6.8\text{ k}\Omega(I_3 - I_2) - 3\text{ V} - 3.3\text{ k}\Omega I_3 = 0$$

with

$$\frac{11.3\text{ k}\Omega I_1 - 9.1\text{ k}\Omega I_2 = 18\text{ V}}{23.4\text{ k}\Omega I_2 - 9.1\text{ k}\Omega I_1 - 6.8\text{ k}\Omega I_3 = -18\text{ V}}$$

$$\frac{10.1\text{ k}\Omega I_3 - 6.8\text{ k}\Omega I_2 = -3\text{ V}}{11.3\text{ k}\Omega I_1 - 9.1\text{ k}\Omega I_2 = 18\text{ V}}$$

or

$$\frac{-9.1\text{ k}\Omega I_2 + 23.4\text{ k}\Omega I_2 - 6.8\text{ k}\Omega I_3 = -18\text{ V}}{-6.8\text{ k}\Omega I_2 + 10.1\text{ k}\Omega I_3 = -3\text{ V}}$$

$$c. \quad I_{E_1} \downarrow = I_1 - I_2 = 1.21\text{ mA} - (-0.48\text{ mA}) = 1.69\text{ mA}$$

$$I_{E_2} \uparrow = -I_3 = -(-0.62\text{ mA}) = 0.62\text{ mA}$$

$$26. \quad a. \quad I_1 I_2 I_3 \quad \frac{-4(I_1 - 3(I_1 - I_2)) - 4(I_1 - I_3) = 0}{-3(I_2 - I_1) - 10I_2 - 15 - 4(I_2 - I_3) = 0}$$

$$\frac{-7I_3 - 4(I_3 - I_1) - 4(I_3 - I_2) = 0}{}$$

$$b. \quad I_1 = -430.4\text{ mA}, I_2 = -1.05\text{ A}, I_3 = -395.1\text{ mA}$$

$$c. \quad I_4 = I_1 = -430.4\text{ mA}$$


$$27. \quad a. \quad I_1 I_2 I_3 \quad \frac{-6.8\text{ k}\Omega I_1 - 4.7\text{ k}\Omega(I_1 - I_2) + 6 - 2.2\text{ k}\Omega(I_1 - I_3) = 0}{-6 - 4.7\text{ k}\Omega(I_2 - I_1) - 8.2\text{ k}\Omega(I_2 - I_3) = 0}$$

$$\frac{-1.1\text{ k}\Omega I_3 - 22\text{ k}\Omega(I_3 - I_2) - 8.2\text{ k}\Omega(I_3 - I_2) - 9 = 0}{-1.2\text{ k}\Omega I_2 - 2\text{ k}\Omega(I_1 - I_2) - 22\text{ k}\Omega(I_1 - I_2) = 0}$$

b.  $I_1 = -0.597 \text{ mA}, I_2 = -2.13 \text{ mA}, I_3 = -2.27 \text{ mA}, I_4 = -2.03 \text{ mA}$

c.  $I_{6V} = I_1 - I_2 = -0.597 \text{ mA} - (-2.13 \text{ mA}) = 1.53 \text{ mA}$   
 $P_{6V} = E I_{6V} = (6 \text{ V})(1.53 \text{ mA}) = 9.18 \text{ mW}$

28. a. Network redrawn:

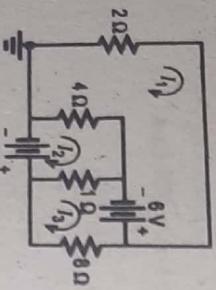

b.  $-2I_1 - 6 - 4I_1 + 4I_2 = 0$   
 $-4I_2 + 4I_1 - I_2 + I_3 - 6 = 0$   
 $-I_3 + I_2 + 6 - 8I_4 = 0$

c.  $I_1 = -3.8 \text{ A}, I_2 = -4.20 \text{ A}, I_3 = 0.20 \text{ A}$

d.  $P_{R_1} = E_1 I_1 = (6 \text{ V})(0.2 \text{ A}) = 1.2 \text{ W}$

$P_R = E_1 I_2 = (6 \text{ V})(4.2 \text{ A}) = 25.2 \text{ W}$

$P_T = P_{R_1} + P_R = 1.2 \text{ W} + 25.2 \text{ W} = 26.4 \text{ W}$


29. a.  $20 \text{ V} - I_E(270 \text{ k}\Omega) - 0.7 \text{ V} - I_E(0.51 \text{ k}\Omega) = 0$   
 $I_E(0.51 \text{ k}\Omega) + 8 \text{ V} + I_E(2.2 \text{ k}\Omega) - 20 \text{ V} = 0$   
 $I_E = I_B + I_C$

$I_B = 63.02 \mu\text{A}, I_C = 4.42 \text{ mA}, I_E = 4.48 \text{ mA}$

b.  $V_B = 20 \text{ V} - I_E(270 \text{ k}\Omega) = 20 \text{ V} - (63.02 \mu\text{A})(270 \text{ k}\Omega) = 20 \text{ V} - 17.02 \text{ V} = 2.98 \text{ V}$   
 $V_E = I_E R_E = (4.48 \text{ mA})(51 \text{ k}\Omega) = 2.28 \text{ V}$   
 $V_C = 20 \text{ V} - I_C(2.2 \text{ k}\Omega) = 20 \text{ V} - (4.42 \text{ mA})(2.2 \text{ k}\Omega) = 20 \text{ V} - 9.72 \text{ V} = 10.28 \text{ V}$

c.  $\beta \equiv I_C/I_B = 4.42 \text{ mA}/63.02 \mu\text{A} = 70.14$

30.

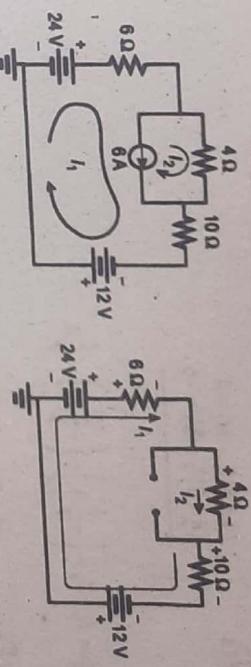

$24 \text{ V} - 6I_1 - 4I_2 - 10I_1 + 12 \text{ V} = 0$   
and  
 $16I_1 + 4I_2 = 36$   
 $16I_2 + 96 + 4I_2 = 36$   
 $20I_2 = -60$   
 $I_2 = -3 \text{ A}$


$I_1 = I_2 + 6 \text{ A}$   
 $I_1 = 6 \text{ A}$

$I_1 = I_2 + 6 \text{ A}$   
 $10I_1 + 4I_2 = 36$   
 $10I_2 + 96 + 4I_2 = 36$   
 $14I_2 = -60$   
 $I_2 = -3 \text{ A}$

$I_1 = I_2 + 6 \text{ A} = -3 \text{ A} + 6 \text{ A} = 3 \text{ A}$

$I_{24V} = I_{6\Omega} = I_{10\Omega} = I_{12V} = 3 \text{ A} (\text{CW})$   
 $I_{4\Omega} = 3 \text{ A} (\text{CCW})$

31.

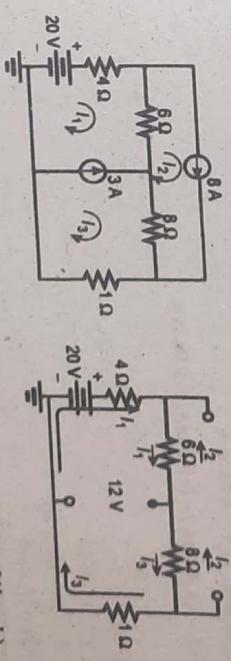

$20 \text{ V} - 4I_1 - 6(I_1 - I_2) - 8(I_3 - I_2) - 1I_3 = 0$   
 $10I_1 - 14I_2 + 9I_3 = 20$   
 $I_2 - I_1 = 3 \text{ A}$

$I_2 = 8 \text{ A}$

$10I_1 - 14(8 \text{ A}) + 9[I_1 + 3 \text{ A}] = 20$   
 $19I_1 = 105$

$I_1 = 5.526 \text{ A}$   
 $I_3 = I_1 + 3 \text{ A} = 5.526 \text{ A} + 3 \text{ A} = 8.526 \text{ A}$

$I_{20V} = I_{4\Omega} = 5.53 \text{ A} (\text{dir. of } I_1)$   
 $I_{6\Omega} = I_2 - I_1 = 2.47 \text{ A} (\text{dir. of } I_2)$   
 $I_{10\Omega} = I_3 - I_2 = 0.53 \text{ A} (\text{dir. of } I_3)$   
 $I_{12V} = 8.53 \text{ A} (\text{dir. of } I_3)$

32. a.  $\overrightarrow{I_1} \overrightarrow{I_2}$

$$\frac{(4+8)I_1 - 8I_2 = 4}{(8+2)I_2 - 8I_1 = -6}$$

b.  $I_{\text{an}} \downarrow = I_1 - I_2 = \left(-\frac{1}{7}\text{A}\right) - \left(-\frac{5}{7}\text{A}\right) = \frac{4}{7}\text{A}$

33. a.  $\overrightarrow{I_1} \overrightarrow{I_2}$        $\frac{(4+3)I_1 - 3I_2 = -10 - 12}{(3+12)I_2 - 3I_1 = 12}$

b.  $I_{\text{an}} \uparrow = I_2 - I_1 = 0.19\text{ A} - (-3.06\text{ A}) = 3.25\text{ A}$

34. a.  $\overrightarrow{I_1} \overrightarrow{I_2}$

$$\begin{aligned} I_1(5.6\text{ k}\Omega + 2.2\text{ k}\Omega) - 2.2\text{ k}\Omega(I_2) &= 10 + 20 \\ I_2(2.2\text{ k}\Omega + 3.3\text{ k}\Omega) - 2.2\text{ k}\Omega(I_1) &= -20 - 30 \end{aligned}$$

b.  $I_{E_1} = I_1 = 1.45\text{ mA}, I_{E_2} \uparrow = 8.51\text{ mA},$

$$I_{E_2} \downarrow = I_1 - I_2 = (1.45\text{ mA}) - (-8.5\text{ mA}) = 9.96\text{ mA}$$

35. a.  $I_1 \downarrow I_2 \uparrow I_3 \uparrow$

$$\begin{aligned} I_1(2+1) - 1I_2 &= 10 \\ I_2(1+4+5) - 1I_1 - 5I_3 &= 0 \\ I_3(5+3) - 5I_2 &= -6 \end{aligned}$$

b.  $I_1 = 3.31\text{ A}, I_2 = -63.69\text{ mA}, I_3 = -789.8\text{ mA}$

c.  $I_{k_1} = I_1 - I_2 = (3.31\text{ A}) - (-63.69\text{ mA}) = 3.37\text{ A}$

36. a.  $I_1 \downarrow I_2 \uparrow I_3 \uparrow$

$$\begin{aligned} (2.2\text{ k}\Omega + 9.1\text{ k}\Omega)I_1 - 9.1\text{ k}\Omega I_2 &= 18 \\ (9.1\text{ k}\Omega + 7.5\text{ k}\Omega + 6.8\text{ k}\Omega)I_2 - 9.1\text{ k}\Omega I_1 - 6.8\text{ k}\Omega I_3 &= -18 \\ (6.8\text{ k}\Omega + 3.3\text{ k}\Omega)I_3 - 6.8\text{ k}\Omega I_2 &= -3 \end{aligned}$$

b.  $I_1 = 1.21\text{ mA}, I_2 = -0.48\text{ mA}, I_3 = -0.62\text{ mA}$

c.  $I_{k_1} \downarrow = I_1 - I_2 = 1.21\text{ mA} - (-0.48\text{ mA}) = 1.69\text{ mA}$

$$I_{k_2} \uparrow = -I_3 = -(-0.62\text{ mA}) = 0.62\text{ mA}$$

40.

$$\begin{aligned} \text{a. } & \frac{V_1}{I_1}, \frac{V_2}{I_2}, \frac{V_3}{I_3} \\ & \frac{(2\Omega + 4\Omega) - I_1 4\Omega = -6V}{I_1 (4\Omega + 1\Omega) - I_2 4\Omega - I_3 1\Omega = -6V} \\ & \frac{I_1 (1\Omega + 8\Omega) - I_2 1\Omega = 6V}{\underline{\underline{}} \quad \underline{\underline{}}} \end{aligned}$$

$$\begin{aligned} 6I_1 - 4I_2 &= -6V \\ -4I_1 + 5I_2 - I_3 &= -6V \\ -I_2 + 9I_3 &= 6V \end{aligned}$$

$$\begin{aligned} I_{10} &= -3.8A, I_2 = -4.20A, I_3 = 0.2A \\ I_{R_1} &= I_1 - I_2 = -3.8A - (-4.20A) \\ &= -3.8A + 4.20A \\ &= 0.4A \end{aligned}$$

$$\begin{aligned} I_{10} &= I_2 - I_3 = -4.20A - 0.2A \\ &= -4.4A \end{aligned}$$

$$\begin{aligned} V_{10} &= (I_{10})(1\Omega) = (-4.4A)(1\Omega) \\ &= -4.4V \end{aligned}$$

$$\begin{aligned} \text{41. a. } & \frac{V_1}{\circ}, \frac{V_2}{\circ} \\ \text{At } V_1: \Sigma I_i &= \Sigma I_o \\ 0 &= \frac{V_1}{2\Omega} + 5A + \frac{V_1 - V_2}{8\Omega} \end{aligned}$$

$$\text{At } V_2: \Sigma I_i = \Sigma I_o$$

$$\frac{V_1 - V_2}{8\Omega} = 3A + \frac{V_2}{4\Omega}$$

$$\text{and } V_1 \left[ \frac{1}{2} + \frac{1}{8} \right] - V_2 \left[ \frac{1}{8} \right] = -5$$

$$\begin{aligned} -V_1 \left[ \frac{1}{8} \right] + V_2 \left[ \frac{1}{8} + \frac{1}{4} \right] &= 3 \\ \underline{\underline{}} \quad \underline{\underline{}} \end{aligned}$$

$$\text{b. } V_1 = -10.27V, V_2 = -11.36V$$

$$\text{c. } V_{8\Omega} = V_1 - V_2 = -10.27V - (-11.36V) = 1.09V$$

$$\text{d. } I_{2\Omega} \uparrow = \frac{V_1}{2\Omega} = \frac{10.27V}{2\Omega} = 5.14A$$

$$I_{4\Omega} \uparrow = \frac{V_2}{4\Omega} = \frac{11.36V}{4\Omega} = 2.84A$$

$$\begin{aligned} \text{42. a. } & \frac{V_1}{\circ}, \frac{V_2}{\circ} \\ \text{At } V_1: \Sigma I_i &= \Sigma I_o \\ 0 &= \frac{V_1}{8\Omega} + 12A + I_{20} \text{ and } V_1 - I_6 6\Omega - 54V - V_2 = 0 \end{aligned}$$

$$\text{or } I = \frac{V_1 - V_2 - 54V}{6\Omega} = \frac{V_1}{6\Omega} + \frac{V_2}{6\Omega} - 9A$$

$$\text{so that } 0 = \frac{V_1}{8\Omega} + 12A + \frac{V_1}{6\Omega} - \frac{V_2}{6\Omega} - 9A$$

$$\text{or } V_1 \left[ \frac{1}{8\Omega} + \frac{1}{6\Omega} \right] - V_2 \left[ \frac{1}{6\Omega} \right] = -12A + 9A = -3A$$

$$\text{At } V_2: \Sigma I_i = \Sigma I_o$$

$$I = \frac{V_2}{20\Omega} + \frac{V_2}{5\Omega}$$

$$\text{or } \frac{V_1}{6\Omega} - \frac{V_2}{6\Omega} - 9A = \frac{V_2}{20\Omega} + \frac{V_2}{5\Omega}$$

$$\text{and } V_2 \left[ \frac{1}{6\Omega} + \frac{1}{20\Omega} + \frac{1}{5\Omega} \right] - V_1 \left[ \frac{1}{6\Omega} \right] = -9A$$

$$\text{resulting in } V_1 \left[ \frac{1}{8\Omega} + \frac{1}{6\Omega} \right] - V_2 \left[ \frac{1}{6\Omega} \right] = -3A$$

$$\begin{aligned} -V_1 \left[ \frac{1}{6\Omega} \right] + V_2 \left[ \frac{1}{6\Omega} + \frac{1}{20\Omega} + \frac{1}{5\Omega} \right] &= -9A \\ \underline{\underline{}} \quad \underline{\underline{}} \end{aligned}$$

$$\text{b. } V_1 = -29.29V, V_2 = -33.34V$$

$$\text{c. } I_{20\Omega} \uparrow = \frac{V_2}{20\Omega} - \frac{33.34V}{20\Omega} = 1.67A$$

$$\begin{aligned} \text{43. a. } & \frac{V_1}{\circ}, \frac{V_2}{\circ} \\ \text{At } V_1: \Sigma I_i &= \Sigma I_o \end{aligned}$$

$$\begin{aligned} 4A &= \frac{V_1}{2\Omega} + \frac{V_1 - V_2}{4\Omega} + 2A \\ \text{At } V_2: \Sigma I_i &= \Sigma I_o \end{aligned}$$

$$2A + \frac{V_1 - V_2}{4\Omega} = \frac{V_2}{20\Omega} + \frac{V_2}{5\Omega}$$

or

$$\begin{aligned} V_1 \left[ \frac{1}{2} + \frac{1}{4} \right] - V_2 \left[ \frac{1}{4} \right] &= 2 \\ -V_1 \left[ \frac{1}{4} \right] + V_2 \left[ \frac{1}{4} + \frac{1}{20} + \frac{1}{5} \right] &= 2 \end{aligned}$$

$$\text{b. } V_1 = 4.8V, V_2 = 6.4V$$

c.  
 i<sub>1</sub>:  $P = V_1 I_1 = (4.8 \text{ V})(4 \text{ A}) = 19.2 \text{ W}$   
 i<sub>2</sub>:  $P = |(V_1 - V_2)I_2| = |(4.8 \text{ V} - 6.4 \text{ V})(2 \text{ A})| = 3.2 \text{ W}$

44. a.  $\begin{matrix} V_1 & V_2 \\ \circ & \circ \end{matrix}$

At  $V_1$ :  $\Sigma I_i = \Sigma I_o$

$$0 = 6 \text{ A} + \frac{V_1 - V_2}{5\Omega} + \frac{V_1 - V_2}{3\Omega} + \frac{V_1 - V_2}{2\Omega}$$

At  $V_2$ :  $\Sigma I_i = \Sigma I_o$

$$7 \text{ A} + \frac{V_1 - V_2}{3\Omega} + \frac{V_1 - V_2}{2\Omega} = \frac{V_2}{4\Omega} + \frac{V_2}{8\Omega}$$

$$\text{so that } V_1 \left[ \frac{1}{5\Omega} + \frac{1}{3\Omega} + \frac{1}{2\Omega} \right] - V_2 \left[ \frac{1}{3\Omega} + \frac{1}{2\Omega} \right] = -6 \text{ A}$$

$$V_2 \left[ \frac{1}{4\Omega} + \frac{1}{8\Omega} + \frac{1}{3\Omega} + \frac{1}{2\Omega} \right] - V_1 \left[ \frac{1}{3\Omega} + \frac{1}{2\Omega} \right] = 7 \text{ A}$$

$$\text{or } \begin{aligned} 1.03V_1 - 0.833V_2 &= -6 \\ -0.833V_1 + 1.21V_2 &= 7 \end{aligned}$$

b.  $V_1 = -2.59 \text{ V}, V_2 = 4 \text{ V}$

c.  $V_{2\Omega} = V_{3\Omega} = V_2 - V_1 = 4 \text{ V} - (-2.59 \text{ V}) = 6.59 \text{ V}$   
 $V_{3\Omega} = V_1 = -2.59 \text{ V}$   
 $V_{4\Omega} = V_{8\Omega} = V_2 = 4 \text{ V}$

45. a.  $\begin{matrix} V_1 & V_2 \\ \circ & \circ \end{matrix}$

Source conversion:  $I_3 = \frac{12 \text{ V}}{4\Omega} = 3 \text{ A}, R_p = R_3 = 4 \Omega$

At  $V_1$ :  $\Sigma I_i = \Sigma I_o$

$$0 = \frac{V_1}{3\Omega} + \frac{V_1}{6\Omega} + 5 \text{ A} + \frac{V_1 - V_2}{4\Omega} + 3 \text{ A}$$

At  $V_2$ :  $\Sigma I_i = \Sigma I_o$

$$3 \text{ A} + \frac{V_1 - V_2}{4\Omega} = \frac{V_2}{8\Omega} + 4 \text{ A}$$

Rewritten:  $V_1 \left[ \frac{1}{3\Omega} + \frac{1}{6\Omega} + \frac{1}{4\Omega} \right] - \frac{V_2}{4\Omega} = -5 \text{ A} - 3 \text{ A}$   
 $-V_1 \left[ \frac{1}{4\Omega} \right] + V_2 \left[ \frac{1}{4\Omega} + \frac{1}{8\Omega} \right] = -4 \text{ A} + 3 \text{ A}$

b.  $V_1 = -14.86 \text{ V}, V_2 = -12.57 \text{ V}$

c.  $I_{6\Omega} \uparrow = \frac{14.86 \text{ V}}{6\Omega} = 2.48 \text{ A}$

$$c. V_{R_4} = V_1 - V_2$$

$$= (-5.43 \text{ V}) - (8.53 \text{ V})$$


$$= -13.96 \text{ V}$$

Rewritten:

$$V_1 \left[ \frac{1}{2\Omega} + \frac{1}{6\Omega} \right] - \frac{1}{6\Omega} V_1 = -5 \text{ A}$$

$$V_1 \left[ \frac{1}{4\Omega} \right] = 5 \text{ A} - 2 \text{ A}$$
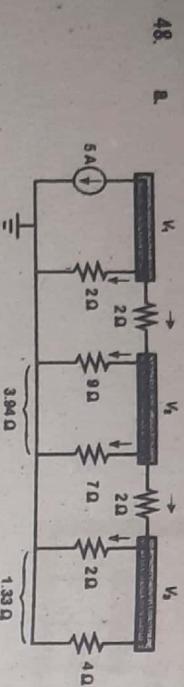
$$V_1 \left[ \frac{1}{6\Omega} + \frac{1}{5\Omega} \right] - \frac{1}{6\Omega} V_1 = 2 \text{ A}$$



$$V_1: \Sigma I_i = \Sigma I_o$$

$$0 = 5 \text{ A} + \frac{V_1 - V_2}{2\Omega} + \frac{V_1 - V_3}{2\Omega}$$

$$V_2: \Sigma I_i = \Sigma I_o$$

$$\frac{V_1 - V_2}{2\Omega} = \frac{V_2}{3.94\Omega} + \frac{V_2 - V_3}{2\Omega}$$

$$V_3: \Sigma I_i = \Sigma I_o$$

$$\frac{V_2 - V_3}{2\Omega} = \frac{V_3}{1.33\Omega}$$

$$b. V_1 = -6.556 \text{ V}, V_2 = -3.113 \text{ V}$$

$$V_3 = -1.245 \text{ V}$$

$$c. I_{9\Omega} = \frac{V_2}{9\Omega} = \frac{3.113 \text{ V}}{9\Omega} = 0.346 \text{ A} \uparrow$$

49.

$$a. \frac{V_1}{6\Omega} + \frac{V_2}{4\Omega} = 0$$

b.

$$At V_1: \Sigma I_i = \Sigma I_o$$

$$0 = 5 \text{ A} + \frac{V_1 - V_3}{2\Omega} + \frac{V_1 - V_2}{6\Omega}$$

$$At V_2: \Sigma I_i = \Sigma I_o$$

$$5 \text{ A} = 2 \text{ A} + \frac{V_2}{4\Omega}$$

$$At V_3: \Sigma I_i = \Sigma I_o$$

$$\frac{V_1 - V_3}{2\Omega} + 2 \text{ A} + \frac{V_3}{5\Omega} = 0$$

Rewritten:

$$V_1 \left[ \frac{1}{6\Omega} + \frac{1}{10\Omega} \right] - \frac{1}{10\Omega} V_1 = 2 \text{ A}$$

$$V_2 \left[ \frac{1}{4\Omega} + \frac{1}{12\Omega} \right] - \frac{1}{12\Omega} V_2 = 0$$


$$Node V_1: \Sigma I_i = \Sigma I_o$$

$$2 \text{ A} = \frac{V_1}{6\Omega} + \frac{V_1 - V_2}{10\Omega}$$

$$b. V_1 = -6.92 \text{ V}, V_2 = 12 \text{ V}, V_3 = 2.3 \text{ V}$$

$$c. I_{9\Omega} = \frac{V_2}{9\Omega} = \frac{12 \text{ V}}{9\Omega} = 3 \text{ A}$$

50. a.

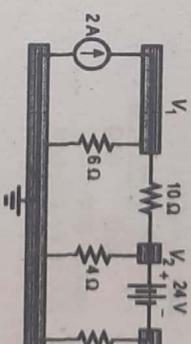

Node V1:

$$\Sigma I_i = \Sigma I_o$$

$$2 \text{ A} = \frac{V_1}{6\Omega} + \frac{V_1 - V_2}{10\Omega}$$

Supernode V3, V4:

$$0 = \frac{V_2 - V_1}{10\Omega} + \frac{V_3 - V_1}{4\Omega} + \frac{V_3}{12\Omega}$$

Independent source:

$$V_2 - V_3 = 24 \text{ V} \text{ or } V_3 = V_2 - 24 \text{ V}$$

2 eq. 2 unknowns:

$$\frac{V_1}{6\Omega} + \frac{V_1 - V_2}{10\Omega} = 2 \text{ A}$$

$$\frac{V_3 - V_1}{10\Omega} + \frac{V_3 - V_2}{4\Omega} + \frac{V_3}{12\Omega} = 0$$


$$0.267V_1 - 0.1V_2 = 2$$

$$+0.1V_1 - 0.433V_2 = -2$$

---


$$V_1 = 10.08 \text{ V}, V_2 = 6.94 \text{ V}$$
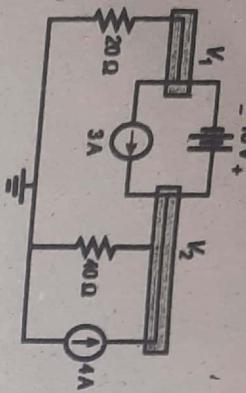
$$V_3 = V_2 - 24 \text{ V} = -17.06 \text{ V}$$



Supernode:


$$\begin{aligned} 3A + 4A &= 3A + \frac{V_1}{20\Omega} + \frac{V_2}{40\Omega} \\ 2 \text{ eq. 2 unk. } \quad \left\{ \begin{array}{l} I_A = \frac{V_1}{20\Omega} + \frac{V_2}{40\Omega} \\ V_2 - V_1 = 16V \end{array} \right. \end{aligned}$$

Subt  $V_2 = 16V + V_1$

$$4A = \frac{V_1}{20\Omega} + \frac{(16V + V_1)}{40\Omega}$$

and  $V_1 = 48V$

$$V_2 = 16V + V_1 = 64V$$

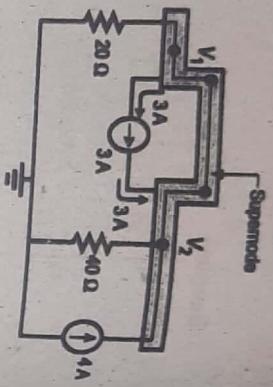

$\Sigma I_i = \Sigma I_o$

$$\begin{aligned} 54. \quad \text{a.} \quad & V_1 \left[ \frac{1}{9\Omega} + \frac{1}{10\Omega} \right] - V_2 \left[ \frac{1}{10\Omega} \right] = -2A \\ & V_2 \left[ \frac{1}{10\Omega} + \frac{1}{18\Omega} + \frac{1}{4\Omega} \right] - V_1 \left[ \frac{1}{10\Omega} \right] = 4A \end{aligned}$$

$$\begin{aligned} \underline{\underline{\begin{array}{l} 0.21V_1 - 0.1V_2 = -2 \\ -0.1V_1 + .405V_2 = 4 \end{array}}}\end{aligned}$$

$$V_1 = -5.43V, V_2 = 8.53V$$

$$\text{d. } I_{40} = \frac{V_2}{4\Omega} = \frac{8.53V}{4\Omega} = 2.13A \downarrow$$

$$55. \quad \text{a. } V_1 \left[ \frac{1}{2\Omega} + \frac{1}{2\Omega} \right] - V_2 \left[ \frac{1}{2\Omega} \right] = -5A$$

$$\begin{aligned} V_2 \left[ \frac{1}{2\Omega} + \frac{1}{9\Omega} + \frac{1}{7\Omega} + \frac{1}{2\Omega} \right] - V_1 \left[ \frac{1}{2\Omega} \right] - V_3 \left[ \frac{1}{2\Omega} \right] = 0 \\ V_3 \left[ \frac{1}{2\Omega} + \frac{1}{2\Omega} + \frac{1}{4\Omega} \right] - V_2 \left[ \frac{1}{2\Omega} \right] = 0 \end{aligned}$$

$$\begin{aligned} V_1 &= -6.556V, V_2 = -3.113V \\ V_3 &= -1.245V \end{aligned}$$

$$\begin{aligned} 52. \quad \text{a. } & V_1 \quad V_2 \\ & 0 \quad 0 \\ & V_1 \left[ \frac{1}{2} + \frac{1}{8} \right] - V_2 \left[ \frac{1}{8} \right] = -5 \\ & V_1 \left[ \frac{1}{2} + \frac{1}{8} \right] + V_2 \left[ \frac{1}{8} \right] = 3 \end{aligned}$$

$$\begin{aligned} V_1 &= -10.27V, V_2 = -11.36V \\ \text{b. } V_4 &= V_1 = -10.27V, V_4 = V_2 = -11.36V \end{aligned}$$


$$\begin{aligned} 53. \quad \text{a. } & V_1 \quad V_2 \\ & 0 \quad 0 \\ & V_1 \left[ \frac{1}{8} + \frac{1}{6} \right] - V_2 \left[ \frac{1}{6} \right] = -12A + 9A = -3A \\ & V_2 \left[ \frac{1}{20} + \frac{1}{5} + \frac{1}{6} \right] - V_1 \left[ \frac{1}{6} \right] = -9A \\ & V_2 \left[ \frac{1}{20} + \frac{1}{5} + \frac{1}{6} \right] - V_1 \left[ \frac{1}{6} \right] = 2A \end{aligned}$$

$$V_1 = -29.29V, V_2 = -33.34V$$

$$\begin{aligned} \text{b. } & V_1 - V_{40} - 54V - V_2 = 0 \\ & V_{40} = V_1 - V_2 - 54V = -29.29V - (-33.34V) - 54V = -49.95V \end{aligned}$$

b.  $V_1 = -6.92 \text{ V}$ ,  $V_2 = 12 \text{ V}$ ,  $V_3 = 2.3 \text{ V}$

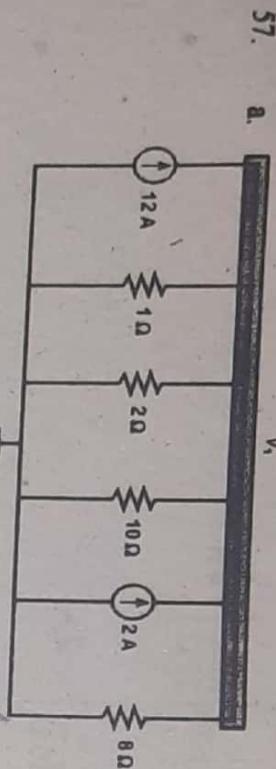c.  $I_{2\Omega} = \frac{V_2}{2\Omega} = \frac{6.92 \text{ V}}{2\Omega} = 3.46 \text{ A}$



$$V_1 \left[ \frac{1}{1\Omega} + \frac{1}{2\Omega} + \frac{1}{10\Omega} + \frac{1}{8\Omega} \right] = 14 \text{ A}$$

$$V_1[1.725 \text{ S}] = 14 \text{ A}$$

$$V_1 = \frac{14}{1.725} \text{ V}$$

$$= 8.1 \text{ V}$$

b.  $V_a = 0 \text{ V}$ ,  $V_b = 8.12 \text{ V}$

$$V_{ab} = V_a - V_b = 0 \text{ V} - 8.12 \text{ V} = -8.12 \text{ V}$$

58. a. Same figure used for problem 46.

$$V_2 \left[ \frac{1}{6\Omega} + \frac{1}{4\Omega} + \frac{1}{5\Omega} \right] - \frac{1}{6\Omega} V_1 = -3 \text{ A}$$

b.  $V_1 = 0 \text{ V}$

$\therefore V_2[0.617 \text{ S}] = -3 \text{ A}$

$$V_2 = \frac{-3}{0.617} \text{ V}$$

$$= -4.86 \text{ V}$$

c.  $I_{5\Omega} = \frac{V_2}{5\Omega} = \frac{4.86 \text{ V}}{5\Omega} = .972 \text{ A}$

59. a.



$$I_1(6\Omega + 2\Omega + 10\Omega) - 2\Omega I_2 - 10\Omega I_3 = 12 \text{ V}$$

$$I_2(2\Omega + 2\Omega + 5\Omega) - 5\Omega I_3 - 2\Omega I_1 = 0$$

$$I_3(5\Omega + 20\Omega + 10\Omega) - 5\Omega I_2 - 10\Omega I_1 = 0$$

$$18I_1 - 2I_2 - 10I_3 = 12$$

$$-2I_1 + 9I_2 - 5I_3 = 0$$

$$-10I_1 - 5I_2 + 35I_3 = 0$$

62. a.  $\frac{dV_1}{I_2}$   
 $\frac{dV_2}{I_3}$

$$\begin{aligned} V_1 \left[ \frac{1}{2\text{k}\Omega} + \frac{1}{33\text{k}\Omega} + \frac{1}{56\text{k}\Omega} \right] - \frac{1}{33\text{k}\Omega} V_2 - \frac{1}{56\text{k}\Omega} V_3 &= 12 \text{ mA} \\ V_2 \left[ \frac{1}{33\text{k}\Omega} + \frac{1}{3.3\text{k}\Omega} + \frac{1}{36\text{k}\Omega} \right] - \frac{1}{33\text{k}\Omega} V_1 - \frac{1}{36\text{k}\Omega} V_3 &= 0 \\ V_3 \left[ \frac{1}{56\text{k}\Omega} + \frac{1}{36\text{k}\Omega} + \frac{1}{5.6\text{k}\Omega} \right] - \frac{1}{36\text{k}\Omega} V_2 - \frac{1}{56\text{k}\Omega} V_1 &= 0 \end{aligned}$$

Rewritten:

$$\begin{aligned} 548.16V_1 - 30.3V_2 - 17.86V_3 &= 12 \times 10^3 \\ -30.3V_1 + 361.11V_2 - 27.78V_3 &= 0 \\ -17.86V_1 - 27.78V_2 + 224.21V_3 &= 0 \end{aligned}$$

63.

b.  $V_{A_1} = V_2 - V_3 = 2.01 \text{ V} - 2.01 \text{ V} = 0 \text{ V}$

c, d. yes

Mesh Analysis

$$I_1, I_2, I_3$$

$$\begin{aligned} (1\text{k}\Omega + 2\text{k}\Omega + 2\text{k}\Omega)I_1 - 2\text{k}\Omega I_2 - 2\text{k}\Omega I_3 &= 10 \\ (2\text{k}\Omega + 2\text{k}\Omega + 2\text{k}\Omega)I_2 - 2\text{k}\Omega I_1 - 2\text{k}\Omega I_3 &= 0 \\ (2\text{k}\Omega + 2\text{k}\Omega + 2\text{k}\Omega)I_3 - 2\text{k}\Omega I_1 - 2\text{k}\Omega I_2 &= 0 \end{aligned}$$

$I_1 = I_{\text{AV}} = 3.33 \text{ mA}$


64.

Mesh Analysis  
Source conversion:  $E = 20 \text{ V}, R = 10 \Omega$

$$I_1, I_2$$

$$\begin{aligned} (10 + 10 + 20)I_1 - 10I_2 - 20I_3 &= 20 \\ (10 + 20 + 20)I_2 - 10I_1 - 20I_3 &= 20 \\ (20 + 20 + 10)I_3 - 20I_1 - 20I_2 &= 0 \end{aligned}$$

$$I_1 = I_{\text{AV}} = 0.83 \text{ A}$$

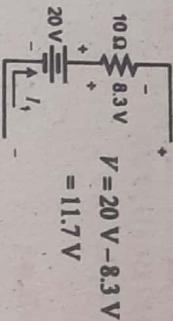

Nodal Analysis:

$$\begin{aligned} \frac{dV_1}{I_2} & V_1 \left[ \frac{1}{10} + \frac{1}{20} \right] \frac{1}{20} V_2 - \frac{1}{10} V_3 = 2 \\ \frac{dV_2}{I_3} & V_2 \left[ \frac{1}{20} + \frac{1}{10} \right] \frac{1}{20} V_1 - \frac{1}{10} V_3 = 0 \\ \frac{dV_3}{I_1} & V_3 \left[ \frac{1}{10} + \frac{1}{20} \right] \frac{1}{10} V_1 - \frac{1}{20} V_2 = 0 \end{aligned}$$

$$I_4 = \frac{V_1}{R} = 1.17 \text{ A}$$

Nodal Analysis:


Source conversion:  $I = 10 \text{ V}/1 \text{ k}\Omega = 10 \text{ mA}$ ,  $1 \text{ k}\Omega$

$$\begin{aligned} \frac{dV_1}{I_2} & V_1 \left[ \frac{1}{10} + \frac{1}{2\text{k}\Omega} + \frac{1}{2\text{k}\Omega} \right] \frac{1}{2\text{k}\Omega} V_2 - \frac{1}{2\text{k}\Omega} V_3 = 10 \text{ mA} \\ \frac{dV_2}{I_3} & V_2 \left[ \frac{1}{2\text{k}\Omega} + \frac{1}{2\text{k}\Omega} + \frac{1}{2\text{k}\Omega} \right] \frac{1}{2\text{k}\Omega} V_1 - \frac{1}{2\text{k}\Omega} V_3 = 0 \\ \frac{dV_3}{I_1} & V_3 \left[ \frac{1}{2\text{k}\Omega} + \frac{1}{2\text{k}\Omega} + \frac{1}{2\text{k}\Omega} \right] \frac{1}{2\text{k}\Omega} V_1 - \frac{1}{2\text{k}\Omega} V_2 = 0 \end{aligned}$$


$$V_1 = 6.67 \text{ V} = E - IR = 10 \text{ V} - I(1 \text{ k}\Omega)$$

$$I = \frac{10 - 6.67 \text{ V}}{1 \text{ k}\Omega} = 3.33 \text{ mA}$$

65.

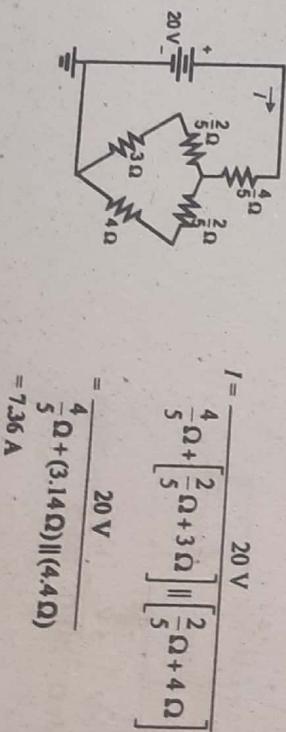
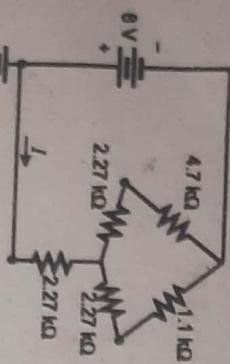
$$I = \frac{20 \text{ V}}{\frac{4\Omega}{\frac{4\Omega + (3.14\Omega)}{5\Omega + (3.14\Omega)}} \parallel \frac{2\Omega + 4\Omega}{5\Omega + (3.14\Omega)}} = 7.36 \text{ A}$$



$$R_T = 2.27 \text{ k}\Omega + [4.7 \text{ k}\Omega + 2.27 \text{ k}\Omega] \parallel [1.1 \text{ k}\Omega + 2.27 \text{ k}\Omega]$$


$$= 2.27 \text{ k}\Omega + [6.97 \text{ k}\Omega] \parallel [3.37 \text{ k}\Omega]$$

$$= 2.27 \text{ k}\Omega + 2.27 \text{ k}\Omega$$

$$= 4.54 \text{ k}\Omega$$

$$I = \frac{8 \text{ V}}{4.54 \text{ k}\Omega} = 1.76 \text{ mA}$$

67.

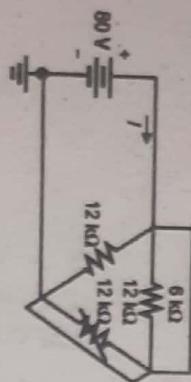

(Y-Δ conversion)

$$I = \frac{80 \text{ V}}{12 \text{ k}\Omega \parallel 12 \text{ k}\Omega \parallel 6 \text{ k}\Omega} = \frac{80 \text{ V}}{3 \text{ k}\Omega}$$

$$= 26.67 \text{ mA}$$


68. a.

$$I = \frac{42 \text{ V}}{(18 \Omega \parallel 18 \Omega) \parallel [(18 \Omega \parallel 18 \Omega) + (18 \Omega \parallel 18 \Omega)]} = \frac{42 \text{ V}}{9 \Omega \parallel [9 \Omega + 9 \Omega]}$$


= 7 A (Y-Δ conversion)

b. Δ - Y conversion

69.

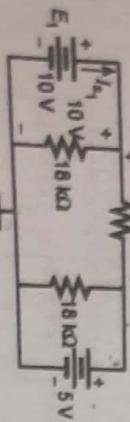
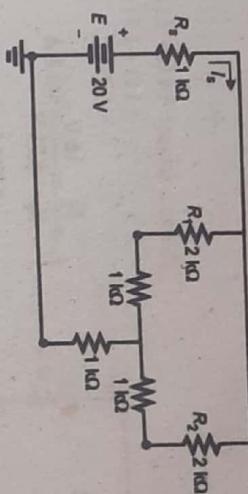
$$I_h = \frac{10 \text{ V}}{18 \text{ k}\Omega} + \frac{5 \text{ V}}{18 \text{ k}\Omega} = \frac{15 \text{ V}}{18 \text{ k}\Omega} = 0.83 \text{ mA}$$



$$\text{b. } R' = R_1 + 1 \text{ k}\Omega = 3 \text{ k}\Omega$$


$$R'' = R_2 + 1 \text{ k}\Omega = 3 \text{ k}\Omega$$

$$R'_T = \frac{3 \text{ k}\Omega}{2} = 1.5 \text{ k}\Omega$$

$$R_T = 1 \text{ k}\Omega + 1.5 \text{ k}\Omega + 1 \text{ k}\Omega = 3.5 \text{ k}\Omega$$


$$I_r = \frac{E}{R_T} = \frac{20 \text{ V}}{3.5 \text{ k}\Omega} = 5.71 \text{ mA}$$

71. Using two Δ - Y conversions:

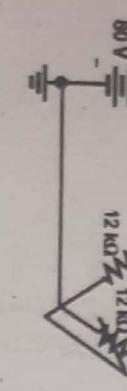

$$\text{c - g: } 27 \Omega \parallel 9 \Omega \parallel 27 \Omega = 5.4 \Omega$$

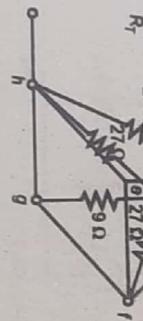
$$\text{a - h: } 27 \Omega \parallel 9 \Omega \parallel 27 \Omega = 5.4 \Omega$$



$$R_T = 5.4 \Omega \parallel (13.5 \Omega + 5.4 \Omega) \\ = 5.4 \Omega \parallel 18.9 \Omega \\ = 4.2 \Omega$$

## Chapter 9

1. a.  $E_T$ :

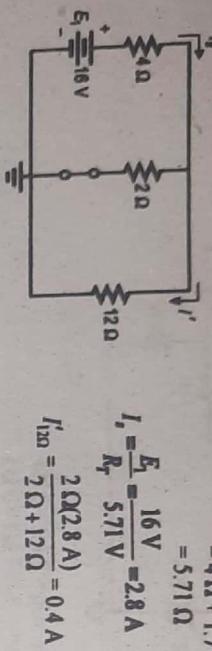

$$R_T(\text{from source}) = 4\Omega + 2\Omega \parallel 12\Omega = 4\Omega + 1.71\Omega = 5.71\Omega$$


$$I_T = \frac{E_1}{R_T} = \frac{16V}{5.71\Omega} = 2.8A$$

$$I'_{12\Omega} = \frac{2\Omega(2.8A)}{2\Omega+12\Omega} = 0.4A$$

$$23.79W + 0.661W \neq 16.51W$$

$$24.45W \neq 16.51W$$

b.

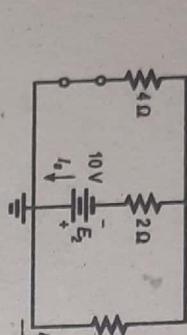


$$R_T(\text{from source}) = 2\Omega + 4\Omega \parallel 12\Omega = 2\Omega + 3\Omega = 5\Omega$$

$$I_S = \frac{E_2}{R_T} = \frac{10V}{5\Omega} = 2A$$

$$I''_{12\Omega} = \frac{4\Omega(2A)}{4\Omega+12\Omega} = 0.5A$$

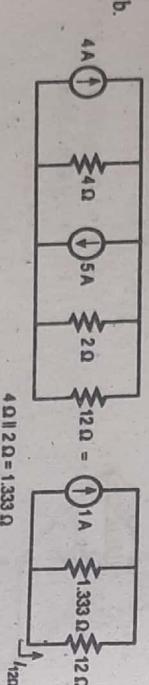c.  $I_{12\Omega} \uparrow = 0.5A - 0.4A = 0.1A$




$$I_{12\Omega} \uparrow = 0.5A - 0.4A = 0.1A$$

$$4\Omega \parallel 2\Omega = 1.333\Omega$$

$$I_{12\Omega} = I' + I'' = 0.25A + 1A = 1.25A \downarrow$$

d.

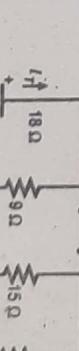


e. the same

2.

a.

$$I' = \frac{24\Omega(3A)}{24\Omega+8\Omega} = 2.25A$$
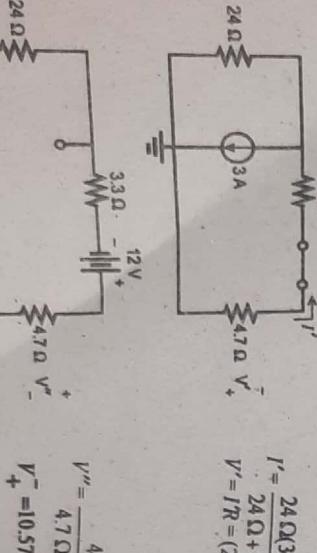
$$V' = IR = (2.25)(4.7\Omega) = 10.575V$$



$$V''' = \frac{4.7\Omega(12V)}{4.7\Omega+3.3\Omega+24\Omega} = 1.763V$$

$$V'_+ = 10.575V - 1.763V = 8.81V$$

$$I_{24V} = I_T + I_1 = 2A + 1.17A = 3.17A \text{ (dir. of } I_1)$$


$$b. P = \frac{V^2}{R} = \frac{(10.575V)^2}{4.7\Omega} = 22.79W$$

$$c. P = \frac{V'^2}{R} = \frac{(1.763V)^2}{4.7\Omega} = 0.661W$$

$$d. P = \frac{V^2}{R} = \frac{(8.81V)^2}{4.7\Omega} = 16.51W$$

$$e. 23.79W + 0.661W \neq 16.51W$$

f.

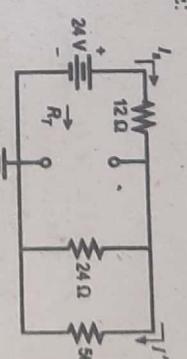


$$R_T = 12\Omega + 24\Omega \parallel 56\Omega = 28.8\Omega$$

$$I_S = \frac{E_1}{R_T} = \frac{24V}{28.8\Omega} = 0.833A$$

$$I''_{24\Omega} = \frac{24\Omega(0.833A)}{24\Omega+56\Omega} = 0.25A$$

g.

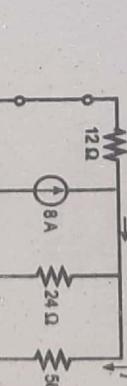

$$24\Omega \parallel 56\Omega = 16.8\Omega$$

$$I'' = \frac{12\Omega(8A)}{12\Omega+16.8\Omega} = 3.33A$$

$$I''_{24\Omega} = \frac{24\Omega(3.33A)}{24\Omega+56\Omega} = 1A$$

h.

i.

j.

k.

l.

m.

n.

o.

p.

q.

r.

s.

t.

u.


v.

w.

x.

y.


z.

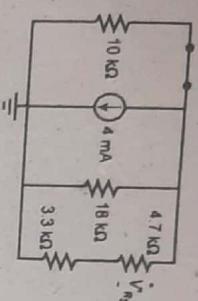

$$I = \frac{6.43 \text{ k}\Omega(4 \text{ mA})}{6.43 \text{ k}\Omega + 8 \text{ k}\Omega} = 1.78 \text{ mA}$$

$$V'_{R_3} = -IR_3 = -(1.78 \text{ mA})(4.7 \text{ k}\Omega)$$

$$V''_{R_3} = -8.37 \text{ V}$$

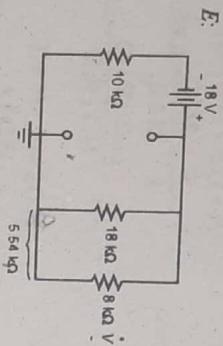

$$E:$$

$$V = \frac{5.54 \text{ k}\Omega(18 \text{ V})}{5.54 \text{ k}\Omega + 10 \text{ k}\Omega} = 6.42 \text{ V}$$

$$V'_{R_3} = \frac{4.7 \text{ k}\Omega(6.42 \text{ V})}{4.7 \text{ k}\Omega + 3.3 \text{ k}\Omega} = 3.77 \text{ V}$$


$$V_{R_3} = V'_{R_3} + V''_{R_3}$$

$$= -8.37 \text{ V} + 3.77 \text{ V}$$


$$= -4.6 \text{ V}$$

6.


E:

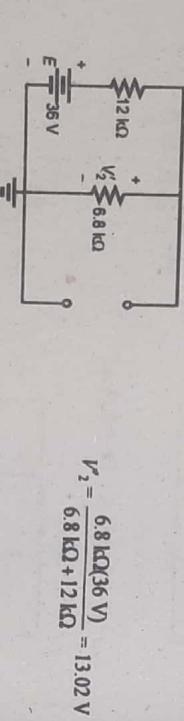
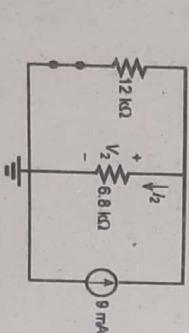
$$V'_{R_2} = \frac{6.8 \text{ k}\Omega(36 \text{ V})}{6.8 \text{ k}\Omega + 12 \text{ k}\Omega} = 13.02 \text{ V}$$





I(5 mA):

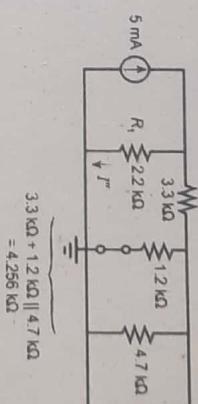

$$I'' = \frac{4.256 \text{ k}\Omega(5 \text{ mA})}{4.256 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 3.296 \text{ mA}$$

$$V = \frac{2.53 \text{ k}\Omega(8 \text{ V})}{2.53 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 5.43 \text{ V}$$
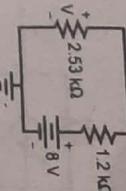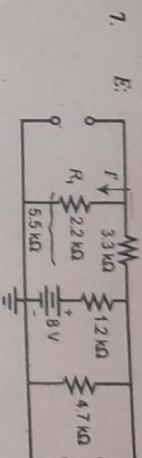
$$I' = \frac{V}{R_1 + R_2} = \frac{5.43 \text{ V}}{5.5 \text{ k}\Omega} = 0.987 \text{ mA}$$



$$I(9 \text{ mA}):$$


$$I''' = \frac{0.956 \text{ k}\Omega(2 \text{ mA})}{0.956 \text{ k}\Omega + 5.5 \text{ k}\Omega} = 0.296 \text{ mA}$$

$$I_{R_1} = I' + I'' - I'''$$

$$= 0.987 \text{ mA} + 3.296 \text{ mA} - 0.296 \text{ mA}$$

$$= 3.99 \text{ mA} \downarrow$$

E:

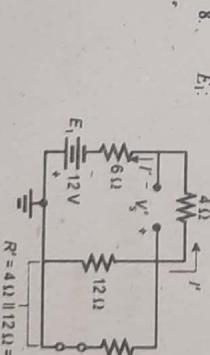

$$V''_2 = I_2 R_2 = (5.75 \text{ mA})(6.8 \text{ k}\Omega) = 39.10 \text{ V}$$

$$V_2 = V'_2 + V''_2 = 13.02 \text{ V} + 39.10 \text{ V} = 52.12 \text{ V}$$

$$I' = \frac{12 \text{ V}}{12 \Omega \parallel 4 \Omega + 4 \Omega + 6 \Omega}$$

$$= \frac{12 \text{ V}}{\frac{12 \text{ V}}{3 \Omega + 10 \Omega}} = \frac{12 \text{ V}}{13 \Omega}$$

$$= 923.1 \text{ mA}$$

$$V'_1 = IR = (923.1 \text{ mA})(4 \Omega) = 2.492 \text{ V}$$

b.  $I_3 = \frac{E_3}{R_3 + R} = \frac{6V}{6\Omega + 100\Omega} = 56.60 \text{ mA}$

b.  $I_1 = \frac{E_1}{R_1 + R} = \frac{6V}{6\Omega + 2\Omega} = 0.75 \text{ A}$

$I_2 = \frac{6V}{6\Omega + 30\Omega} = 166.67 \text{ mA}$

$I_3 = \frac{6V}{6\Omega + 100\Omega} = 56.60 \text{ mA}$

9. a.  $R_{Th} = R_3 + R_1 \parallel R_2 = 4\Omega + 6\Omega \parallel 3\Omega = 4\Omega + 2\Omega = 6\Omega$

E<sub>Th</sub> =  $\frac{R_3 E}{R_3 + R_1 + R_2} = \frac{3\Omega(18V)}{3\Omega + 6\Omega} = 6V$

$V'_t = I''(4\Omega) = 0.462 \text{ A}(4\Omega) = 1.848 \text{ V}$

$V_t (\text{polarity of } V'_t) = V''_t - V'_t - V'''_t$

$= 16.62 \text{ V} - 2.492 \text{ V} - 1.848 \text{ V} = 12.28 \text{ V}$


$R'_{Th} = 12\Omega \parallel (4\Omega + 6\Omega) = 12\Omega \parallel 10\Omega = 5.455\Omega$

$I = \frac{E_2}{R'_T} = \frac{8V}{4\Omega + 5.455\Omega} = 0.846 \text{ A}$


$I''' = \frac{12\Omega(I)}{12\Omega + 10\Omega} = \frac{12\Omega(0.846 \text{ A})}{22\Omega} = 0.462 \text{ A}$

$V'''_t = I'''(4\Omega) = 0.462 \text{ A}(4\Omega) = 1.848 \text{ V}$

$E_2: V'_t + V''_t + V'''_t = 8V$

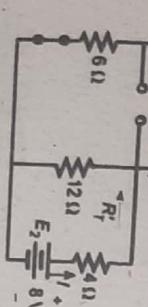



E<sub>2</sub>:

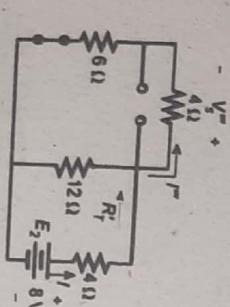

$R' = 12\Omega \parallel 4\Omega = 3\Omega$

$I'' = \frac{9\Omega(6A)}{9\Omega + 4\Omega} = 4.154 \text{ A}$

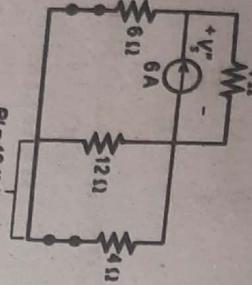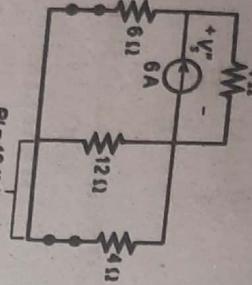$V''_t = I''(4\Omega) = (4.154 \text{ A})(4\Omega) = 16.62 \text{ V}$



$R_{Th} = 3.3 \text{ k}\Omega + 1.2 \text{ k}\Omega \parallel 2.4 \text{ k}\Omega = 3.3 \text{ k}\Omega + 0.8 \text{ k}\Omega = 4.1 \text{ k}\Omega$

$I'' = \frac{9\Omega(6A)}{9\Omega + 4\Omega} = 4.154 \text{ A}$

$V''_t = I''(4\Omega) = (4.154 \text{ A})(4\Omega) = 16.62 \text{ V}$

$I'' = \frac{9\Omega(6A)}{9\Omega + 4\Omega} = 4.154 \text{ A}$

$V''_t = I''(4\Omega) = (4.154 \text{ A})(4\Omega) = 16.62 \text{ V}$

$I'' = \frac{9\Omega(6A)}{9\Omega + 4\Omega} = 4.154 \text{ A}$

$V''_t = I''(4\Omega) = (4.154 \text{ A})(4\Omega) = 16.62 \text{ V}$

$I'' = \frac{9\Omega(6A)}{9\Omega + 4\Omega} = 4.154 \text{ A}$

$V''_t = I''(4\Omega) = (4.154 \text{ A})(4\Omega) = 16.62 \text{ V}$

10. a.  $R_{Th}$ :

b.  $R_{Th}$ :

c.  $R_{Th}$ :

d.  $R_{Th}$ :

e.  $R_{Th}$ :

f.  $R_{Th}$ :

g.  $R_{Th}$ :

h.  $R_{Th}$ :

i.  $R_{Th}$ :

j.  $R_{Th}$ :

k.  $R_{Th}$ :

l.  $R_{Th}$ :

m.  $R_{Th}$ :

n.  $R_{Th}$ :

o.  $R_{Th}$ :

p.  $R_{Th}$ :

q.  $R_{Th}$ :

r.  $R_{Th}$ :

s.  $R_{Th}$ :

t.  $R_{Th}$ :

u.  $R_{Th}$ :

v.  $R_{Th}$ :

w.  $R_{Th}$ :

x.  $R_{Th}$ :

y.  $R_{Th}$ :

z.  $R_{Th}$ :

aa.  $R_{Th}$ :

bb.  $R_{Th}$ :

cc.  $R_{Th}$ :

dd.  $R_{Th}$ :

ee.  $R_{Th}$ :

ff.  $R_{Th}$ :

gg.  $R_{Th}$ :

hh.  $R_{Th}$ :

ii.  $R_{Th}$ :

jj.  $R_{Th}$ :

kk.  $R_{Th}$ :

ll.  $R_{Th}$ :

mm.  $R_{Th}$ :

nn.  $R_{Th}$ :

oo.  $R_{Th}$ :

pp.  $R_{Th}$ :

qq.  $R_{Th}$ :

rr.  $R_{Th}$ :

ss.  $R_{Th}$ :

tt.  $R_{Th}$ :

uu.  $R_{Th}$ :

vv.  $R_{Th}$ :

ww.  $R_{Th}$ :

xx.  $R_{Th}$ :

yy.  $R_{Th}$ :

zz.  $R_{Th}$ :

aa.  $R_{Th}$ :

bb.  $R_{Th}$ :

cc.  $R_{Th}$ :

dd.  $R_{Th}$ :

ee.  $R_{Th}$ :

ff.  $R_{Th}$ :

gg.  $R_{Th}$ :

hh.  $R_{Th}$ :

ii.  $R_{Th}$ :

jj.  $R_{Th}$ :

kk.  $R_{Th}$ :

ll.  $R_{Th}$ :

mm.  $R_{Th}$ :

nn.  $R_{Th}$ :

oo.  $R_{Th}$ :

pp.  $R_{Th}$ :

qq.  $R_{Th}$ :

rr.  $R_{Th}$ :

uu.  $R_{Th}$ :

vv.  $R_{Th}$ :

ww.  $R_{Th}$ :

xx.  $R_{Th}$ :

yy.  $R_{Th}$ :

zz.  $R_{Th}$ :

aa.  $R_{Th}$ :

bb.  $R_{Th}$ :

cc.  $R_{Th}$ :

dd.  $R_{Th}$ :

ee.  $R_{Th}$ :

ff.  $R_{Th}$ :

gg.  $R_{Th}$ :

hh.  $R_{Th}$ :

ii.  $R_{Th}$ :

jj.  $R_{Th}$ :

kk.  $R_{Th}$ :

ll.  $R_{Th}$ :

mm.  $R_{Th}$ :

nn.  $R_{Th}$ :

oo.  $R_{Th}$ :

pp.  $R_{Th}$ :

qq.  $R_{Th}$ :

rr.  $R_{Th}$ :

uu.  $R_{Th}$ :

vv.  $R_{Th}$ :

ww.  $R_{Th}$ :

xx.  $R_{Th}$ :

yy.  $R_{Th}$ :

zz.  $R_{Th}$ :

aa.  $R_{Th}$ :

bb.  $R_{Th}$ :

cc.  $R_{Th}$ :

dd.  $R_{Th}$ :

ee.  $R_{Th}$ :

ff.  $R_{Th}$ :

gg.  $R_{Th}$ :

hh.  $R_{Th}$ :

ii.  $R_{Th}$ :

jj.  $R_{Th}$ :

kk.  $R_{Th}$ :

ll.  $R_{Th}$ :

mm.  $R_{Th}$ :

nn.  $R_{Th}$ :

oo.  $R_{Th}$ :

pp.  $R_{Th}$ :

qq.  $R_{Th}$ :

rr.  $R_{Th}$ :

uu.  $R_{Th}$ :

vv.  $R_{Th}$ :

ww.  $R_{Th}$ :

xx.  $R_{Th}$ :

yy.  $R_{Th}$ :

zz.  $R_{Th}$ :

aa.  $R_{Th}$ :

bb.  $R_{Th}$ :

cc.  $R_{Th}$ :

dd.  $R_{Th}$ :

ee.  $R_{Th}$ :

ff.  $R_{Th}$ :

gg.  $R_{Th}$ :

hh.  $R_{Th}$ :

ii.  $R_{Th}$ :

jj.  $R_{Th}$ :

kk.  $R_{Th}$ :

ll.  $R_{Th}$ :

mm.  $R_{Th}$ :

nn.  $R_{Th}$ :

oo.  $R_{Th}$ :

pp.  $R_{Th}$ :

qq.  $R_{Th}$ :

rr.  $R_{Th}$ :

uu.  $R_{Th}$ :

vv.  $R_{Th}$ :

ww.  $R_{Th}$ :

xx.  $R_{Th}$ :

yy.  $R_{Th}$ :


zz.  $R_{Th}$ :

aa.  $R_{Th}$ :

bb.  $R_{Th}$ :

cc.  $R_{Th}$ :

12.

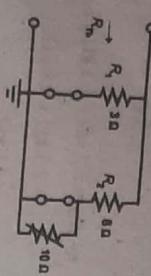

$$R_{Th} = 3 \parallel 8\Omega = 2.18\Omega$$

$$\begin{aligned} V_{Th} &= I/R = (0.667\text{ A})(2\Omega) = 1.333\text{ V} \\ E_{Th} &= 6\Omega + V_{Th} = (2\text{ A})(6\Omega) + 1.333\text{ V} \\ E_{Th} &= 12\text{ V} + 1.333\text{ V} = 13.33\text{ V} \end{aligned}$$

13.  $R_{Th}$

$$\begin{aligned} I &= \frac{18\text{ V} + 12\text{ V}}{3\Omega + 8\Omega} = \frac{30\text{ V}}{11\Omega} = 2.73\text{ A} \\ V_{Th} &= IR_1 = (2.73\text{ A})(3\Omega) = 8.19\text{ V} \\ E_{Th} &= E_1 - V_{Th} = 18\text{ V} - 8.19\text{ V} = 9.81\text{ V} \end{aligned}$$

13.  $R_{Th}$

$$R_{Th} = 5.6\text{ k}\Omega \parallel 2.2\text{ k}\Omega = 1.58\text{ k}\Omega$$

$E_{Th}$ : Superposition:

I.


$$\begin{aligned} E'_{Th} &= IR_T \\ &= 8\text{ mA}(5.6\text{ k}\Omega \parallel 2.2\text{ k}\Omega) \\ &= 8\text{ mA}(1.579\text{ k}\Omega) \\ &= 12.64\text{ V} \end{aligned}$$

$$\begin{aligned} E''_{Th} &= \frac{5.6\text{ k}\Omega(16\text{ V})}{5.6\text{ k}\Omega + 2.2\text{ k}\Omega} \\ &= 11.49\text{ V} \end{aligned}$$

$$E_{Th} = 11.49\text{ V} - 12.64\text{ V} = -1.15\text{ V}$$

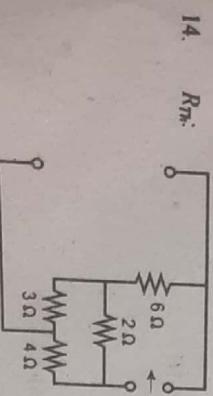14.  $R_{Th}$ :

$$R_{Th} = 6\Omega + 2\Omega \parallel 7\Omega = 6\Omega + 1.56\Omega = 7.56\Omega$$



$$E_{Th}:$$

$$\begin{aligned} I &= 2\text{ A} \\ I' &= \frac{3\Omega(2\text{ A})}{3\Omega + 6\Omega} = 0.667\text{ A} \end{aligned}$$


15. a.  $R_{Th}$ :

$$R_{Th} = \frac{4\text{ k}\Omega}{4} = 1\text{ k}\Omega$$

Source conversion:

$$\begin{aligned} \frac{4\text{ k}\Omega}{3} &= 1.333\text{ k}\Omega \\ 20\text{ V} &\xrightarrow{\quad} 8\text{ mA} \quad E_{Th} \\ I &= \frac{20\text{ V}}{4\text{ k}\Omega} = 5\text{ mA}, R_p = 4\text{ k}\Omega \end{aligned}$$


16. a.  $R_{Th}$ :

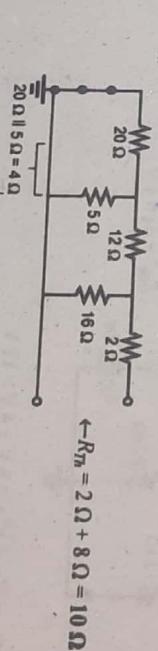

$$16\Omega \parallel (12\Omega + 4\Omega) = 8\Omega$$

$$I_{load} = \frac{3\text{ V}}{1\text{ k}\Omega + 10\text{ k}\Omega} = \frac{3\text{ V}}{11\text{ k}\Omega} = 0.273\text{ mA}$$
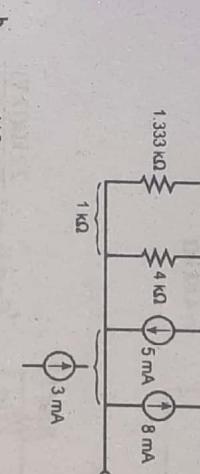
$$E_{Th} = I_{load} R_{Th} = (3\text{ mA})(1\text{ k}\Omega) = 3\text{ V}$$



$$E_{Th} = V_{16\Omega}$$

$$I_T = \frac{20 \text{ V}}{20 \Omega + 4.24 \Omega} = 825.08 \text{ mA}$$

$$I' = \frac{5 \Omega (I_T)}{5 \Omega + 28 \Omega} = \frac{5 \Omega (825.08 \text{ mA})}{33 \Omega} = 125.01 \text{ mA}$$


$$E_{Th} = V_{Th} = (I')(16 \Omega) = (125.01 \text{ mA})(16 \Omega) = 2 \text{ V}$$

b.  $20 \Omega: I = \frac{E_{Th}}{R_{Th} + R} = \frac{2 \text{ V}}{10 \Omega + 20 \Omega} = \frac{2 \text{ V}}{30 \Omega} = 66.67 \text{ mA}$

$$50 \Omega: I = \frac{2 \text{ V}}{10 \Omega + 50 \Omega} = \frac{2 \text{ V}}{60 \Omega} = 33.33 \text{ mA}$$

$$100 \Omega: I = \frac{2 \text{ V}}{10 \Omega + 100 \Omega} = \frac{2 \text{ V}}{110 \Omega} = 18.18 \text{ mA}$$

17. a.  $R_{Th}$ :

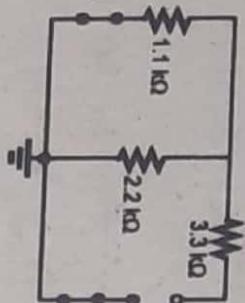


$E_{Th}$ : Superposition:

$E_1$ :

$$E_{Th} = V_{2,3\text{k}\Omega} = \frac{2.2 \text{ k}\Omega(12 \text{ V})}{2.2 \text{ k}\Omega + 1.1 \text{ k}\Omega} = 4.03 \text{ k}\Omega$$


$E_2$ : Superposition:
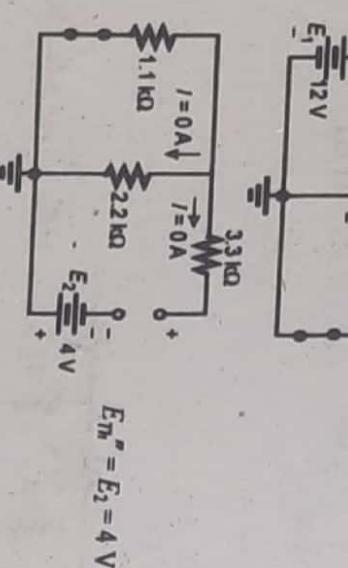
$$E_{Th} = V_{2,3\text{k}\Omega} = \frac{2.2 \text{ k}\Omega(12 \text{ V})}{2.2 \text{ k}\Omega + 1.1 \text{ k}\Omega} = 8 \text{ V}$$



$$E_{Th} = E_{Th} + E''_{Th} = 8 \text{ V} + 4 \text{ V} = 12 \text{ V}$$

b.

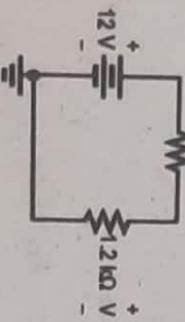


$$4.03 \text{ k}\Omega$$

$$1.2 \text{ k}\Omega$$

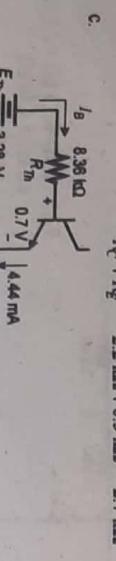b.  $I_E R_E + V_{CE} + I_C R_C = 20 \text{ V}$

but  $I_C = I_E$   
and  $I_E (R_C + R_E) + V_{CE} = 20 \text{ V}$

$$\text{or } I_E = \frac{20 \text{ V} - V_{CE}}{R_C + R_E} = \frac{20 \text{ V} - 8 \text{ V}}{2.2 \text{ k}\Omega + 0.5 \text{ k}\Omega} = \frac{12 \text{ V}}{2.7 \text{ k}\Omega} = 4.44 \text{ mA}$$



E<sub>m</sub> - I<sub>B</sub>R<sub>T</sub> - V<sub>BE</sub> - V<sub>E</sub> = 0

$$\text{and } I_B = \frac{E_m - V_{BE} - V_E}{R_{Tn}} = \frac{3.28 \text{ V} - 0.7 \text{ V} - (4.44 \text{ mA})(0.5 \text{ k}\Omega)}{8.36 \text{ k}\Omega}$$

$$= \frac{2.58 \text{ V} - 2.22 \text{ V}}{8.36 \text{ k}\Omega} = \frac{0.36 \text{ V}}{8.36 \text{ k}\Omega} = 43.06 \mu\text{A}$$

$$\begin{aligned} \text{d. } V_C &= 20 \text{ V} - I_C R_C = 20 \text{ V} - (4.44 \text{ mA})(2.2 \text{ k}\Omega) \\ &= 20 \text{ V} - 9.77 \text{ V} \\ &= 10.23 \text{ V} \end{aligned}$$


20. a.  $E_{Tn} = 20 \text{ V}$

$$I = 1.6 \text{ mA} = \frac{E_{Tn}}{R_{Tn}} = \frac{20 \text{ V}}{R_{Tn}}, R_{Tn} = \frac{20 \text{ V}}{1.6 \text{ mA}} = 12.5 \text{ k}\Omega$$

b.  $E_{Tn} = 60 \text{ mV}, R_{Tn} = 2.72 \text{ k}\Omega$


c.  $E_{Tn} = 16 \text{ V}, R_{Tn} = 2.2 \text{ k}\Omega$

21.

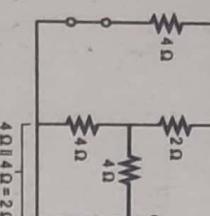

$$R_{Tn} = 4\Omega \parallel (2\Omega + 2\Omega) = \frac{4\Omega}{2} = 2\Omega$$


22.

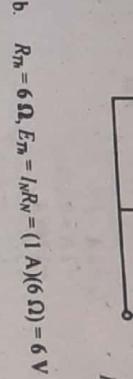

b.  $R_{Tn} = 6 \Omega, E_{Tn} = I_N R_N = (1 \text{ A})(6 \Omega) = 6 \text{ V}$


c. same results

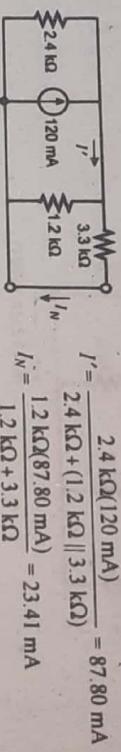23. a. From Problem 10,  $R_N = R_{Tn} = 4.1 \text{ k}\Omega$




$$\begin{aligned} \text{b. } R_{Tn} &= 4.1 \text{ k}\Omega, E_{Tn} = I_N R_N = (23.41 \text{ mA})(4.1 \text{ k}\Omega) = 96 \text{ V} \\ \text{c. } \text{same results.} \end{aligned}$$

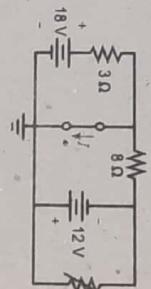24. From Problem 12,  $R_N = R_{Tn} = 2.18 \Omega$



$$I_N = 6 \text{ A} - 1.5 \text{ A} = 4.5 \text{ A}$$

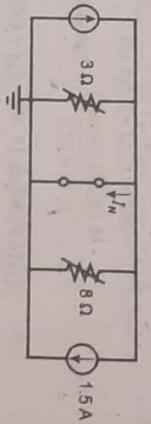
25. From Problem 13,  $R_N = R_{Tn} = 1.58 \text{ k}\Omega$



$$I_N = 8 \text{ mA} - 7.27 \text{ mA} = 0.73 \text{ mA}$$

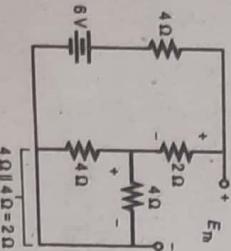26. From Problem 14,  $R_N = R_{Tn} = 7.56 \text{ }\Omega$

$$\begin{aligned} V_{A0} &= \frac{2 \Omega (6 \text{ V})}{2 \Omega + 4 \Omega + 2 \Omega} = \frac{12 \text{ V}}{8 \Omega} = 1.5 \text{ V} \\ V_{20} &= V_{A0} = 1.5 \text{ V} \\ E_{Tn} &= V_{A0} + V_{20} = 1.5 \text{ V} + 1.5 \text{ V} = 3 \text{ V} \end{aligned}$$




$$\begin{aligned} R_T &= 6 \Omega + 3 \Omega \parallel 4 \Omega \\ &= 6 \Omega + 1.714 \Omega = 7.714 \Omega \\ I_T &= \frac{E}{R_T} = \frac{18 \text{ V}}{7.714 \Omega} = 2.333 \text{ A} \\ I_N &= \frac{E}{R_N} = \frac{18 \text{ V}}{7.56 \Omega} \\ I_N &= \frac{3 \Omega / (2.333 \text{ A})}{3 \Omega + 4 \Omega} = 1 \text{ A} \end{aligned}$$

$$I' = \frac{4\Omega(2A)}{4\Omega + 3\Omega + 6\Omega \parallel 2\Omega}$$

$$= \frac{4\Omega(2A)}{7\Omega + 1.5\Omega} = 0.941A$$

$$I'' = \frac{2\Omega I'}{2\Omega + 6\Omega} = \frac{12\Omega(0.941A)}{8\Omega} = 0.235A$$

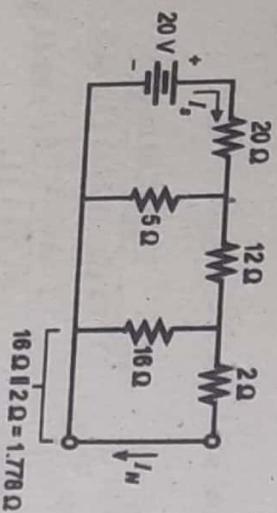27. From Problem 16,  $R_N = R_{Th} = 10\Omega$



$$R_T = 20\Omega + 5\Omega \parallel (12\Omega + 1.778\Omega) = 23.67\Omega$$


$$I_o = \frac{E_T}{R_T} = \frac{20V}{23.67\Omega} = 844.95\text{ mA}$$

$$I_{12\Omega} = \frac{5\Omega(844.95\text{ mA})}{5\Omega + (12\Omega + 1.778\Omega)} = 224.98\text{ mA}$$


$$I_N = \frac{16\Omega(224.98\text{ mA})}{16\Omega + 2\Omega} = 200\text{ mA}$$

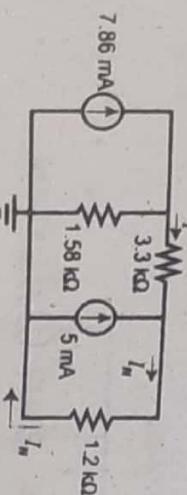28. From Problem 18,  $R_N = R_{Th} = 6.08\text{ k}\Omega$

$I_N$ : Starting with figure from problem 18:



and converting sources:

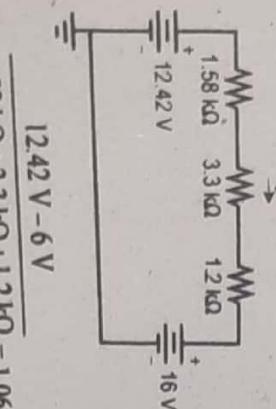


$$I' = \frac{12.42V - 6V}{1.58\text{ k}\Omega + 3.3\text{ k}\Omega + 12\text{ k}\Omega} = 1.06\text{ mA}$$

34. a.  $R = R_{Th} = 6.08 \text{ k}\Omega$  from Problem 18  
 b.  $E_{Th} = 36.8 \text{ V}$  from Problem 18

$$P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(36.8 \text{ V})^2}{4(6.08 \text{ k}\Omega)} = 55.51 \text{ mW}$$

35. a.

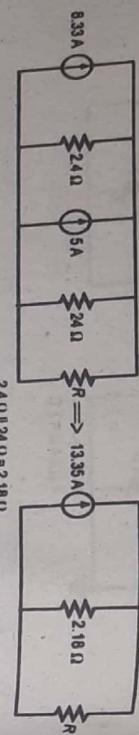


$$R = R_L = R_{Th} = 2.18 \Omega$$

$$\text{b. } P_{\max} = \frac{I_N^2 R_N}{4} = \frac{(13.33 \text{ A})^2 2.18 \Omega}{4} = 96.84 \text{ W}$$

$$P_{\max} = \left[ \frac{E_{Th}}{R_{Th} + R_L} \right]^2 R_L$$

with  $R_L = 0 \Omega$ ,  $E_{Th}$  is a maximum and  $R_{Th}$  is a minimum.  
 $\therefore R_L = 0 \Omega$

37.

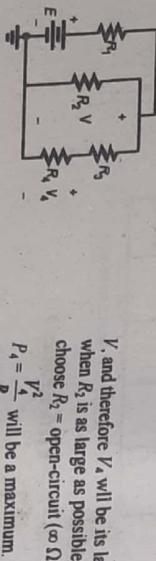

$V_4$  and therefore  $V_4$  will be its largest value when  $R_2$  is as large as possible. Therefore, choose  $R_2 = \text{open-circuit} (\infty \Omega)$  and

$$P_4 = \frac{V_4^2}{R_4}$$


$$\text{will be a maximum.}$$

- b. No, examine each individually.

38. The voltage  $V_L$  across  $R_L$  will be a maximum when  $R$  of the potentiometer =  $500 \Omega$  because the full voltage,  $E$ , will appear across  $R_L$ .

$$P_{\max} = \frac{V_L^2}{R_L} = \frac{E^2}{R_L} = \frac{(12 \text{ V})^2}{500 \Omega} = 1.44 \text{ W}$$

39.

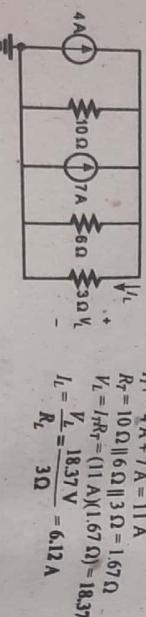

$$I_{T\uparrow} = 4 \text{ A} + 7 \text{ A} = 11 \text{ A}$$

$$R_T = 10 \Omega \parallel 6 \Omega \parallel 3 \Omega = 1.67 \Omega$$

$$V_L = I_T R_T = (11 \text{ A})(1.67 \Omega) = 18.37 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{18.37 \text{ V}}{3 \Omega} = 6.12 \text{ A}$$

$$40. E_{eq} = \frac{-5 \text{ V}/2.2 \text{ k}\Omega + 20 \text{ V}/8.2 \text{ k}\Omega}{1/2.2 \text{ k}\Omega + 1/8.2 \text{ k}\Omega} = 0.2879 \text{ V}$$

$$R_{eq} = \frac{1}{1/2.2 \text{ k}\Omega + 1/8.2 \text{ k}\Omega} = 1.7346 \text{ k}\Omega$$

$$I_L = \frac{E_{eq}}{R_{eq} + R_L} = \frac{0.2879 \text{ V}}{1.7346 \text{ k}\Omega + 5.6 \text{ k}\Omega} = 39.3 \mu\text{A}$$

$$V_L = I_L R_L = (39.3 \mu\text{A})(5.6 \text{ k}\Omega) = 220 \text{ mV}$$

$$I_T = 5 \text{ A} - 0.4 \text{ A} - 0.2 \text{ A} = 4.40 \text{ A}$$

$$R_T = 200 \Omega \parallel 80 \Omega \parallel 50 \Omega \parallel 50 \Omega = 17.39 \Omega$$

$$V_L = I_T R_T = (4.40 \text{ A})(17.39 \Omega) = 75.52 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{75.52 \text{ V}}{200 \Omega} = 0.38 \text{ A}$$

$$42. I_{eq} = \frac{(4 \text{ A})(4.7 \text{ k}\Omega) + (1.6 \text{ A})(3.3 \text{ k}\Omega)}{4.7 \text{ k}\Omega + 3.3 \text{ k}\Omega} = \frac{18.8 \text{ V} + 52.8 \text{ V}}{8 \text{ k}\Omega} = 3.01 \text{ A}$$

$$R_{eq} = 4.7 \Omega + 3.3 \Omega = 8 \Omega$$

$$I_L = \frac{R_{eq}(I_{eq})}{R_{eq} + R_L} = \frac{8 \Omega(3.01 \text{ A})}{8 \Omega + 2.7 \Omega} = 2.25 \text{ A}$$

$$V_L = I_L R_L = (2.25 \text{ A})(2.7 \Omega) = 6.08 \text{ V}$$

$$43. I_{eq} = \frac{(4 \text{ mA})(8.2 \text{ k}\Omega) + (8 \text{ mA})(4.7 \text{ k}\Omega) - (10 \text{ mA})(2 \text{ k}\Omega)}{8.2 \text{ k}\Omega + 4.7 \text{ k}\Omega + 2 \text{ k}\Omega}$$

$$= \frac{32.8 \text{ V} + 37.6 \text{ V} - 20 \text{ V}}{14.9 \text{ k}\Omega} = 3.38 \text{ mA}$$

$$R_{eq} = 8.2 \text{ k}\Omega + 4.7 \text{ k}\Omega + 2 \text{ k}\Omega = 14.9 \text{ k}\Omega$$


$$I_L = \frac{E_{eq} I_{eq}}{R_{eq} + R_L} = \frac{(14.9 \text{ k}\Omega)(3.38 \text{ mA})}{14.9 \text{ k}\Omega + 6.8 \text{ k}\Omega} = 2.32 \text{ mA}$$

$$V_L = I_L R_L = (2.32 \text{ mA})(6.8 \text{ k}\Omega) = 15.78 \text{ V}$$


$$44. 15 \text{ k}\Omega \parallel (8 \text{ k}\Omega + 7 \text{ k}\Omega) = 15 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$V_{ab} = \frac{7.5 \text{ k}\Omega(60 \text{ V})}{7.5 \text{ k}\Omega + 2.5 \text{ k}\Omega} = 45 \text{ V}$$
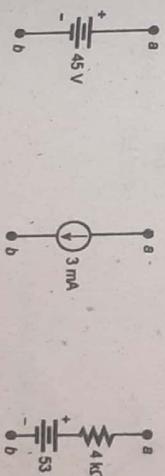
$$I_{ab} = \frac{45 \text{ V}}{15 \text{ k}\Omega} = 3 \text{ mA}$$



45.

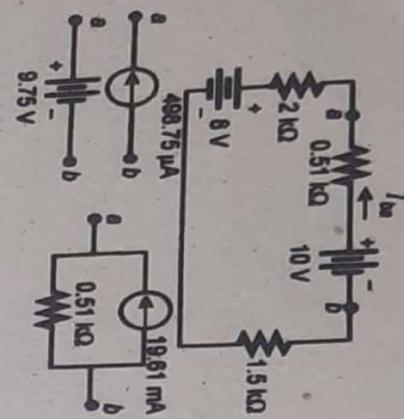


$$I_{ab} = \frac{10V - 8V}{2k\Omega + 0.51k\Omega + 1.5k\Omega} = 498.75 \mu A$$

$$V_{0.51k\Omega} = (498.75 \mu A)(0.51 k\Omega) = 0.25 V$$

$$V_{ab} = 10V - 0.25V = 9.75V$$

46.

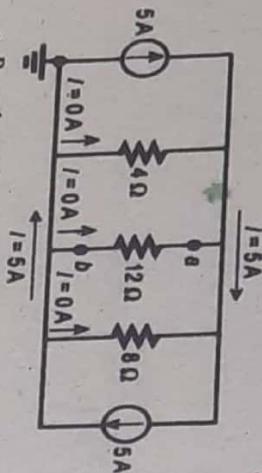


$$V_{ab} = 0V \text{ (short)} \\ I_{ab} = 0A \text{ (open)}$$

$R_2$  any resistive value


$\therefore R_2$  = short-circuit, open-circuit, any value
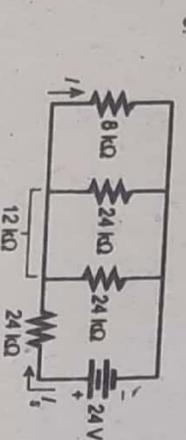
$$47. \quad \text{a.} \quad I_t = \frac{24V}{8k\Omega + \frac{24k\Omega}{3}} = 1.5 \text{ mA}, \quad I = \frac{I_t}{3} = 0.5 \text{ mA}$$



c. yes

48. (a)

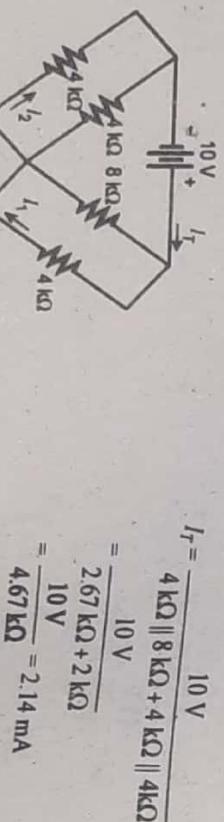

$$I_1 = \frac{8\Omega(I_T)}{8\Omega + 4\Omega} = 1.43 \text{ mA}, \quad I_2 = I_1/2 = 1.07 \text{ mA}$$


$$I = I_1 - I_2 = 1.43 \text{ mA} - 1.07 \text{ mA} = 0.36 \text{ mA}$$

# Chapter 10

1. (a)  $\sigma = k \frac{Q}{r^2} = \frac{(9 \times 10^9)(4 \mu C)}{(1 \text{ mm})^2} = 36 \times 10^9 \text{ NC}$
- (b)  $\sigma = k \frac{Q}{r^2} = \frac{(9 \times 10^9)(4 \mu C)}{(1 \text{ mm})^2} = 36 \times 10^9 \text{ NC}$   
 $\sigma(1 \text{ mm})$ :  $\sigma(2 \text{ m}) = 36 \times 10^9 \cdot 36 \times 10^1 = 1 \times 10^6$
2.  $\sigma = \frac{kQ}{r^2} \Rightarrow \sqrt{\frac{kQ}{\sigma}} = \sqrt{\frac{(9 \times 10^9)(2 \mu C)}{72 \text{ NC}}} = 15.81 \text{ m}$
3.  $C = \frac{Q}{V} = \frac{1200 \mu C}{24 \text{ V}} = 50 \mu F$
4.  $Q = CV = (0.15 \mu F)(120 \text{ V}) = 18 \mu C$
5. a.  $1'' \left[ \frac{1 \text{ m}}{39.37''} \right] = 25.4 \text{ mm}$
- b.  $\frac{25.4 \text{ mm}}{100} = 0.254 \text{ mm}$
- c.  $\sigma = \frac{V}{d} = \frac{500 \text{ mV}}{0.254 \text{ mm}} = 1.97 \text{ kV/mm}$
- d.  $V = \frac{Q}{C} = \frac{160 \mu C}{6.8 \mu F} = 23.53 \text{ V}$
- e.  $\sigma = \frac{V}{d} = \frac{23.53 \text{ V}}{5 \text{ mm}} = 4.71 \text{ kV/mm}$
- f.  $d = \frac{8.85 \times 10^{-12} \epsilon_r A}{C} = \frac{(8.85 \times 10^{-12})(5)(0.02 \text{ m}^2)}{6800 \text{ pF}} = 130.15 \mu \text{m}$
- g.  $d = 130.15 \mu \text{m} \left[ \frac{10^{-6} \text{ m}}{1 \mu \text{m}} \right] \left[ \frac{39.37 \mu \text{m}}{1 \text{ m}} \right] \left[ \frac{1000 \text{ mils}}{1 \mu \text{m}} \right] = 5.12 \text{ mils}$
- h.  $5.12 \text{ mils} \left[ \frac{5000 \text{ V}}{\text{mils}} \right] = 25.6 \text{ kV}$
- i.  $0.24 \text{ mils} \left[ \frac{1200 \text{ V}}{5000 \text{ V}} \right] \left[ \frac{\text{mils}}{39.37 \mu \text{m}} \right] = 6.10 \mu \text{m}$
- j.  $0.1'' \left[ \frac{1 \text{ m}}{39.37''} \right] = 2.54 \text{ mm}$
- k.  $C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} = 8.85 \times 10^{-12} (1) \frac{(0.1 \text{ m}^2)}{2.54 \text{ mm}} = 348.43 \text{ pF}$
- l.  $C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} = 8.85 \times 10^{-12} (2.5) \frac{(0.1 \text{ m}^2)}{2.54 \text{ mm}} = 871.06 \text{ pF}$
- m.  $C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} \Rightarrow d = \frac{8.85 \times 10^{-12} (4)(0.15 \text{ m}^2)}{2 \mu \text{F}} = 2.66 \mu \text{m}$
- n.  $C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} \Rightarrow d = \frac{8.85 \times 10^{-12} (4)(0.15 \text{ m}^2)}{2 \mu \text{F}} = 2.66 \mu \text{m}$
- o.  $C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} \Rightarrow d = \frac{8.85 \times 10^{-12} (4)(0.15 \text{ m}^2)}{2 \mu \text{F}} = 2.66 \mu \text{m}$
10.  $C = \epsilon_r C_0 \Rightarrow \epsilon_r = \frac{C}{C_0} = \frac{6.8 \text{ nF}}{1360 \text{ pF}} = 5 (\text{mica})$
11. a.  $C = 8.85 \times 10^{-12} (7) \frac{(0.08 \text{ m}^2)}{0.2 \text{ mm}} = 24.78 \text{ nF}$
- b.  $\sigma = \frac{V}{d} = \frac{80 \text{ V}}{0.2 \text{ mm}} = 400 \text{ kV/m}$
- c.  $Q = CV = (24.78 \text{ nF})(200 \text{ V}) = 4.96 \mu \text{C}$
12. a.  $C = \frac{1}{2} (4.7 \mu F) = 2.35 \mu F$
- b.  $C = 2(4.7 \mu F) = 9.4 \mu F$
- c.  $C = 20(4.7 \mu F) = 94 \mu F$
- d.  $C = \frac{(4)}{3} \left( \frac{1}{4} (4.7 \mu F) \right) = 25.1 \mu F$



e.

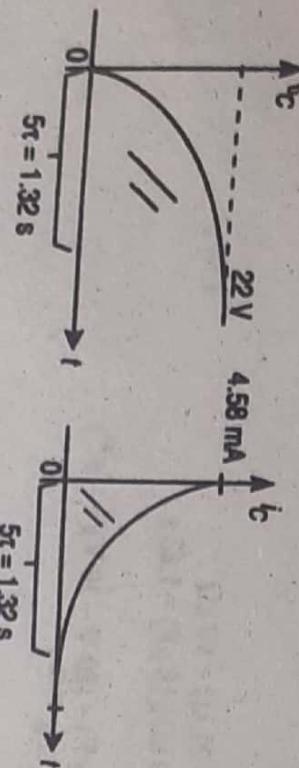

26.

a.  $\tau = RC = (3 \text{ k}\Omega + 2 \text{ k}\Omega)(2 \mu\text{F}) = 10 \text{ ms}$

$$v_C = 30 \text{ V}(1 - e^{-t/10\text{ms}})$$

$$i_C = \frac{30 \text{ V}}{5 \text{ k}\Omega} e^{-t/10\text{ms}} = 6 \text{ mA} e^{-t/10\text{ms}}$$

$$v_{R_1} = i_C R_1 = (6 \text{ mA})(3 \text{ k}\Omega) e^{-t/10\text{ms}} = 18 \text{ V} e^{-t/10\text{ms}}$$

b. 100ms:  $e^{-10} = 45.4 \times 10^{-6}$

$$v_C = 30 \text{ V}(1 - 45.4 \times 10^{-6}) = 30 \text{ V}$$

$$i_C = 6 \text{ mA}(45.4 \times 10^{-6}) = 0.27 \mu\text{A}$$

$$v_{R_1} = 18 \text{ V}(45.4 \times 10^{-6}) = 0.82 \text{ mV}$$

c. 200 ms:  $\tau' = R_2 C = (2 \text{ k}\Omega)(2 \mu\text{F}) = 4 \text{ ms}$

$$v_C = 30 \text{ V} e^{-t/4\text{ms}}$$

$$i_C = -\frac{30 \text{ V}}{2 \text{ k}\Omega} e^{-t/4\text{ms}} = -15 \text{ mA} e^{-t/4\text{ms}}$$


At  $t = 0$ :  $v_{R_1} = i_C R_1 = (6 \text{ mA})(2 \text{ k}\Omega) e^{-t/10\text{ms}}$

$$= 12 \text{ V} e^{-t/10\text{ms}}$$

At  $t = 200 \text{ ms}$ :  $v_{R_1} = -(15 \text{ mA})(2 \text{ k}\Omega) e^{-t/4\text{ms}}$

$$= -30 \text{ V} e^{-t/4\text{ms}}$$

d.

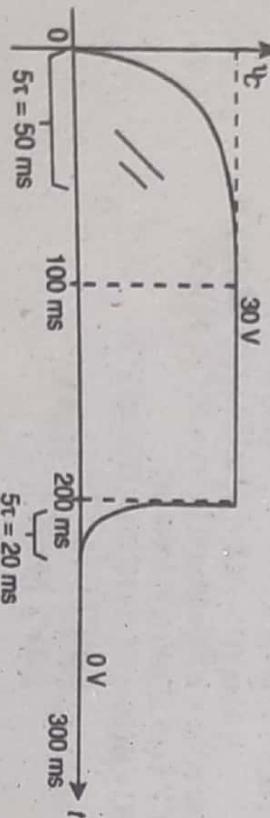

$$i_C = \frac{30 \text{ V}}{2 \text{ k}\Omega} e^{-t/50\text{ms}} = 6 \text{ mA} e^{-t/50\text{ms}}$$

$$v_{R_1} = 6 \text{ mA} R_1 = 6 \text{ mA} (3 \text{ k}\Omega) = 18 \text{ V}$$

$$v_C = 30 \text{ V} - 18 \text{ V} e^{-t/50\text{ms}}$$

$$i_C = \frac{18 \text{ V}}{2 \text{ k}\Omega} e^{-t/50\text{ms}} = 9 \text{ mA} e^{-t/50\text{ms}}$$

$$v_{R_1} = 9 \text{ mA} R_1 = 9 \text{ mA} (3 \text{ k}\Omega) = 27 \text{ V}$$

$$v_C = 30 \text{ V} - 27 \text{ V} e^{-t/50\text{ms}}$$

$$i_C = \frac{27 \text{ V}}{2 \text{ k}\Omega} e^{-t/50\text{ms}} = 13.5 \text{ mA} e^{-t/50\text{ms}}$$

$$v_{R_1} = 13.5 \text{ mA} R_1 = 13.5 \text{ mA} (3 \text{ k}\Omega) = 40.5 \text{ V}$$

$$v_C = 30 \text{ V} - 40.5 \text{ V} e^{-t/50\text{ms}}$$

$$i_C = \frac{40.5 \text{ V}}{2 \text{ k}\Omega} e^{-t/50\text{ms}} = 20.25 \text{ mA} e^{-t/50\text{ms}}$$

$$v_{R_1} = 20.25 \text{ mA} R_1 = 20.25 \text{ mA} (3 \text{ k}\Omega) = 60.75 \text{ V}$$

$$v_C = 30 \text{ V} - 60.75 \text{ V} e^{-t/50\text{ms}}$$

$$i_C = \frac{60.75 \text{ V}}{2 \text{ k}\Omega} e^{-t/50\text{ms}} = 30.375 \text{ mA} e^{-t/50\text{ms}}$$

$$v_{R_1} = 30.375 \text{ mA} R_1 = 30.375 \text{ mA} (3 \text{ k}\Omega) = 91.125 \text{ V}$$

$$v_C = 30 \text{ V} - 91.125 \text{ V} e^{-t/50\text{ms}}$$

28.

a.  $\tau = RC = (2 \text{ m}\Omega)(1000 \mu\text{F}) = 2 \mu\text{s}$   
 $5\tau = 10 \mu\text{s}$

b.  $I_m = \frac{V}{R} = \frac{12 \text{ V}}{2 \text{ m}\Omega} = 6 \text{ mA}$

c. yes


29.

a.  $u_C = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$   
 $\tau = RC = (4.7 \text{ k}\Omega)(4.7 \mu\text{F}) = 22.1 \text{ ms}$ ,  $V_f = 40 \text{ V}$ ,  $V_i = 6 \text{ V}$


$u_C = 40 \text{ V} + (6 \text{ V} - 40 \text{ V})e^{-\frac{t}{22.1 \text{ ms}}}$

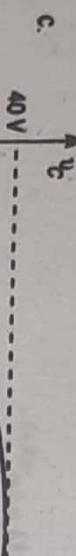b. Initially  $V_R = E + u_C = 40 \text{ V} - 6 \text{ V} = 34 \text{ V}$

$i_C = \frac{V_R}{R} e^{-\frac{t}{\tau}} = \frac{34 \text{ V}}{4.7 \text{ k}\Omega} e^{-\frac{t}{22.1 \text{ ms}}} = 7.23 \text{ mA} e^{-\frac{t}{22.1 \text{ ms}}}$



d.

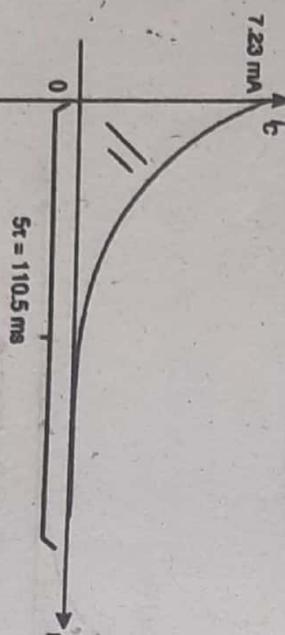


30.

a.  $\tau = RC = (4.7 \text{ k}\Omega)(4.7 \mu\text{F}) = 22.1 \text{ ms}$ ,  $V_f = 40 \text{ V}$ ,  $V_i = -40 \text{ V}$   
 $u_C = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$   
 $= 40 \text{ V} + (-40 \text{ V} - 40 \text{ V})e^{-\frac{t}{22.1 \text{ ms}}}$   
 $u_C = 40 \text{ V} - 80 \text{ V} e^{-\frac{t}{22.1 \text{ ms}}}$

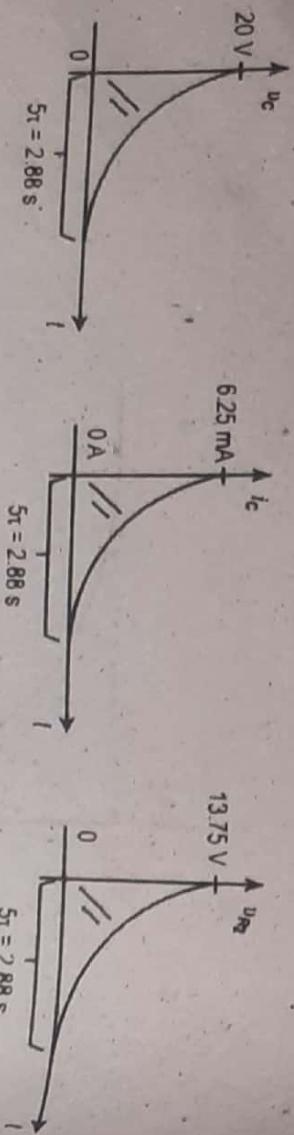b. Initially  $V_R = E + u_C = 40 \text{ V} - (-40 \text{ V}) = 80 \text{ V}$

and  $i_C = \frac{V_R}{R} = \frac{80 \text{ V}}{4.7 \text{ k}\Omega} e^{-\frac{t}{22.1 \text{ ms}}} = 17.02 \text{ mA} e^{-\frac{t}{22.1 \text{ ms}}}$



33.

$$v_C = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

$$\tau = RC = (820 \Omega)(3300 \text{ pF}) = 2.71 \mu\text{s}, \quad V_f = -20 \text{ V}, \quad V_i = -10 \text{ V}$$

$$v_C = -20 \text{ V} + (-10 \text{ V} - (-20 \text{ V}))e^{-\frac{t}{2.71 \mu\text{s}}}$$

$$I_m = \frac{-(20 \text{ V} - 10 \text{ V})}{820 \Omega} = \frac{-10 \text{ V}}{820 \Omega} = -12.2 \text{ mA}$$

$$i_C = i_R = -12.2 \text{ mA} e^{-\frac{t}{2.71 \mu\text{s}}}$$



118

CHAPTER 10

34. a.  $R = 10 \text{ k}\Omega + 8.2 \text{ k}\Omega = 18.2 \text{ k}\Omega$ 

$$\tau = RC = (18.2 \text{ k}\Omega)(6.8 \mu\text{F}) = 123.76 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

$$V_f = 20 \text{ V} + 40 \text{ V} = 60 \text{ V}$$



$$V_i = -8 \text{ V}$$

$$v_C = 60 \text{ V} + (-8 \text{ V} - 60 \text{ V})e^{-\frac{t}{123.76 \text{ ms}}}$$

$$v_C = 60 \text{ V} - 68 \text{ V} e^{-\frac{t}{123.76 \text{ ms}}}$$

$$I_m = \frac{8 \text{ V} + 20 \text{ V} + 40 \text{ V}}{18.2 \text{ k}\Omega} = 3.74 \text{ mA}$$

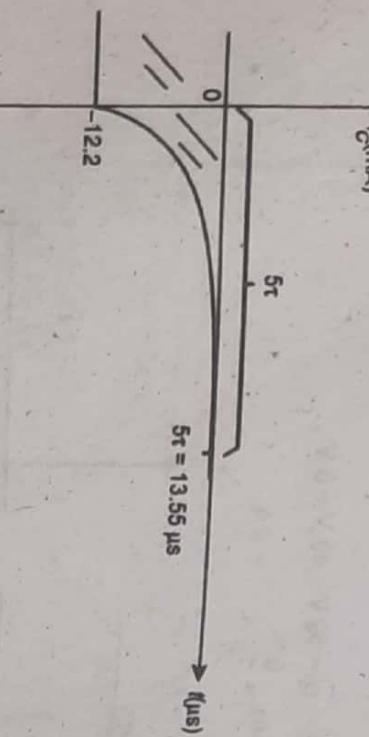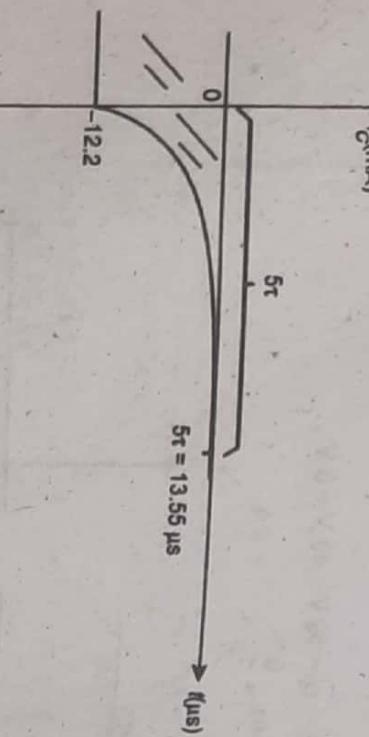
$$i_C = 3.74 \text{ mA} e^{-\frac{t}{123.76 \text{ ms}}}$$



38.  $r = RC = (33 \text{ k}\Omega)(20 \mu\text{F}) = 0.66 \text{ s}$

$$\begin{aligned} u_c &= 12 \text{ V}(1 - e^{-t/0.66}) \\ 8 \text{ V} &= 12 \text{ V}(1 - e^{-t/0.66}) \\ 8 \text{ V} &= 12 \text{ V} - 12 \text{ V}(1 - e^{-t/0.66}) \\ -4 \text{ V} &= -12 \text{ V}e^{-t/0.66} \\ 0.333 &= e^{-t/0.66} \end{aligned}$$

36. a. Network redrawn.

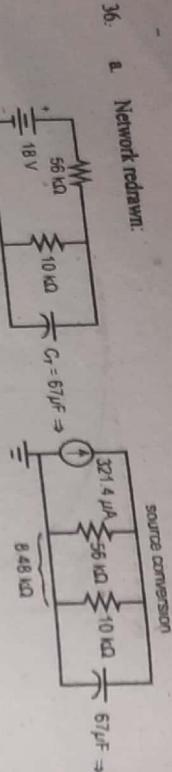

source conversion  

$$r = RC = (8.48 \text{ k}\Omega)(67 \mu\text{F}) = 568.2 \text{ ms}$$
  
 $u_c = 2.73 \text{ V}(1 - e^{-t/568.2 \text{ ms}})$

b.  $u_c = 2.73 \text{ V}(1 - e^{-10 \text{ ms}})$   
 $= 2.73 \text{ V}(1 - e^{-1/6})$   
 $= 2.73 \text{ V}(1 - 2.72 \times 10^{-6})$   
 $\approx 2.73 \text{ V}$

c.  $u_c = 2.73 \text{ V}(1 - e^{-t}) = 2.73 \text{ V}(0.993) = 2.72 \text{ V}$   
 $Q_{200\mu\text{F}} = CV = (20 \mu\text{F})(2.72 \text{ V}) = 54.4 \mu\text{C}$   
 $Q_{47\mu\text{F}} = CV = (47 \mu\text{F})(2.72 \text{ V}) = 127.84 \mu\text{C}$

37. a.  $u_c = 140 \text{ mV}(1 - e^{-1000 \text{ ms}}) = 140 \text{ mV}(1 - e^{-t}) = 140 \text{ mV}(1 - 0.6065)$   
 $= 140 \text{ mV}(0.3935) = 55.99 \text{ mV}$

b.  $u_c = 140 \text{ mV}(1 - e^{-10}) = 140 \text{ mV}(1 - 45.4 \times 10^{-6})$   
 $\approx 139.99 \text{ mV}$

c.  $100 \text{ mV} = 140 \text{ mV}(1 - e^{-t})$   
 $0.714 = 1 - e^{-t/2.5 \text{ ms}}$

$$\begin{aligned} 0.286 &= e^{-t/2.5 \text{ ms}} \\ \log_0 0.286 &= \log_e e^{-t/2.5 \text{ ms}} \\ 1.252 &= -t/2.5 \text{ ms} \\ t &= 1.252 (2 \text{ ms}) = 2.5 \text{ ms} \end{aligned}$$

d.  $u_c = 138 \text{ mV} = 140 \text{ mV}(1 - e^{-t})$   
 $0.986 = 1 - e^{-t/2.5 \text{ ms}}$   
 $-14 \times 10^{-3} = -e^{-t/2.5 \text{ ms}}$   
 $\log 14 \times 10^{-3} = -t/2 \text{ ms}$   
 $-4.268 = -t/2 \text{ ms}$   
 $t = (4.268)(2 \text{ ms}) = 8.54 \mu\text{s}$

39.  $i = -\tau \log_e \left( 1 - \frac{u_c}{E} \right)$   
 $10 \text{ s} = -\tau \log_e \left( 1 - \frac{12 \text{ V}}{20 \text{ V}} \right)$

$$-916.29 \times 10^{-3}$$

$$\tau = \frac{10 \text{ s}}{0.916} = 10.92 \text{ s}$$

40. a.  $r = RC = (12 \text{ k}\Omega + 8.2 \text{ k}\Omega)(6.8 \mu\text{F}) = 137.36 \text{ ms}$   
 $u_c = 60 \text{ V}(1 - e^{-t})$   
 $48 \text{ V} = 60 \text{ V}(1 - e^{-t})$   
 $0.8 = 1 - e^{-t}$   
 $0.2 = 1 - e^{-t}$   
 $\log_0 0.2 = \log_e e^{-t}$   
 $-1.61 = -t/137.36 \text{ ms}$   
 $t = (1.61)r = (1.61)(137.36 \text{ ms}) = 221.15 \text{ ms}$

b.  $i_c = \frac{E}{R} e^{-t/137.36 \text{ ms}} = \frac{60 \text{ V}}{20.2 \text{ k}\Omega} e^{-t/137.36 \text{ ms}}$   
 $= 2.97 \text{ mA} e^{-t/137.36 \text{ ms}}$   
 $i_d(221.15 \text{ ms}) = 2.97 \text{ mA} e^{-221.15 \text{ ms}/137.36 \text{ ms}}$   
 $= 2.97 \text{ mA} e^{-1.61}$   
 $= 2.97 \text{ mA} (199.89 \times 10^{-3})$   
 $= 0.594 \text{ mA}$

c.  $i = 2I$   
 $i_c = 2.97 \text{ mA} e^{-2t} = 2.97 \text{ mA} e^{-t}$   
 $= 0.4 \text{ mA}$   
 $0.135$

$P = EI = (60 \text{ V})(0.4 \text{ mA}) = 24 \text{ mW}$

41.

a.  $v_m = v_R = Ee^{-rt} = 60 \text{ V} e^{-10t} = 60 \text{ V} e^{-1}$

$$= 60 \text{ V}(0.3679)$$

$$= 22.07 \text{ V}$$

b.

$$i_C = \frac{E}{R} e^{-rt} = \frac{60 \text{ V}}{10 \text{ M}\Omega} e^{-2\pi f t} = 6 \mu\text{A} e^{-2}$$

$$= 6 \mu\text{A}(0.1353)$$

$$= 0.81 \mu\text{A}$$

c.

$$v_C = E(1 - e^{-rt})$$


$$50 \text{ V} = 60 \text{ V}(1 - e^{-rt})$$

$$0.8333 = 1 - e^{-rt}$$

$$\log_e 0.1667 = -rt/2$$

$$t = -(2 \text{ s})(-1.792) \\ = 3.58 \text{ s}$$

42. a. Thevenin's theorem:

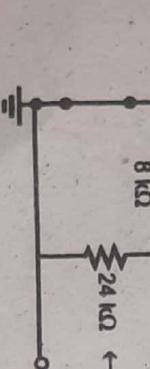 $R_{Th}$ : $E_{Th}$ :

$$E_{Th} = \frac{-24 \text{ k}\Omega (20 \text{ V})}{24 \text{ k}\Omega + 8 \text{ k}\Omega} = -15 \text{ V}$$

43. a. Source conversion and combining series resistors:

$$E = -(4 \text{ mA})(6.8 \text{ k}\Omega) = -27.2 \text{ V}$$

$$R_T = 6.8 \text{ k}\Omega + 1.5 \text{ k}\Omega = 8.3 \text{ k}\Omega$$

$$V_f = -27.2 \text{ V}, V_i = 10 \text{ V}$$

$$r = RC = (8.3 \text{ k}\Omega)(2.2 \mu\text{F}) = 18.26 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-rt} \\ = -27.2 \text{ V} + (10 \text{ V} - (-27.2 \text{ V}))e^{-rt/18.26 \text{ ms}}$$


$$v_C = -27.2 \text{ V} + 37.2 \text{ V} e^{-rt/18.26 \text{ ms}}$$

$$v_R(0+) = -27.2 \text{ V} - (-27.2 \text{ V})e^{-rt/18.26 \text{ ms}} = -37.2 \text{ V}$$

$$i_C = \frac{E}{R} e^{-rt} = -\frac{15 \text{ V}}{10 \text{ k}\Omega} e^{-rt/10.15} = -1.5 \text{ mA} e^{-rt/10.15},$$

$$i_C = -\frac{32.7 \text{ V}}{8.3 \text{ k}\Omega} e^{-rt/18.26 \text{ ms}}$$

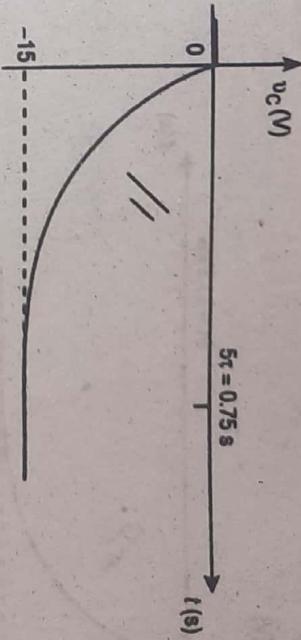
$$i_C = -4.48 \text{ mA} e^{-rt/18.26 \text{ ms}}$$



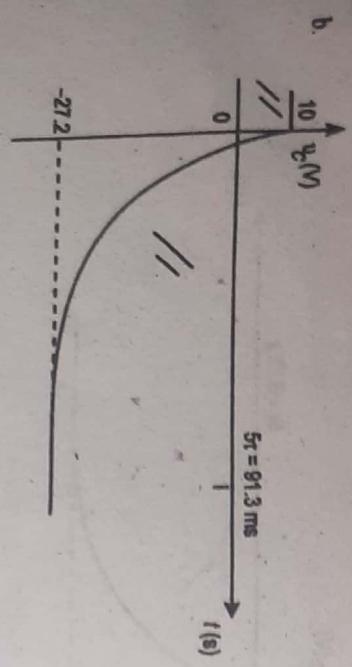45. Source conversion:

$$E = I/R_1 = (5 \text{ mA})(0.56 \text{ k}\Omega) = 2.8 \text{ V}$$

$$R' = R_1 + R_2 = 0.56 \text{ k}\Omega + 3.9 \text{ k}\Omega = 4.46 \text{ k}\Omega$$




$$R_{Th} = 4.46 \text{ k}\Omega \parallel 6.8 \text{ k}\Omega = 2.69 \text{ k}\Omega$$

$$I = \frac{4 \text{ V} - 2.8 \text{ V}}{6.8 \text{ k}\Omega + 4.46 \text{ k}\Omega} = \frac{1.2 \text{ V}}{11.26 \text{ k}\Omega} = 0.107 \text{ mA}$$

$$E_{Th} = 4 \text{ V} - (0.107 \text{ mA})(6.8 \text{ k}\Omega)$$

$$= 4 \text{ V} - 0.727 \text{ V}$$


$$= 3.27 \text{ V}$$

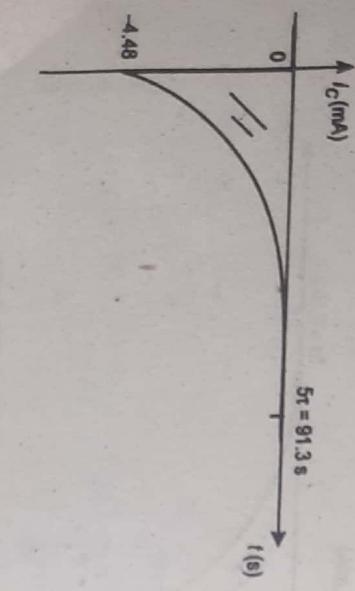

44.

a.  $R_{Th} = 3.9 \text{ k}\Omega + 0 \Omega \parallel 1.8 \text{ k}\Omega = 3.9 \text{ k}\Omega$

 $E_{Th} = 36 \text{ V}$

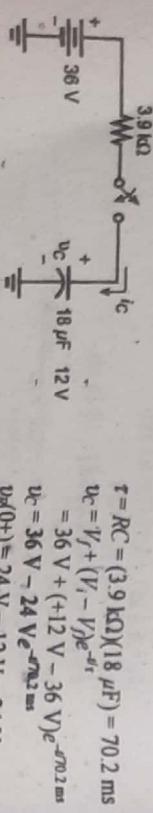

$$r = RC = (3.9 \text{ k}\Omega)(18 \mu\text{F}) = 70.2 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-rt}$$
 $= 36 \text{ V} + (12 \text{ V} - 36 \text{ V})e^{-t/70.2 \text{ ms}}$


$$v_C = 36 \text{ V} - 24 \text{ V} e^{-t/70.2 \text{ ms}}$$

$$v_C(0+) = 24 \text{ V} - 12 \text{ V} = 12 \text{ V}$$

$$i_C = \frac{24 \text{ V}}{3.9 \text{ k}\Omega} e^{-t/70.2 \text{ ms}}$$

$$i_C = 6.15 \text{ mA} e^{-t/70.2 \text{ ms}}$$


b.

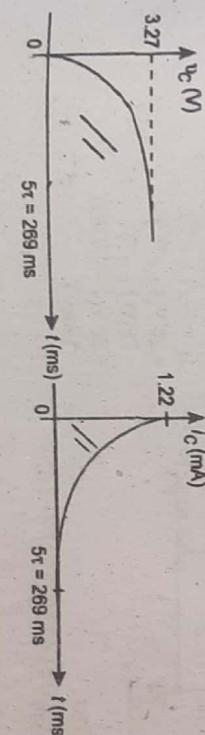

45.

a.  $R_{Th} = 4.46 \text{ k}\Omega \parallel 6.8 \text{ k}\Omega = 2.69 \text{ k}\Omega$

 $E_{Th} = 36 \text{ V}$

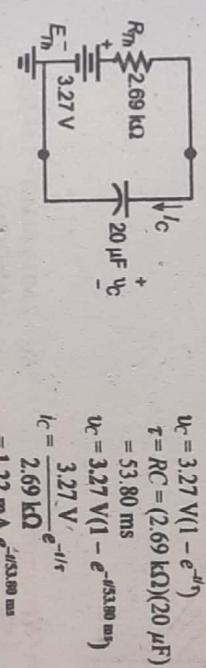

$$v_C = 3.27 \text{ V}(1 - e^{-rt})$$

$$r = RC = (2.69 \text{ k}\Omega)(20 \mu\text{F})$$


$$= 53.80 \text{ ms}$$

$$v_C = 3.27 \text{ V}(1 - e^{-t/53.80 \text{ ms}})$$

$$i_C = \frac{3.27 \text{ V}}{2.69 \text{ k}\Omega} e^{-rt}$$

$$i_C = 1.22 \text{ mA} e^{-t/53.80 \text{ ms}}$$


a.

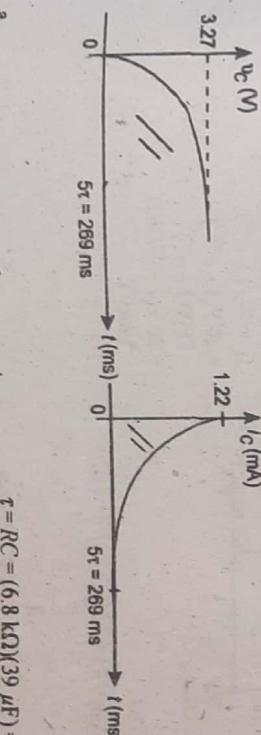

46.

a.  $R_{Th} = 6.8 \text{ k}\Omega + 0 \Omega \parallel 39 \mu\text{F} = 6.8 \text{ k}\Omega$

 $E_{Th} = 4 \text{ V}$

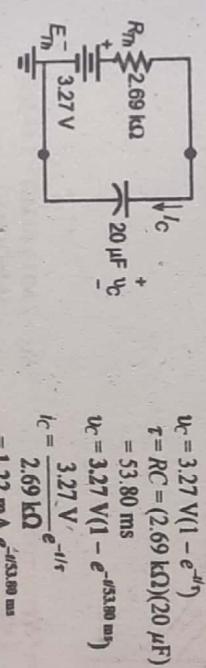

$$v_C = V_f + (V_i - V_f)e^{-rt}$$

$$= -20 \text{ V} + (-8 \text{ V} - (-20 \text{ V}))e^{-t/265.2 \text{ ms}}$$


$$v_C = -20 \text{ V} + 12 \text{ V} e^{-t/265.2 \text{ ms}}$$

$$v_C(0+) = +8 \text{ V} - 20 \text{ V} = -12 \text{ V}$$

$$i_C = \frac{-12 \text{ V}}{6.8 \text{ k}\Omega} e^{-t/265.2 \text{ ms}}$$

$$i_C = -1.76 \text{ mA} e^{-t/265.2 \text{ ms}}$$

b.  $v_C(V)$

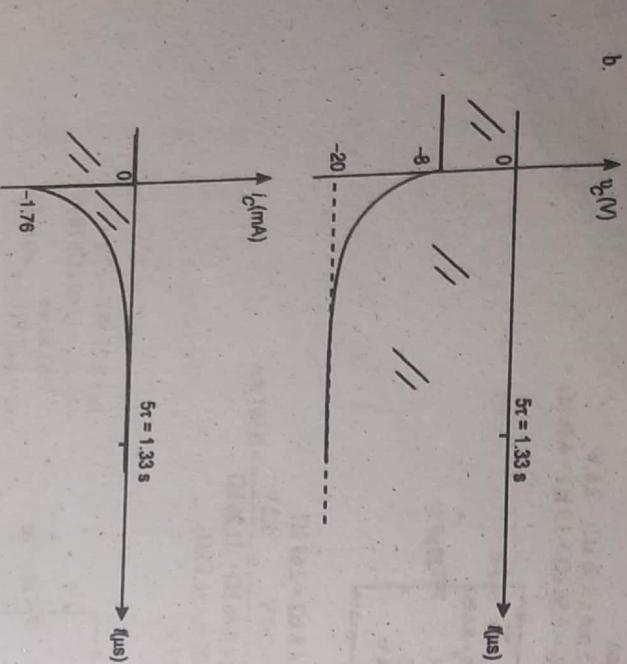

$$48. i_C = C \frac{\Delta v_C}{\Delta t}$$

$$0 \rightarrow 1 \text{ ms}: i_C = 2 \times 10^{-6} \frac{(20 \text{ V})}{1 \text{ ms}} = 40 \text{ mA}$$


$$1 \rightarrow 3 \text{ ms}: i_C = 2 \times 10^{-6} \frac{(0 \text{ V})}{1 \text{ ms}} = 0 \text{ mA}$$

$$3 \rightarrow 6 \text{ ms}: i_C = -2 \times 10^{-6} \frac{(10 \text{ V})}{3 \text{ ms}} = -6.67 \text{ mA}$$

$$6 \rightarrow 12 \text{ ms}: i_C = -2 \times 10^{-6} \frac{(10 \text{ V})}{6 \text{ ms}} = -3.33 \text{ mA}$$

$$i_C(mA)$$

$$(d/mA)$$

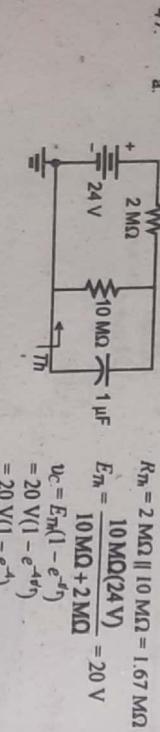

$$R_{Th} = 2 \text{ M}\Omega \parallel 10 \text{ M}\Omega = 1.67 \text{ M}\Omega$$

$$E_{Th} = \frac{10 \text{ M}\Omega (24 \text{ V})}{10 \text{ M}\Omega + 2 \text{ M}\Omega} = 20 \text{ V}$$

$$v_C = E_{Th}(1 - e^{-t/\tau})$$

$$= 20 \text{ V}(1 - e^{-t/1.67 \text{ s}})$$

$$= 20 \text{ V}(1 - e^{-t})$$

$$= 20 \text{ V}(1 - 0.0183)$$

$$= 19.63 \text{ V}$$

$$\tau = R_{Th}C = (1.67 \text{ M}\Omega)(1 \mu\text{F}) = 1.67 \text{ s}$$

$$i_C = \frac{E}{R} e^{-t/\tau}$$

$$= \frac{20 \text{ V}}{1.67 \text{ M}\Omega} e^{-t/1.67 \text{ s}}$$

$$49. i_C = C \frac{\Delta v_C}{\Delta t}$$

$$0 \rightarrow 20 \text{ } \mu\text{s}: i_C = -4.7 \text{ } \mu\text{F} \frac{(5 \text{ V})}{20 \text{ } \mu\text{s}} = -1.18 \text{ A}$$

$$20 \rightarrow 30 \text{ } \mu\text{s}: i_C = 4.7 \text{ } \mu\text{F} \frac{(10 \text{ V})}{10 \text{ } \mu\text{s}} = 4.7 \text{ A}$$

$$30 \rightarrow 60 \text{ } \mu\text{s}: i_C = 4.7 \text{ } \mu\text{F} \frac{(10 \text{ V})}{30 \text{ } \mu\text{s}} = -1.57 \text{ A}$$

$$60 \rightarrow 70 \text{ } \mu\text{s}: i_C = 4.7 \text{ } \mu\text{F} \frac{(0 \text{ V})}{10 \text{ } \mu\text{s}} = 0 \text{ A}$$

$$70 \rightarrow 80 \text{ } \mu\text{s}: i_C = 4.7 \text{ } \mu\text{F} \frac{(10 \text{ V})}{10 \text{ } \mu\text{s}} = 4.7 \text{ A}$$

$$80 \text{ } \mu\text{s} \rightarrow 100 \text{ } \mu\text{s}: i_C = -4.7 \text{ } \mu\text{F} \frac{(5 \text{ V})}{20 \text{ } \mu\text{s}} = -1.175 \text{ A}$$

$$v_{meter} = v_C$$

$$v_C = E_{Th}(1 - e^{-t/\tau})$$

$$10 \text{ V} = 20 \text{ V}(1 - e^{-t/1.67 \text{ s}})$$


$$0.5 = 1 - e^{-t/1.67 \text{ s}}$$

$$-0.5 = -e^{-t/1.67 \text{ s}}$$

$$\log_2 0.5 = -t/1.67 \text{ s}$$

$$t = -(1.67 \text{ s})(-0.69)$$

$$= 1.15 \text{ s}$$

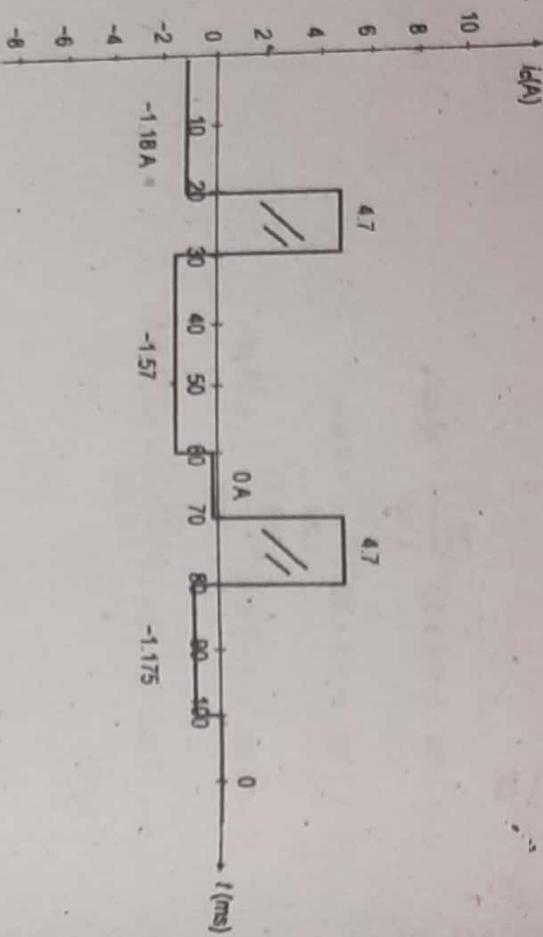

50.  $i_C = C \frac{\Delta v_C}{\Delta t} \Rightarrow \Delta v_C = \frac{C}{i_C} (\Delta t)$


$0 \rightarrow 4 \text{ ms}: i_C = 0 \text{ mA } \Delta v_C = 0 \text{ V}$

$4 \rightarrow 6 \text{ ms}: i_C = -40 \text{ mA } \Delta v_C = \frac{(2 \text{ ms})}{20 \mu\text{F}} (-40 \text{ mA}) = -4 \text{ V}$

$16 \rightarrow 20 \text{ ms}: i_C = +40 \text{ mA } \Delta v_C = \frac{(4 \text{ ms})}{20 \mu\text{s}} (40 \text{ mA}) = +20 \text{ V}$

$20 \rightarrow 25 \text{ ms}: i_C = 0 \text{ mA } \Delta v_C = 0 \text{ V}$

$\uparrow \psi(\mathcal{W})$

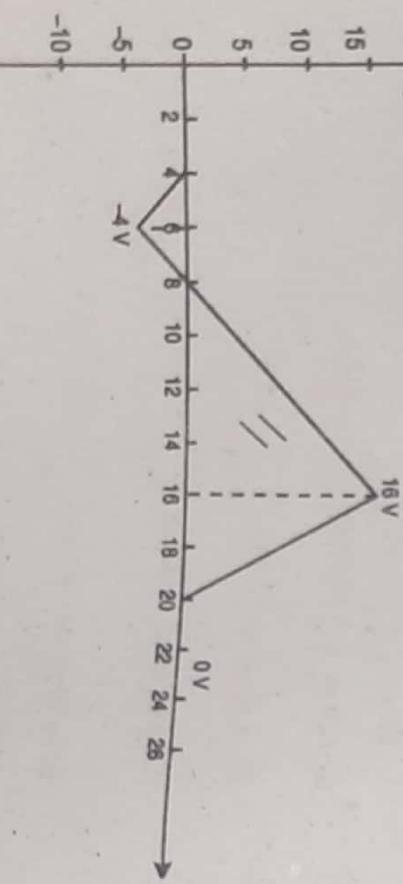

51.  $6 \mu\text{F} + 4 \mu\text{F} = 10 \mu\text{F}, 8 \mu\text{F} + 12 \mu\text{F} = 20 \mu\text{F}$   
 $10 \mu\text{F} // 20 \mu\text{F} = 6.67 \mu\text{F}$

52.  $C'_T = 6 \mu\text{F} // 12 \mu\text{F} = 4 \mu\text{F}$   
 $C''_T = C'_T + 12 \mu\text{F} = 4 \mu\text{F} + 12 \mu\text{F} = 16 \mu\text{F}$

$6 \mu\text{F} // 6 \mu\text{F} = 3 \mu\text{F}$   
 $3 \mu\text{F} // 16 \mu\text{F} = 2.53 \mu\text{F}$   
 $C_T = 2.53 \mu\text{F}$

## Chapter 11

$$W_{200\mu F} = \frac{1}{2}(200 \mu F)(9.85 \text{ V})^2 = 970 \text{ mJ}$$

$$W_{100\mu F} = \frac{1}{2}(100 \mu F)(5.91 \text{ V})^2 = 1.75 \text{ mJ}$$

60. a.  $W_C = \frac{1}{2}CV^2 = \frac{1}{2}(1000 \mu F)(100 \text{ V})^2 = 5 \text{ pJ}$

b.  $Q = CV = (1000 \mu F)(100 \text{ V}) = 0.1 \text{ C}$

c.  $I = Q/t = 0.1 \text{ C}/(1/2000) = 200 \text{ A}$

d.  $P = V_A I_{av} = W/t = 5 \text{ J}/(1/2000 \text{ s}) = 10,000 \text{ W}$

e.  $t = Q/I = 0.1 \text{ C}/10 \text{ mA} = 10 \text{ s}$

1. a.  $B = \frac{\Phi}{A} = \frac{4 \times 10^{-4} \text{ Wb}}{0.01 \text{ m}^2} = 4 \times 10^{-2} \text{ Wb/m}^2 = 0.04 \text{ Wb/m}^2$

b.  $0.04 \text{ T} = 0.04 \text{ T}$

c.  $F = NI = (40 \text{ t})(2.2 \text{ A}) = 88 \text{ At}$

d.  $0.04 \mathcal{T} \left[ \frac{0^4 \text{ gauss}}{\mathcal{T}} \right] = 0.4 \times 10^3 \text{ gauss}$

2.  $0.2' \left[ \frac{2.54 \text{ cm}}{J'} \right] \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] = 5.08 \text{ mm}$

$$J' \left[ \frac{2.54 \text{ cm}}{J'} \right] \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] = 25.4 \text{ mm}$$

$$A = \frac{\pi d^2}{4} = \frac{\pi (5.08 \text{ mm})^2}{4} = 20.27 \times 10^{-6} \text{ m}^2$$

$$L = \frac{N^2 \mu A}{l} = \frac{(200)^2 (4\pi \times 10^{-7})(20.27 \times 10^{-6} \text{ m}^2)}{25.4 \text{ mm}} = 40.1 \mu \text{H}$$

3. a.  $L = \frac{N^2 \mu \mu_o A}{l} = \frac{(200)^2 (500)(4\pi \times 10^{-7})(20.27 \times 10^{-6} \text{ m}^2)}{25.4 \text{ mm}} = 20.06 \text{ mH}$

b. increase = change in  $\mu$ .

$$L_{new} = \mu L_o$$

4.  $L = N^2 \frac{\mu \mu_o}{l} = \frac{(200)^2 (1000)(4\pi \times 10^{-7})(1.5 \times 10^{-4} \text{ m}^2)}{0.15 \text{ m}} = 50.27 \text{ mH}$

5.  $L = \frac{N^2 \mu \mu_o A}{l}$

a.  $L' = (3)^2 L_o = 9L_o = 9(4.7 \text{ mH}) = 42.3 \text{ mH}$

b.  $L' = \frac{1}{3} L_o = \frac{1}{3} (4.7 \text{ mH}) = 1.57 \text{ mH}$

c.  $L' = \frac{(2)(2)^2}{2} L_o = 16 (4.7 \text{ mH}) = 75.2 \text{ mH}$

d.  $L' = \frac{\left(\frac{1}{2}\right)^2 \frac{1}{2} (1500)L_o}{\frac{1}{2}} = 375(4.7 \text{ mH}) = 1.76 \text{ mH}$

6. a.  $39 \times 10^2 \mu \text{H} \pm 10\% \Rightarrow 3900 \mu \text{H} \pm 10\% \Rightarrow 3.9 \text{ mH} \pm 10\%$

$$i_t = 9.23 \text{ mA} + (8 \text{ mA} - 9.23 \text{ mA})e^{-t/30.77 \mu s}$$

$$i_L = 9.23 \text{ mA} - 1.23 \text{ mA} e^{-t/30.77 \mu s}$$

$$+E - v_L - v_R = 0 \text{ and } v_L = E - v_R$$

$$v_R = i_R R = i_L R = (8 \text{ mA})(3.9 \text{ k}\Omega) = 31.2 \text{ V}$$

$$v_L = E - v_R = 36 \text{ V} - 31.2 \text{ V} = 4.8 \text{ V}$$

$$v_L = 4.8 \text{ V} e^{-t/30.77 \mu s}$$

b.

$$i_t = 9.23 \text{ mA} + (8 \text{ mA} - 9.23 \text{ mA})e^{-t/30.77 \mu s}$$

$$i_L = 9.23 \text{ mA} - 1.23 \text{ mA} e^{-t/30.77 \mu s}$$


$$+E - v_L - v_R = 0 \text{ and } v_L = E - v_R$$

$$v_R = i_R R = i_L R = (8 \text{ mA})(3.9 \text{ k}\Omega) = 31.2 \text{ V}$$

$$v_L = E - v_R = 36 \text{ V} - 31.2 \text{ V} = 4.8 \text{ V}$$

$$v_L = 4.8 \text{ V} e^{-t/30.77 \mu s}$$

c. Source conversion:

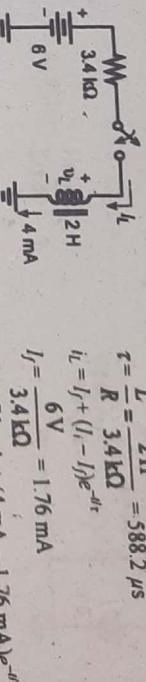

$$r = \frac{L}{R} = \frac{2\text{H}}{3.4\text{k}\Omega} = 588.2 \mu\text{s}$$

$$i_L = i_f + (I_f - I_f)e^{-rt}$$

$$I_f = \frac{6\text{V}}{3.4\text{k}\Omega} = 1.76 \text{ mA}$$

$$i_L = 1.76 \text{ mA} + (4 \text{ mA} - 1.76 \text{ mA})e^{-0.588.2\mu\text{s}}$$

$$i_L = 1.76 \text{ mA} + 2.24 \text{ mA} e^{-0.588.2\mu\text{s}}$$

16. a.  $i_t = 9.23 \text{ mA}, I_f = 9.23 \text{ mA}, r = \frac{L}{R} = \frac{120 \text{ mH}}{3.9 \text{ k}\Omega} = 30.77 \mu\text{s}$

$$i_L = i_f + (I_f - I_f)e^{-rt}$$

$$= 9.23 \text{ mA} + (-8 \text{ mA} - 9.23 \text{ mA})e^{-t/30.77 \mu s}$$

$$i_L = 9.23 \text{ mA} - 17.23 \text{ mA} e^{-t/30.77 \mu s}$$


$$+E - v_L - v_R = 0 \text{ (at } t = 0^+)$$

$$\text{but, } v_R = i_R R = -i_L R = (-8 \text{ mA})(3.9 \text{ k}\Omega) = -31.2 \text{ V}$$

$$v_L = E - v_R = 36 \text{ V} - (-31.2 \text{ V}) = 67.2 \text{ V}$$

$$v_L = 67.2 \text{ V} e^{-t/30.77 \mu s}$$

b.

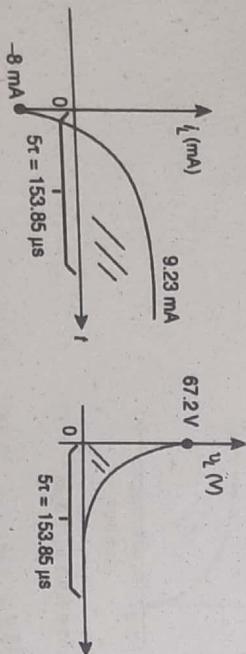

c. Final levels are the same. Transition period defined by 5τ is also the same.

19. a.



$$I_f = \frac{20.8\text{V}}{10.4\text{k}\Omega} = 2 \text{ mA}$$

$$r = \frac{L}{R} = \frac{200 \text{ mH}}{10.4 \text{ k}\Omega} = 19.23 \mu\text{s}$$

$$i_L = i_f + (I_f - I_f)e^{-rt}$$

$$= 2 \text{ mA} + (6 \text{ mA} - 2 \text{ mA})e^{-t/19.23 \mu s}$$

$$i_L = 2 \text{ mA} + 4 \text{ mA} e^{-t/19.23 \mu s}$$

KVL:  $20.8 \text{ V} - 62.4 \text{ V} - v_L(0+) = 0$


$$v_L(0+) = -41.6 \text{ V} e^{-t/19.23 \mu s}$$

a.  $i_t = \frac{E}{R_1 + R_2} (1 - e^{-t/(\tau_{RC})}) = \frac{20 \text{ V}}{3.4 \text{ k}\Omega} (1 - e^{-t/(29.41 \mu s)})$


b.  $i_t = \frac{E}{R_1 + R_2} (1 - e^{-t/(\tau_{RC})})$

$$i_t = 5.88 \text{ mA} (1 - e^{-t/(29.41 \mu s)})$$

b.

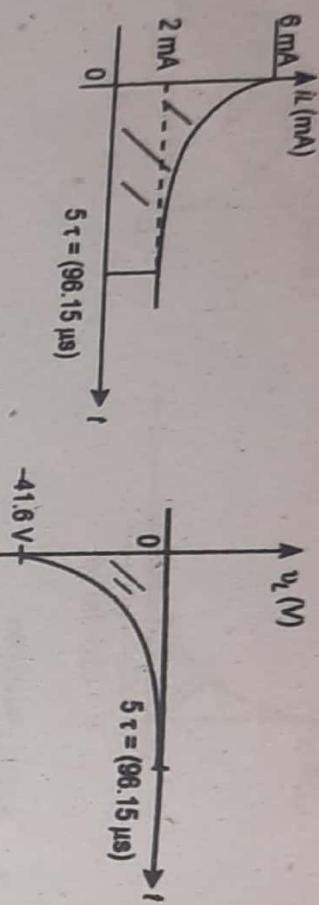

20.

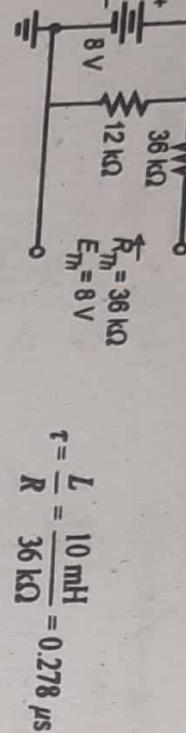


$$v_L = 8V e^{-\frac{t}{\tau}}, i_L = \frac{E}{R}(1 - e^{-\frac{t}{\tau}}) = 0.222 \text{ mA}(1 - e^{-\frac{t}{0.278 \mu s}})$$

b.  $5\tau \Rightarrow$  steady state

$$\tau' = \frac{L}{R} = \frac{10 \text{ mH}}{12 \text{ k}\Omega + 36 \text{ k}\Omega} = 0.208 \mu s$$

$$i_L = I_{\text{ss}} e^{-\frac{t}{\tau'}} = 0.222 \text{ mA} e^{-\frac{t}{0.208 \mu s}}$$
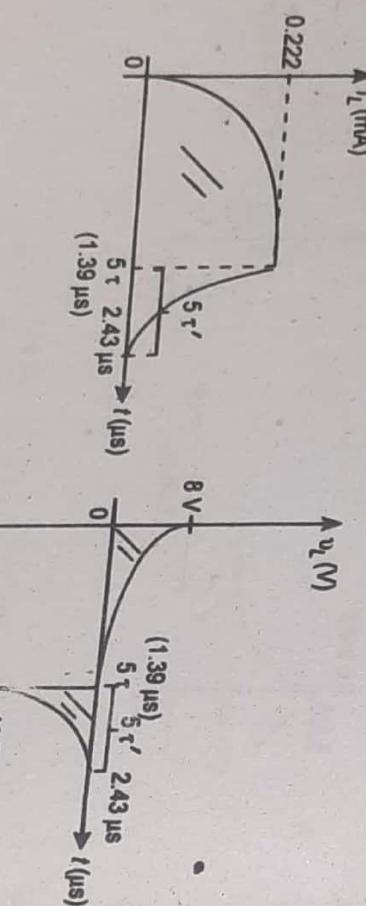
$$v_L = -(0.222 \text{ mA})(48 \text{ k}\Omega) e^{-\frac{t}{\tau'}} = -10.66 \text{ V} e^{-\frac{t}{0.208 \mu s}}$$



21.

a.  $\tau = \frac{L}{R} = \frac{4.7 \text{ mH}}{2 \text{ k}\Omega} = 2.35 \mu s$

$$i_L = \frac{E}{R}(1 - e^{-\frac{t}{\tau}}) = \frac{12 \text{ V}}{2 \text{ k}\Omega}(1 - e^{-\frac{t}{\tau}}) = 6 \text{ mA}(1 - e^{-\frac{t}{2.35 \mu s}})$$

$$v_L = E e^{-\frac{t}{\tau}} = 12 \text{ V} e^{-\frac{t}{2.35 \mu s}}$$

b.  $i_L = 6 \text{ mA}(1 - e^{-\frac{t}{2.35 \mu s}}) = 6 \text{ mA}(1 - e^{-\frac{t}{0.653 \mu s}}) = 6 \text{ mA}(1 - e^{-0.426})$

$$= 6 \text{ mA}(1 - 0.653) = 6 \text{ mA}(0.347) = 2.08 \text{ mA}$$


$$\tau' = \frac{L}{R_1 + R_2} = \frac{4.7 \text{ mH}}{12 \text{ k}\Omega} = 392 \text{ ns}$$

$$i_L = 2.08 \text{ mA} e^{-\frac{t}{392 \text{ ns}}}$$

$$v_L = 12 \text{ V} e^{-\frac{t}{0.235 \mu s}} = 12 \text{ V} e^{-\frac{t}{0.653 \mu s}} = 12 \text{ V} e^{-0.426}$$

$$= 12 \text{ V}(0.653) = 7.84 \text{ V}$$

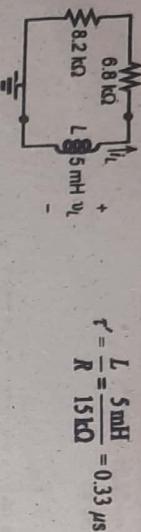b. Assume steady state and  $I_L = 0.88 \text{ mA}$



$$i_L = 1.3 \text{ mA} (1 - e^{-\frac{t}{\tau}})$$

$$V_L = 8.09 \text{ V} e^{-\frac{t}{\tau}}$$

$$b. 0.632(1.3 \text{ mA}) = 0.822 \text{ mA}$$

$$0.368(8.09 \text{ V}) = 2.98 \text{ V}$$


$$i_L = I_m e^{-\frac{t}{\tau}} = 0.88 \text{ mA} e^{-\frac{t}{0.33 \mu s}}$$

$$V_L = -V_m e^{-\frac{t}{\tau}}$$

$$V_m = I_m R = (0.88 \text{ mA})(15 \text{ k}\Omega) = 13.23 \text{ V}$$

$$V_L = -13.23 \text{ V} e^{-\frac{t}{0.33 \mu s}}$$

c.

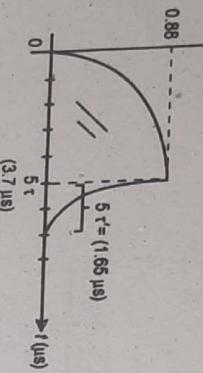


$$b. r = \frac{L}{R} = \frac{5 \text{ mH}}{15 \text{ k}\Omega} = 0.33 \mu \text{s}$$

$$i_L = E e^{-\frac{t}{r}} = 28 \text{ V} e^{-\frac{t}{0.33 \mu \text{s}}}$$

$$i_L = \frac{E}{R} (1 - e^{-\frac{t}{r}}) = \frac{28 \text{ V}}{36 \text{ k}\Omega} (1 - e^{-\frac{t}{0.33 \mu \text{s}}}) = 0.778 \text{ mA} (1 - e^{-\frac{t}{0.33 \mu \text{s}}})$$

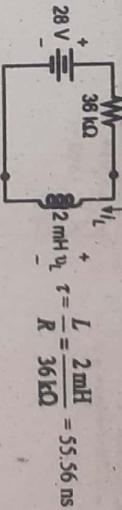
$$24. a. \text{Source conversion: } E = IR = (4 \text{ mA})(12 \text{ k}\Omega) = 48 \text{ V}, E_{NEA} = 48 \text{ V} - 20 \text{ V} = 28 \text{ V}$$



$$b. r = \frac{L}{R} = \frac{2 \text{ mH}}{36 \text{ k}\Omega} = 55.56 \text{ ns}$$

$$i_L = \frac{E}{R} (1 - e^{-\frac{t}{r}}) = \frac{28 \text{ V}}{36 \text{ k}\Omega} (1 - e^{-\frac{t}{55.56 \text{ ns}}})$$

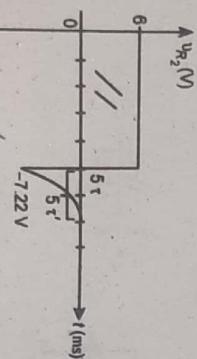d.  $V_{L_{\text{max}}} = I_m R_2 = (0.88 \text{ mA})(8.2 \text{ k}\Omega) = 7.22 \text{ V}$



$$V_L = 28 \text{ V} e^{\frac{t}{\tau}} = 4.62 \text{ V}$$

$$23. a. R_{Th} = 2 \text{ k}\Omega + 2.2 \text{ k}\Omega + 6.2 \text{ k}\Omega \parallel 3 \text{ k}\Omega = 6.22 \text{ k}\Omega$$

$$E_{Th} = \frac{6.2 \text{ k}\Omega(12 \text{ V})}{6.2 \text{ k}\Omega + 3 \text{ k}\Omega} = 8.09 \text{ V}$$

$$I_f = \frac{8.09 \text{ V}}{6.22 \text{ k}\Omega} = 1.3 \text{ mA}, \tau = \frac{L}{R} = \frac{47 \text{ mH}}{6.22 \text{ k}\Omega} = 7.56 \mu \text{s}$$

$$25. a. R_{Th} = 1.5 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega = 1.50 \text{ k}\Omega$$

$$E_{Th} = -\frac{4.7 \text{ k}\Omega(10 \text{ V})}{4.7 \text{ k}\Omega + 2.2 \text{ k}\Omega} = -6.81 \text{ V}$$

$$b. r = \frac{L}{R} = \frac{10 \text{ mH}}{1.50 \text{ k}\Omega} = 6.67 \mu \text{s}$$

$$i_L = -\frac{E}{R} (1 - e^{-\frac{t}{r}}) = -\frac{6.81 \text{ V}}{1.5 \text{ k}\Omega} (1 - e^{-\frac{t}{6.67 \mu \text{s}}}) = -4.54 \text{ mA} (1 - e^{-\frac{t}{6.67 \mu \text{s}}})$$

$$V_L = E e^{-\frac{t}{r}} = -E_{Th} e^{-\frac{t}{r}} = -6.81 \text{ V} e^{-\frac{t}{6.67 \mu \text{s}}}$$

$$b. r = 10 \mu \text{s},$$

$$i_L = -4.54 \text{ mA} (1 - e^{-\frac{t}{10 \mu \text{s}}}) = -4.54 \text{ mA} (\underbrace{1 - e^{-\frac{t}{10 \mu \text{s}}}}_{0.223})$$

$$= -3.53 \text{ mA}$$


$$V_L = -6.81 \text{ V}(0.223) = -1.52 \text{ V}$$

$$At t = 10 \mu \text{s}$$

$$V_L = (3.53 \text{ mA})(4.7 \text{ k}\Omega) = 16.59 \text{ V}$$

$$V_L = 16.59 \text{ V} e^{-\frac{10 \mu \text{s}}{10 \mu \text{s}}}$$

d.

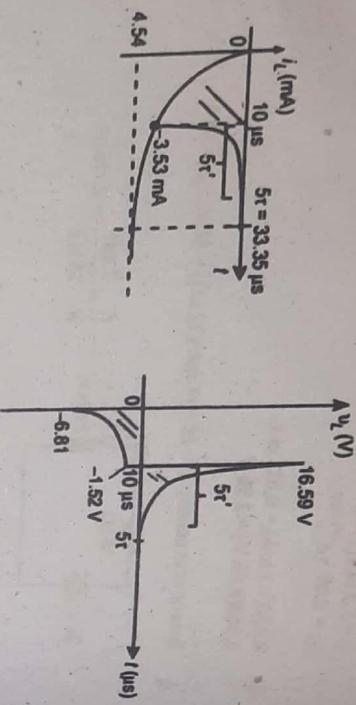


26.

a.

Finding the Thevenin circuit for the inductor:
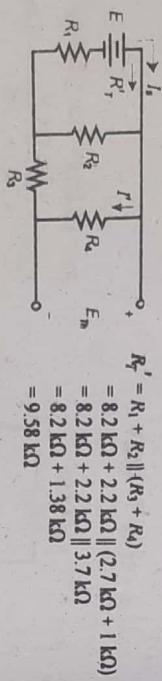
$$\begin{aligned} R_{Th} &= R_4 \parallel (R_3 + R_1 \parallel R_2) \\ &= 1 \text{k}\Omega \parallel (2.7 \text{k}\Omega + 8.2 \text{k}\Omega \parallel 2.2 \text{k}\Omega) \\ &= 1 \text{k}\Omega \parallel 4.43 \text{k}\Omega \\ &= 0.816 \text{k}\Omega \end{aligned}$$



$$\text{Then } I_s = \frac{E}{R_7'} = \frac{36 \text{ V}}{9.58 \text{ k}\Omega} = 3.76 \text{ mA}$$

$$\text{and } I'' = \frac{R_2(I_s)}{R_1 + R_3 + R_4} = \frac{2.2 \text{ k}\Omega(3.76 \text{ mA})}{2.2 \text{ k}\Omega + 2.7 \text{ k}\Omega + 1 \text{ k}\Omega} = 1.4 \text{ mA}$$

$$\text{and finally } E_{Th} = I/R_4 = (1.4 \text{ mA})(1 \text{ k}\Omega) = 1.4 \text{ V}$$

$$\tau = \frac{L}{R} = \frac{10 \text{ mH}}{0.816 \text{ k}\Omega} = 12.25 \mu\text{s}$$

$$V_t = 1.4 \text{ V} e^{-\frac{t}{12.25 \mu\text{s}}}$$


$$= 1.4 \text{ V} e^{-2.05 \mu\text{s}}$$

$$= 1.4 \text{ V}(128.73 \times 10^{-3})$$


$$= 180 \text{ mV}$$

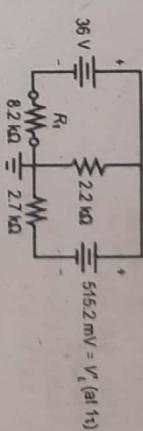c. Finding the Thevenin equivalent for  $R_1$  at  $t = 1\tau$ 

$$At 1\tau, u_L = 1.4 \text{ V} e^{-t/\tau} = 1.4 \text{ V} e^{-1} = 1.4 \text{ V}(0.368) = 515.2 \text{ mV}$$


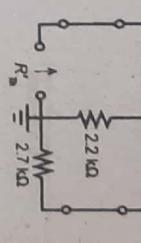
$$R_{Th}' = 2.2 \text{ k}\Omega \parallel 2.7 \text{ k}\Omega = 1.21 \text{ k}\Omega$$




$$-E_{Th}' + 36 \text{ V} - u_{R_1} = 0$$

$$E_{Th}' = 36 - u_{R_1}$$

$$u_{R_1} = \frac{2.2 \text{ k}\Omega(515.2 \text{ mV})}{2.2 \text{ k}\Omega + 2.7 \text{ k}\Omega} = 0.231 \text{ V}$$
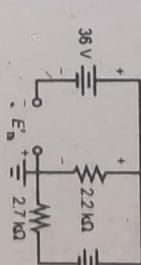
$$\therefore E_{Th}' = 36 \text{ V} - 0.231 \text{ V} = 35.77 \text{ V}$$



$$u_{R_1} = \frac{8.2 \text{ k}\Omega(35.77 \text{ V})}{8.2 \text{ k}\Omega + 1.21 \text{ k}\Omega} = 31.34 \text{ V}$$

$$d. i_t = \frac{E_{Th}}{R_{Th}}(1 - e^{-t/\tau})$$

$$= \frac{1.4 \text{ V}}{0.816 \text{ k}\Omega} (1 - e^{-t/(12.25 \mu\text{s})})$$

$$= 1.72 \text{ mA}(1 - e^{-t/(12.25 \mu\text{s})})$$

$$1 \text{ mA} = 1.72 \text{ mA}(1 - e^{-t/(12.25 \mu\text{s})})$$

$$0.581 = 1 - e^{-t/(12.25 \mu\text{s})}$$

$$0.419 = e^{-t/(12.25 \mu\text{s})}$$

$$t = 12.25 \mu\text{s} \log 0.419$$

$$= 12.25 \mu\text{s}(0.87)$$

$$= 10.66 \mu\text{s}$$

$$27. a. I_t = \frac{16 \text{ V}}{4.7 \text{ k}\Omega + 3.3 \text{ k}\Omega} = 2 \text{ mA}$$

$$I = 0 \text{ s. Thevenin:}$$

$$R_{Th} = 3.3 \text{ k}\Omega + 1 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega = 3.3 \text{ k}\Omega + 0.82 \text{ k}\Omega = 4.12 \text{ k}\Omega$$

$$E_{Th} = \frac{1 \text{ k}\Omega(6 \text{ V})}{1 \text{ k}\Omega + 4.7 \text{ k}\Omega} = 2.81 \text{ V}$$

$$\begin{aligned} i_t &= I_t + (I_t - I)/k^{\alpha} \\ &= 1.29 \text{ V} \end{aligned}$$

$$I_f = \frac{2.81 \text{ V}}{4.12 \text{ k}\Omega} = 0.68 \text{ mA}, \tau = \frac{L}{R} = \frac{2 \text{ H}}{4.12 \text{ k}\Omega} = 0.49 \text{ ms}$$

$$\begin{aligned} i_L &= 0.68 \text{ mA} + (2 \text{ mA} - 0.68 \text{ mA})e^{-0.49 \text{ ms}} \\ i_L &= 0.68 \text{ mA} + 1.32 \text{ mA}e^{-0.49 \text{ ms}} \end{aligned}$$


$$u_R(0+) = 2 \text{ mA}(4.12 \text{ k}\Omega) = 8.24 \text{ V}$$

$$KVL(0+): 2.81 \text{ V} - 8.24 \text{ V} - u_L = 0$$

$$u_L = -5.43 \text{ V} e^{-0.49 \text{ ms}}$$

$$v_L = -5.43 \text{ V} e^{-0.49 \text{ ms}}$$

b.

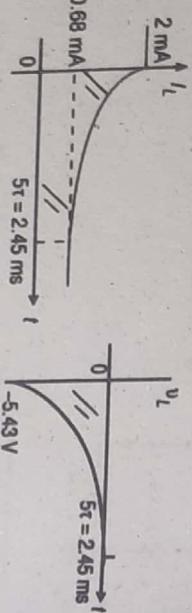


c.

$$\text{Steady-state: } i_L = \frac{8 \text{ V}}{1.5 \text{ k}\Omega} = 5.33 \text{ mA}, V_L = 0 \text{ V}$$

$$R_{Th} = (3 \text{ k}\Omega \parallel 12 \text{ k}\Omega) \parallel 4 \text{ k}\Omega = 1.5 \text{ k}\Omega$$
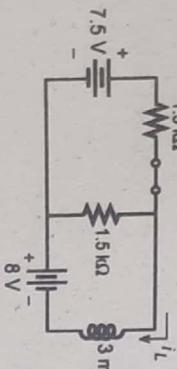
$$E_{Th} = \frac{2.4 \text{ k}\Omega(20 \text{ V})}{2.4 \text{ k}\Omega + 4 \text{ k}\Omega} = 7.5 \text{ V}$$




$$R_{Th}' = 1.5 \text{ k}\Omega \parallel 1.5 \text{ k}\Omega = 0.75 \text{ k}\Omega$$


$$E_{Th}' = 8 \text{ V} + 7.5 \text{ V} = 15.5 \text{ V}$$

$$\begin{aligned} i_L' &= 1.5 \text{ k}\Omega \parallel 1.5 \text{ k}\Omega = 0.75 \text{ k}\Omega \\ E_{Th}' &= 8 \text{ V} + 7.5 \text{ V} = 15.5 \text{ V} \end{aligned}$$

d.

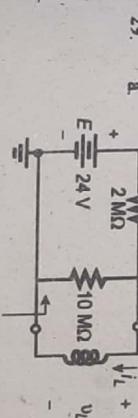

e.

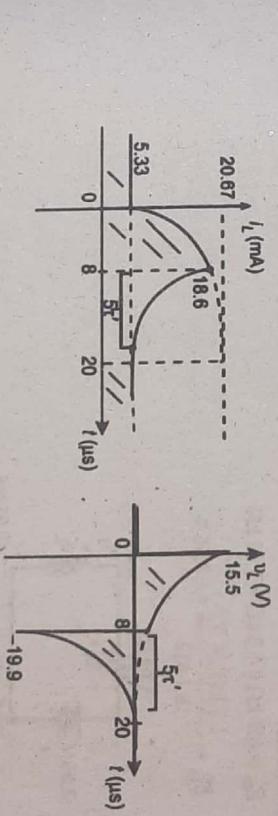

$$i_L = 18.6 \text{ mA}$$

$$i_L = \frac{8 \text{ V}}{1.5 \text{ k}\Omega} = 5.33 \text{ mA}$$

$$\begin{aligned} i_L &= i_L + (i_L - I_f)e^{-\frac{t}{\tau}} = 5.33 \text{ mA} + (18.6 \text{ mA} - 5.33 \text{ mA})e^{-\frac{t}{0.49 \mu s}} \\ &= 5.33 \text{ mA} + 13.27 \text{ mA}e^{-\frac{t}{0.49 \mu s}} \end{aligned}$$

$$v_L = 8 \text{ V} - 0.68 \text{ mA} \cdot 10 \text{ M}\Omega = 8 \text{ V} - (18.6 \text{ mA} - 5.33 \text{ mA})(1.5 \text{ k}\Omega)$$

$$\tau' = \frac{L}{R} = \frac{3 \text{ mH}}{1.5 \text{ k}\Omega} = 2 \mu\text{s}$$

$$\begin{aligned} b. \quad i_L(2\tau) &= 20.67 \text{ mA} - 15.34 \text{ mA} e^{-\frac{2\tau}{0.135}} \\ &= 18.6 \text{ mA} \end{aligned}$$

$$v_L(2\tau) = 15.5 \text{ V} e^{-2} = 15.5 \text{ V} (0.135) = 2.09 \text{ V}$$

$$\begin{aligned} b. \quad i_L(2\tau) &= 20.67 \text{ mA} - 15.34 \text{ mA} e^{-\frac{2\tau}{0.135}} \\ &= 18.6 \text{ mA} \end{aligned}$$

$$\begin{aligned} b. \quad i_L(2\tau) &= 20.67 \text{ mA} - 15.34 \text{ mA} e^{-\frac{2\tau}{0.135}} \\ &= 18.6 \text{ mA} \end{aligned}$$

$$I_f = \frac{15.5 \text{ V}}{0.75 \text{ k}\Omega} = 20.67 \text{ mA} \quad I_f = 5.33 \text{ mA}$$

$$\begin{aligned} i_L &= i_L + (I_f - i_L)e^{-\frac{t}{\tau}} \\ &= 20.67 \text{ mA} + (5.33 \text{ mA} - 20.67 \text{ mA})e^{-\frac{t}{0.49 \mu s}} \end{aligned}$$

$$\begin{aligned} i_L &= 20.67 \text{ mA} - 15.34 \text{ mA} e^{-\frac{t}{0.49 \mu s}} \\ i_L &= 15.5 \text{ V} e^{-\frac{t}{0.49 \mu s}} \end{aligned}$$

$$\begin{aligned} I_f &= \frac{15.5 \text{ V}}{0.75 \text{ k}\Omega} = 20.67 \text{ mA} \\ i_L &= i_L + (I_f - i_L)e^{-\frac{t}{\tau}} \\ &= 20.67 \text{ mA} + (5.33 \text{ mA} - 20.67 \text{ mA})e^{-\frac{t}{0.49 \mu s}} \\ i_L &= 20.67 \text{ mA} - 15.34 \text{ mA} e^{-\frac{t}{0.49 \mu s}} \\ i_L &= 15.5 \text{ V} e^{-\frac{t}{0.49 \mu s}} \end{aligned}$$

$$\begin{aligned} I_f(0') &= \frac{E_{Th}}{R_{Th}} = \frac{20 \text{ V}}{1.67 \text{ M}\Omega} = 12 \mu\text{A} \\ E_{Th} &= \frac{10 \text{ M}\Omega(24 \text{ V})}{10 \text{ M}\Omega + 2 \text{ M}\Omega} = 20 \text{ V} \end{aligned}$$

$$i_L' = \frac{L}{R_{Th}} = \frac{5 \text{ H}}{10 \text{ M}\Omega} = 5 \mu\text{s}$$

$$\begin{aligned} i_L &= 12 \mu\text{A} e^{-\frac{t}{5 \mu\text{s}}} \\ i_L &= 12 \mu\text{A} e^{-\frac{t}{5 \mu\text{s}}} \end{aligned}$$

$$0.833 = e^{-t/5 \mu s}$$

$$\log_e 0.833 = -t/5 \mu s$$

$$0.183 = t/5 \mu s$$

$$t = 0.183(5 \mu s) = 0.92 \mu s$$


b.  $v_L(0^+) = i_L(0^+)R_m = (12 \mu A)(10 M\Omega) = 120 V$   
 $v_L = 120 V e^{-t/5 \mu s} = 120 V e^{-10 \mu s / 5 \mu s} = 120 V e^{-2} = 120 V(0.135) = 16.2 V$

c.  $v_L = 120 V e^{-5t/\tau} = 120 V e^{-5} = 120 V(6.74 \times 10^{-3}) = 0.81 V$

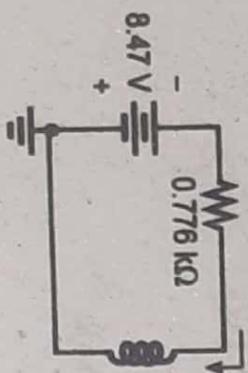30. a. Closed Switch:

$$R_{Th} = 1.2 k\Omega \parallel 2.2 k\Omega = 0.776 k\Omega$$


$$E_{Th} = \frac{1.2 k\Omega(24 V)}{1.2 k\Omega + 2.2 k\Omega} = 8.47 V$$



Open Switch:

$$R_{Th}' = 6.9 k\Omega \parallel 1.2 k\Omega = 1.02 k\Omega$$
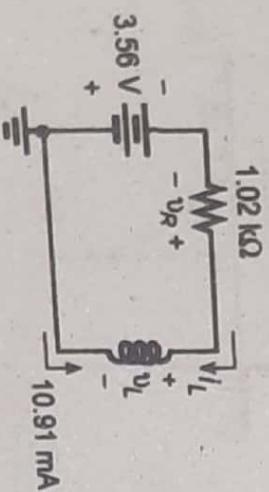
$$E_{Th}' = \frac{1.2 k\Omega(24 V)}{8.1 k\Omega} = -3.56 V$$



$$-3.56 V + v_R - v_L = 0$$

$$v_L = -3.56 V + (10.91 \text{ mA})(1.02 \text{ k}\Omega)$$

$$= 7.57 V$$

$$v_L = 7.57 V e^{-t/1.18 \text{ ms}}$$

$$\tau = \frac{L}{R} = \frac{1.24 \text{ H}}{1.02 \text{ k}\Omega} = 1.18 \text{ ms}$$

$$I_{ss} = \frac{3.56 \text{ V}}{1.02 \text{ k}\Omega} = 3.49 \text{ mA} = I_f$$

$$i_L = I_f + (I_f - I_f)e^{-t/\tau} \\ = I_f + (I_f - I_f)e^{-t/1.18 \text{ ms}} \\ = -3.49 \text{ mA} + ((-10.91 \text{ mA} - (-3.49 \text{ mA}))e^{-t/1.18 \text{ ms}} \\ i_L = -3.49 \text{ mA} - 7.42 \text{ mA} e^{-t/1.18 \text{ ms}}$$

32. a.  $I_L(t) = 0.632 I_{\max} = 126.4 \mu\text{A}$   
 $I_{\max} = \frac{126.4}{0.632} = 200 \mu\text{A}$

$$i_t = I_{\max}(1 - e^{-t/\tau})$$

$$160 \mu\text{A} = 200 \mu\text{A} \left(1 - e^{-\frac{64.4 \mu\text{s}}{\tau}}\right)$$

$$0.8 = 1 - e^{-\frac{64.4 \mu\text{s}}{\tau}}$$

$$0.2 = e^{-\frac{64.4 \mu\text{s}}{\tau}}$$

$$\log_e 0.2 = -1.61 = \frac{-64.4 \mu\text{s}}{\tau}$$


$$\tau = \frac{64.4 \mu\text{s}}{1.61} = 40 \mu\text{s}$$

c.  $\tau = \frac{L}{R} = 40 \mu\text{s} = \frac{L}{500 \text{k}\Omega}, L = (500 \text{k}\Omega)(40 \mu\text{s}) = 20 \text{ mH}$

d.  $I_a = \frac{E}{R} \Rightarrow E = (200 \mu\text{A})(500 \Omega) = 100 \text{ mV}$

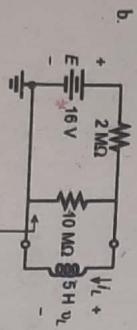33. a.  $L \Rightarrow$  open circuit equivalent

$$V_L = \frac{10 \text{ M}\Omega(16 \text{ V})}{10 \text{ M}\Omega + 2 \text{ M}\Omega} = 13.33 \text{ V}$$



$$R_{Th} = 2 \text{ M}\Omega \parallel 10 \text{ M}\Omega = 1.67 \text{ M}\Omega$$

$$E_{Th} = \frac{10 \text{ M}\Omega(16 \text{ V})}{10 \text{ M}\Omega + 2 \text{ M}\Omega} = 13.33 \text{ V}$$

$$I_{L\text{final}} = \frac{E_{Th}}{R_{Th}} = \frac{13.33 \text{ V}}{1.67 \text{ M}\Omega} = 7.98 \mu\text{A}$$

c.  $i_t = 7.98 \mu\text{A}(1 - e^{-t/3 \mu\text{s}})$

$$10 \mu\text{A} = 7.98 \mu\text{A}(1 - e^{-t/3 \mu\text{s}})$$

$$1.253 = 1 - e^{-t/3 \mu\text{s}}$$

$$0.253 = e^{-t/3 \mu\text{s}}$$

$$\log_e(0.253) = -t/3 \mu\text{s}$$

$$1.374 = t/3 \mu\text{s}$$

$$t = 1.374(3 \mu\text{s}) = 4.12 \mu\text{s}$$

d.  $v_L = 13.33 \text{ V } e^{-t/3 \mu\text{s}} = 13.33 \text{ V } e^{-12 \text{ ms}/\mu\text{s}} = 13.33 \text{ V } e^{-4}$   
 $= 13.33 \text{ V}(0.0183) = 0.244 \text{ V}$

34.  $e_L = L \frac{\Delta I}{\Delta t}; \quad 0 - 4 \text{ ms}, e_L = (200 \text{ mH}) \left[ \frac{15 \text{ mA}}{4 \text{ ms}} \right] = 750 \text{ mV}$

$$4 - 10 \text{ ms}, e_L = (200 \text{ mH}) \left[ \frac{0 \text{ mA}}{6 \text{ ms}} \right] = 0 \text{ V}$$


$$10 - 14 \text{ ms}, e_L = (200 \text{ mH}) \left[ \frac{15 \text{ mA}}{4 \text{ ms}} \right] = 750 \text{ mV}$$

$$14 - 18 \text{ ms}, e_L = -(200 \text{ mH}) \left[ \frac{15 \text{ mA}}{4 \text{ ms}} \right] = -750 \text{ mV}$$

$$18 - 19 \text{ ms}, e_L = 0 \text{ V}$$

$$19 - 22 \text{ ms}, e_L = -(200 \text{ mH}) \left[ \frac{15 \text{ mA}}{3 \text{ ms}} \right] = -1 \text{ V}$$
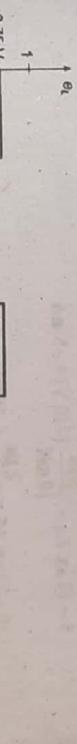
$$22 \text{ ms} \rightarrow, e_L = 0 \text{ V}$$



35.  $v_L = L \frac{\Delta I}{\Delta t}$

$$0 \rightarrow 2 \text{ ms}: v_L = 0 \text{ V}$$

$$2 \rightarrow 6 \text{ ms}: v_L = -(5 \text{ mA}) \left( \frac{30 \text{ mA}}{4 \text{ ms}} \right) = -37.5 \text{ mV}$$


$$6 \rightarrow 10 \text{ ms}: v_L = 0 \text{ V}$$

$$10 \rightarrow 14 \text{ ms}: v_L = (5 \text{ mA}) \left( \frac{20 \text{ mA}}{4 \text{ ms}} \right) = 25 \text{ mV}$$

$$14 \rightarrow 17 \text{ ms}: v_L = 0 \text{ V}$$

$$17 \rightarrow 19 \text{ ms}: v_L = -(5 \text{ mA}) \left( \frac{5 \text{ mA}}{2 \text{ ms}} \right) = -12.5 \text{ mV}$$

$$19 \rightarrow, v_L = 0 \text{ V}$$

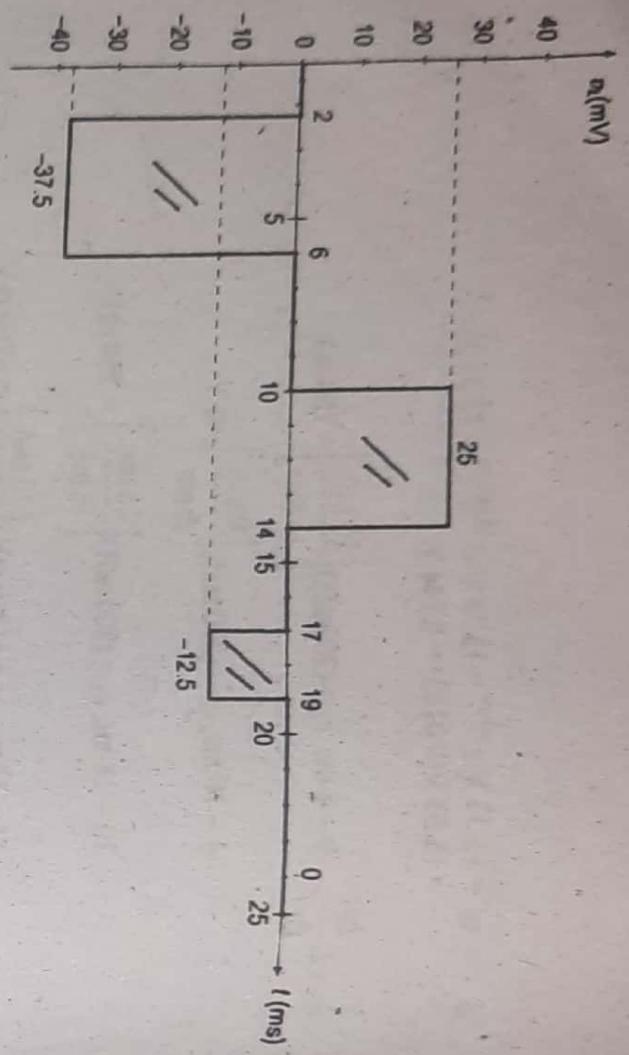

36.  $L = 10 \text{ mH}$ ,  $4 \text{ mA}$  at  $t = 0 \text{ s}$

$$v_L = L \frac{\Delta i}{\Delta t} \Rightarrow \Delta i = \frac{\Delta v}{L} v_L$$


$0 - 5 \mu\text{s}$ :  $v_L = 0 \text{ V}$ ,  $\Delta i_L = 0 \text{ mA}$  and  $i_L = 4 \text{ mA}$

$$5 - 10 \mu\text{s}: \Delta i_L = \frac{5 \mu\text{s}}{10 \text{ mH}} (-10 \text{ V}) = -5 \text{ mA}$$

$$10 - 12 \mu\text{s}: \Delta i_L = \frac{2 \mu\text{s}}{10 \text{ mH}} (-25 \text{ V}) = -5 \text{ mA}$$

$12 - 16 \mu\text{s}$ :  $v_L = 0 \text{ V}$ ,  $\Delta i_L = 0 \text{ mA}$  and  $i_L = -6 \text{ mA}$
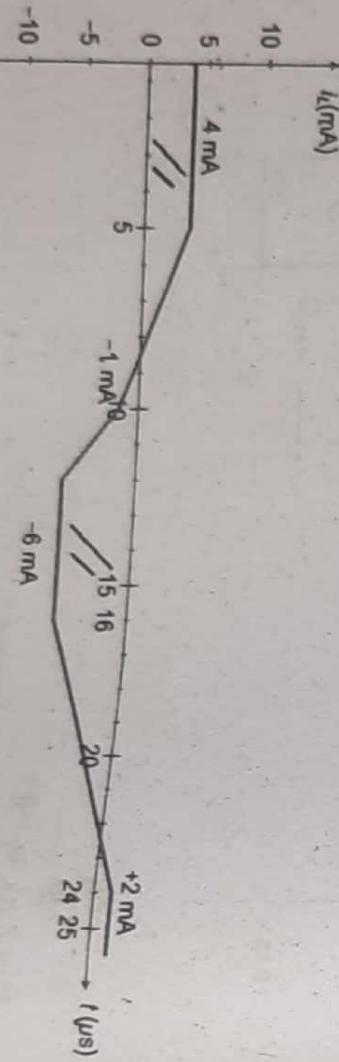
$$16 - 24 \mu\text{s}: \Delta i_L = \frac{8 \mu\text{s}}{10 \text{ mH}} 10 \text{ V} = 8 \text{ mA}$$



37. a.  $L_4 + L_5 = 5.6 \text{ mH} + 2 \text{ mH} = 7.6 \text{ mH}$

$$L_3 \parallel 7.6 \text{ mH} = 3 \text{ mH} \parallel 7.6 \text{ mH} = 2.15 \text{ mH}$$

$$L_2 + 2.18 \text{ mH} = 3.3 \text{ mH} + 2.15 \text{ mH} = 5.45 \text{ mH}$$

$$L_1 \parallel 5.45 \text{ mH} = 2.4 \text{ mH} \parallel 5.45 \text{ mH} = 1.67 \text{ mH}$$

$$L_T = L_6 + 1.67 \text{ mH} = 9.1 \text{ mH} + 1.67 \text{ mH} = 10.77 \text{ mH}$$

38.  $L_2 \parallel L_4 = 10 \text{ mH} \parallel 30 \text{ mH} = 7.5 \text{ mH}$

$$L_3 + L_2 \parallel L_4 = 47 \text{ mH} + 7.5 \text{ mH} = 54.5 \text{ mH}$$

$$54.5 \text{ mH} \parallel 22 \text{ mH} = 15.67 \text{ mH}$$

$$L_T = L_1 + 15.67 \text{ mH} = 18 \text{ mH} + 15.67 \text{ mH} = 33.67 \text{ mH}$$

43.

- a. Source conversion:  $E = 16 \text{ V}$ ,  $R_i = 2 \text{ k}\Omega$   
 $R_{Th} = 2 \text{ k}\Omega + 2 \text{ k}\Omega \parallel 8.2 \text{ k}\Omega = 2 \text{ k}\Omega + 1.61 \text{ k}\Omega = 3.61 \text{ k}\Omega$   
 $E_{Th} = \frac{8.2 \text{ k}\Omega(16 \text{ V})}{8.2 \text{ k}\Omega + 2 \text{ k}\Omega} = 12.86 \text{ V}$

$$I_m = \frac{E_{Th}}{R_m} = \frac{12.86 \text{ V}}{3.61 \text{ k}\Omega} = 3.56 \text{ mA}, \quad \tau = \frac{L}{R} = \frac{30 \text{ mH}}{3.61 \text{ k}\Omega} = 8.31 \mu\text{s}$$

$$i_L = 3.56 \text{ mA}(1 - e^{-0.31 \mu\text{s}})$$

$$v_L + v_{L_1} = 12.86 \text{ V initially } (t = 0+)$$

$$v_L = \frac{10 \text{ mH}}{10 \text{ mH} + 20 \text{ mH}} \text{ of total} = \frac{1}{3}(12.86 \text{ V}) = 4.29 \text{ V}$$

$$v_L = 4.29 \text{ V} e^{-0.31 \mu\text{s}}$$



$$3.56 \text{ mA}$$

$$5\tau = 41.55 \mu\text{s}$$

$$4.29 \text{ V}$$

$$5\tau = 41.55 \mu\text{s}$$

c.

$$v_L = \frac{3.197 \text{ H}}{3 \text{ H} + 3.197 \text{ H}} = 0.52 v_{L_1}$$

$$v_{L_1} = (0.52)(13.33 e^{-0.93 \mu\text{s}}) = 6.93 \text{ V} e^{-0.93 \mu\text{s}}$$

$$45. \quad I_{k_1} = \frac{E}{R_1} = \frac{20 \text{ V}}{4 \Omega} = 5 \text{ A}$$

$$I_2 = 0 \text{ A}$$

$$I_1 + I_{k_1} + I_2 = 5 \text{ A} + 0 \text{ A} = 5 \text{ A}$$


$$46. \quad I_1 = I_2 = 0 \text{ A}$$

$$V_1 = V_2 = E = 60 \text{ V}$$

$$47. \quad I_1 = \frac{12 \text{ V}}{4 \Omega} = 3 \text{ A}, \quad I_2 = 0 \text{ A}$$

$$V_1 = 12 \text{ V}, \quad V_2 = 0 \text{ V}$$

48.

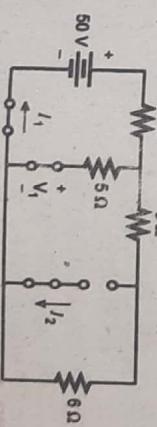

$$V_1 = \frac{6 \Omega(50 \text{ V})}{6 \Omega + 20 \Omega + 3 \Omega} = 10.34 \text{ V}$$

$$V_1 = \frac{(3 \Omega + 6 \Omega)(50 \text{ V})}{29 \Omega} = 15.52 \text{ V}$$

$$I_1 = \frac{50 \text{ V}}{20 \Omega + 3 \Omega + 6 \Omega} = 1.72 \text{ A}$$

$$I_2 = 0 \text{ A}$$

$$L_T = 3 \text{ H} + 4.7 \text{ H} \parallel 10 \text{ H} = 3 \text{ H} + 3.197 \text{ H} = 6.197 \text{ H}$$

$$\tau = \frac{L_T}{R} = \frac{6.197 \text{ H}}{6.67 \text{ k}\Omega} = 0.93 \text{ ms}$$

$$V_L = 13.33 \text{ V} e^{-0.93 \mu\text{s}}$$

$$I_L = \frac{13.33 \text{ V}}{6.67 \text{ k}\Omega} (1 - e^{-0.93 \mu\text{s}}) = 2 \text{ mA}(1 - e^{-0.93 \mu\text{s}})$$

# Chapter 12

1.  $\Phi$ : CGS:  $5 \times 10^4$  Maxwells, English:  $5 \times 10^4$  lines  
 $B$ : CGS: 8 Gauss, English:  $51.62 \text{ lines/in.}^2$

2.  $\Phi$ :  $SI 6 \times 10^{-4}$  Wb, English 60,000 lines  
 $B$ : SI  $0.465$  T, CGS  $4.65 \times 10^3$  Gauss, English 30,000 lines/in.<sup>2</sup>

3. a.  $B = \frac{\Phi}{A} = \frac{4 \times 10^{-4} \text{ Wb}}{0.01 \text{ m}^2} = 0.04 \text{ T}$

4. a.  $\mathcal{O} = \frac{I}{\mu A} = \frac{0.06 \text{ m}}{\mu 2 \times 10^{-4} \text{ m}^2} = \frac{300}{\mu \text{m}}$

b.  $\mathcal{O} = \frac{I}{\mu A} = \frac{0.0762 \text{ m}}{\mu 5 \times 10^{-4} \text{ m}^2} = \frac{152.4}{\mu \text{m}}$

c.  $\mathcal{O} = \frac{I}{\mu A} = \frac{0.1 \text{ m}}{\mu 1 \times 10^{-4} \text{ m}^2} = \frac{1000}{\mu \text{m}}$

from the above  $\mathcal{O}_{(c)} > \mathcal{O}_{(a)} > \mathcal{O}_{(b)}$

5.  $\mathcal{O} = \frac{\mathcal{F}}{\Phi} = \frac{400 \text{ At}}{4.2 \times 10^{-4} \text{ Wb}} = 952.4 \times 10^3 \text{ At/Wb}$

6.  $\mathcal{O} = \frac{\mathcal{F}}{\Phi} = \frac{120 \text{ gilberts}}{72,000 \text{ max wells}} = 1.67 \times 10^{-3} \text{ rebs (CGS)}$

7.  $6 \text{ j} \cdot \text{d} = \left[ \frac{1 \text{ m}}{39.37 \text{ j} \cdot \text{d}} \right] = 0.1524 \text{ m}$

$H = \frac{\mathcal{F}}{l} = \frac{400 \text{ At}}{0.1524 \text{ m}} = 2624.67 \text{ At/m}$

8.  $\mu = \frac{2B}{H} = \frac{2(1200 \times 10^{-4} \text{ T})}{600 \text{ At/m}} = 4 \times 10^{-4} \text{ Wb/Am}$

9.  $B = \frac{\Phi}{A} = \frac{10 \times 10^{-4} \text{ Wb}}{3 \times 10^{-3} \text{ m}^2} = 0.33 \text{ T}$

Fig. 12.7:  $H \equiv 800 \text{ At/m}$   
 $N = HI \Rightarrow I = HI/N = (800 \text{ At/m})(0.2 \text{ m})/75 \text{ t} = 2.13 \text{ A}$

$$13. N_1 + N_2 = \frac{H_1}{\text{cast steel}} + \frac{H_2}{\text{cast iron}}$$

$$(20 \text{ t}) + (30 \text{ t}) = \\ (50 \text{ t}) =$$

$$B = \frac{\Phi}{A} \text{ with } 0.25 \text{ m}^2 \left[ \frac{1 \text{ m}}{39.37 \text{ m}} \right] \left[ \frac{1 \text{ m}}{39.37 \text{ m}} \right] = 1.6 \times 10^{-4} \text{ m}^2$$

$$B = \frac{0.8 \times 10^{-4} \text{ Wb}}{1.6 \times 10^{-4} \text{ m}^2} = 0.5 \text{ T}$$

Fig. 12.8:  $H_{\text{cast iron}} \equiv 280 \text{ A/m}$

Fig. 12.7:  $H_{\text{cast steel}} \equiv 1500 \text{ A/m}$

$$l_{\text{cast steel}} = 5.5 \text{ m} \left[ \frac{1 \text{ m}}{39.37 \text{ m}} \right] = 0.14 \text{ m}$$

$$l_{\text{cast iron}} = 2.5 \text{ m} \left[ \frac{1 \text{ m}}{39.37 \text{ m}} \right] = 0.064 \text{ m}$$

$$(50 \text{ t})I = (280 \text{ A/m})(0.14 \text{ m}) + (1500 \text{ A/m})(0.064 \text{ m})$$

$$50I = 39.20 + 96.00 = 135.20$$

$$I = 2.70 \text{ A}$$

$$l_{ab} = l_{cd} = 0.05 \text{ m}, l_{ef} = 0.02 \text{ m}, l_{bc} = l_{de} = 0.0085 \text{ m}$$

$$NI = 2H_{ab}l_{ab} + 2H_{cd}l_{cd} + H_{bc}l_{bc} + H_{de}l_{de}$$

$$B = \frac{\Phi}{A} = \frac{2.4 \times 10^{-4} \text{ Wb}}{2 \times 10^{-4} \text{ m}^2} = 1.2 \text{ T} \Rightarrow H \equiv 360 \text{ A/m} \text{ (Fig. 12.8)}$$

$$100I = 2(360 \text{ A/m})(0.05 \text{ m}) + 2(360 \text{ A/m})(0.0085 \text{ m})$$

$$= 36 \text{ At} + 6.12 \text{ At} + 7.2 \text{ At} + 2869 \text{ At}$$

$$100I = 2918.32 \text{ At}$$

$$I \equiv 29.18 \text{ A}$$

$$\text{b. air gap: metal} = 2869 \text{ At}; 49.72 \text{ At} = 58.17:1$$

$$\mu_{\text{steel steel}} = \frac{B}{H} = \frac{1.2 \text{ T}}{360 \text{ A/m}} = 3.33 \times 10^{-3} \text{ Wb/A.m}$$

$$\mu_{\text{air}} = 4\pi \times 10^{-7} \text{ Wb/A.m} \\ \mu_{\text{steel steel}} : \mu_{\text{air}} = 3.33 \times 10^{-3} \text{ Wb/A.m} : 4\pi \times 10^{-7} \equiv 2627:1$$

$$15. 4 \text{ cm} \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] = 0.04 \text{ m}$$

$$f = \frac{1}{2} NI \frac{d\phi}{dx} = \frac{1}{2} (80 \text{ t})(0.9 \text{ A}) \frac{(8 \times 10^{-4} \text{ Wb} - 0.5 \times 10^{-4} \text{ Wb})}{\frac{1}{2} (0.04 \text{ m})} = \frac{367.5 \times 10^{-4}}{0.02}$$

$$= 1.35 \text{ N}$$

$$16. C = 2\pi r = (6.28)(0.3 \text{ m}) = 1.88 \text{ m}$$

$$B = \frac{\Phi}{A} = \frac{2 \times 10^{-4} \text{ Wb}}{1.3 \times 10^{-4} \text{ m}^2} = 1.54 \text{ T}$$

$$\text{Fig. 12.7: } H_{\text{steel steel}} \equiv 2100 \text{ A/m}$$

$$H_g = 7.97 \times 10^5 B_g = (7.97 \times 10^5)(1.54 \text{ T}) = 1.23 \times 10^6 \text{ A/m}$$

$$N_1 I_1 + N_2 I_2 = H_g I_g + H_{\text{steel steel}} I_{\text{steel steel}} \\ (200 \text{ t})I_1 + (40 \text{ t})(0.3 \text{ A}) = (1.23 \times 10^6 \text{ A/m})(2 \text{ mm}) + (2100 \text{ A/m})(1.88 \text{ m})$$

$$I_1 = 31.98 \text{ A}$$

$$17. \text{ a. } 0.2 \text{ cm} \left[ \frac{1 \text{ m}}{100 \text{ cm}} \right] = 2 \times 10^{-3} \text{ m}$$

$$A = \frac{\pi d^2}{4} = \frac{(3.14)(0.01 \text{ m})^2}{4} = 0.79 \times 10^{-4} \text{ m}^2$$

$$NI = H_g I_g$$

$$H_g = 7.96 \times 10^5 B_g$$

$$(200 \text{ t})I = \left[ (7.96 \times 10^5) \left( \frac{0.2 \times 10^{-4} \text{ Wb}}{0.79 \times 10^{-4} \text{ m}^2} \right) \right] 2 \times 10^{-3} \text{ m}$$

$$I = 2.02 \text{ A}$$

$$\text{b. } B_g = \frac{\Phi}{A} = \frac{2 \times 10^{-4} \text{ Wb}}{0.79 \times 10^{-4} \text{ m}^2} = 0.25 \text{ T}$$

$$F \equiv \frac{1}{2} \frac{B_g^2 A}{\mu_0} = \frac{1}{2} \frac{(0.25 \text{ T})^2 (0.79 \times 10^{-4} \text{ m}^2)}{4\pi \times 10^{-7}} \\ \equiv 2 \text{ N}$$

18. Table:

Section	$\Phi(\text{Wb})$	$A(\text{m}^2)$	$B(\text{T})$	$H$	$I(\text{m})$	$HI$
a-b, g-h	$5 \times 10^{-4}$				0.2	
b-c, f-g	$2 \times 10^{-4}$	$5 \times 10^{-4}$			0.1	
c-d, e-f	$2 \times 10^{-4}$	$5 \times 10^{-4}$			0.099	
a-h		$5 \times 10^{-4}$			0.2	
b-g		$2 \times 10^{-4}$			0.2	
d-e	$2 \times 10^{-4}$	$5 \times 10^{-4}$			0.002	

$$B_{lk} = B_{ad} = B_g = B_{g'} = B_{fg} = \frac{\Phi}{A} = \frac{2 \times 10^{-4} \text{ Wb}}{5 \times 10^{-4} \text{ m}^2} = 0.4 \text{ T}$$

Air gap:  $H_g = 7.97 \times 10^5 (0.4 \text{ T}) = 3.19 \times 10^5 \text{ A/m}$

$$H_{fg} = (3.19 \times 10^5 \text{ A/m})(2 \text{ mm}) = 638 \text{ At}$$

Fig 12.8:  $H_{lk} = H_{ad} = H_{g'} = H_{fg} = 55 \text{ A/m}$

$$H_{ad} = H_{g'} = (55 \text{ A/m})(0.1 \text{ m}) = 5.5 \text{ At}$$

$$H_{ad} = H_{g'} = (55 \text{ A/m})(0.099 \text{ m}) = 5.45 \text{ At}$$

For loop 2:  $\Sigma \mathcal{G} = 0$

$$H_{lk} + H_{ad} + H_{g'} + H_{g'/g} + H_{g'/g} - H_{g/g'} = 0$$

$$5.5 \text{ At} + 5.45 \text{ At} + 638 \text{ At} + 5.45 \text{ At} + 5.50 \text{ At} - H_{g/g'} = 0$$

$$H_{g/g'} = 639.90 \text{ At}$$

$$\text{and } H_{g'} = \frac{639.90 \text{ At}}{0.2 \text{ m}} = 3300 \text{ A/m}$$

Fig 12.7:  $B_{g'} \equiv 1.55 \text{ T}$

with  $\Phi_2 = B_{g'} A = (1.55 \text{ T})(2 \times 10^{-4} \text{ m}^2) = 3.1 \times 10^{-4} \text{ Wb}$

$$\Phi_T = \Phi_1 + \Phi_2$$

$$= 2 \times 10^{-4} \text{ Wb} + 3.1 \times 10^{-4} \text{ Wb}$$

$$= 5.1 \times 10^{-4} \text{ Wb} = \Phi_{ab} = \Phi_{ha} = \Phi_{gh}$$

$$B_{ab} = B_{ha} = B_{gh} = \frac{\Phi_T}{A} = \frac{5.1 \times 10^{-4} \text{ Wb}}{5 \times 10^{-4} \text{ m}^2} = 1.02 \text{ T}$$

B-H curve: (Fig 12.8):

$$H_{ab} = H_{ha} = H_{gh} \equiv 180 \text{ A/m}$$

$$H_{ab}/_{ab} = (180 \text{ A/m})(0.2 \text{ m}) = 36 \text{ At}$$

$$H_{ha}/_{ha} = (180 \text{ A/m})(0.2 \text{ m}) = 36 \text{ At}$$

$$H_{gh}/_{gh} = (180 \text{ A/m})(0.2 \text{ m}) = 36 \text{ At}$$

which completes the table!

Loop #1:  $\Sigma \mathcal{G} = 0$

$$NI = H_{ab}l_{ab} + H_{g/g'}l_{g'} + H_{ad}l_{ad}$$

$$(200 \text{ t})l = 36 \text{ At} + 639.49 \text{ At} + 36 \text{ At} + 36 \text{ At}$$

$$(200 \text{ t})l = 767.49 \text{ At}$$

$$l \equiv 3.84 \text{ A}$$

$$19. \quad NI = HI \\ l = 2\pi r = (6.28)(0.08 \text{ m}) = 0.50 \text{ m}$$

$$(100 \text{ t})(2 \text{ A}) = H(0.50 \text{ m})$$

$$H = 400 \text{ A/m}$$

Fig 12.8:  $B \equiv 0.68 \text{ T}$

$$\Phi = BA = (0.68 \text{ T})(0.009 \text{ m}^2)$$

$$\Phi = 6.12 \text{ mWb}$$

20.

$$NI = H_{ab}(l_{ab} + l_{ha} + l_{gh} + l_{fg}) + H_{fg} \\ 300 \text{ At} = H_{ab}(0.8 \text{ m}) + 7.97 \times 10^5 B_g(0.8 \text{ mm}) \\ 300 \text{ At} = H_{ab}(0.8 \text{ m}) + 637.6 B_g$$

Assuming  $637.6 B_g \gg H_{ab}(0.8 \text{ m})$   
then  $300 \text{ At} = 637.6 B_g$   
and  $B_g = 0.47 \text{ T}$

$$\Phi = BA = (0.47 \text{ T})(2 \times 10^{-4} \text{ m}^2) = 0.94 \times 10^{-4} \text{ Wb}$$

$$B_{ab} = B_g = 0.47 \text{ T} \Rightarrow H \equiv 270 \text{ A/m} (\text{Fig. 12.8})$$

$$300 \text{ At} = (270 \text{ A/m})(0.8 \text{ m}) + 637.6(0.47 \text{ T})$$

$$300 \text{ At} \neq 515.67 \text{ At}$$

∴ Poor approximation!

$$\frac{300 \text{ At}}{515.67 \text{ At}} \times 100\% = 58\%$$

Reduce  $\Phi$  to 58%

$$\frac{0.58(0.94 \times 10^{-4} \text{ Wb})}{0.58(0.94 \times 10^{-4} \text{ Wb})} = 0.55 \times 10^{-4} \text{ Wb}$$

$$B = \frac{\Phi}{A} = \frac{0.55 \times 10^{-4} \text{ Wb}}{2 \times 10^{-4} \text{ m}^2} = 0.28 \text{ T} \Rightarrow H \equiv 190 \text{ A/m} (\text{Fig. 12.8})$$

$$300 \text{ At} = (190 \text{ A/m})(0.8 \text{ m}) + 637.6(0.28 \text{ T})$$

$$300 \text{ At} \neq 330.53 \text{ At}$$

$$\text{Reduce } \Phi \text{ another } 10\% = 0.55 \times 10^{-4} \text{ Wb} - 0.1(0.55 \times 10^{-4} \text{ Wb}) \\ = 0.495 \times 10^{-4} \text{ Wb}$$

$$B = \frac{\Phi}{A} = \frac{0.495 \times 10^{-4} \text{ Wb}}{2 \times 10^{-4} \text{ m}^2} = 0.25 \text{ T} \Rightarrow H \equiv 175 \text{ A/m} (\text{Fig. 12.7})$$

$$300 \text{ At} = (175 \text{ A/m})(0.8 \text{ m}) + 637.6(0.28 \text{ T})$$

$$300 \text{ At} \neq 318.53 \text{ At} \text{ but within } 5\% \therefore \text{OK}$$

$$\Phi \equiv 0.55 \times 10^{-4} \text{ Wb}$$

$$21. \quad a. \quad l_r = 0.632 T_{\max}$$

$$T_{\max} \equiv 1.5 \text{ T for cast steel}$$

$$0.632(1.5 \text{ T}) = 0.945 \text{ T}$$

$$At 0.945 \text{ T}, H \equiv 700 \text{ A/m} (\text{Fig. 12.7})$$

$$\therefore B = 1.5 \text{ T} (1 - e^{-H/700 \text{ A/m}})$$

$$b. \quad H = 900 \text{ A/m:}$$

$$B = 1.5 \text{ T} \left( 1 - e^{-\frac{900 \text{ A/m}}{700 \text{ A/m}}} \right) = 1.09 \text{ T}$$

$$\text{Graph: } \equiv 1.1 \text{ T}$$

$$H = 1800 \text{ A/m:}$$

$$B = 1.5 \text{ T} \left( 1 - e^{-\frac{1800 \text{ A/m}}{700 \text{ A/m}}} \right) = 1.39 \text{ T}$$

$$\text{Graph: } \equiv 1.38 \text{ T}$$

$$H = 2700 \text{ A/m:}$$

$$B = 1.5 \left( 1 - e^{-\frac{2700 \text{ A/m}}{700 \text{ A/m}}} \right) = 1.47 \text{ T}$$

$$\text{Graph: } \equiv 1.47 \text{ T}$$

Excellent comparison!

c.  $B = 1.5 \text{ T} (1 - e^{-H/700 \text{ At/m}}) = 1.5 \text{ T} - 1.5 \text{ T} e^{-H/700 \text{ At/m}}$

$$B - 1.5 \text{ T} = -1.5 \text{ T} e^{-H/700 \text{ At/m}}$$

$$1.5 - B = 1.5 \text{ T} e^{-H/700 \text{ At/m}}$$

$$\frac{1.5 \text{ T} - B}{1.5 \text{ T}} = e^{-H/700 \text{ At/m}}$$

$$\log\left(1 - \frac{B}{1.5 \text{ T}}\right) = \frac{-H}{700 \text{ At/m}}$$

$$\text{and } H = -700 \log_e\left(1 - \frac{B}{1.5 \text{ T}}\right)$$

d.  $B = 1 \text{ T}$ :

$$H = -700 \log_e\left(1 - \frac{1 \text{ T}}{1.5 \text{ T}}\right) = 769.03 \text{ At/m}$$

Graph:  $\cong 750 \text{ At/m}$

$B = 1.4 \text{ T}$ :

$$H = -700 \log_e\left(1 - \frac{1.4 \text{ T}}{1.5 \text{ T}}\right) = 1895.64 \text{ At/m}$$

Graph:  $\cong 1920 \text{ At/m}$

e.  $H = -700 \log_e\left(1 - \frac{B}{1.5 \text{ T}}\right)$

$$= -700 \log_e\left(1 - \frac{0.2 \text{ T}}{1.5 \text{ T}}\right)$$

$$= 100.2 \text{ At/m}$$

$$I = \frac{HI}{N} = \frac{(100.2 \text{ At/m})(0.16 \text{ m})}{400 \text{ t}} = 40.1 \text{ mA}$$

vs 44 mA for Ex. 12.1