

Chapter-2

Voltage and Current

Atom and their structure:

A atom has three parts. Electron, Proton and neutron. Electron carries negative charge, proton carries positive charge and neutron is neutral.

$$\frac{e}{f} = R$$

$$fR = p \neq$$

Voltage:

Voltage is the total work required to move a unit of charge between two points in a static electric field.

hole \rightarrow is the absence of electron

The negative charge associated with a single electron is called $1.6 \times 10^{-19} C$

Q \rightarrow W J

$$1 \rightarrow \frac{W}{Q} J$$

$$V = \frac{W}{Q}$$

$$W = VQ$$

Current:

current

Normally,

Current is the flow of negative charge

Applied mechanism is voltage

result is Current,

motor coil rotates around axis and makes θ in t sec, there is flow $q \propto C$

in 1 sec, in n seconds $\frac{q}{t} \propto C$ motor is rotating

$$I = \frac{q}{t}$$

$$\Rightarrow q = It$$

: spot V

1 volt: When ~~1 joule of work is done in 1 sec~~

~~carrying 1 coulomb of charge, from infinity~~

to a point \bullet in the electric field, then the potential at the point is called 1 volt.

1 ampere: If ~~1 coulomb of charge flows~~

~~through a conductor in one second, the current~~

~~flowing through the conductor is known as~~

1 ampere (1 A)

$$[W = V]$$

$$\frac{W}{V} = I$$

$$\frac{W}{I} = V$$

* The feature which has capability to flow electrons is called voltage.

voltage source is better.

There are two kinds of Bettercy.

① Primary (Non-rechargeable)

② Secondary (rechargeable)

Conductors: Conductors are the materials or substances which allow electricity to flow through them.

Semiconductors: Semiconductors are the materials which have a conductivity between conductors and nonconductors or insulators!

Insulators: Insulators are the materials that hinder the free flow of electrons from one particle of the element to another.

Ammeters: An Ammeter is a device used to measure either alternating or direct current.

Voltmeter: A voltmeter is an instrument that measures the voltage or potential difference between two points of an electronic or electrical circuit.

Mathematical Term: The volt is the unit of potential difference.

2.1 Find the voltage between two points, if 60 J of energy are required to move a charge of 20 C between the two points.

Solution: $W = VQ$

$$V = \frac{W}{Q}$$
$$= \frac{60}{20}$$
$$= 3 \text{ V}$$

2.2 Determine the energy expended moving a charge of $50 \mu C$ between two points if the voltage between the points is 6V

$$\text{Solution: } W = VQ$$

$$W = 6 (50 \times 10^{-6})$$

$$= 300 \times 10^{-6} \text{ J}$$

$$= 3 \times 10^{-4} \text{ J}$$

2.3 The charge flowing through the imaginary surface 0.16 C every 64 ms . Determine the current in Amphere.

$$I = \frac{q}{t}$$

$$= \frac{0.16}{64 \times 10^{-3}}$$

$$= 2.50 \text{ A}$$

2.4. Determine the long it will take 2×10^{16} electrons to pass through the imaginary surface if the current is 5 mA

$$I = \frac{q}{t}$$

$$t = \frac{q}{I} = \underline{\underline{}}$$

• Dosis 6.02×10^{23} e⁻ \rightarrow 1C \rightarrow 1000 rad

später mit 1 e⁻ einheiten \rightarrow $\frac{1}{6.02 \times 10^{23}}$ zu 20 rad

$$4 \times 10^{-16} \text{ e}^- \rightarrow \frac{1 \times 4 \times 10^{16}}{6.02 \times 10^{23}} \text{ PV = 17.25 milliA?}$$
$$= 6.41 \text{ mC}$$
$$(0.01 \times 0.1) \text{ A}^2$$

$$t = \frac{Q}{I} =$$

$$= \frac{6.41 \times 10^{-3}}{5 \times 10^{-3}}$$

$= 1.28 \text{ s}$

Wiederholung: periodisch wiederholte
Vorgänge mit abwechselnden
Zeitintervallen. Ein Vorgang ist
gekennzeichnet durch die
Periodendauer.

$$\frac{P}{f} = I$$

$$\frac{A \cdot C}{T \cdot A \cdot P} =$$

$$A \cdot C =$$

Abstand einer Teilprobe von
einer anderen Teilprobe auf einem Band
gleich dem Abstand zweier Teilproben

Ausdruck für den Abstand zweier Teilproben

$$\frac{P}{f} = I$$

$$A \cdot C = \frac{P}{f} = I$$

sub of workshop chapter-3 position off

to A separate note of Wrokshop

Resistor \rightarrow घासा

Resistance \rightarrow घासी

Resistivity \rightarrow घासी

Resistor: A resistor is an electrical component that limits or regulates the flow of electrical current in an electronic circuit.

Resistance: Resistance is the opposition that a substance offers to the flow of electric current. It is measured in ohms.

Resistivity: Resistivity is a property that describes the extent to which a material opposes the flow of electric current through it.

■ The resistance of any material is due primarily to four factors:

1. Material

2. Length

3. Cross-sectional area

4. Temperature of the material.

for example length of a resistor A : stated

$$R \propto \frac{l}{A}$$

which shows that resistance is proportional to length and inversely proportional to area.

■ Types of resistor

→ Fixed

→ Variable

so that resistance of a conductor is proportional to length and inversely proportional to area.

■ Conductance: Conductance is defined as the ability of a substance to conduct electricity.

Conductance is the inverse of resistance.

$$G = \frac{1}{R}$$

Unit → Simens (S) or mho (m)

Chapter - 4

Ohm's Law, Power & Work

and Energy

Ohm's law: The voltage or potential difference between two points is directly proportional to the current or electricity passing through the resistance and directly proportional to the resistance of the circuit.

The formula for ohm's law $V = IR$

Easy to know:

Current (Effect) or cause of voltage.

Push ~~to~~ voltage

Want to move ~~to~~ move ~~to~~ move prob to start result \rightarrow current

Want to move ~~to~~ move ~~to~~ move prob to utilida
 $I \propto V$

$$I = \frac{1}{R} V$$

$$V = IR$$

$$I = \frac{V}{R}$$

For resistor ~~to~~ voltage 225 , then V


For supplying current (battery) ~~to~~ voltage 225 , then E

$$E = 225 = f k w$$

■ Plotting Ohm's law:

If we plot voltage on the x-axis of a graph

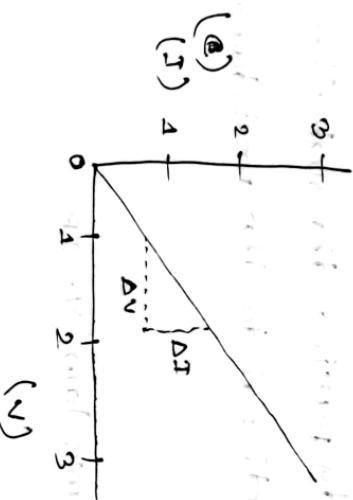and current on the y-axis of the graph, we will get a straight line.



(v)

Power (ক্ষমতা)

ক্ষমতা কর্মের হার

Rate of doing work \rightarrow Power \rightarrow watt/HP

Ability of doing works \rightarrow Energy \rightarrow J

in t sec, work is done $W \rightarrow$

$$W = F \cdot S = \frac{F \cdot S}{t} \cdot t = \frac{P \cdot t}{t} = P$$

∴ Rate of doing work \rightarrow Power \rightarrow Watt/HP

$$\text{Power} = \text{Work} / \text{Time}$$

1 Watt = 1 Joule per second
1 Joule = 1 Newton meter
1 Newton = 1 kg m/s²

$$P = \frac{W}{t} \quad \text{Power formula}$$

current formula $P = \frac{V\theta}{t}$ with resistance θ (imp)

current $\theta \Rightarrow P = V^2 / R$ we can calculate power

$$P = V \frac{V}{R}$$

$$P = \frac{V^2}{R}$$

$$P = IR \times I$$

$$P = I^2 R$$

Ansatz:

Efficiency: The ratio between useful energy (out)

to non-useful power output divided by the total electrical power consumed is called

efficiency

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%$$

Ansatz:

total power consumed from resistors \rightarrow P_{in}

total power consumed from resistors \rightarrow P_{out}

$$\frac{V}{R} = I$$

Ansatz:

- 4.1) Determine the current resulting from the application of a 9V battery across a network with a resistance of 2.2Ω .

$$I = \frac{V}{R}$$

$$= \frac{9}{2.2}$$

$$= 4.09A$$

(Ans)

- 4.2) Calculate the resistance of a 60W bulb if a current of 500mA results from a applied voltage of 120V.

$$R = \frac{V}{I}$$

$$= \frac{120}{500 \times 10^{-3}}$$

$$= 240\Omega$$

- 4.3) Calculate the current through the $2\mu\Omega$ resistor, if the voltage drop across it is 16V

$$I = \frac{V}{R}$$

$$= \frac{16V}{2 \times 10^3 \Omega}$$

$$= 8mA$$

4.6) Find the power delivered to the demotor

Voltage 120V, Current 5A

$$P = VI$$

$$= 120 \times 5$$

$$= 600 \text{ W}$$

$$P = 0.6 \text{ kW}$$

4.2) What is the power dissipated by a 5Ω

resistor if the current is 4A?

$$P = I^2 R$$

$$= 4^2 \times 5$$

$$= 80 \text{ W}$$

4.16) What is the output in horsepower of a motor with an efficiency of 80% and an input current of 8A at 120 V?

$$\left[\frac{P_o}{P_i} = \frac{\eta}{100} \right] \times 100$$

$$\Rightarrow 0.8 = \frac{P_o}{120 \times 8} \times 100$$

$$\Rightarrow P_o = 868 \text{ W}$$

Output horsepower of a DC motor


Introduction to Electronics and Circuits

Series DC circuit analysis



IV = Q

Q = C V

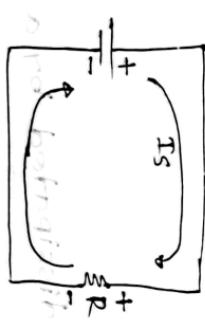

$I_S = \text{Supplied current}$

$I_S = I_R$

Q = C V = C I_S t
Q = I_S t


A circuit: In electronics, a circuit is a complete circular path that electricity flows through.

A simple circuit consists of a current source,


conductors and a load. In addition there is a switch.

Current flows from the positive terminal of the current source through the conductors, the load, the switch, and back to the negative terminal.

Series resistors:

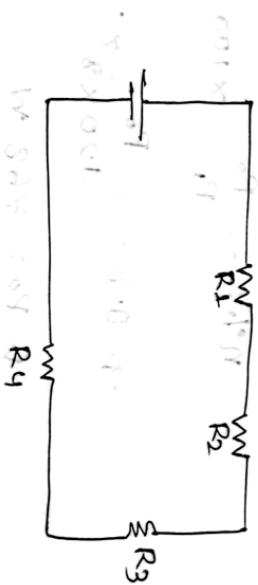


There is one pathway to flow current.

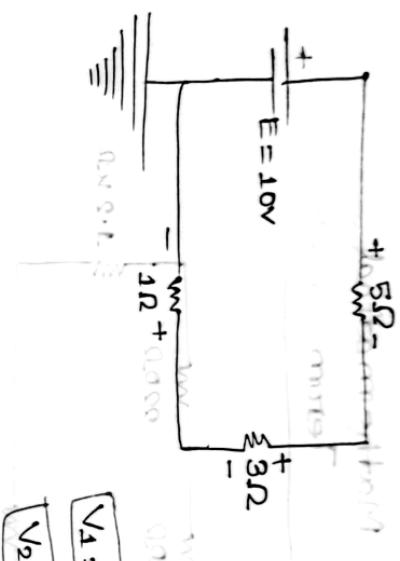

Power distribution in series circuit:

Ques. No. 7
Ques. No. 8
Ques. No. 9

$$V_2 = I_2 R_2$$

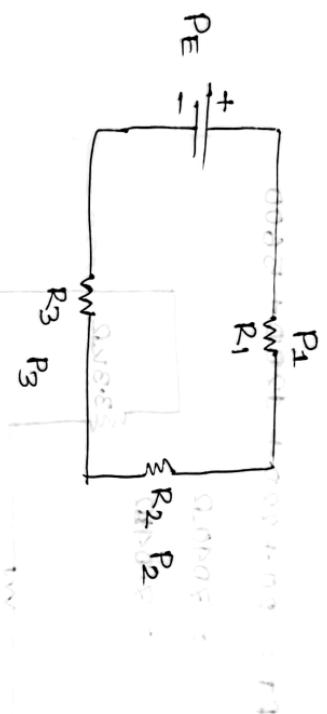

$$P_E = P_1 + P_2 + P_3$$


$$P = V I = \frac{V^2}{R}$$

$$10 \times 8.8 \times 10^{-3} = 79$$

$$\Delta V \text{ Ques. No. } 1$$

Mathematical Term

5.1)

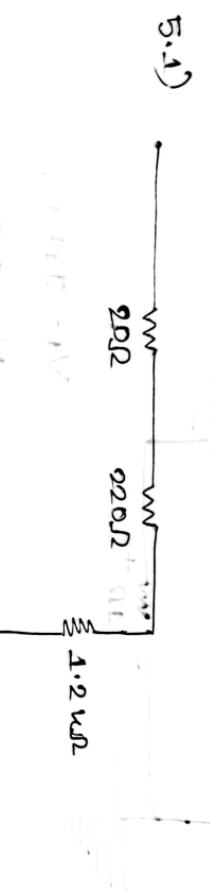


Total resistance?

$$R_T = 20 + 220 + 1200 + 5600$$

$$= 7040\Omega$$

$$= 7.04\text{k}\Omega$$

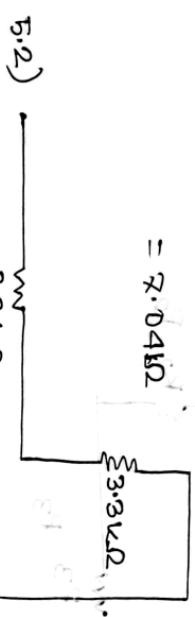


$$\frac{1}{R_T} = \frac{1}{3.3\text{ k}\Omega} + \frac{1}{3.3\text{ k}\Omega} = \frac{2}{3.3\text{ k}\Omega} = \frac{2}{3.3 \times 10^3} = \frac{2}{3.3} \times 10^{-3}$$

$$R_T = 4 \times 3.3\text{ k}\Omega$$

$$= 13.2\text{ k}\Omega$$

Q.3)

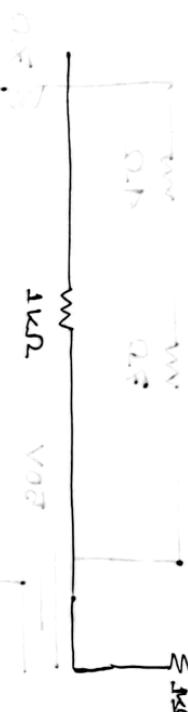


$$R_T = 4.7 + 1 + 2.2 + 1 + 1 \text{ k}\Omega$$

$$= 9.0 \text{ k}\Omega$$

Q.4)

Given $R_{T1} = 10\Omega$

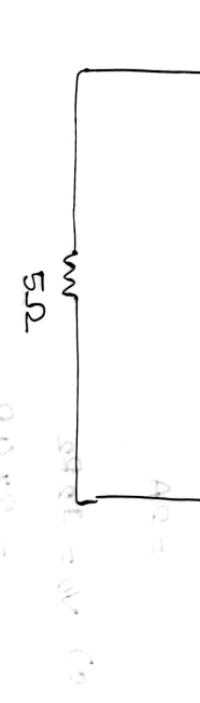

a) Total Resistance $R_T = 2 + 1 + 5 \Omega = 8\Omega$

$$b) I_S = \frac{E}{R_{T1} + R_1}$$

$$= \frac{20}{8} \text{ A}$$


$$= 2.5 \text{ A}$$

c) $V_1 = I_S R_1 = 2.5 \times 2 = 5 \text{ V}$

$$V_2 = I_S \times 1 = 2.5 \times 1 = 2.5 \text{ V}$$

$$V_3 = I_S \times 5 = 2.5 \times 5 = 12.5 \text{ V}$$

5.5)

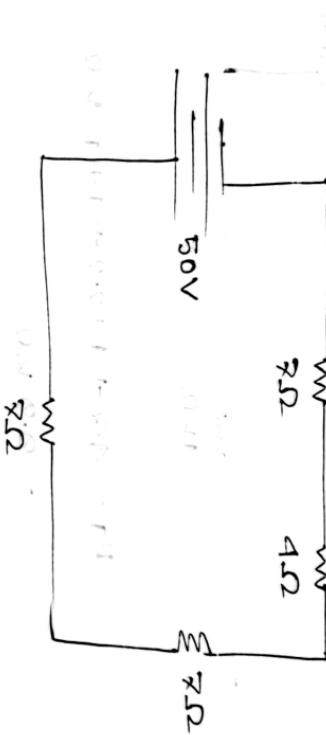

$$\text{a) } R_T = 2 + 4 + 2 + 2$$

$$= 12 \Omega$$

$$\text{b) } I_S = \frac{E}{R_T}$$

$$= \frac{50}{12}$$


$$= 2A$$

$$\text{c) } V_2 = I_2 R_2$$

$$= 2 \times 4 \Omega$$

$\rightarrow R_S = 8 \Omega$ ist die äußere Last für Verstärker

5.6)

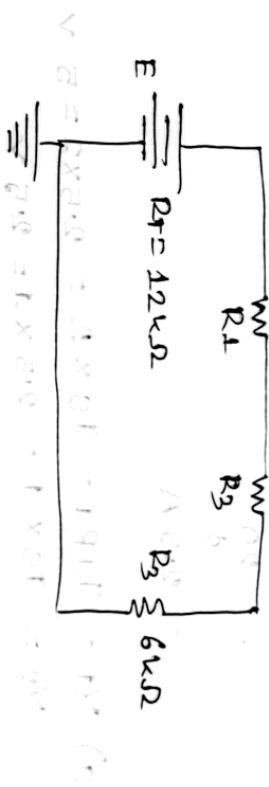

*

$$R_T = R_1 + R_2 + R_3$$

$$\Rightarrow 12000 = R_A + 4 + 6$$

$$\Rightarrow R_A = 2 \text{ k}\Omega$$

Current through resistor R_A is same as current through R_1 & R_2

*

$$E = I_S R_T$$


$$= 6 \times 10^{-3} \times 12000$$

$$= 6 \times 10^{-3} \times 12 \times 10^3$$

$$= 72 \text{ V}$$

K.H *Derive superposition theorem for DC circuit analysis*

Voltage sources in series:

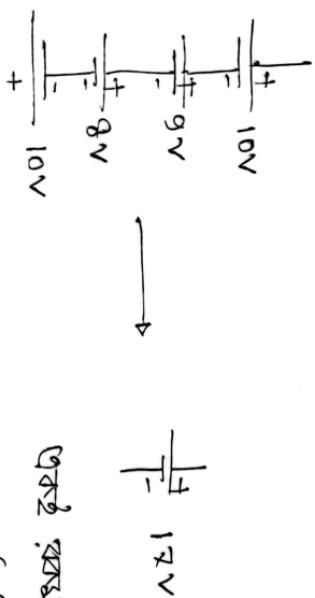

কেবল ধৰ্ম

সোনারগাঁও মাদ্দা,
তালড় মাদ্দা

Kirchhoff's voltage law; ~~current law~~

The voltage around a loop equals the sum of every voltage drop in the same loop for any closed network, and equals zero.

$$V_{loop} = 0$$

Kirchhoff's current law: ~~current law~~

The algebraic sum of all currents entering and exiting a node must equal zero.

$$\sum I_{entering} - \sum I_{exiting} = 0$$

$$V_{loop} = \sum V_{drop}$$

$$V_{loop} = 0$$

$$V_{loop} = \sum V_{drop}$$

$$V_{loop} = 0$$

Voltage source in series:

$$E_0 = E_1 + E_2 + E_3$$

$E_1 = 15V$

$E_2 = 9V$

$E_3 = 2.7V$


$E_0 = \frac{1}{1} 37V$

Series drop across
resistor, owing to
current flow.

$$\frac{1}{1} 15V$$

$$\frac{1}{1} 9V$$


$$\frac{1}{1} 2.7V$$

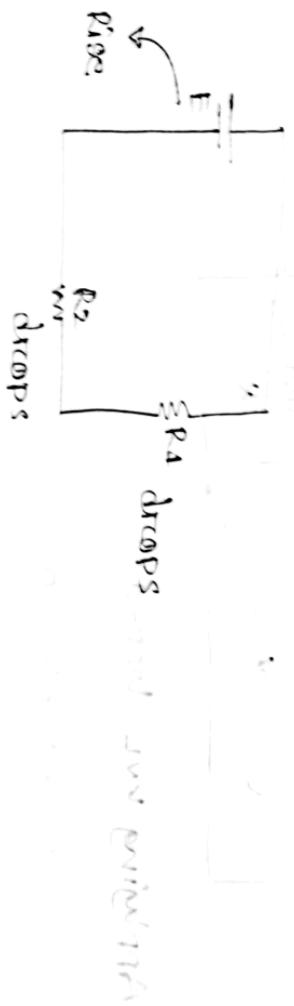

Δ drops


Σ rise : Σ drops

Applying KVL across loop 1

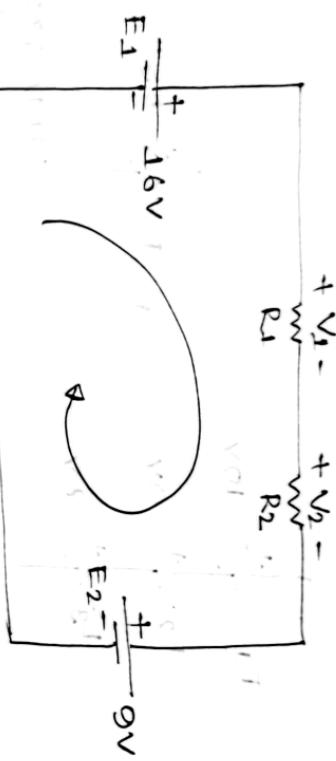

$$+E_1 - R_1 - R_2 - E_2 = 0$$

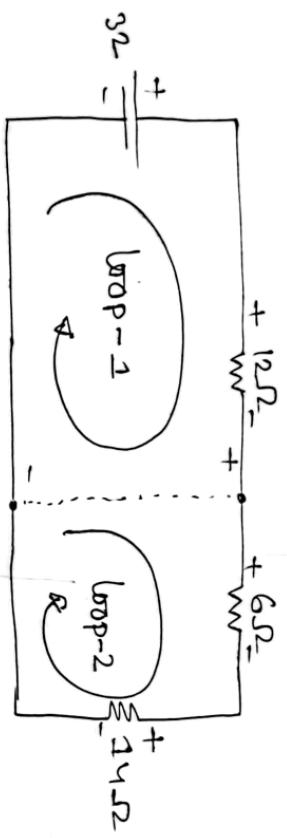- to $\oplus \rightarrow +$
+ to $\ominus \rightarrow -$



Applying KVL loop-1:

$$+3R - 12 - VR = 0$$



$$\Rightarrow VR = 20V$$

Chapter 5

5.5

b)

$$R_{\text{parallel}} = r \Omega$$

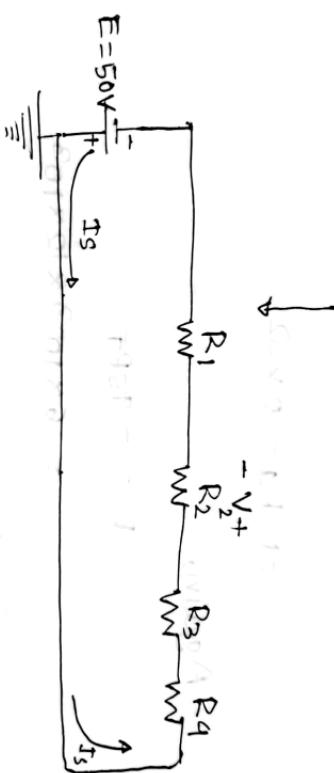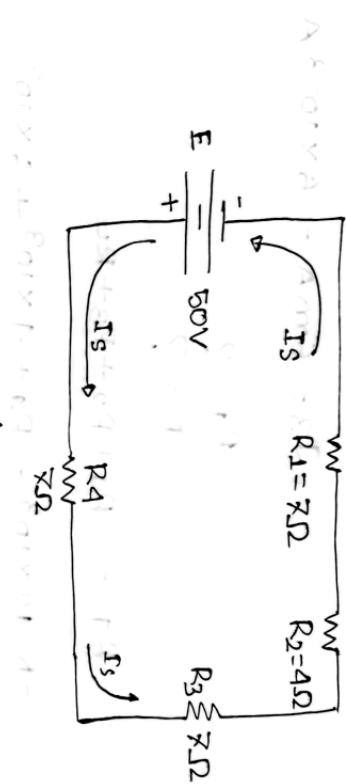

The current now has a anticlockwise direction as shown in Figure 5.5.

$$I_S = \frac{E}{R_T} = \frac{50}{2.5} = 2A$$

c)

$$\begin{aligned} V_2 &= I R_2 && \because \text{The total current of } I_S \\ R_2 &= \frac{V_2}{I_S} \\ &= (2A)(4\Omega) \\ &= 8V \end{aligned}$$

\therefore The voltage across R_2 is 8V

5.6

Given that,

$$R_T = 12 \text{ k}\Omega \quad = 12000 \Omega$$

$$I_3 = 6 \text{ mA} = 6 \times 10^{-3} \text{ A}$$

$$R_1 = ?$$

$$E = ?$$

$$R_T = R_1 + R_2 + R_3 + R_{eq}$$

$$\Rightarrow 12 \times 10^3 = R_1 + 4 \times 10^3 + 6 \times 10^3$$

$$\Rightarrow R_1 = 2 \text{ k}\Omega$$

Again,

$$E = -I_3 R_T$$

$$= 6 \times 10^{-3} \times 12 \times 10^3$$

$$= 48 \text{ V}$$

$$\therefore R_1 = 2 \text{ k}\Omega$$

$$E = 48 \text{ V}$$

5.7

a) Given that,

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 3 \text{ k}\Omega$$

$$R_3 = 2 \text{ k}\Omega$$

$$R_T = ?$$

$$R_T = R_1 + R_2 + R_3$$

$$= 1 \text{ k}\Omega + 3 \text{ k}\Omega + 2 \text{ k}\Omega$$

$$= 5 \text{ k}\Omega$$

b) From a, we got $R_T = 5 \text{ k}\Omega$

$$I_S = \frac{E}{R_T}$$

$$= \frac{36}{5 \times 10^3}$$

$$= 6 \text{ mA}$$

c) From a, we got $R_T = 5 \text{ k}\Omega$

From b, we got $I_S = 6 \text{ mA}$

$$V_1 = I R_1$$

$$= 6 \times 10^{-3} \times 1 \times 10^3 \text{ V}$$

$$= 6 \text{ V}$$

$$V_2 =$$


$$d) \quad P = \varrho E I_s$$

$$= 36 \times 6 \times 10^{-3} \text{ W}$$

$$= 216 \text{ mW}$$

$$e) \quad P_1 = \varrho I^2 R$$

5.9

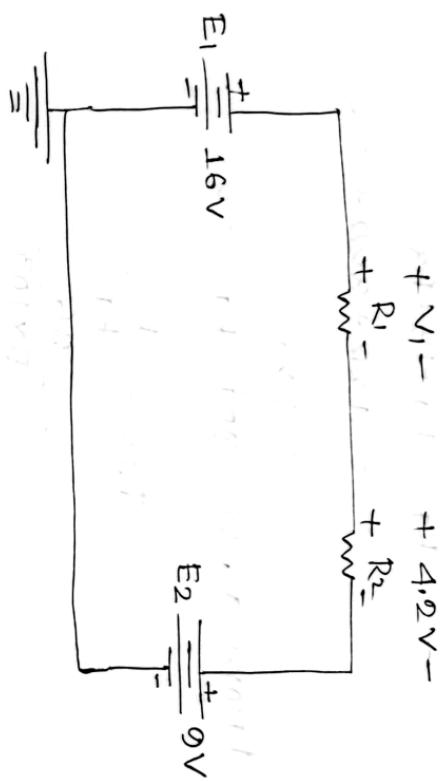


Applying KVL,

$$16V - V_1 + 4.2 + 9 = 0$$

$$\Rightarrow V_1 = 24.8 \text{ V}$$

5.9

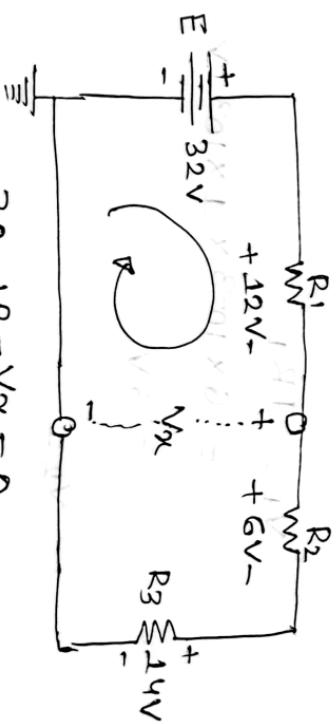

$$32 - 12 - V_x = 0$$

$$\Rightarrow V_x = 20 \text{ V}$$

Home Work

7.3

Given that,

$$R_A = R_1 = 4\Omega$$

$$R_2 = 4\Omega$$

$$R_3 = 4\Omega$$

$$\therefore R_B = R_2 \parallel R_3$$

$$= \frac{4 \times 4}{8}$$
$$= 2\Omega$$

$$R_A = 0.5\Omega$$

$$R_5 = 1.5\Omega$$

$$\therefore R_C = 0.5 + 1.5$$
$$= 2\Omega$$

$$R_T = \underline{\underline{R_A \parallel R_B \parallel R_C}}$$
$$= \underline{\underline{2\Omega}}$$

Given that $R_A = R_1 = 4\Omega$

$$R_T = 4\Omega + R_B \parallel R_C$$
$$= 4\Omega + \frac{2 \times 2}{4}$$
$$= 5\Omega$$

$$\therefore I_S = \frac{10}{5}$$
$$= 2A$$

$$\therefore I_A = I_S = 2A$$

$$\text{and } I_B = I_C = \frac{I_A}{2} = \frac{2A}{2} = 1A$$

Now,

$$\begin{aligned}\text{Voltage } V_A &= I_A R_A \\ &= 2 \times 4 \\ &= 8V\end{aligned}$$

$$\begin{aligned}V_B &= I_B R_B \\ &= 1 \times 2 \\ &= 2V\end{aligned}$$

$$V_C = V_B = 2V$$

Q4:

Given that,

$$\begin{aligned}R_1 &= 9\Omega \\ R_2 &= 6\Omega\end{aligned}$$

$$\therefore R_A = R_1 || R_2$$

$$= \frac{9 \times 6}{15} = \frac{54}{15} = 3.6\Omega$$

$$R_3 = 4\Omega$$

$$R_4 = 6\Omega$$

$$R_5 = 3\Omega$$

$$\begin{aligned}\therefore R_B &= 4 + \frac{6 \times 3}{9} \\ &= 6\Omega\end{aligned}$$

$$R_C = 3\Omega$$

$$\therefore R_T = 2\Omega + 6\Omega + 3\Omega$$

$$= 11\Omega$$

$$\therefore R_t = 3.6\Omega + \frac{6 \times 3}{9}$$

$$= 5.6\Omega$$

$$\therefore I_S = \frac{16.8}{5.6} = 3A$$

$$\therefore I_A = I_S = 3A$$

$$I_B = \frac{16.8}{R_S} = \frac{R_C I_A}{R_C + R_B}$$

$$= \frac{(3\Omega)(3A)}{6\Omega + 3\Omega} = \frac{9A}{9} = 1A$$

~~Given~~
By KCL,
~~Currents~~

$$I_C = I_A - I_B \\ = 3A - 1A \\ = 2A$$

By ohm's law,


$$V_A = I_A R_A = (3A)(3.6\Omega) = 10.8V$$

$$V_B = I_B R_B = V_C = I_C R_C = (1A)(3\Omega) \\ = 6V$$


Required
Voltage across resistor A is 10.8V

From the diagram

R.A

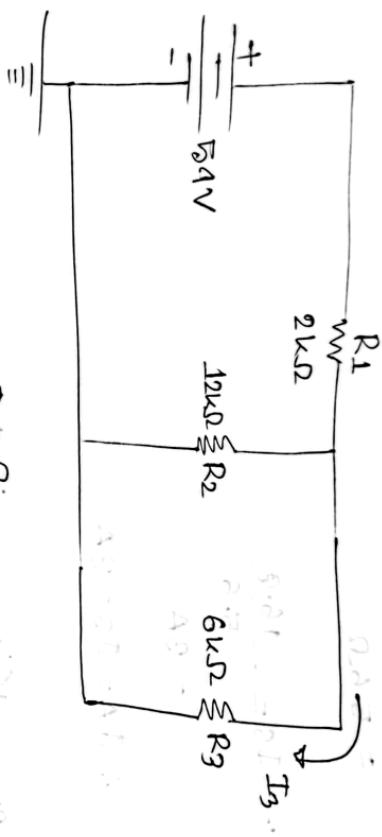

$$I_3 = ?$$

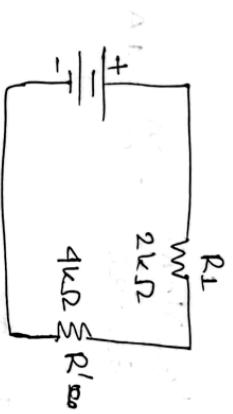

$$R'' = \frac{R_1 R'}{R_1 + R'} = \frac{2 \times 4}{2 + 4} = \frac{8}{6} = 1.33 \text{ k}\Omega$$

$$R'' = R_1 + R' = 2 + 4 = 6 \text{ k}\Omega$$

V = 8.0

$$\text{Given } V = 8.0 \text{ and } I_S = \frac{5A}{6k\Omega}$$
$$= 0.833 \text{ mA}$$

Since R_1 and R' are in series, they have the same current I_S .

The result is $I_1 = I_S = 0.833 \text{ mA}$

$$I_3 = \frac{R_2}{R_2 + R_3} I_1$$


$$= \left(\frac{12 \text{ k}\Omega}{12 \text{ k}\Omega + 6 \text{ k}\Omega} \right) \times 9 \text{ mA}$$

$$= \frac{12}{18 \times 10^3} \times 9$$


$$= 6 \times 10^{-3}$$

$$= 6 \text{ mA}$$

Q.2

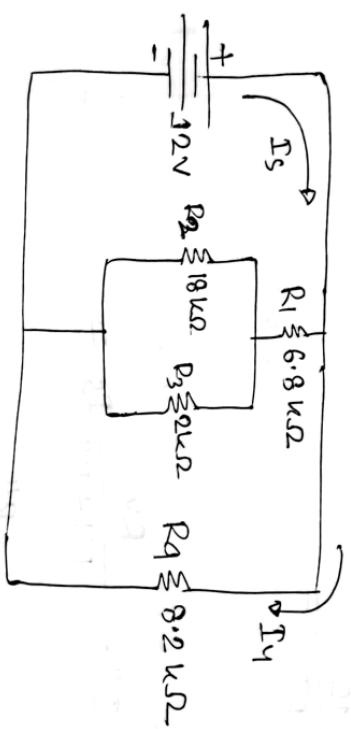

F. Q.5

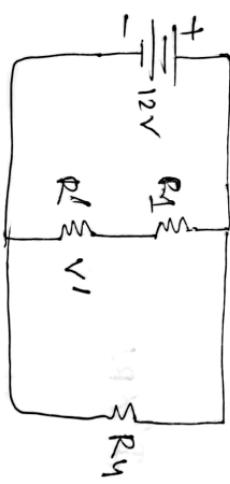

F. Q.4

$$R' = \frac{18 \times 2}{18 + 2}$$

$$= \frac{36}{20}$$

$$= 1.8 \text{ k}\Omega$$

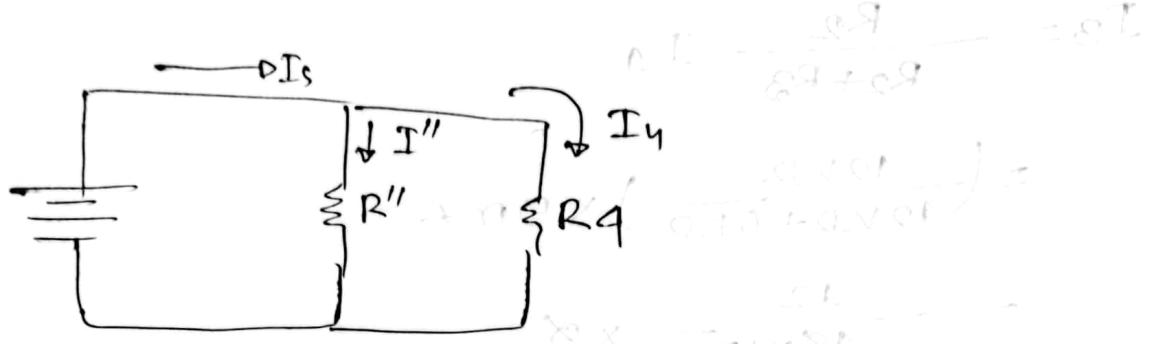


Fig 2

$$R'' = R_1 + R'$$

$$= \dots$$

$$R_T = \frac{R'' \times R_y}{R'' + R_y}$$

=

$$I_s = \frac{12}{R_T} =$$

From Fig-2

$$I'' = \frac{R_y}{R_y + R''} I_s =$$

$$I_y = \frac{R''}{R_y + R''} I_s =$$

From Fig-01,



$$\bullet V_2 = I'' \times R'$$

$$\frac{V_2}{R'} = I'' =$$

$$\frac{V_2}{R'} = I''$$


$\therefore I'' =$

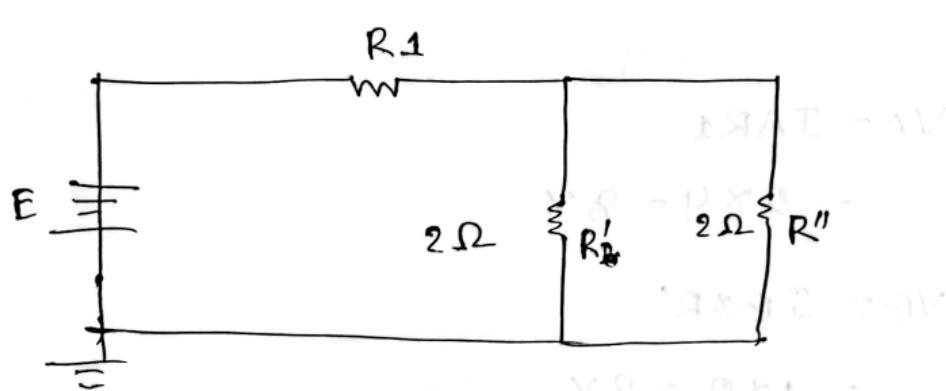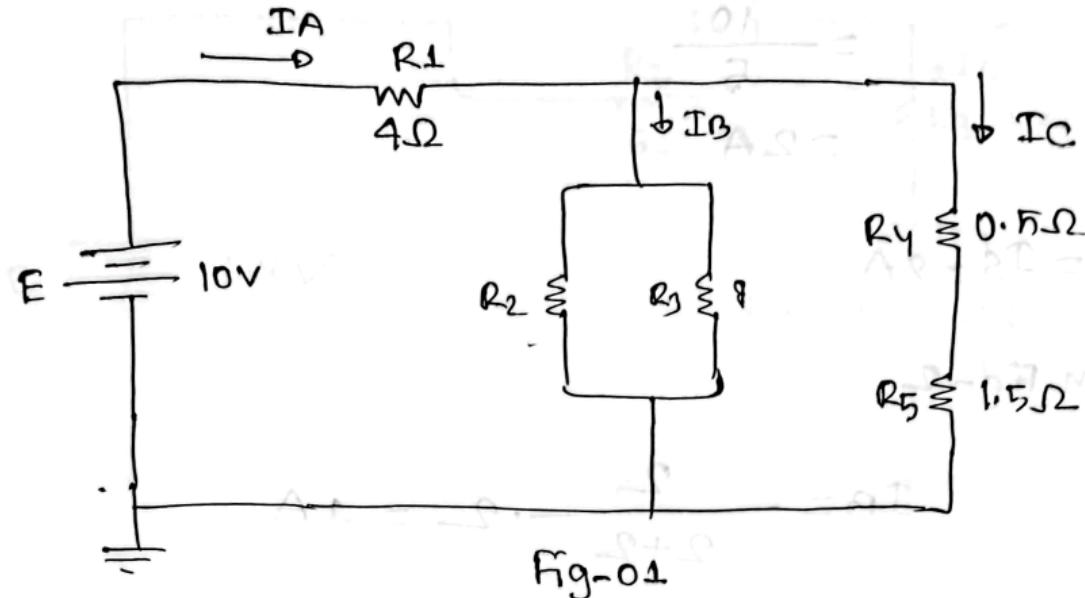7.3: Determine all the current and voltage.



$$R' = \frac{R_2 \times R_3}{R_2 + R_3}$$

$$= \frac{4 \times 4}{8} = 2\Omega$$

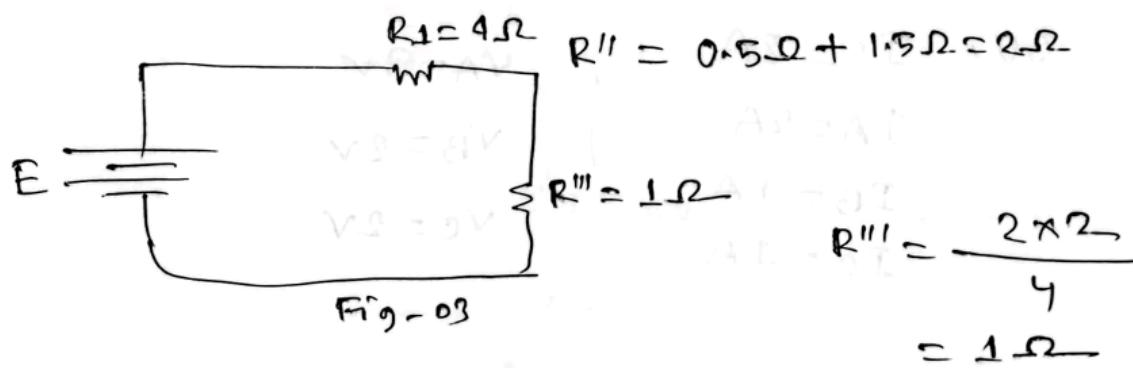

$$\therefore R_T = 5\Omega$$

$$\therefore I_T = \frac{E}{RT}$$

$$= \frac{10}{5} \\ = 2A$$

①

$$I_A = I_S = 2A$$

② From Fig-2,

$$I_B = \frac{2}{2+2} \cdot 2 = 1A$$

$$I_C = \frac{2}{2+2} \cdot 2 = 1A$$

Now,

$$V_A = I_A R_1$$

$$= 2 \times 4 = 8V$$

$$V_B = I_B \times R'$$

$$= 1 \times 2 = 2V$$

$$V_C = I_C \times R'''$$

$$= 1 \times 2 = 2V$$

$$\text{So, } I_S = 2A$$

$$I_A = 2A$$

$$I_B = 1A$$

$$I_C = 1A$$

$$V_A = 8V$$

$$V_B = 2V$$

$$V_C = 2V$$

7.4

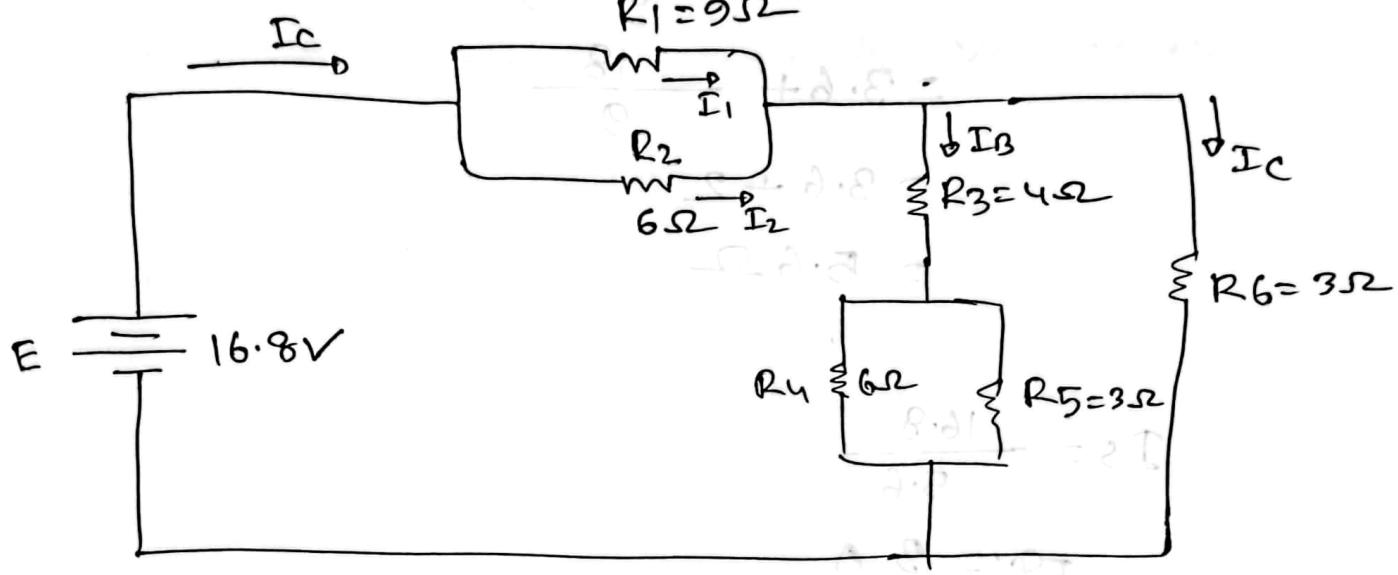


Fig-01

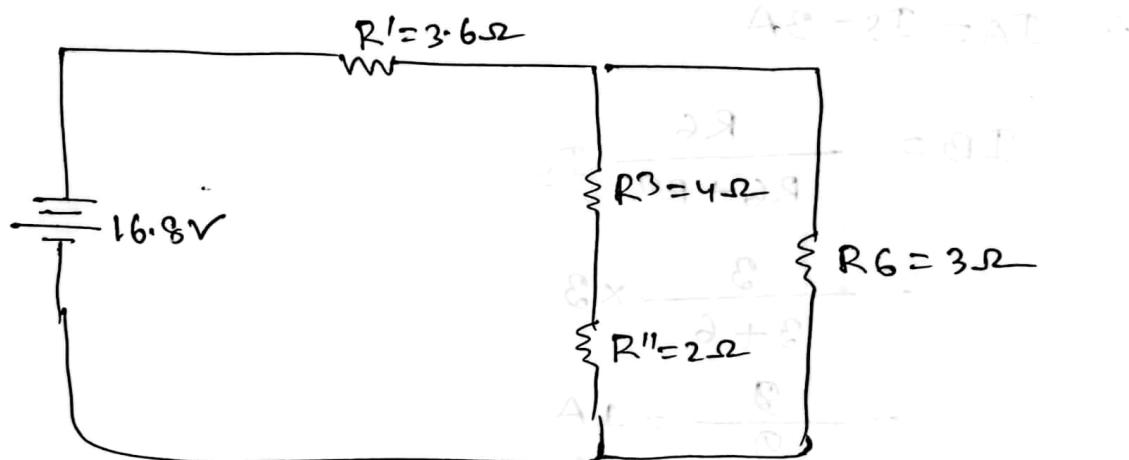


Fig-02

$$R'^{eq} = \frac{9 \times 6}{15} = \frac{54}{15} = 3.6\Omega$$

$$R''^{eq} = \frac{18}{9} = 2\Omega$$



$$\begin{aligned} R_T &= R' + (R''' \parallel R_6) \\ &= 4 + 2 \\ &= 6\Omega \end{aligned}$$

$$\therefore R_T = R' + (R''' \parallel R_6)$$

$$\begin{aligned}
 R_T &= 3 \cdot 6 + \left(\frac{3 \times 6}{9} \right) \\
 &= 3 \cdot 6 + \frac{18}{9} \\
 &= 3 \cdot 6 + 2 \\
 &= 5.6 \Omega
 \end{aligned}$$

$$I_S = \frac{16.8}{5.6}$$

$$\textcircled{I}_S = 3 \text{ A}$$

$$\therefore I_A = I_S = 3 \text{ A}$$

$$\begin{aligned}
 I_B &= \frac{R_6}{R_6 + R'''} I_S \\
 &= \frac{3}{3+6} \times 3 \\
 &= \frac{9}{15} = 1 \text{ A}
 \end{aligned}$$

~~I_C~~ - ~~0.0~~

$$I_C = I_S - I_B = 3 - 1 = 2 \text{ A}$$

$$\begin{aligned}
 \textcircled{I}_1 &= \frac{6}{9+6} I_S \\
 &= \frac{6}{15} \times 3 \\
 &= \frac{18}{15} = 1.2 \text{ A}
 \end{aligned}$$

$$I_2 = 3 - 1.2 = 1.8 \text{ A}$$

$$(2 \text{ A}) + 1.8 = I_S = 3$$

$$V_A = I_A R'$$

$$= 3 \times 3.6 = 10.8 \text{ V}$$

$$\frac{8 \times d}{d+8} = 10.8$$

$$V_1 = V_2 = V_A = 10.8 \text{ V}$$

$$V_B = I_B \times R''$$


$$= 1 \times 6 \text{ V}$$

$$V_C = I_C \times R_6$$

$$= 2 \times 3$$


$$= 6 \text{ V}$$

X5

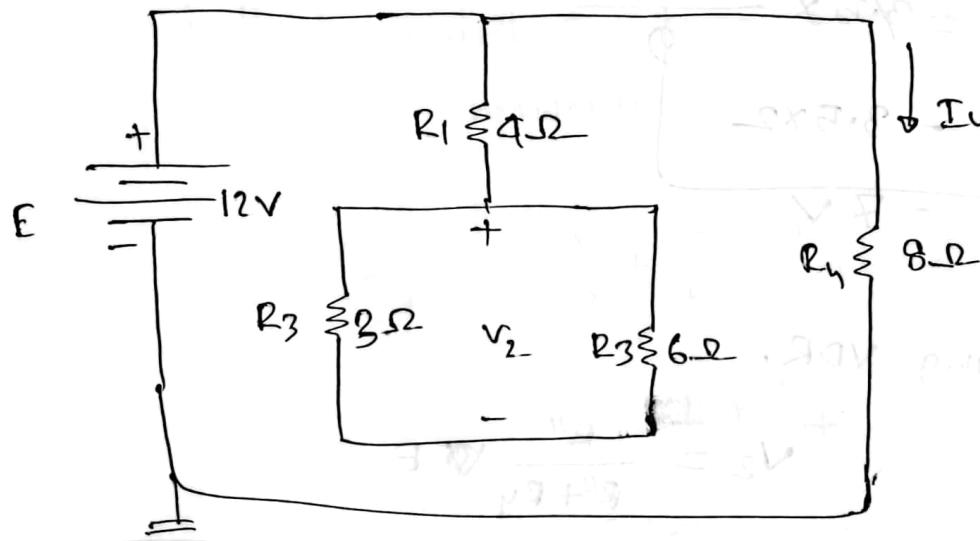

$$I_y = ?$$

$$V_2 = ?$$

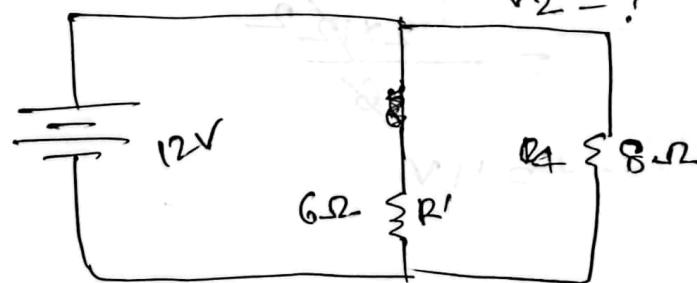

$$R' = R_y + \left(\frac{6 \times 3}{9} \right)$$

$$= 4 + \frac{18}{9}$$

$$= 6 \Omega$$

$$R_T = \frac{6 \times 8}{8+6} = \frac{48}{14} = 3.4$$

~~$I_S = \frac{12}{3.4} = 3.5$~~

$$I_y = \frac{6}{6+8} 3.5 \\ = 1.5 A$$

$$V_2 = I_S \times R''$$
 ~~$= 3.5 \times 3.4$~~
 ~~$= 11.9 V$~~
 $= 3.5 \times \frac{3 \times 6}{6}$
 ~~$= 3.5 \times 2$~~
 $= 7 V$

Applying VDR,


$$V_2 = \frac{R''}{R'' + R_y} \times E$$

$$= \frac{2}{2+4} \times 12$$

$$= \frac{2 \times 12}{6}$$

$$= 4 V$$

7.6

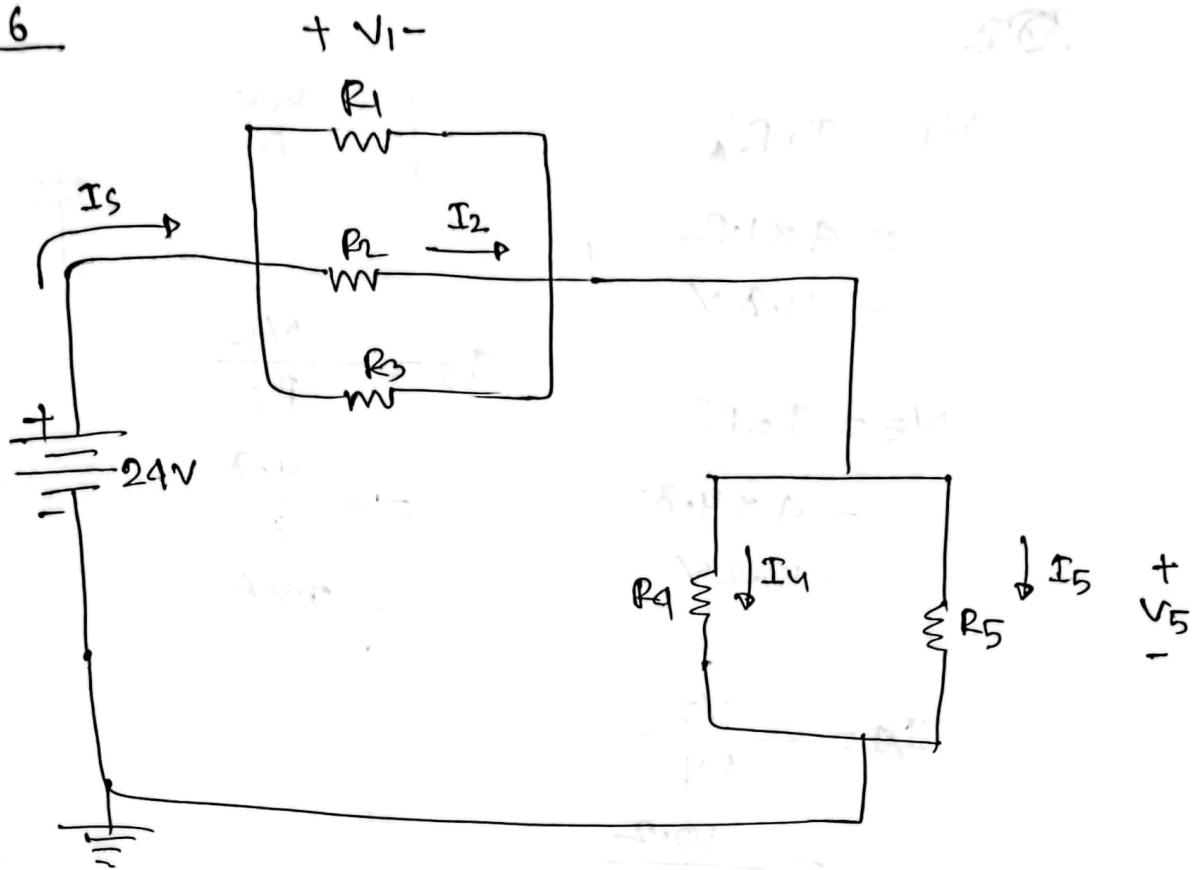

Find the indicated current and voltage for the networks.

$$RT = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} + \frac{R_4 \times R_5}{R_4 + R_5}$$

$$= \left(\frac{1}{6} + \frac{1}{6} + \frac{1}{2} \right)^{-1} + \frac{96}{20}$$

$$= \left(\frac{2+2+6}{12} \right)^{-1} + \frac{96}{20}$$

$$= \left(\frac{10}{12} \right)^{-1} + \frac{96}{20}$$

$$= \frac{12}{10} + \frac{96}{20}$$

$$= 6\Omega$$

$$I_5 = \frac{24}{6} = 4A$$

200

-1V +

-2V -

$$V_1 = I_1 R'_1$$

$$= 4 \times 1.2$$

$$= 4.8 \text{ V}$$

$$V_5 = I_5 R''_5$$

$$= 4 \times 4.8$$

$$= 19.2 \text{ V}$$

$$I_2 = \frac{V_2}{R_2}$$

$$= \frac{4.8}{6}$$

$$= 0.8 \text{ A}$$



$$I_4 = \frac{V_5}{R_4}$$

$$= \frac{19.2}{8}$$

$$= 2.4 \text{ A}$$

7.8

current विद्युत
प्राप्ति, मापदण्ड
ज्ञान

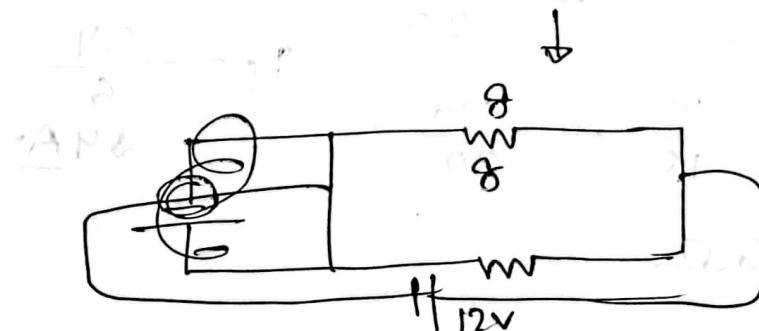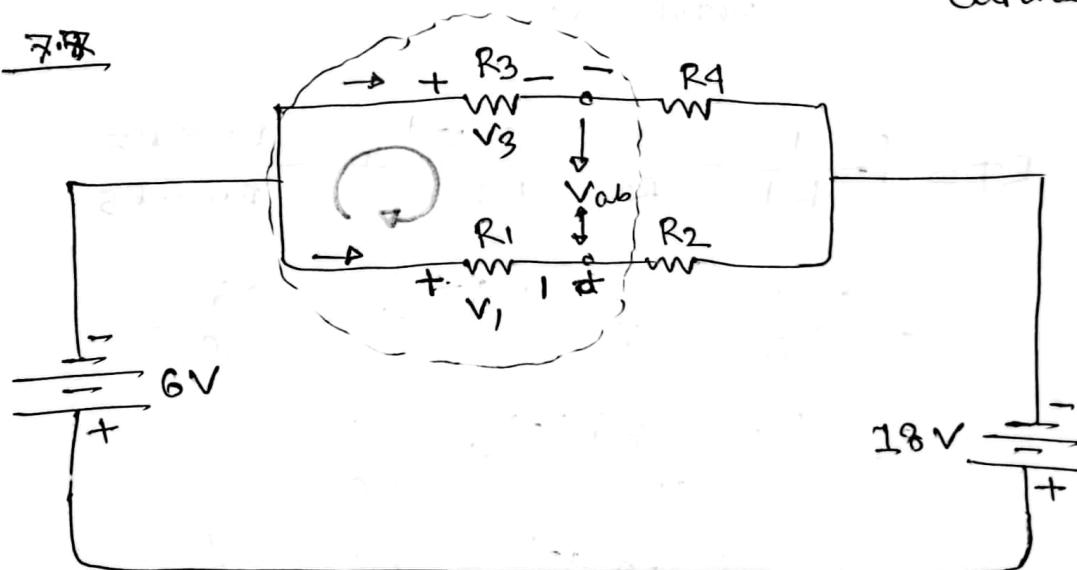

$$M_1 = ?$$

$$V_3 = ?$$

$$V_{ab} = ?$$

$$I_S = ?$$



$$V_1 = \frac{R_1}{R_1 + R_2} E = \frac{5}{5+3} \times 12 = 7.5V$$

$$V_3 = \frac{R_3}{R_3 + R_4} E = \frac{6}{6+2} \times 12 = 9V$$

$\textcircled{2}$

$$I_S = \frac{\frac{12}{9}}{R}$$

$$= \frac{12}{9}$$

$$= 3A$$

Applying KVL,


$$-\cancel{V_2} + V_{ab} + \cancel{V_1}$$

$$-V_3 + V_{ab} + V_1 = 0$$


$$\Rightarrow -9 + V_{ab} + 7.5 = 0$$

$$\Rightarrow V_{ab} = 2.5$$

7.8

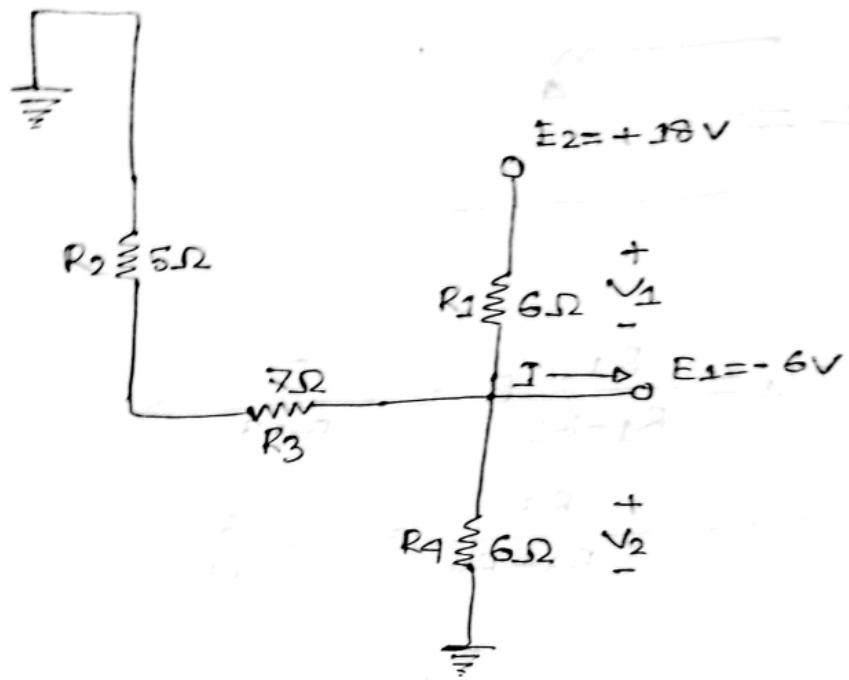

7.10

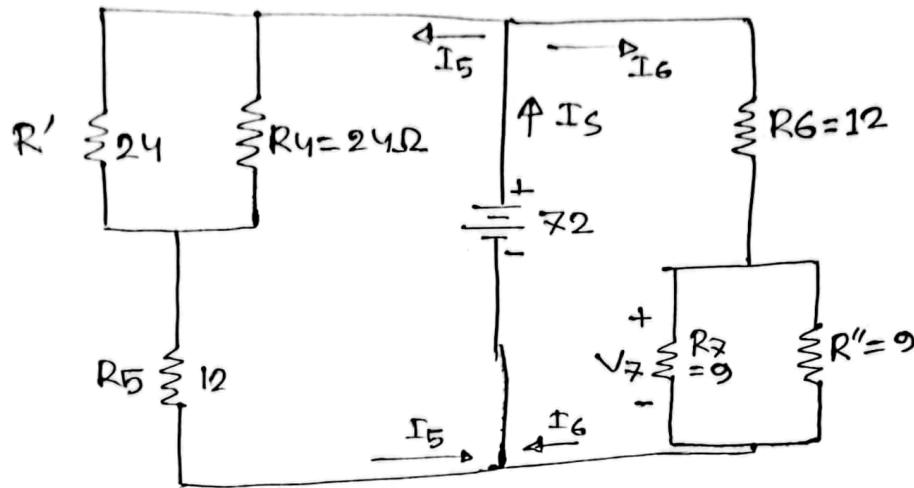


$$\begin{aligned}
 I_5 &= \frac{E}{(R' \parallel R_4) + R_5} \\
 &= \frac{72}{\frac{24 \times 24}{24+24} + 12} \\
 &= 3 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 V_7 &= \frac{R_7 \parallel R''}{R_7 \parallel R'' + R_6} E \\
 &= \frac{(4.5 \text{ k}\Omega)(72 \text{ V})}{4.5 \text{ k}\Omega + 12 \text{ k}\Omega} \\
 &= \frac{324 \text{ V}}{16.5} \\
 &= 19.6 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 I_6 &= \frac{V_7}{R_7 \parallel R''} \\
 &= \frac{19.6}{4.5} \\
 &= 4.35 \text{ mA} \quad \therefore I_S = I_5 + I_6 \\
 &= 3 \text{ mA} + 4.35 \text{ mA} = 7.35 \text{ mA}
 \end{aligned}$$

7.11

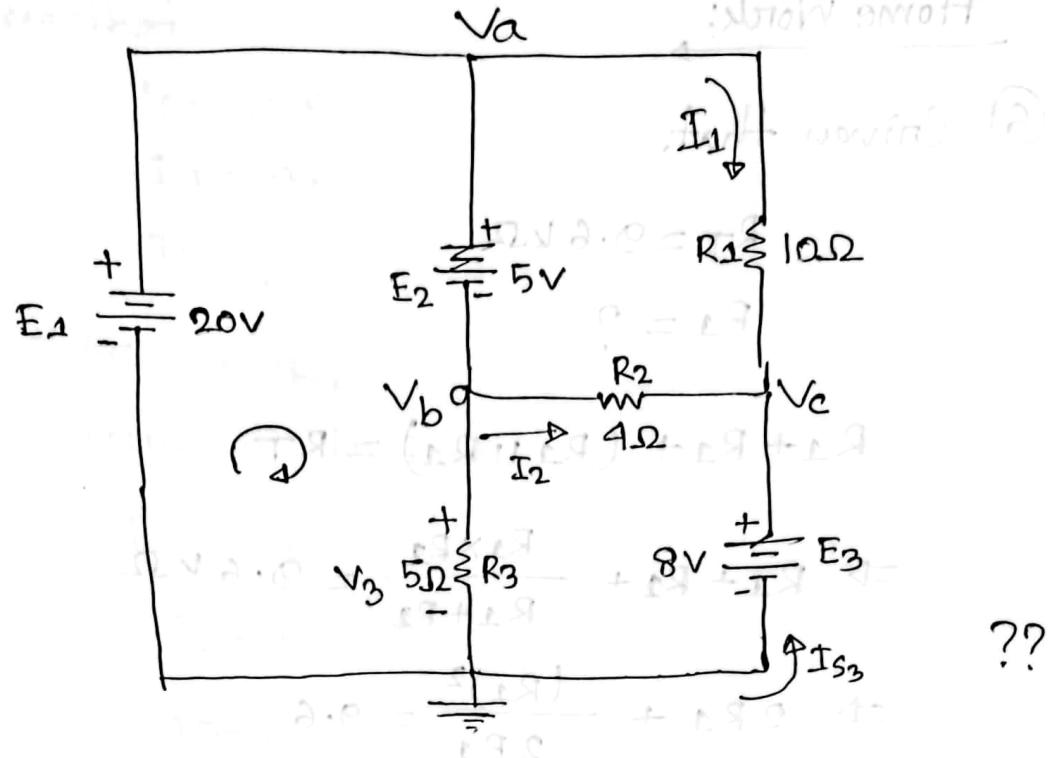

(a)

$$V_a = E_1 = 20V$$

$$V_c = E_3 = 8V$$

For V_b ,

$$+E_1 - E_2 - V_3 = 0$$

$$\Rightarrow 20 - 5 - V_3 = 0$$

$$\Rightarrow V_3 = 15V = V_b$$

(b)

$$V_{ac} = V_a - V_c$$

$$= 20 - 8 = 12V$$

$$V_{bc} = V_b - V_c$$

$$= 15 - 8$$

$$= 7V$$

$$\textcircled{a} \quad I_2 = \frac{V_2}{R_2}$$

$$= \frac{7V}{4\Omega}$$

$$= 1.75A$$

$$\textcircled{d} \quad I_1 = \frac{V_{ac}}{R_1}$$

$$= \frac{12}{10}$$

$$= 1.2A$$

KCL,

$$I_1 + I_2 + I_{S3} = 0$$

$$\Rightarrow I_{S3} + 1.75 + 1.2 = 0$$

$$\Rightarrow I_{S3} = -2.95A$$

Home Work

⑥ Given that,

$$R_T = 9.6 \text{ k}\Omega$$

$$R_1 = ?$$

$$R_1 + R_2 + (R_3 \parallel R_4) = R_T$$

$$\Rightarrow R_1 + R_2 + \frac{R_1 \times R_4}{R_1 + R_4} = 9.6 \text{ k}\Omega$$

$$\Rightarrow 2R_1 + \frac{(R_1)^2}{2R_1} = 9.6$$



$$\Rightarrow 2R_1 + \frac{R_1}{2} = 9.6$$

$$\Rightarrow 4R_1 + R_1 = 19.2$$

$$\Rightarrow 5R_1 = 19.2$$

$$\Rightarrow R_1 =$$

⑦ (a) We know that, in series circuit, current are same. In Figure 2.20,

$I_S = I_G = I_B$. Because, source current, wine,

$(R_1 \parallel R_2)$ combination and $(R_3 \parallel R_4)$ combination are remain parallel.

b) Given that,

$$I_3 = 40A$$

$$I_4 = 4A$$

$$I_2 = ?$$

Applying ~~KCL~~, ~~KIR~~,

Current division Rule,

$$I_3 = I_2 + I_4$$

$$\Rightarrow 10A = I_2 + 4$$

$$\Rightarrow I_2 = 10 - 4$$


$$\Rightarrow I_2 = 6A$$

c) Given that,

$$V_2 = 8V$$

$$E = 14$$

$$V_3 = ?$$

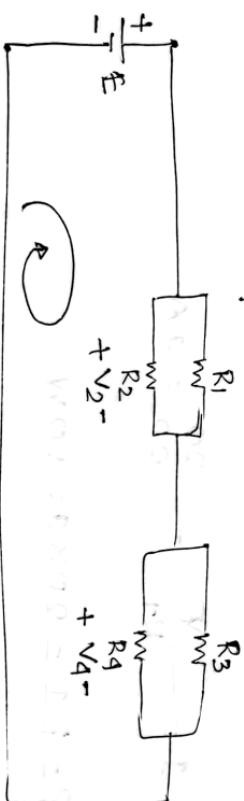

Applying KVL

$$E - V_2 - V_4 = 0$$

$$\Rightarrow 14 - 8 - V_4 = 0$$

$$\Rightarrow 6 - V_4 = 0$$

$$\Rightarrow V_4 = 6V = V_3 \text{ Ans.}$$

⑨ (a)

$$R_T = R_1 + \left\{ (R_2 || R_3) || R_4 \right\}$$

$$R_T = R_1 + (R_2 || R_3 || R_4)$$

$$= 11 + \frac{2\Omega}{3}$$

$$= 20 \Omega$$

$$I_S = \frac{E}{R_T}$$

$$= \frac{80}{20} = 4A$$

$$I_4 = \frac{(R_2 || R_3)}{(R_2 || R_3) + R_4} I_S$$

$$= \frac{\frac{2\Omega}{2}}{\frac{2\Omega}{2} + 2\Omega} \times 4$$

$$= 1.33A$$

b) $V_A = I_1 R_1 = 4 \times 11 = 44V$



$$I_3 = \frac{(R_4 || R_2)}{(R_4 || R_2) + R_3} I_S$$

$$= \frac{\frac{2\Omega}{2}}{\frac{2\Omega}{2} + 2\Omega} \times 4$$

$$= 1.33$$

$$V_B = I_3 R_3 = 1.33 \times 2\Omega = 35.91V$$

12) a)

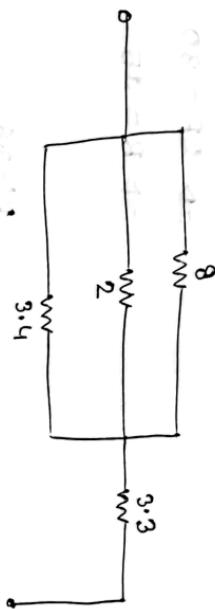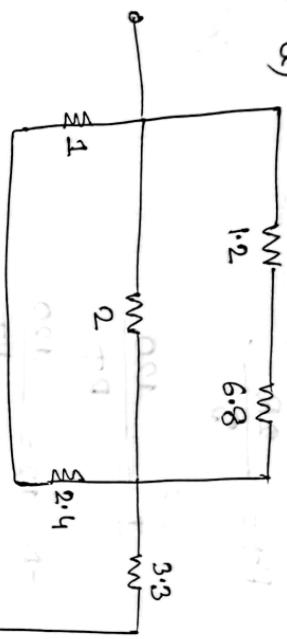

$$R_T = (8 \parallel 1.2 \parallel 3.4) + 3.3$$

$$= \left\{ \left(\frac{8 \times 2}{8+2} \right) \parallel 1.2 \parallel 3.4 \right\} + 3.3$$

$$= 1.026 + 3.33$$

$$= 4.59 \approx 4.6 \Omega$$

$$\therefore E = 4.8 V$$

$$I = \frac{4.8}{4.6} = 10.43 A$$

b)

(13)

$$R_T = \frac{2R}{3}$$



$$I = \frac{120}{R_T}$$


$$\Rightarrow 12 = \frac{120}{R_T}$$

$$\Rightarrow R_T = \frac{120}{12} = 10 = \frac{2R}{3}$$

$$\Rightarrow 2R = 30$$

$$\Rightarrow R = 15$$

(14)

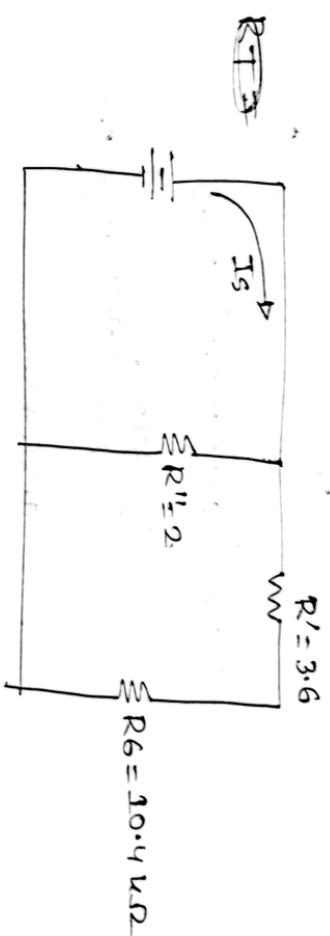

$$R' = \frac{9 \times 6}{15} = \frac{54}{15} = 3.6$$

$$R'' = \frac{12}{2} = 6 \quad \text{if } 3 = 6/13 = \frac{18}{9} = 2$$

Home work

(a)

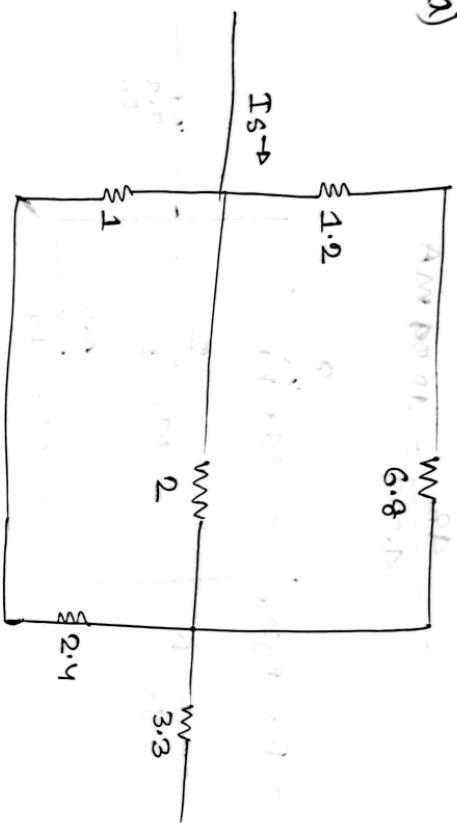


Fig-01

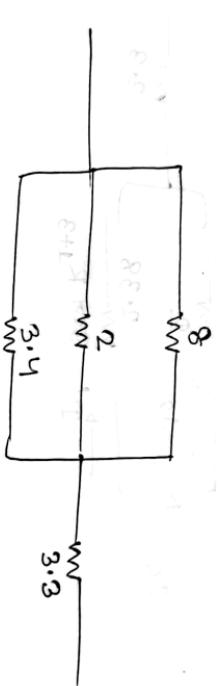


Fig-2

$$R_T = \left(\frac{8 \times 2}{10} \parallel 3.4 \right) + 3.3$$

$$= \left(\frac{16}{10} \parallel 3.4 \right) + 3.3$$

$$= \frac{1.6 \times 3.4}{1.6 + 3.4} + 3.3$$

$$= \frac{5.44}{5} + 3.3$$



$$= 4.388 \text{ k}\Omega$$

b)

$$I_S = \frac{V}{R}$$

$$= \frac{48}{4.388} = 10.99 \text{ mA}$$

c) From Fig. 2,

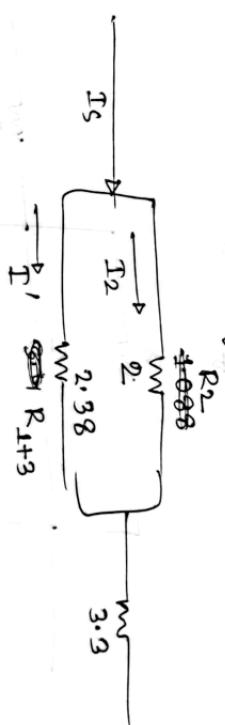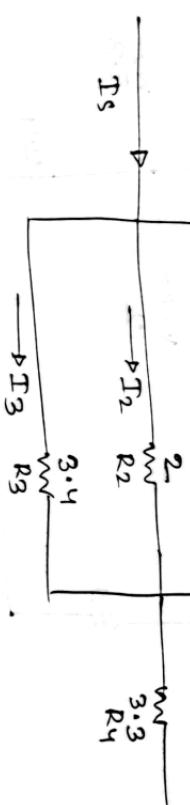


$$R_{1+3} = \frac{3.4 \times 8}{3.4 + 8}$$

$$I_2 = \frac{2.38}{2 + 2.38} I_S = \frac{2.38}{4.38} = 0.54 \text{ A}$$

$$\approx 5.9 \approx 6 \text{ k}\Omega$$

$$\begin{aligned} V_2 &= I_2 R_2 \\ &= 6 \times 2 \\ &= 12 \text{ V} \end{aligned}$$

(x)

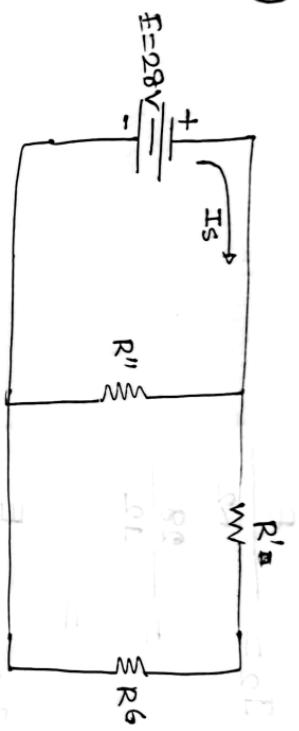

$$R' = \frac{9 \times 6}{9+6} = \frac{54}{15} = 3.6 \text{ k}\Omega$$

$$R'' = \left(\frac{12}{2} \parallel 3 \right) = \frac{6 \times 3}{6+3} = 2 \text{ k}\Omega$$

$$R_T = R'' \parallel (R' + R_6)$$

$$= 2 \parallel (3.6 + 10.4)$$

$$= 2 \parallel 14$$

$$= \frac{14 \times 2}{14+2} = 1.4 \text{ k}\Omega$$

$$= \frac{28}{16} = 1.75 \text{ k}\Omega$$

$$= 1.75 \text{ k}\Omega$$

(a)

$$I_S = \frac{E}{R_T} = \frac{28}{1.75} = 16 \text{ mA}$$

(b)

$$\begin{aligned} I'_S &= \frac{E}{R'_2 + (R_1 \parallel R_3)} \times I_S \\ &= \frac{28}{12 + \frac{12 \times 3}{12+3}} \times 16 \text{ mA} \end{aligned}$$

$$(a) \quad I_2 = \frac{E}{R_2}$$

$$= \frac{28}{1\Omega}$$

=

$$I_6 = \frac{E}{(R_4 || R_5) + R_6}$$

$$= \frac{28}{\frac{9 \times 6}{9+6} + 10\Omega}$$

$$= \frac{28}{15\Omega} + 10\Omega$$

$$(b) \quad V_4 = E = 28 \text{ V}$$

$$V_5 = I_6 \times R_5$$

=


$$(c) \quad I_3 = \frac{E}{R_3}$$

$$= \frac{28}{3} =$$

$$P = EI_3$$

$$= 28 \times$$

Chapter 9

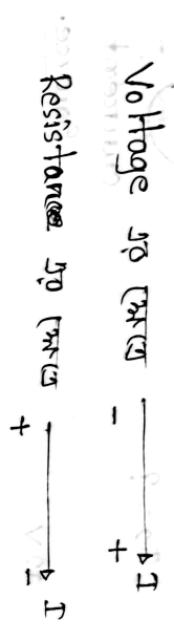

$$I = 10\text{mA} \quad \downarrow I_1$$

$$V_s = ?$$

$$V_1 = ?$$

$$I_1 = ?$$

$$I_1 = I = 10\text{mA}$$

The voltage across R_1 is V_1

$$V_1 = I_1 R_1$$

$$\Rightarrow R_1 = \frac{V_1}{I_1} =$$

$$= (10\text{mA})(20\text{k})$$

$$= 200\text{k}\Omega$$

Since resistors R_1 and current source are in parallel, the voltage across each must be the same.


$$\text{and } V_s = V_1 = 200\text{V}$$

$$8 \cdot 2$$

$$V_S = ?$$

$$I_4 = ?$$

$$I_2 = ?$$

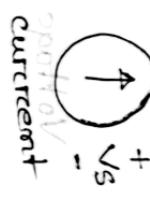

$$V_S = I \cdot R$$

Further,

Since the voltage source and resistor R are in parallel,

$$V_R = R = 12V$$

$$I_2 = \frac{V_R}{R} = \frac{12}{4} = 3A$$

$$\sum I_i = \sum I_o$$

$$\Rightarrow I = I_1 + I_2$$

$$\Rightarrow I_1 = 7 - 3 = 4A$$

Q3


$$I_4 = \frac{R_2}{R_1 + R_2} I$$

$$= \frac{2}{4+2} \times 6$$

$$I_4 = 2A$$


$$V_1 = I_1 R_1 = 2A \cdot 2\Omega = 4V$$


$$V_{OC} = 12V - 2V = 10V$$

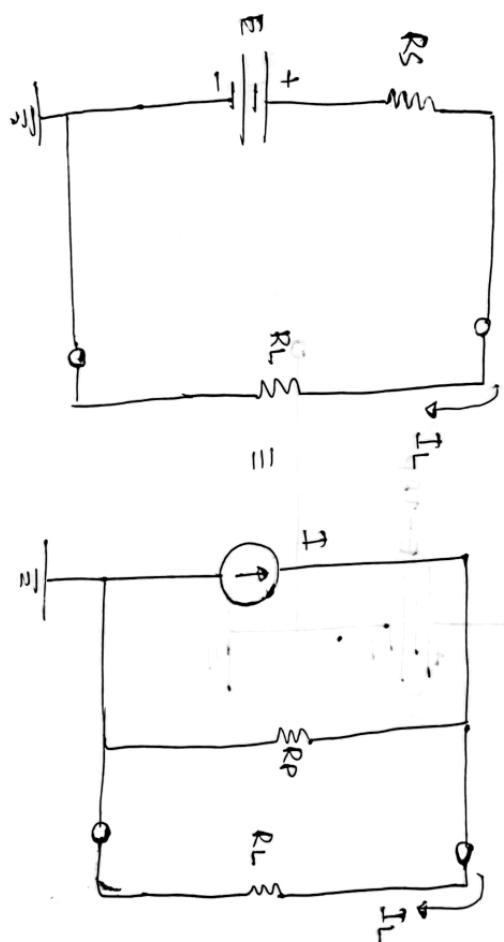


$$\begin{aligned} \Rightarrow V_S - V_A - 20 &= 0 \\ &= 4V + 20 \\ &= 24V \end{aligned}$$

$$V_S - V_A - 20 = 0$$

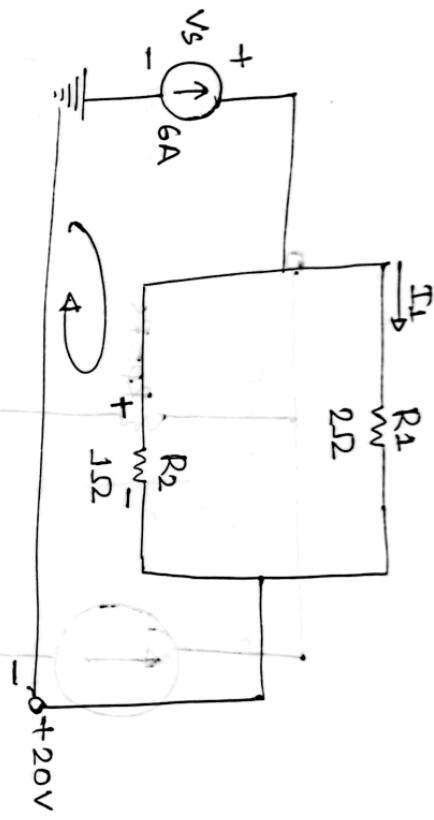

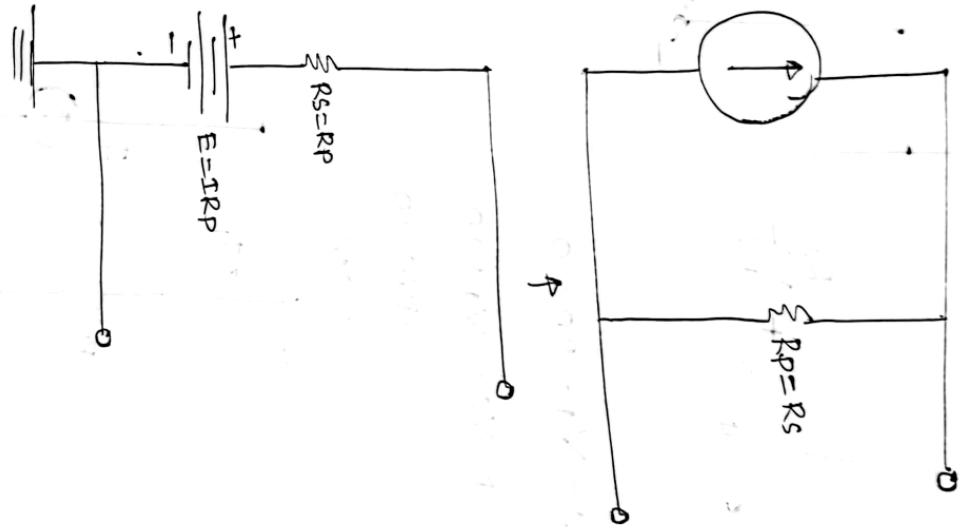

Q.4

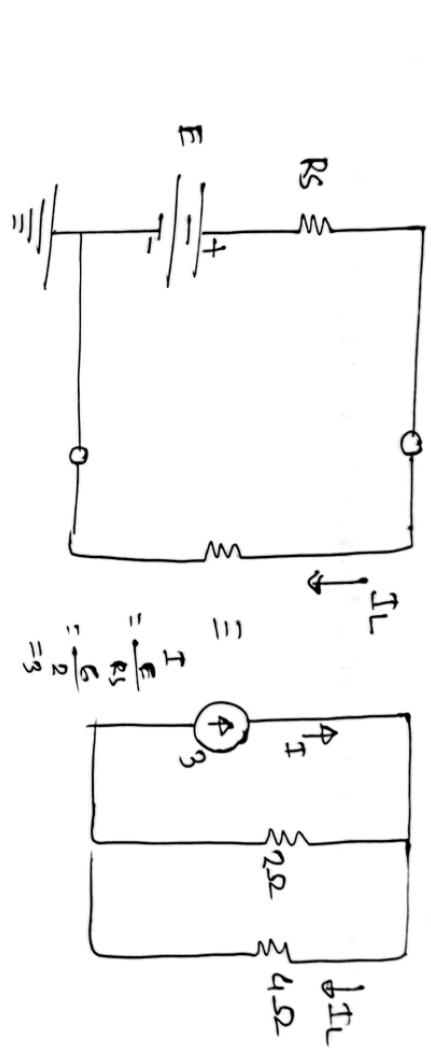

Applying Ohm's law,

$$\text{a) } I_L = \frac{E}{R_s + R_L}$$

$$= \frac{6}{2+4} = \frac{6}{6} = 1\text{ A}$$


c)

$$I_L = \frac{R_p}{R_p + R_L} I$$

$$= \frac{2 \times 3}{2+4} = 1$$

Δ to γ - Delta Formula

$\Delta \rightarrow \gamma$

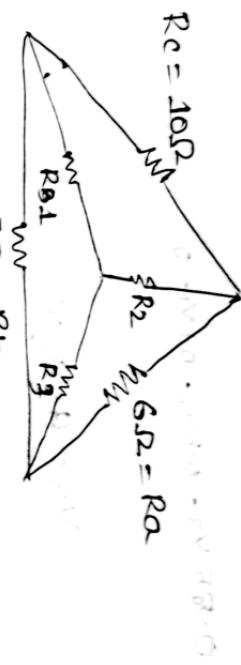

$$3D = R_b$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$


γ to Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Q.27

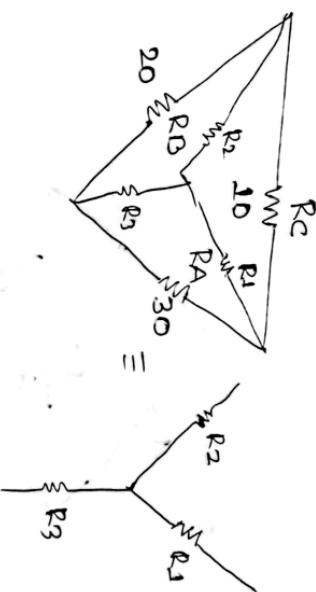


$$R_1 = \frac{10 \times 30}{10 + 20 + 30} = 5\Omega$$

$$R_2 = \frac{10 \times 20}{10 + 20 + 30} = 3\frac{1}{3}\Omega$$

$$R_3 = \frac{20 \times 30}{10 + 20 + 30} = 10\Omega$$


Q. 28

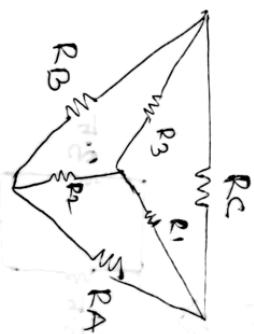

$$R_1 = \frac{R_C \times R_A}{R_1 + R_2 + R_3} =$$

Chapter-9

Superposition theorem

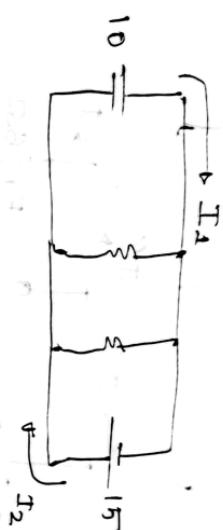

$$I_T = I_4 + I_2$$

$$E = V_4 + V_2$$

"Voltage source to replace short circuit
current source to replace open circuit"



short circuit & open circuit

Current Source to replace short circuit
Open circuit & open circuit


So Solve problem.

- 1) Total resistance
- 2) Total I
- 3) Current divider Rule

Q.1

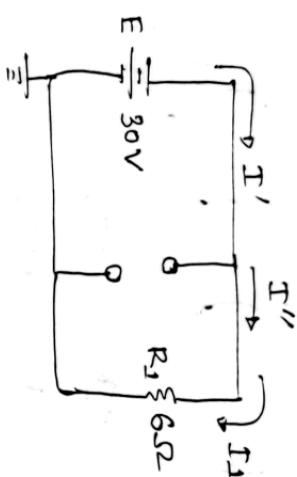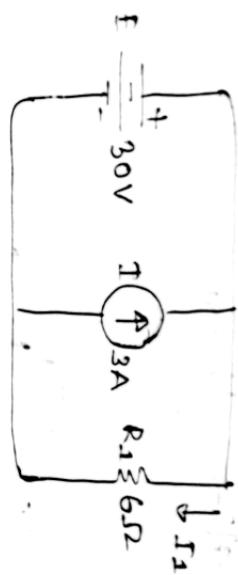


$$I'' = \frac{30}{6} = 5 \text{ A}$$

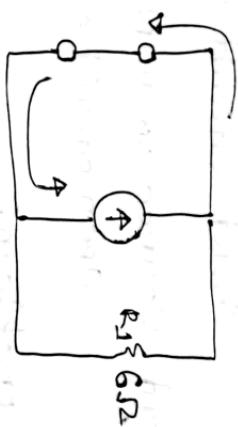


$$\begin{aligned} I &= I' + I'' \\ I' &= 0 \end{aligned}$$
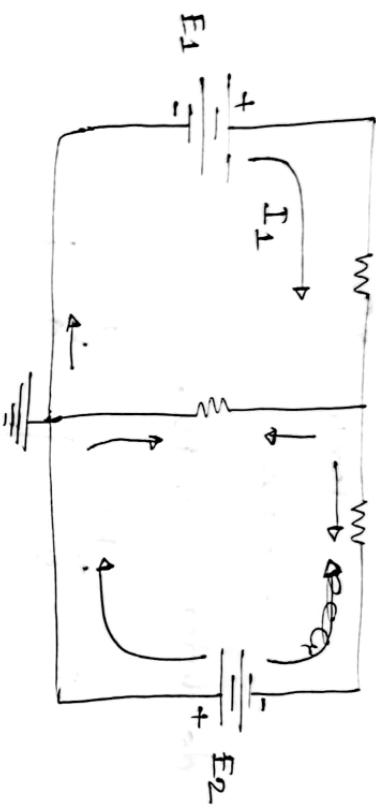
$$\begin{aligned} I_1 &= I' + I'' \\ &= 0 + 5 \\ &= 5 \text{ A} \end{aligned}$$



$$\begin{aligned}
 R_{\text{t}}' &= R_1 + \frac{R_2 \times R_3}{R_2 + R_3} \\
 &= 2 \times 1 + \\
 &= 2 \Omega
 \end{aligned}$$

To determine current from E_1 ,

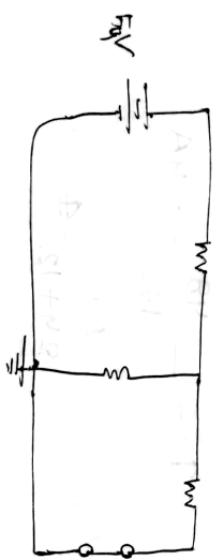

$$R_t = R_1 + \frac{R_2 \times R_3}{R_2 + R_3}$$

$$= 2 \Omega$$


$$I_S = \frac{E_1}{2R} = 2A$$

$$I_2 = \frac{R_3}{R_2 + R_3} I_1$$

$$= \frac{4}{12+4} \times 2$$

$$= 0.5 \text{ A}$$

To determine E_2 ,

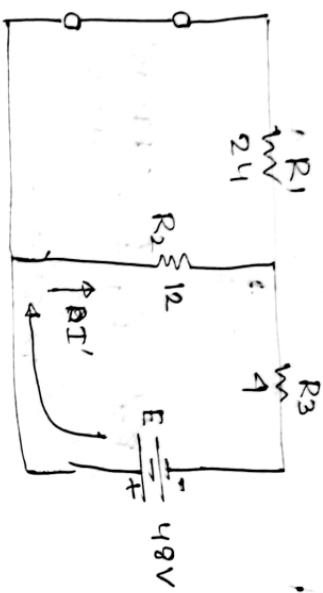

$$R_T = 4 + \frac{24 \times 12}{24+12}$$

$$= 12 \Omega$$

$$I_S = \frac{48}{12} = 4 \text{ A}$$



$$I' = \frac{24}{24+12} 4$$

$$= 2.67 \text{ A}$$

$$I_2 = 2.67 - 0.5$$

$$= 2.17 \text{ A}$$

19.3

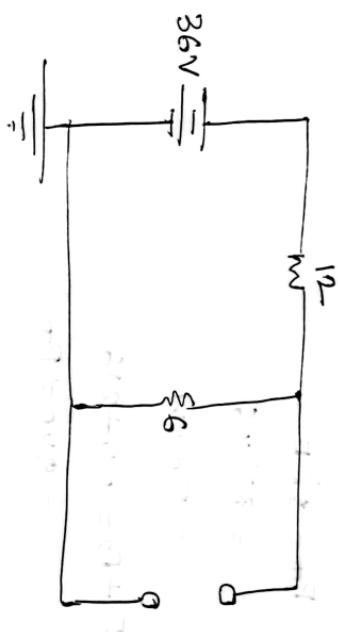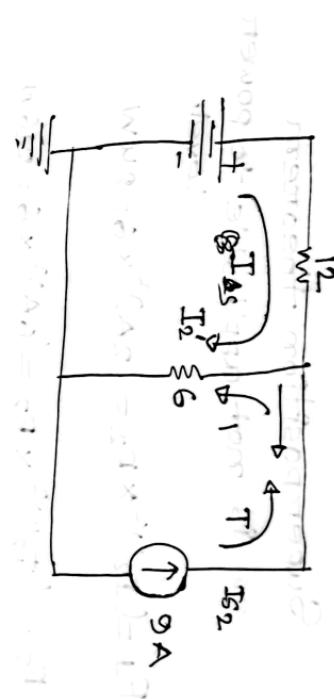

$$I_{B1} = \frac{36}{12+6}$$
$$= \frac{36}{18}$$
$$= 2A$$
$$I_{2'} = \frac{R_1}{R_1+R_2} I_1$$

$$= \frac{12}{12+6} \times 9$$

$$= 6A$$

\therefore Total current $2+6=8A.$

(b) Demonstrate,

Superposition theorem
is not applicable to power
level.

$$P_1 = (I_2')^2 \times R_2 = (2A)^2 \times 6 = 24W$$

$$P_2 = (I_2'')^2 \times R_2 = (6A)^2 \times 6 = 216W$$

$$P_T = I_2'' R$$

$$= (8)^2 \times 6$$

$$= 384W$$

$$\begin{aligned} P_1 + P_2 &= 24 + 216 \\ &= 240 \neq P_T \end{aligned}$$

Q.S. 1

Ans. 1

Ans. 1

Ans. 2 $I_2' = 2A$ for $R_2 = 6\Omega$

Series :

① $V = IR$

~~Start~~

Chapter-6

- ② Circuitts Voltage law: In a close loop circuit, total supplied voltage is equal to total dropped voltage.

Or,

In a close loop circuit, total summation of voltage equal to zero.

- ③ Voltage divider Rule: (VDR)

$$V_1 = \frac{R_1}{R_1 + R_2} \times V_T$$

$$V_2 = \frac{R_2}{R_1 + R_2} \times V_T$$

Parallel circuit solved by 3 formula:

1) $V = IR$

2) KCL : In a junction point/node entering current and leaving current are equal.

$$I_{in} = I_{out}$$

$$I_1 + I_2 + I_3 = I_4 + I_5$$

3) CDR

$$I_1 = \frac{I_T \times R_1}{R_1 + R_2} \quad I_2 = \frac{I_T \times R_2}{R_1 + R_2}$$

* Conductance is reverse of resistance.

$$G_I = \frac{1}{R}$$

6.1


$$\cancel{G_{I1}} = \cancel{\frac{1}{R_1}}$$

$$= \cancel{\frac{1}{3}}$$

$$R_P = \left(\frac{3 \times 6}{6+3} \right) = \frac{12}{9} = 1.33 \Omega$$

$$\therefore G_{IP} = \frac{1}{R_P} =$$


6.3

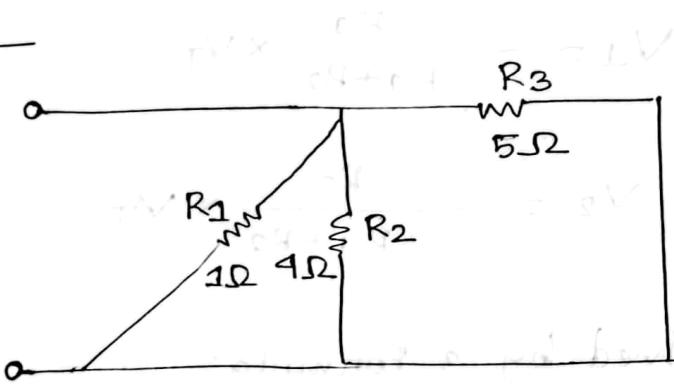


$$R' = \frac{1 \times 4}{1+4} = \frac{4}{5}$$

short circuit current = $I = \frac{12}{5+4} = 1.44 A$

R_3

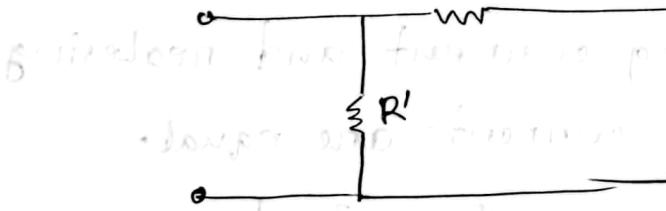
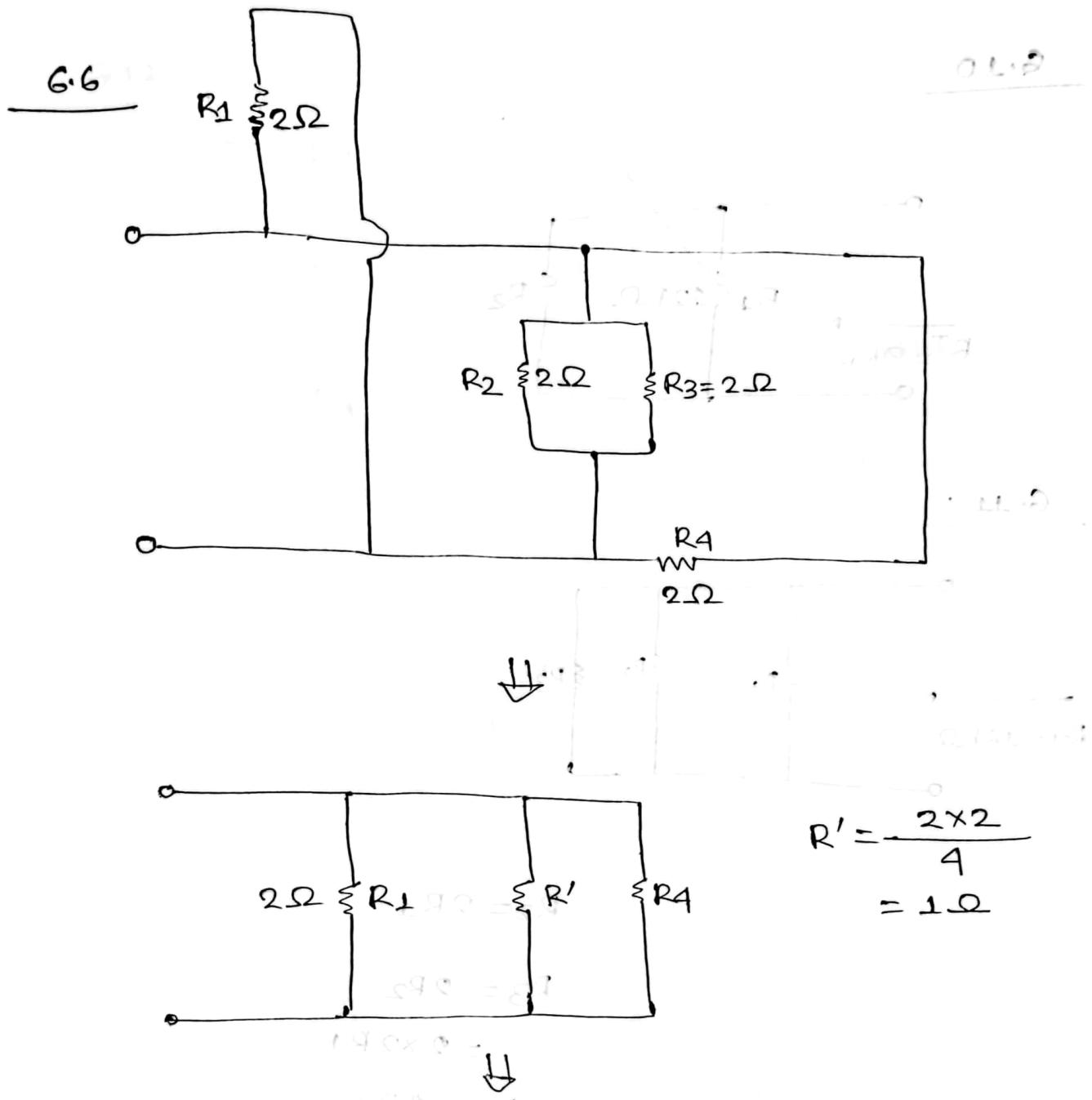
$$R_T = \frac{R_3 \times R'}{R_3 + R'} = \frac{5 \times 4}{5+4} = 4 \Omega$$



$$R'' = \frac{R' \times R_4}{R' + R_4}$$

$$= \frac{1 \times 2}{1+2} =$$

$$R_T = \frac{R'' \times R_1}{R'' + R_1}$$

=


14.0x0

15.0x0


15.0x0

Q.L.B = 64

G.10

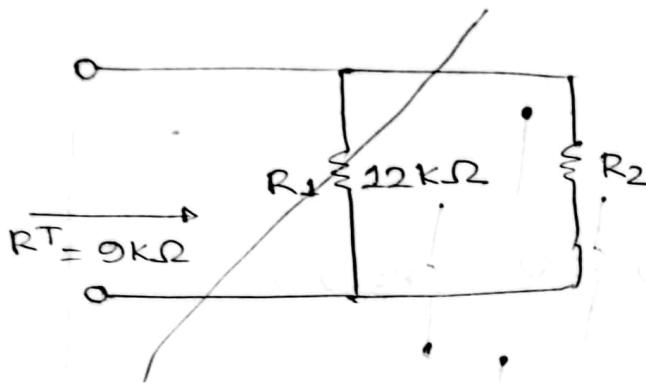

G.11 :

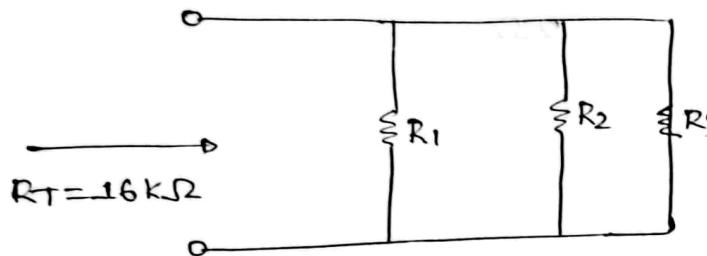

$$R_2 = 2R_1$$

$$R_3 = 2R_2$$

$$= 2 \times 2R_1$$

$$R_P = \left(\frac{1}{R_1} + \frac{1}{2R_1} + \frac{1}{4R_1} \right)^{-1} = 4R_1$$

$$= \left(\frac{4+2+1}{4R_1} \right)^{-1}$$

$$RT = \frac{4R_1}{7}$$

$$\Rightarrow 16 \times 7 = 4R_1$$

$$\Rightarrow R_1 = 28 \text{ k}\Omega$$

$$R_2 = 56 \text{ k}\Omega$$

$$R_3 = 112 \text{ k}\Omega$$

6.12

a) $R_T = \frac{9 \times 18}{9+18} = \frac{9 \times 18}{27} = 18 \Omega$

b) $I_S = \frac{E}{R_T} = \frac{9}{18} = 0.5 A$

c) $I_1 = \frac{R_2}{R_1 + R_2} \times I_S = \frac{9}{9+18} \times 0.5 = 0.25 A$

Another way,
 $I_1 = \frac{V_1}{R_1} = \frac{9}{18} = 0.5 A$

=


$I_2 = \frac{R_1}{R_1 + R_2} \times I_S = \frac{9}{9+18} \times 0.5 = 0.25 A$

values from question statement
 $V_{DD} = 9 V$

=

$I_1 = 0.5 A$

6.14

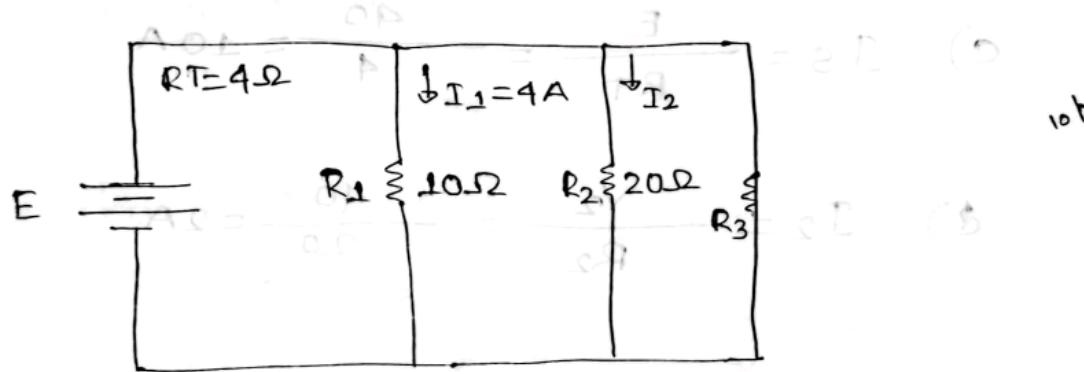

a) ~~$R_T =$~~ $R_T = \left(\frac{1}{10} + \frac{1}{20} + \frac{1}{30} \right)^{-1}$

$\Rightarrow R_T = \left(\frac{2+1}{20} + \frac{1}{30} \right)^{-1}$

$\Rightarrow R_T = \left(\frac{3R_3 + 20}{20R_3} \right)^{-1}$

$$RT = 4 = \frac{20R_3}{3R_3 + 20} \quad \text{since } R_1 = R_2 = R \quad (d)$$

$$\Rightarrow 12R_3 + 80 = 20R_3 \quad \frac{I}{R_3} = \frac{I}{R} \quad (d)$$

$$\Rightarrow 80 = 8R_3$$

$$\Rightarrow R_3 = 10\Omega \quad \text{since } R_1 = R_2 = R \quad (d)$$

b) $V_1 = I_1 R_1$

$$= 4 \times 10$$

$$= 40V$$

in parallel, voltage are equal.

$$\text{So, } V_1 = E$$

c) $I_S = \frac{E}{RT} = \frac{40}{4} = 10A$

d) $I_2 = \frac{V_2}{R_2} = \frac{40}{20} = 2A$

$$\frac{40}{20} = \frac{20}{R_1} \Rightarrow R_1 = 10\Omega$$

$$\frac{40 + 20}{20} = \frac{60}{20} = 3A$$

Q.L.D

Power distribution in parallel circuits

$$P_E = P_{R1} + P_{R2} + P_{R3}$$


Amp Aamp Aamp Aamp R

$$P = EI$$

$$P = EI = I^2 R = \frac{E^2}{R}$$

$$E = V$$

6.16

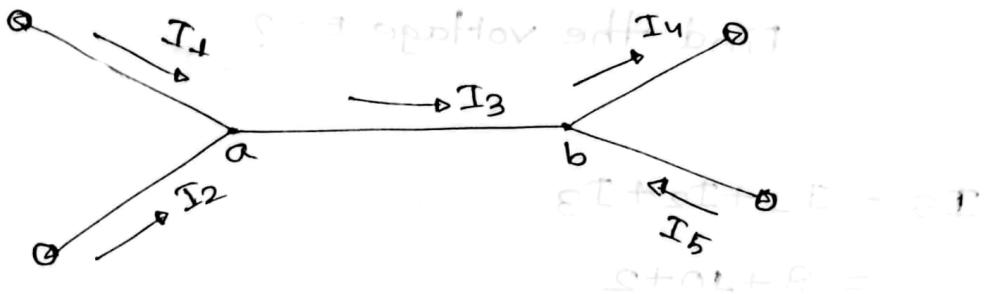

In node a,

$$I_1 + I_2 = I_3$$

In node b,

$$I_3 + I_5 = I_4$$


$$I_2 = 3A$$

6.18

node a,


$$I_2 + I_1 = I_3$$

node b, $I_3 = I_4 + I_5$

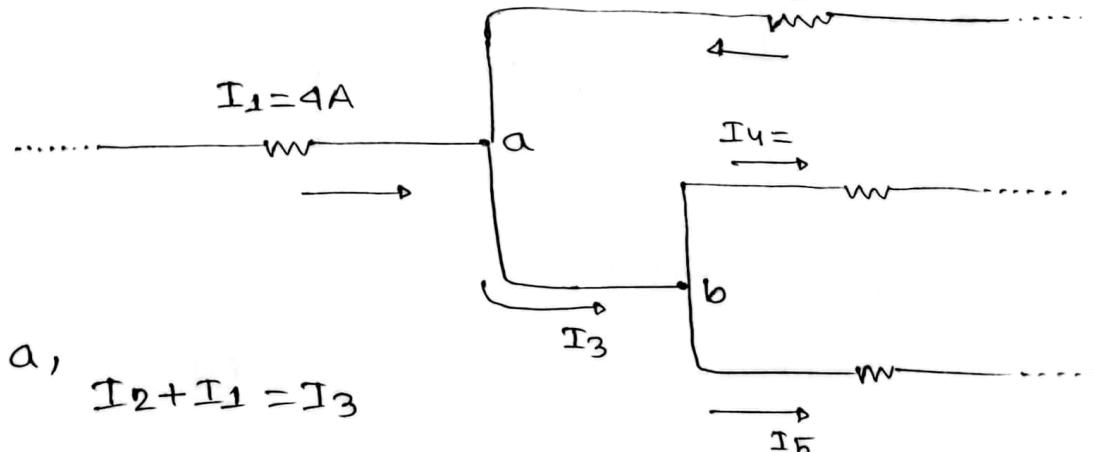

6.10

Given following circuit diagram find

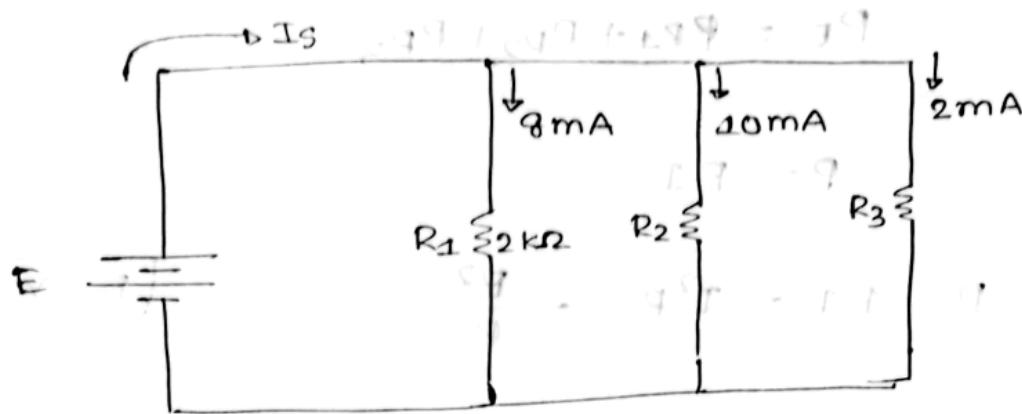

Determine the source current $I_s = ?$


Find the voltage $E = ?$

$$\begin{aligned} I_s &= I_1 + I_2 + I_3 \\ &= 8 + 10 + 2 \\ &= 20 \text{ mA} \end{aligned}$$

$$\begin{aligned} E &= V_1 = I_1 R_1 \\ &= 8 \times 2 \\ &= 16 \text{ V} \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{V_2}{I_2} \\ &= \frac{16}{10 \times 10^{-3}} \\ &= 1.6 \times 10^3 \Omega \end{aligned}$$

Q.24

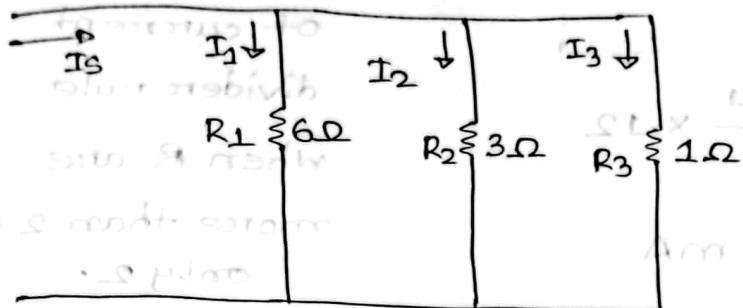

Determine $I_1, I_2, I_3 = ?$

$$I_1 = \frac{I_2}{2} = \frac{2 \text{ mA}}{2} = 1 \text{ mA}$$

$$I_3 = 3 \times I_2$$

$$= 3 \times 2$$


$$= 6 \text{ mA}$$

$$I_S = I_1 + I_2 + I_3$$

$$= 1 \text{ mA} + 2 \text{ mA} + 6 \text{ mA}$$

$$= 9 \text{ mA}$$

Q.22

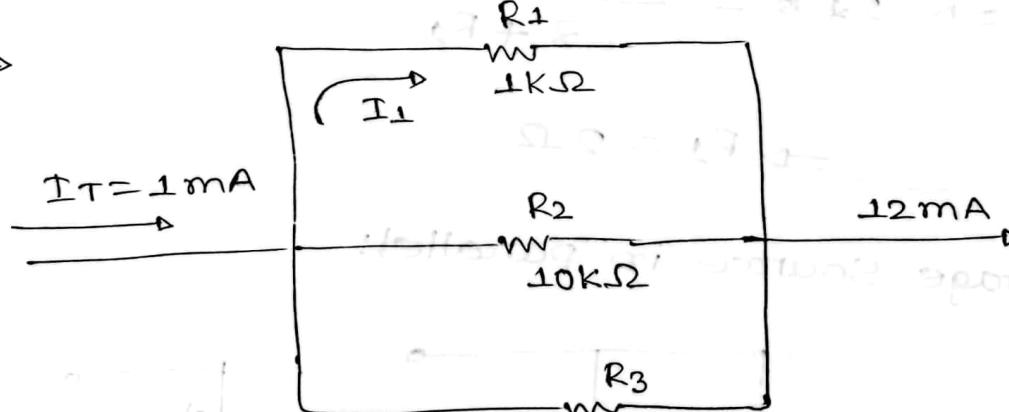

$$I_1 = ?$$

$$R_T = \left(\frac{1}{1} + \frac{1}{10} + \frac{1}{22} \right)^{-1}$$

option following will be $873.01 \text{ }\Omega$ of question below)


$$I_1 R_1 = I_T R_T$$

$$I_1 = \frac{R_T}{R_1} \times I_T$$

$$= \frac{873.01}{1} \times 12 \\ = 10.48 \text{ mA}$$

This is
the equation
of current
divider rule
when R are
more than 2 or
only 2.

6.24

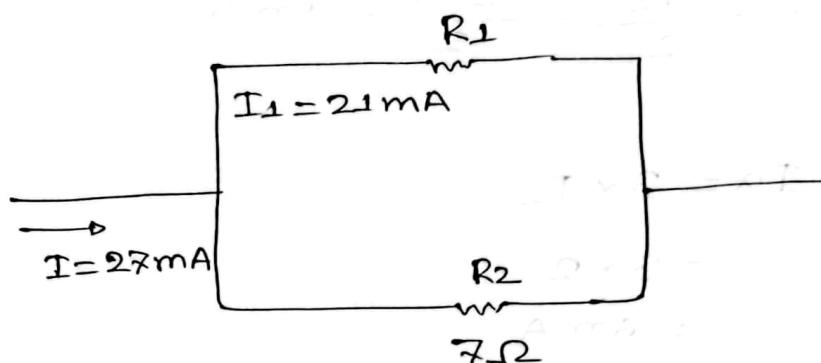


$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$\Rightarrow 21 = \frac{7}{7 + R_1} \times 27$$



$$\Rightarrow R_1 = 2 \Omega$$

Voltage Source in parallel:

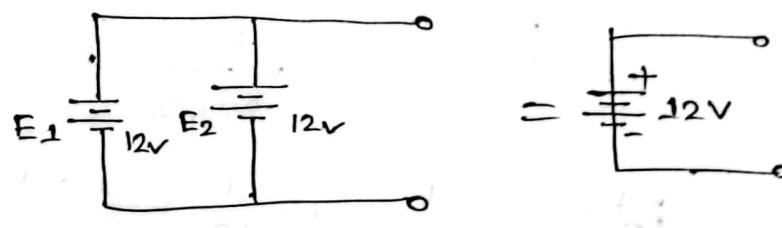

Parallel circuit does not contain parallel voltage.

open circuit and short circuit:

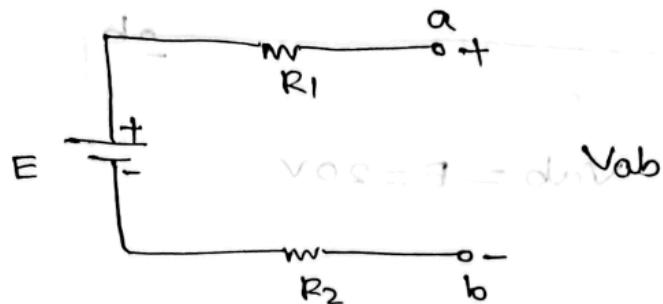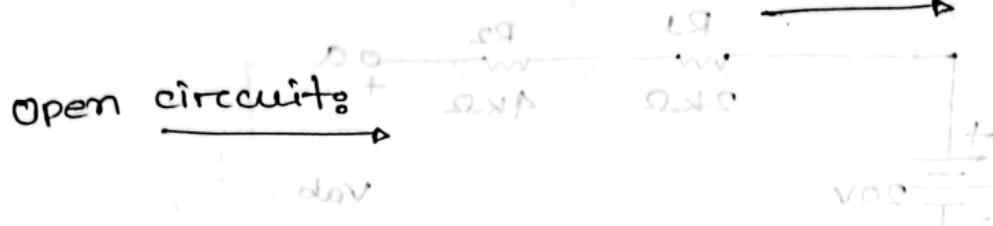


$$V_1 = I_1 R_1$$

$$= 0 \times R_1 \\ = 0$$

E or Supply factor

For open circuit to drop to,

Short circuit:

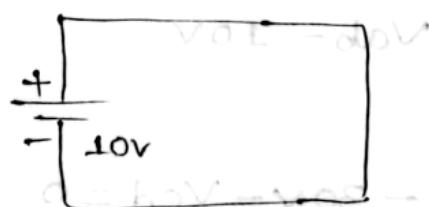


$$\text{current} \\ I = \frac{V}{R} \\ = \frac{V}{0} \\ = \infty$$

$$V_{ab} = 0V - 0V = 0V$$


$V_{ab} = 0V$ तरुण वर्णन

values with both voltage source and current source

analog voltage and current source

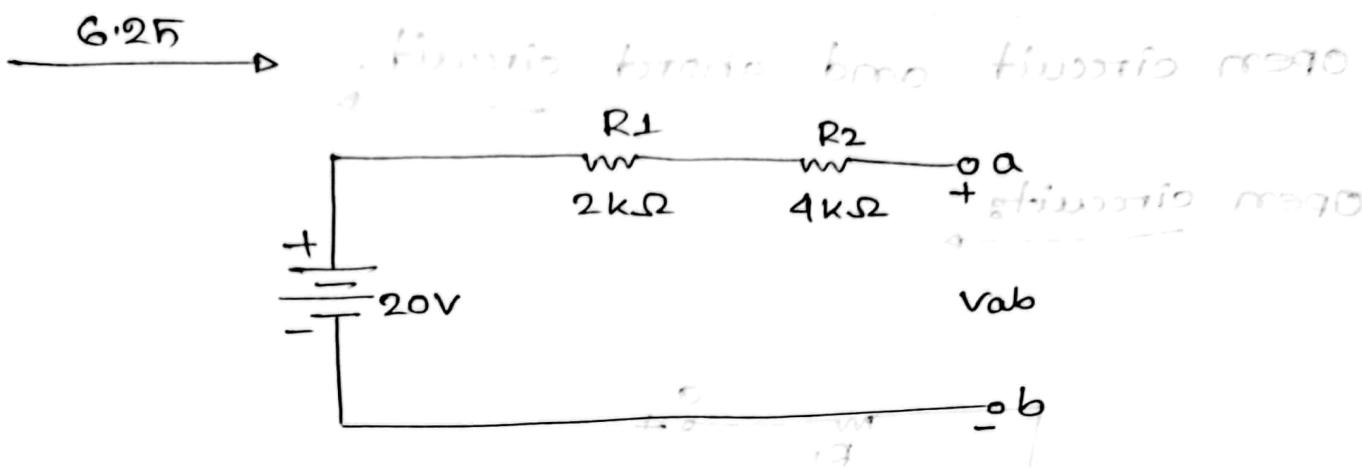

$$V_{ab} = E = 20\text{V}$$

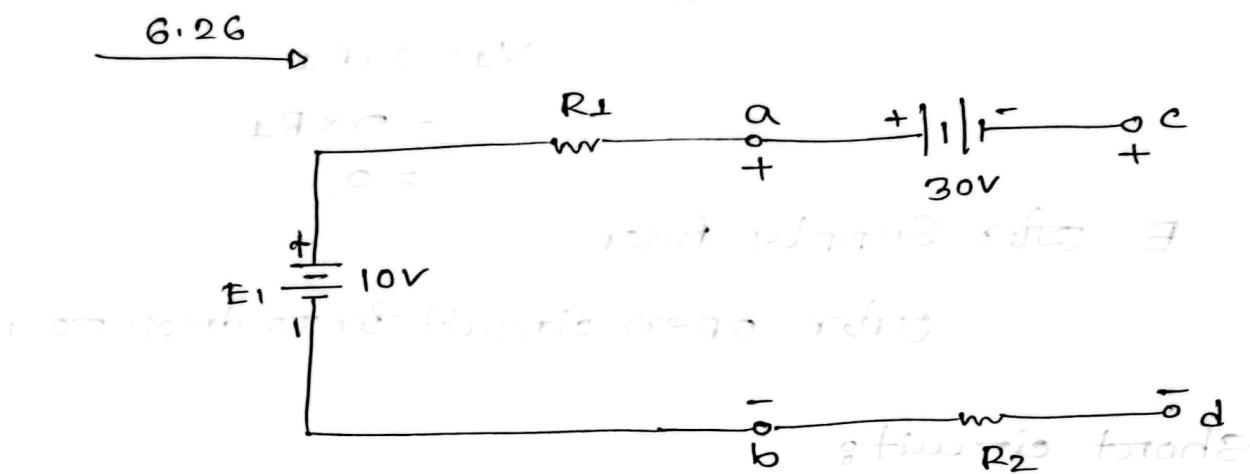

$$V_{ab} = 10\text{V}$$

applying,

KVL,

$$+E_1 - 30\text{V} - V_{cd} = 0$$

$$\Rightarrow 10 - 30 = V_{cd}$$

$$\therefore V_{cd} = -20\text{V}$$





The -ve sign indicates that the actual voltage V_{cd} has the opposite polarity.

chapterc-7

Series parallel circuit

chapterc-8

(dc)

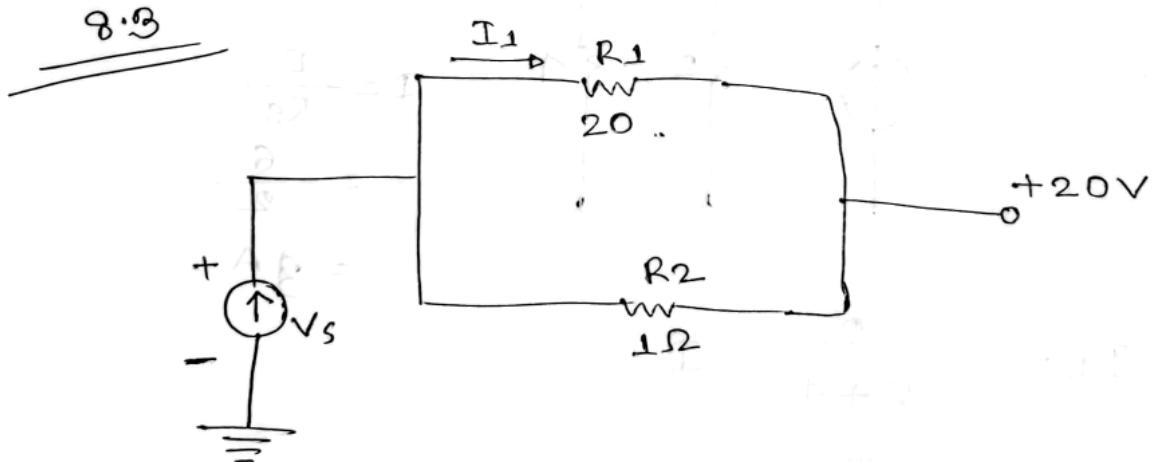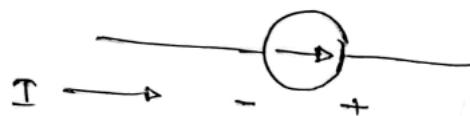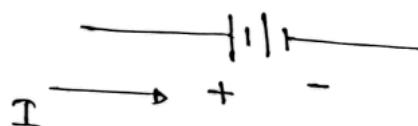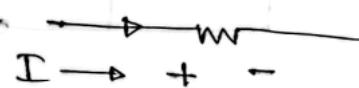

$$+ V_s - V_1 - 20V = 0$$

$$\Rightarrow V_s = V_1 + 20$$


$$= 4 + 20$$

$$= 24V$$

$$= \frac{6}{6} = 1A$$



$$= \frac{6}{2} \times 9 = 54$$

$$T_L = \frac{2+4}{2}$$

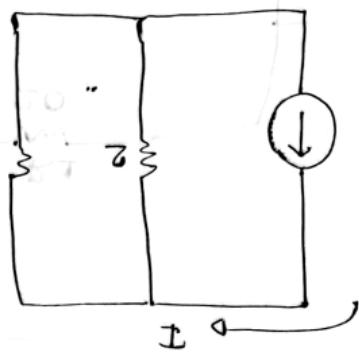

$$= \frac{6}{6} = 1A$$

$$\frac{R_T}{E} = I_L \quad (x)$$


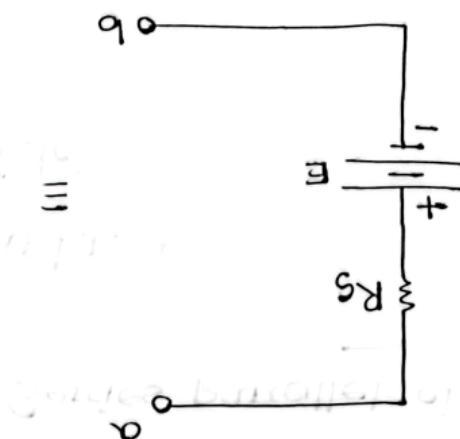
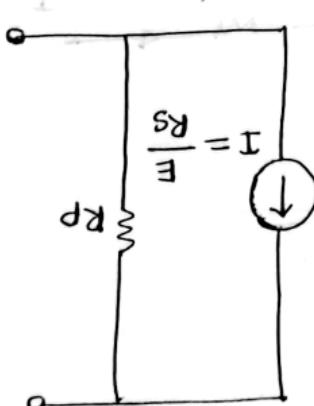


COMVETG1919%

$$= \boxed{\quad}$$

$$I_L = \frac{R' + 14}{R'} \cdot 10$$


$$R_1 = \frac{24 \times 8}{24 + 8}$$

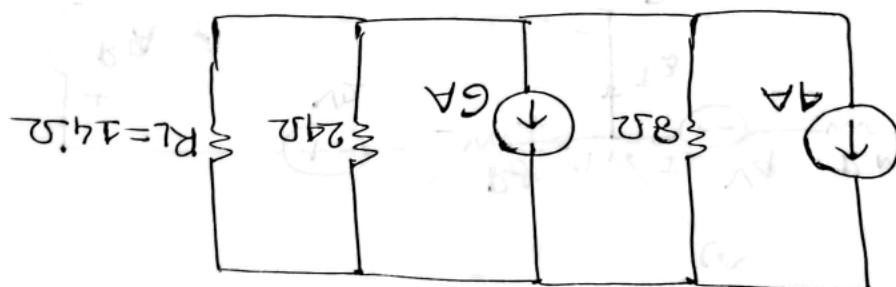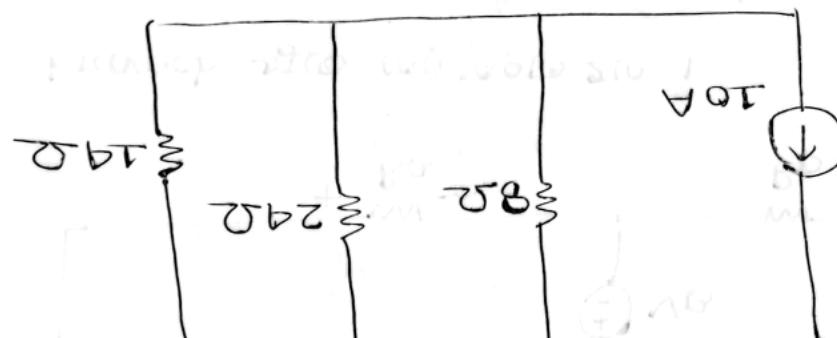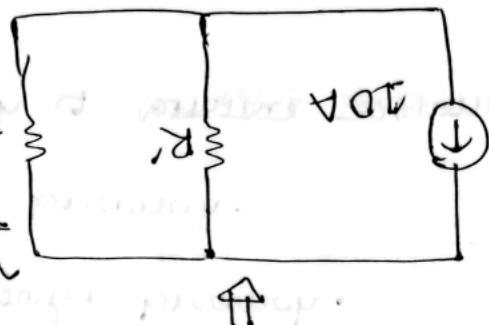

$$I_L = ?$$

After taking current
at start (+) terminal

Value of Resistor


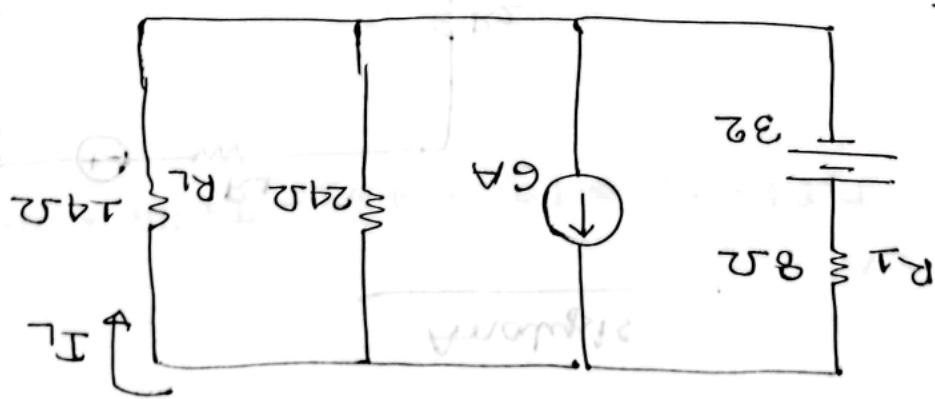


8.0

apply rule 1
 current branch 4 contains same current as current branch 3 for branch.
 (left side branch).


pair always have same current flow too.

→ after branch stage (Q) rule 2 (O)

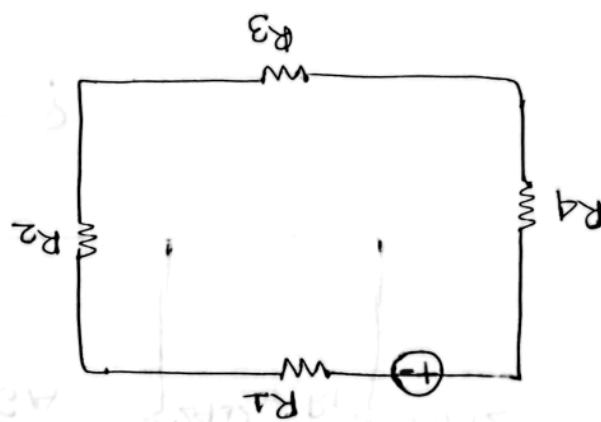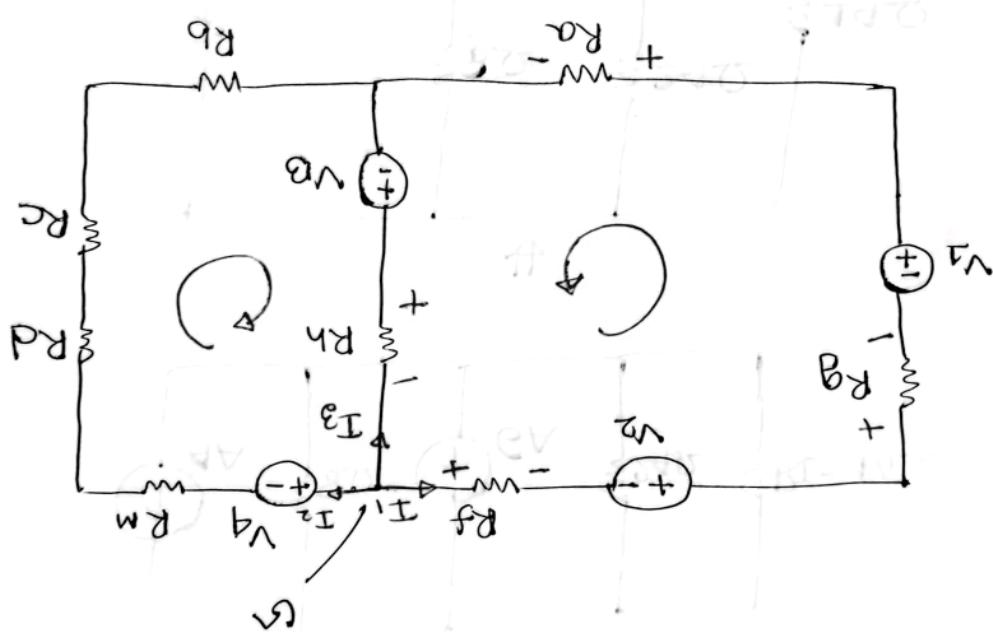

Analogies

Branch - Current

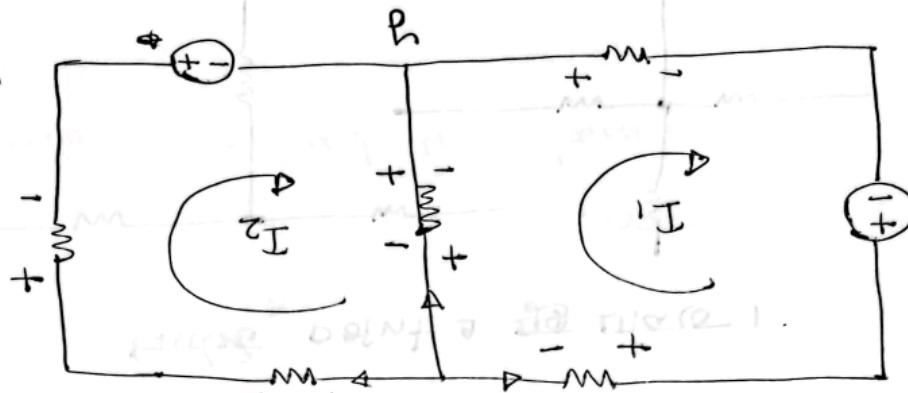

Mesh Analysis

$$I_1 + I_2 + I_3 = 0$$

KCL, at 50mM G_T,

0 =

$$-V_A - I_2 R_m - I_2 R_b - I_2 R_C - I_2 R_b + V_D - I_2 R_h$$


2nd loop. KVL,

$\theta =$

$$-I_2R_f + V_2 - Rg I_3 + V_1 - I_3R_a + V_B - I_2R_h = 0$$

1781, 1001-1st

→ Current direction နှစ်မျက်နှာ ဖော်

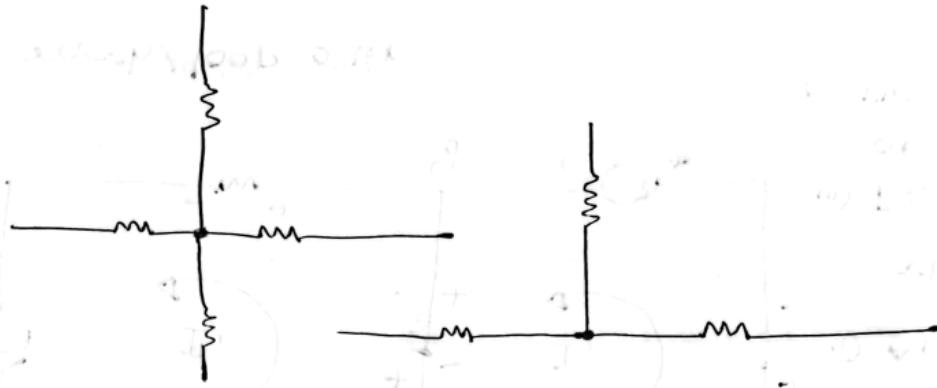

فرزیت پلینت ۲ در چیزی

برای مدار که دارای یک منبع ولتاژ / یک منبع جریان / یک
فرزیت

نامه شوند چنین

پس

آنرا اپنے تصور

* مدار آنالیزیں ۲) چرچنهن سource رکھتے

۳) چرچنهن سource رکھنے کے لئے

۴) مدار آنالیزیں ۱) ولتاژ سource رکھنے کے لئے

۵) مدار آنالیزیں ۱) ولتاژ سource رکھنے کے لئے

۶) نodal آنالیزیں ۱) چرچنهن سource رکھنے کے لئے

$$\frac{V_2 - V_1}{R_3} = I_2$$

Nodal analysis

$$R_3(I_2 - I_1) + R_4 I_2 + R_5 I_2 + V_2 = 0$$

KVL ۲nd way

$$V_2 - R_1 I_1 + R_3 (I_1 - I_2) + R_2 I_2 = 0$$

KVL ۱st way


~~$I = \frac{V}{R}$~~

~~$I = \frac{10}{10+1} A = 1A$~~

Current of emitter = $\frac{1}{10+1} \times 10 = 1A$

Summation of flowing current = summation of $I_A + I_B + I_C$

In any junction,

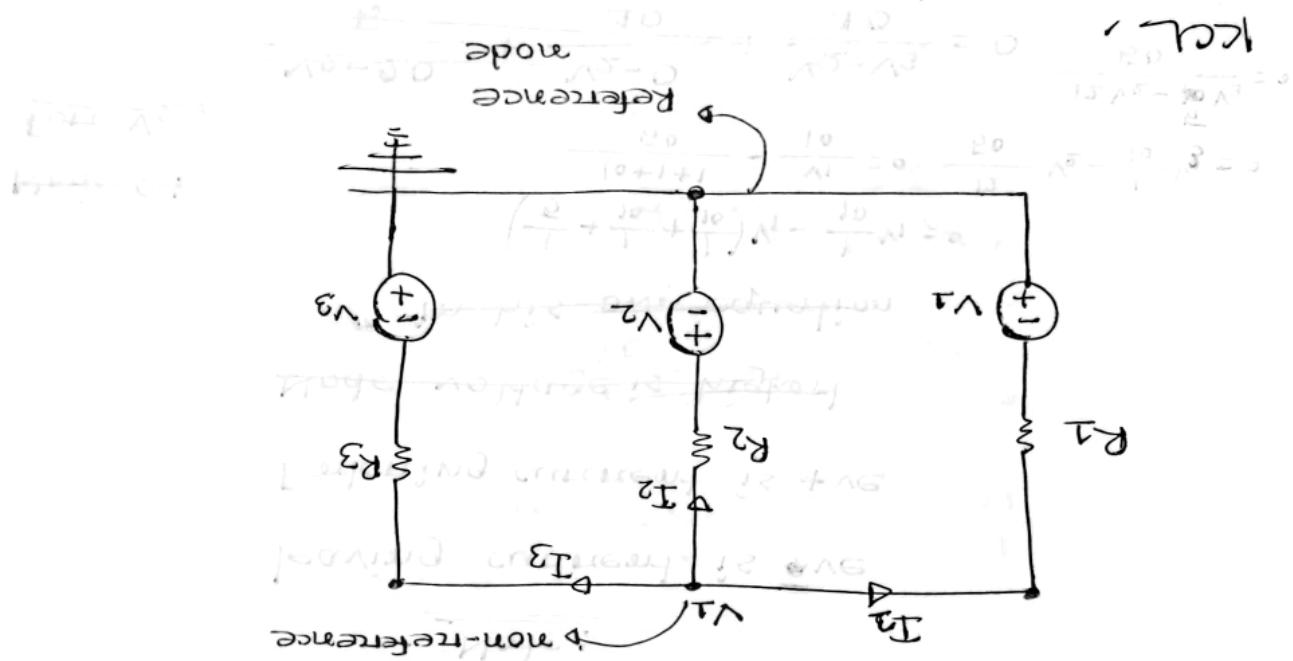

• Solve the equations formed by the above equations.

(ii) After non-referencing node to right we apply KCL

(iii) Non-referencing node to left - (non-referencing node)

(iv) Reference node to left - (non-referencing node)

After this we can do nodal analysis across all

other node i.e. right (i.e. reference voltage remains)

$$4V_2 - V_3 = 40$$

$$\frac{1}{10}V_1 + \left(\frac{1}{10} + \frac{1}{15} \right) V_2 - \frac{1}{10}V_3 = 0$$

$$\frac{1}{10+1+1}V_1 - \frac{1}{12}V_2 - \frac{1}{10}V_3 = 0$$

$$\frac{50}{10+1+1} - \frac{50}{12} - \frac{50}{10} = 0$$

$$\frac{5}{11} - \frac{5}{6} - 5 = 0$$

$$\frac{30}{66} - \frac{50}{66} - \frac{330}{66} = 0$$

$$- \frac{280}{66} = 0$$

$$- \frac{140}{33} = 0$$

~~This question~~


~~Node voltage is higher~~

Efficient current is the

leaving current is the

Note:

Assumption: Current leaves node

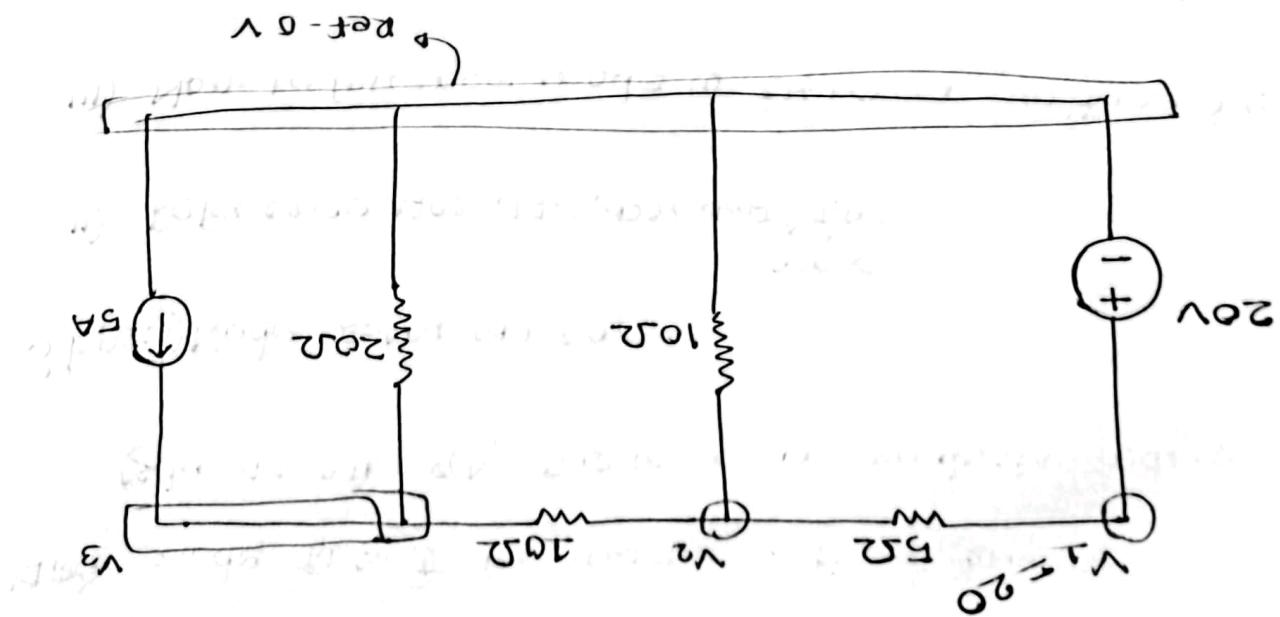

Then eqn solve:

$$-2V_2 + 3V_3 = 100 \quad \text{⑪} \quad \leftarrow$$

$$3V_3 - 2V_2 = 100 \quad \leftarrow \\ (\text{Subtract ⑪ from ⑩})$$

$$\frac{3V_3 - 2V_2}{20} = 5 \quad \leftarrow \\ (\text{Divide by } 10)$$

$$\frac{3}{2}V_3 - \frac{1}{10}V_2 = 5 \quad \leftarrow$$

$$\left(\frac{10}{4} + \frac{1}{2} \right) V_3 - \frac{1}{10}V_2 = 5$$

: V_3


$$4V_2 - V_3 = 0 \quad \text{⑫} \quad \leftarrow$$

$$\frac{20V_2 - 5V_3}{50} = 0 \quad \leftarrow$$


$$\frac{10 + 5 + 5}{10} V_2 - \frac{50}{V_3} = 0 \quad \leftarrow$$

$$0 = \left(\frac{1}{2} + \frac{1}{10} + \frac{1}{10} \right) V_2 - \frac{5}{V_3} \quad \leftarrow$$

: V_2

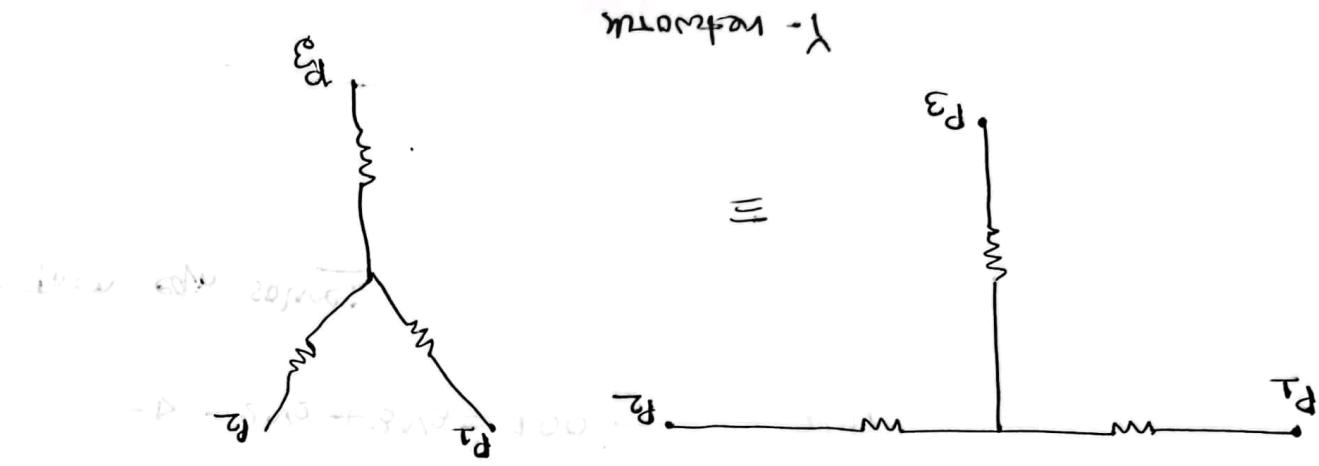


(Δ network)

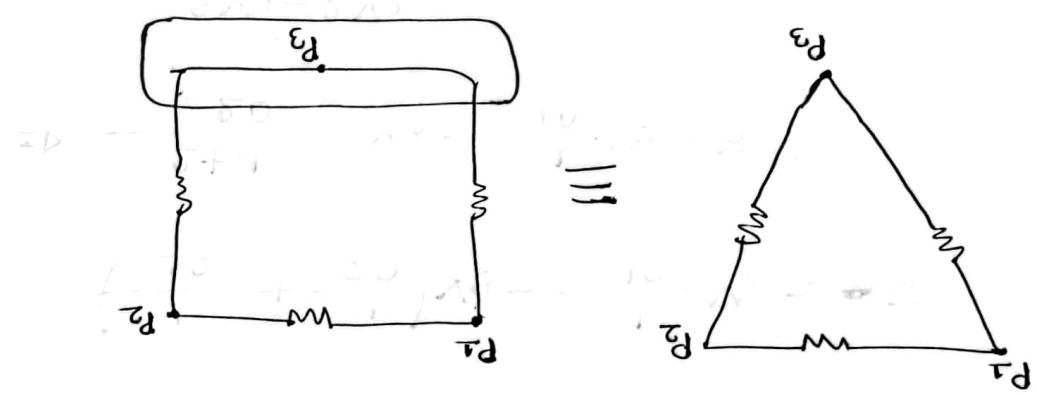

(Δ network)


$$V_o = V_s - V_{out}$$

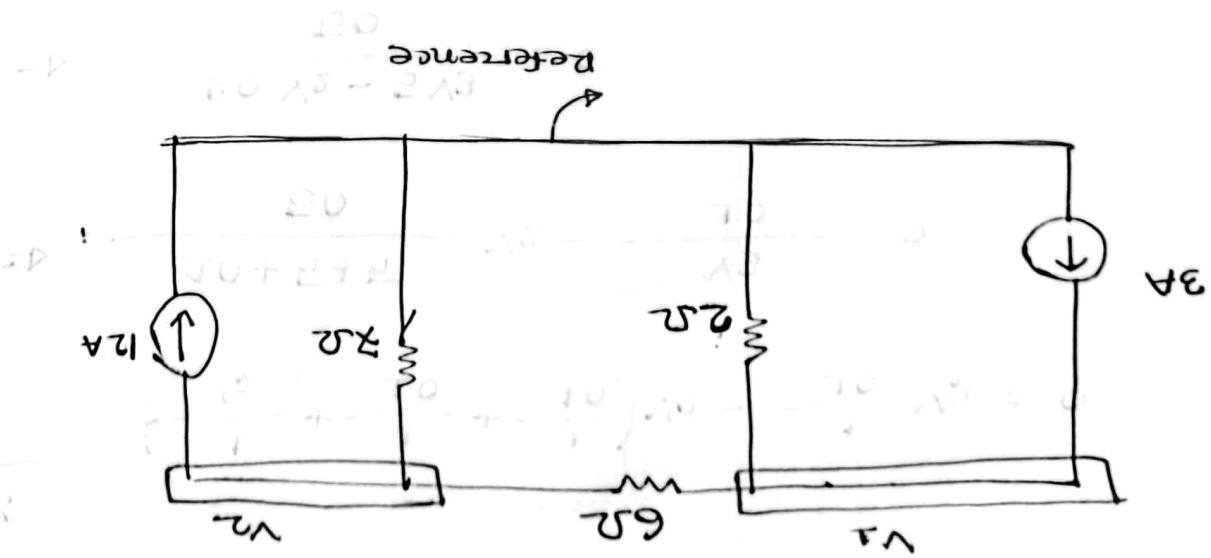

$$R_3 = \frac{R_a + R_b + R_c}{R_a R_b}$$

$$R_2 = \frac{R_a + R_b + R_c}{R_c R_a}$$
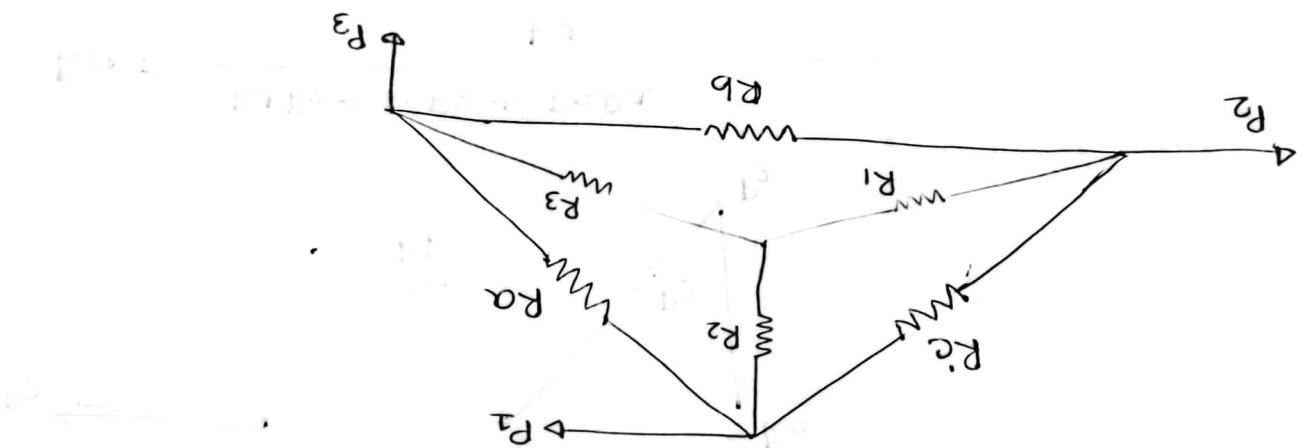
$$R_1 = \frac{R_a + R_b + R_c}{R_b R_c}$$



Conversion: Δ to Y

\rightarrow three-junction delta (Δ) connection.

\rightarrow 3 terminal resistive port at common point Σ -connection

$$R_C =$$


$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$R_B =$$

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$R_A =$$
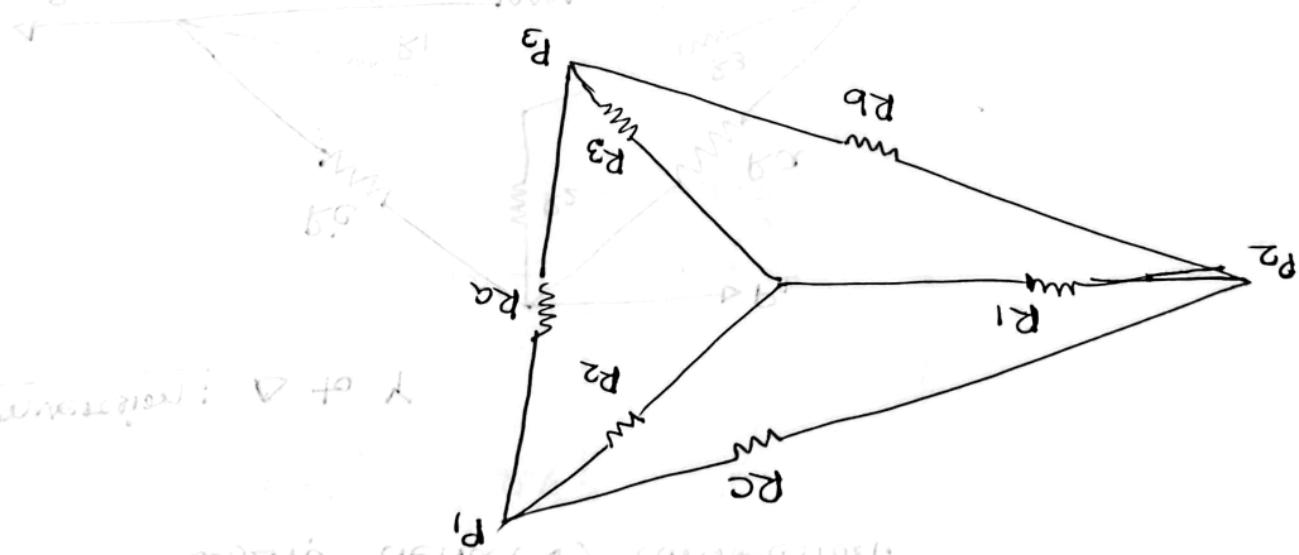
$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$



• umkehrung (D) auf Δ zu bringen

Conversion Y to Δ fiktiv

umkehrung

negative peaks.

the sum of the magnitude of the positive and

⑤ Peak to peak value: Peak to peak value means

peak to peak value.

maximum measured from the zero

④ Peak amplitude: The maximum value of a waveform at any instantaneous

③ Peak amplitude: The maximum value of a

② Instantaneous value: At any instant of time.

① Waveform: The waveform of a waveform

current.

Current can be generated by alternating

shape of one cycle of the voltage or current.

④ Waveform: The waveform describes the

same as the effect of current will differ

③ Charge per unit time.

medium source.

(f) Amplitude of wave : The maximum displacement of particles from their mean position.

(g) Frequency : Number of complete oscillations per second.

Pulse value : 0 - highest

Amplitude : Average value - Highest point

Wavelength : Distance between two consecutive crests or troughs.

Frequency (f) : The number of cycles per second.

Accurate in 1 second.

(h) Frequency (f) : The number of cycles per second.

or one complete oscillation.

Completed in one period of time.

(i) Cycle : The portion of a waveform

waveform.

(j) Period (T) : The time of a periodic

source to repeat itself. It is also called time interval.

(k) Continuity : It repeats the same

(l) Periodic waveform : A waveform that

$$e = \text{Emissivity}$$

$$\tau = \text{Transmissivity}$$

Q1 (a) $\text{Wavelength} = \lambda$ (wavelength)

For the electrical quantities such as current or

Pick value

Sineoidal waveform is $A \sin \omega t$

The basic non-dimensional form for the

$$= 0.875 = 0.875(\omega - 0.0)$$

$$\frac{\omega}{\alpha} = t$$

Angle of phase (Second)

Angular velocity = $\frac{\text{Distance (degree or radians)}}{\text{Time (Second)}}$

$$0.875 = 0.875$$

$$30^\circ \text{ Degree} = \frac{\pi}{180^\circ}$$

$$A \text{ Radians} = \frac{\pi}{180^\circ} \text{ Radians}$$

length of curve

length of curve

$$Q_1 \text{ (Average value)} = \frac{\text{Algebraic sum of areas}}{\text{Length of curve}}$$

$$= Am \sin(\omega t - \theta)$$

$$y = Am \sin(\omega t + \theta)$$

$$\sin \alpha = \sin(\alpha \mp 90^\circ) -$$

$$- \cos \alpha = \sin(\alpha - 90^\circ)$$

$$m = -$$

$$\sin \alpha = \cos(\alpha - 90^\circ)$$

$$\cos(\alpha + 90^\circ) = -\sin \alpha$$

$$\begin{cases} \cos \alpha = (\alpha - 90^\circ) \\ \sin \alpha = (\alpha + 90^\circ) \end{cases}$$

Phase relations: $\pi - 180^\circ$